

***VASAVI COLLEGE OF ENGINEERING  
(AUTONOMOUS)***

***IBRAHIMBAGH, HYDERABAD-31***

***Department of Electrical and Electronics Engineering***



Simulation of Power Electronics using PSIM



## **AC-DC CONVERTERS**

### **Uncontrolled rectifier**

- Half wave with R load
- Centre tapped full wave rectifier
- Bridge rectifier with R load
- Bridge rectifier with RL load
- Bridge rectifier with RE load
- Bridge rectifier with RLE load with discontinuous conduction
- Bridge rectifier with RLE load with continuous conduction
- Bridge rectifier with RL load with free wheeling diode
- Bridge rectifier with RLE load with free wheeling diode

### **Controlled rectifier**

- Controlled rectifier with RL load
- Controlled rectifier with RL load with free wheeling diode

### **Three pulse rectifier**

### **Six pulse rectifier**

### **12 pulse rectifier**

## **DC-DC CONVERTERS**

- Boost converter
- Buck converter
- Buck-Boost converter

## **DC-AC CONVERTERS**

- Single phase converter
- Three phase converter

## **AC-AC CONVERTERS**

- Cycloconverter

## **Electronic circuits**

### **Clippers**

- Above reference
- Below reference



- Above and below reference

### **Clampers**

- Negative clampers
- Positive clampers

### **Multiplier circuit**

### **Integrator**


### **differentiator**




## HALF WAVE RECTIFIER

Selecting the elements:

1) How to select AC Source:

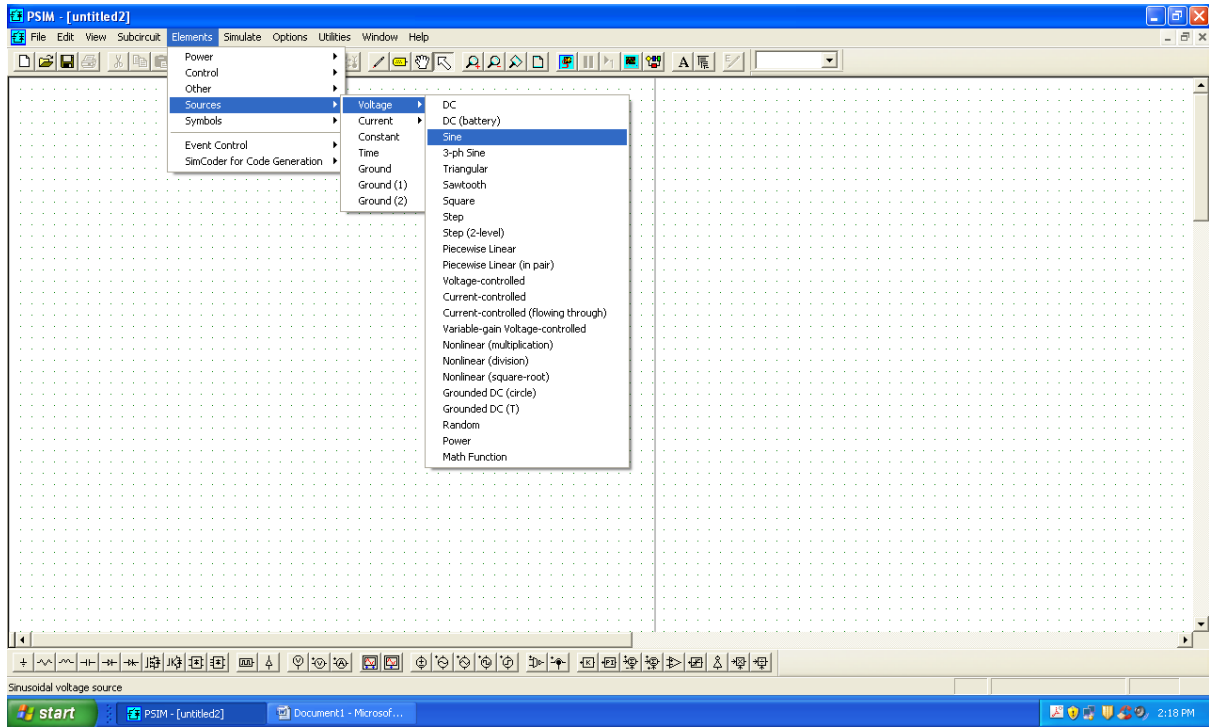


2) Diode:

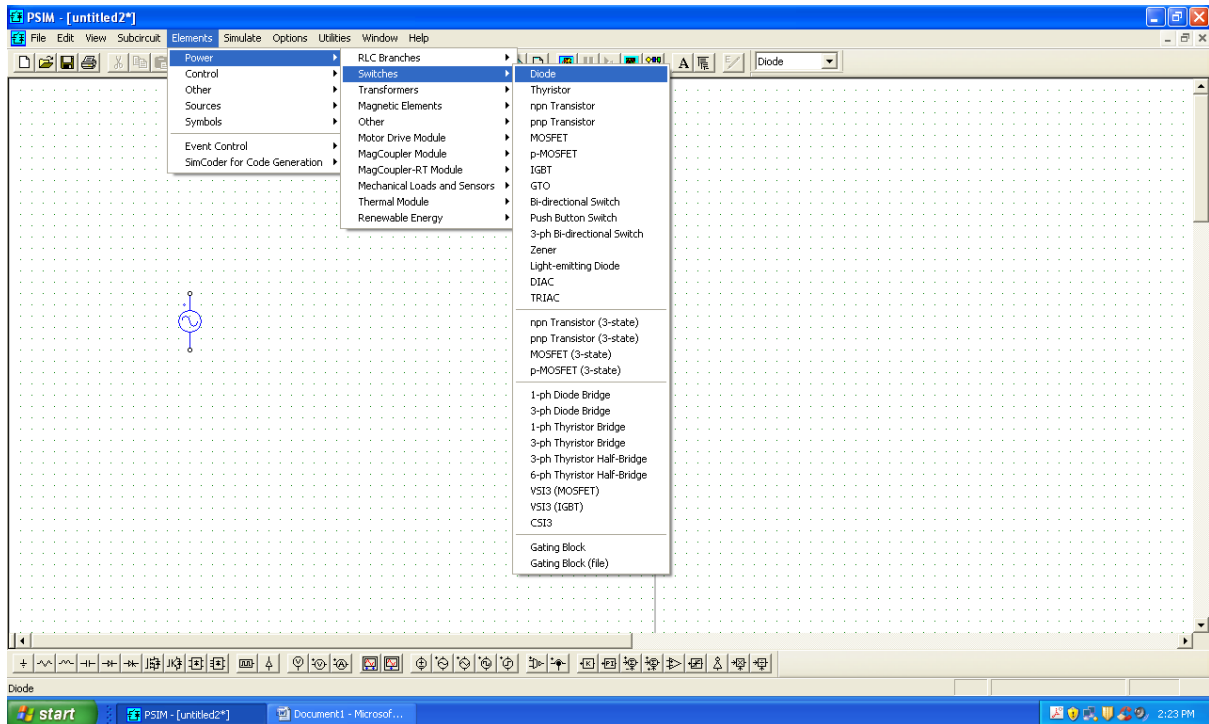






### 3) Resistor:

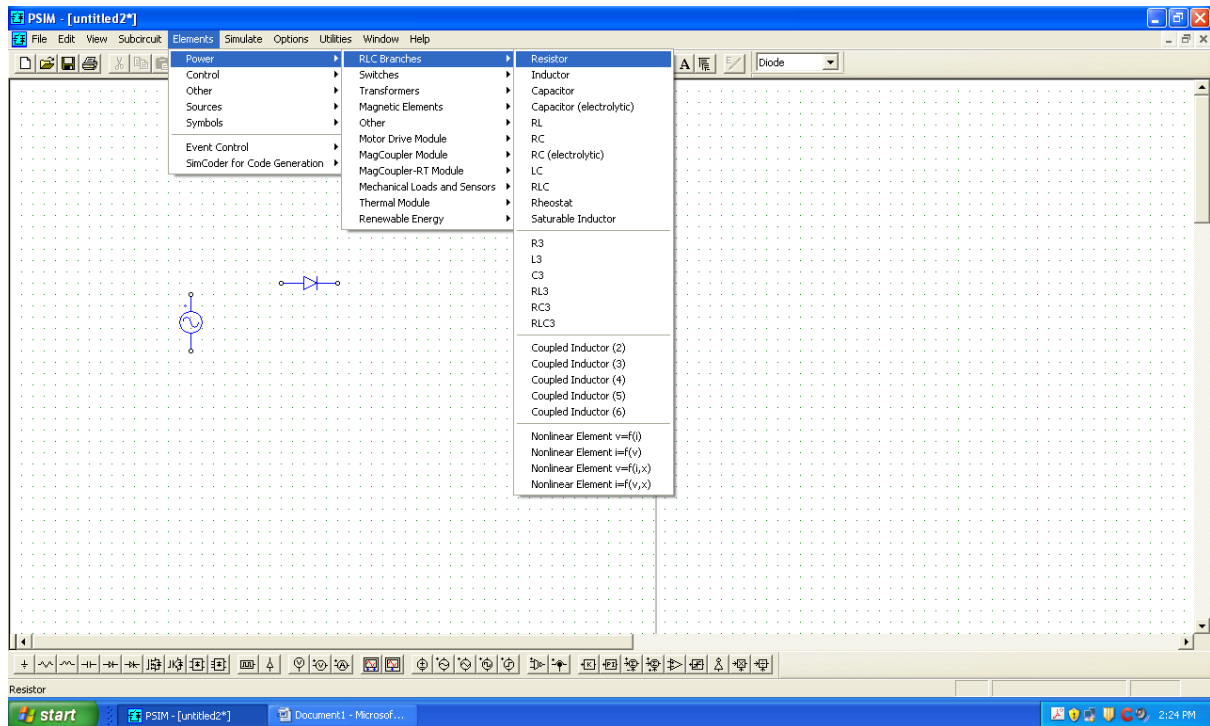


Hint: To rotate the element click right button of the mouse after selecting the element.

### 4) Voltmeter:

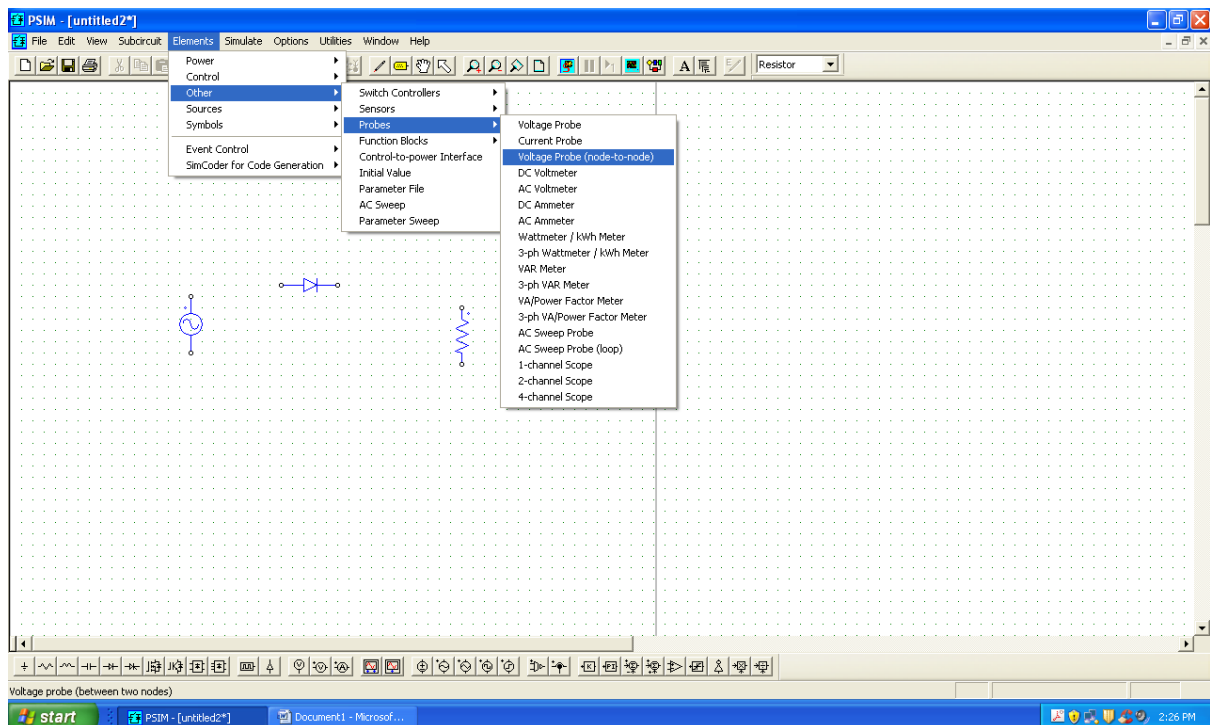




## 5) Ammeter:

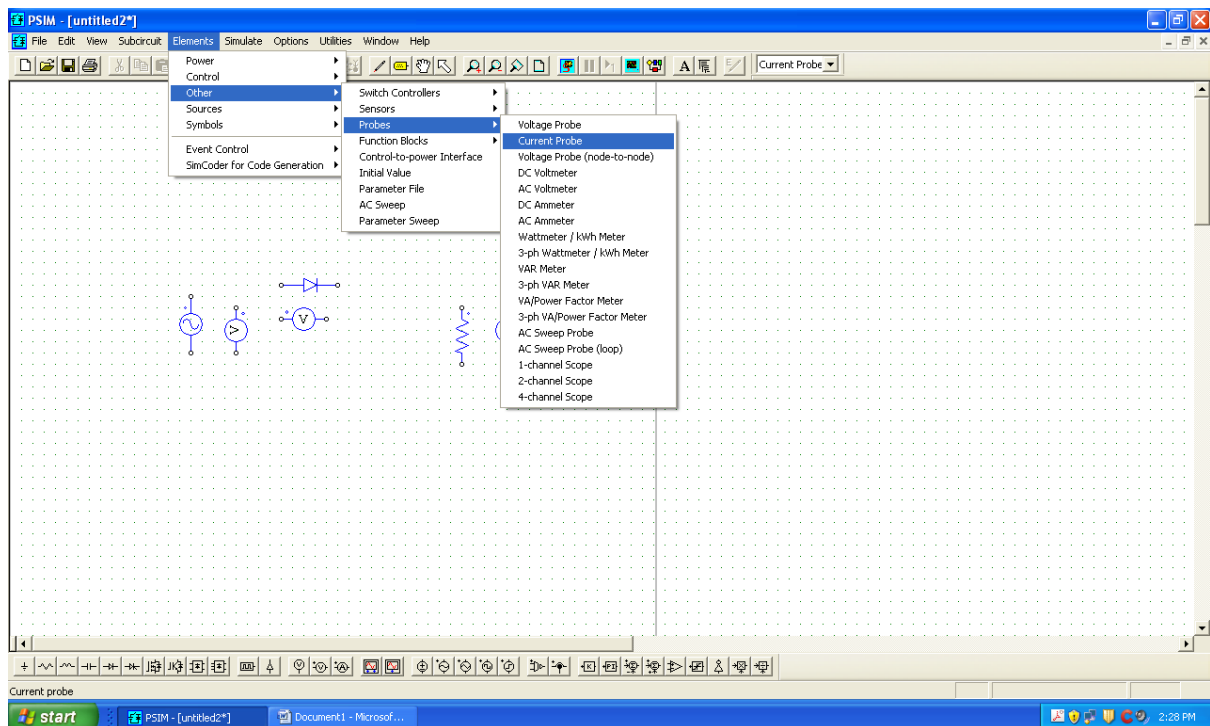


## 6) Simulation Control:

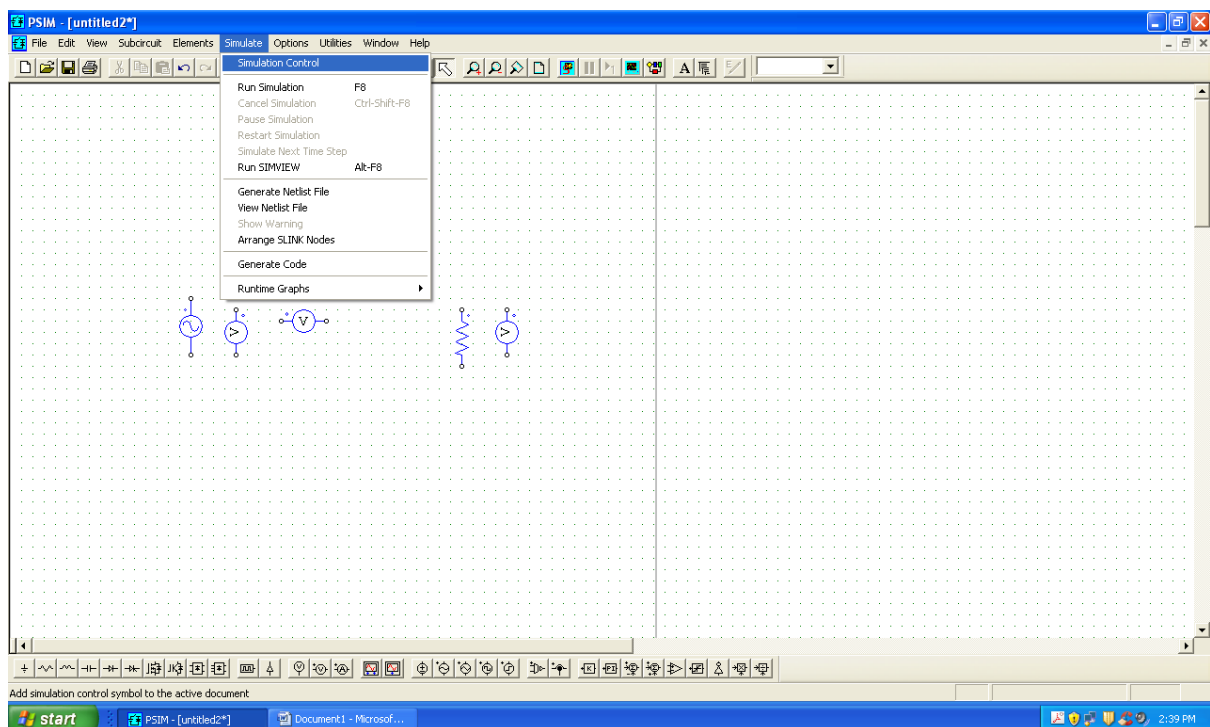




## Simulation Controller Settings:

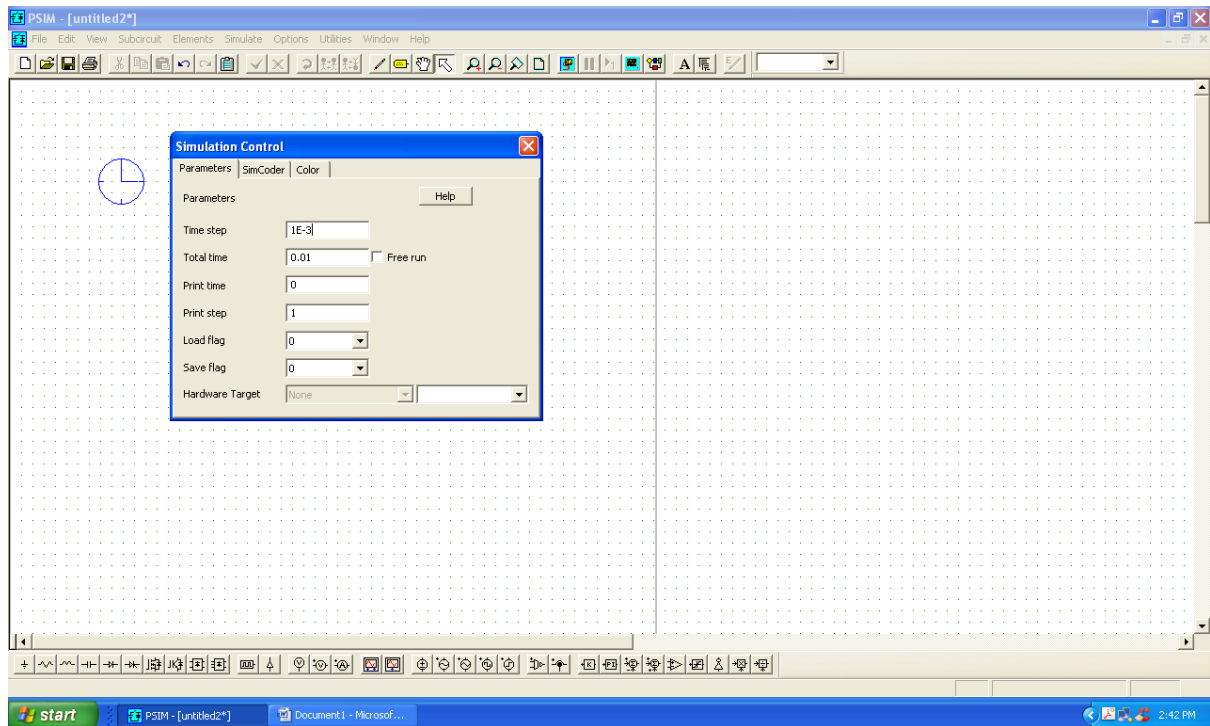

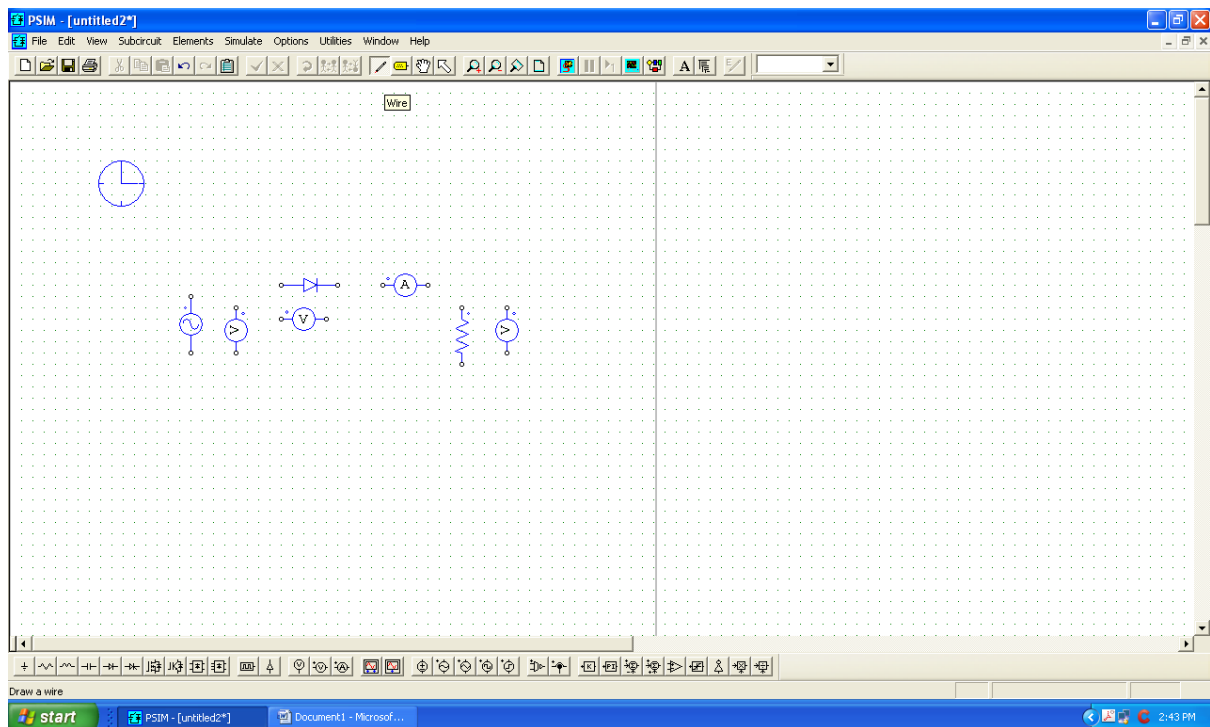
## Connecting the elements:

Select the wire tool from the tool bar as shown:






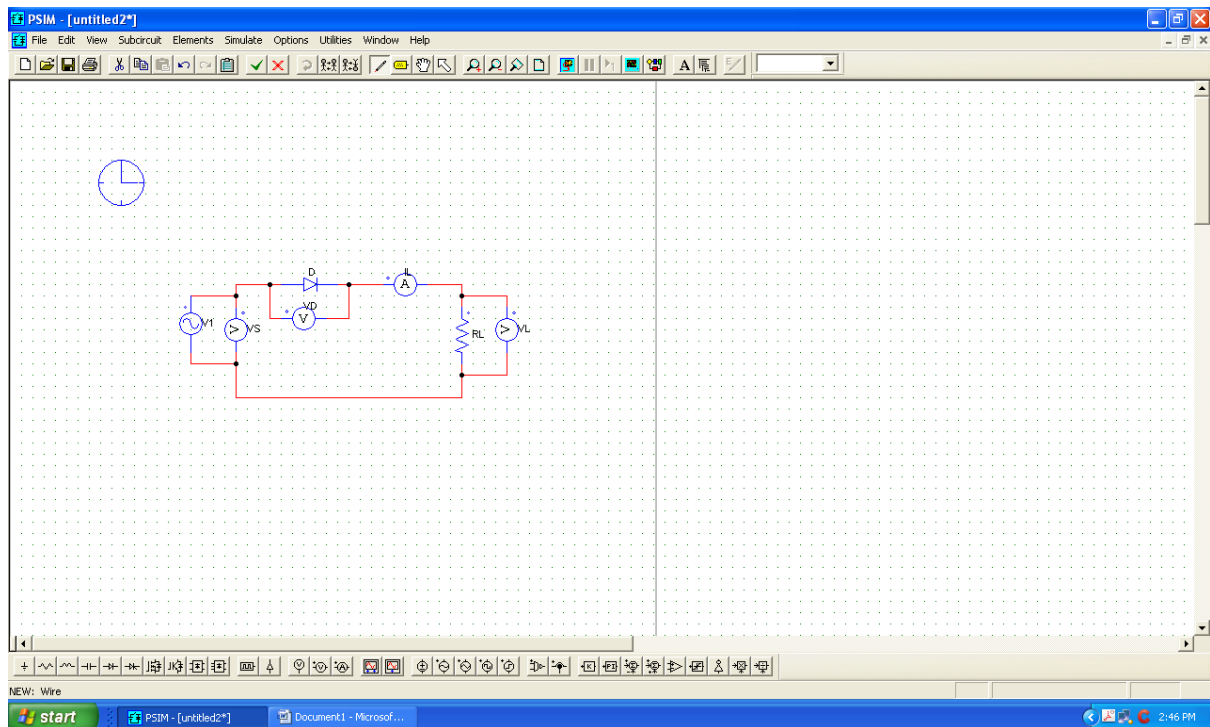Connect the elements using the wire tool selected from the tool bar.




How to run simulation:

Select the Run Simulation:

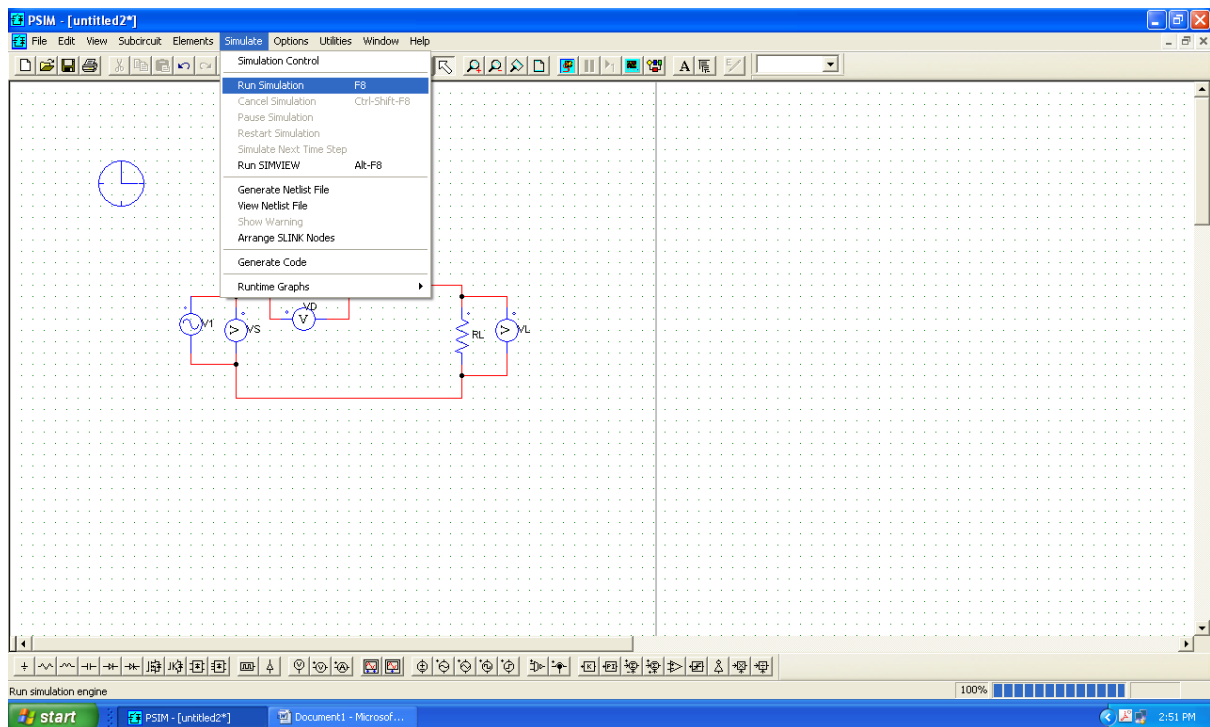




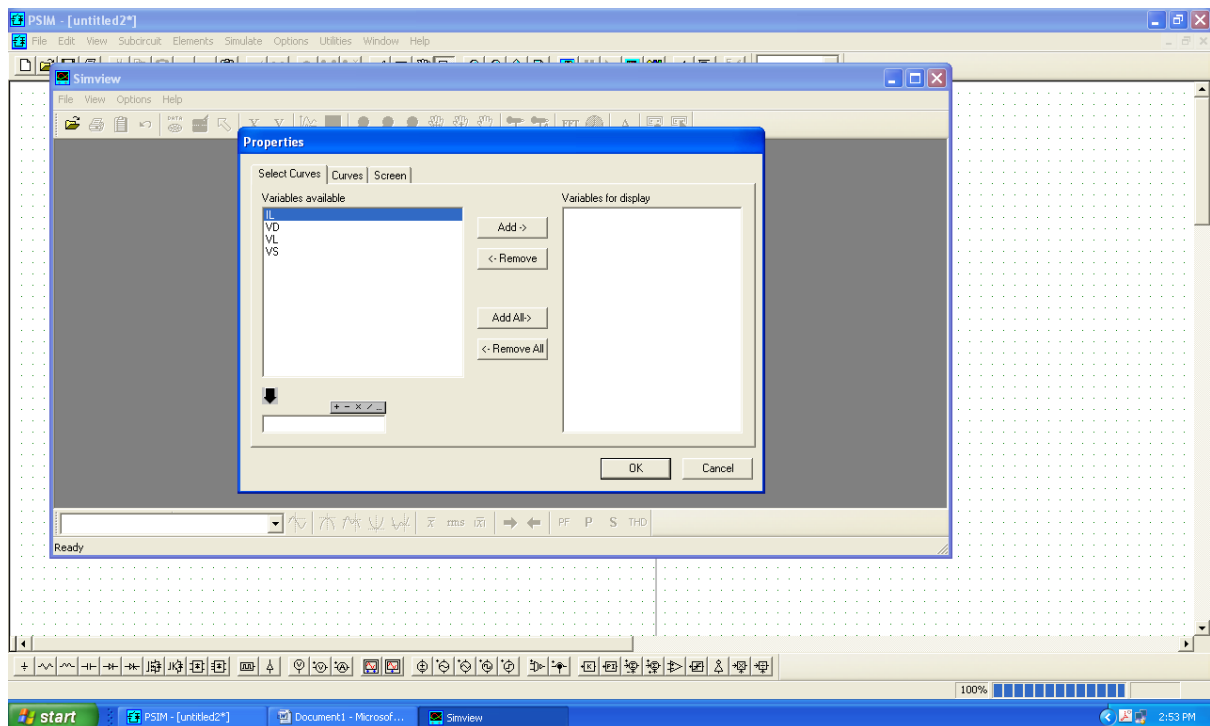
Adding the Variables to SimView for analyzing the waveforms:



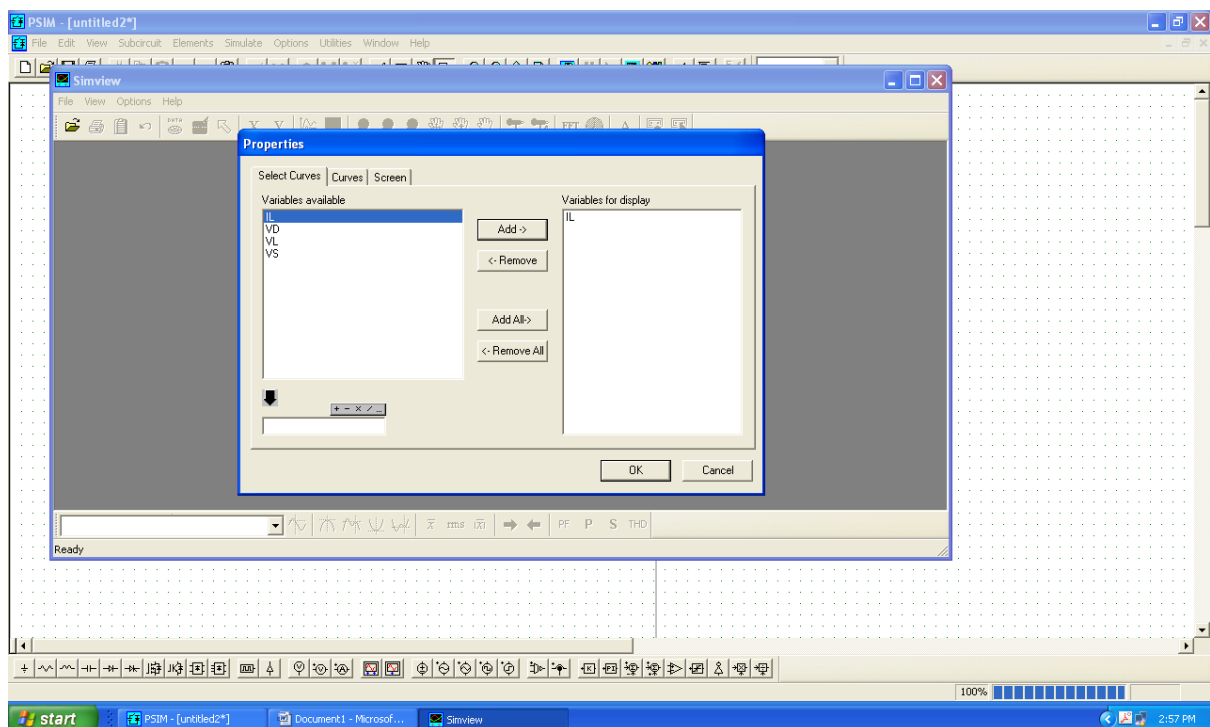
Select the variables and click on “Add” to add the variables.




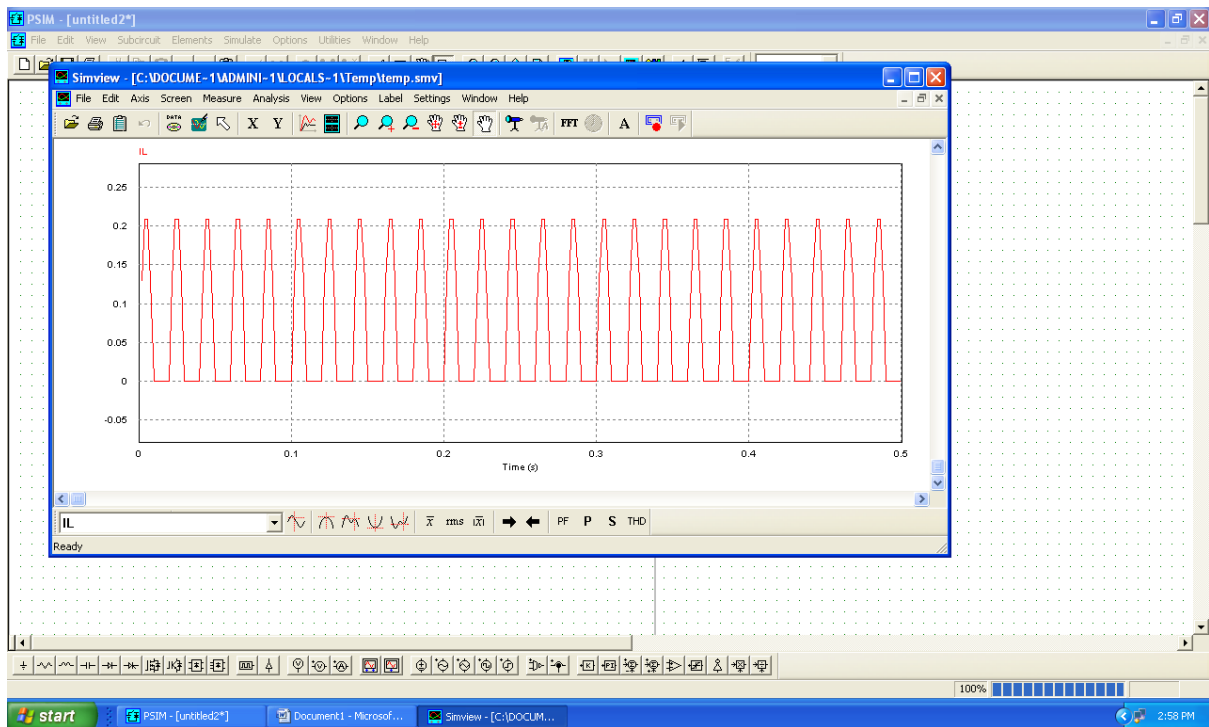After selecting the variables click on “OK” to get waveforms.




To add another variable to SimView:

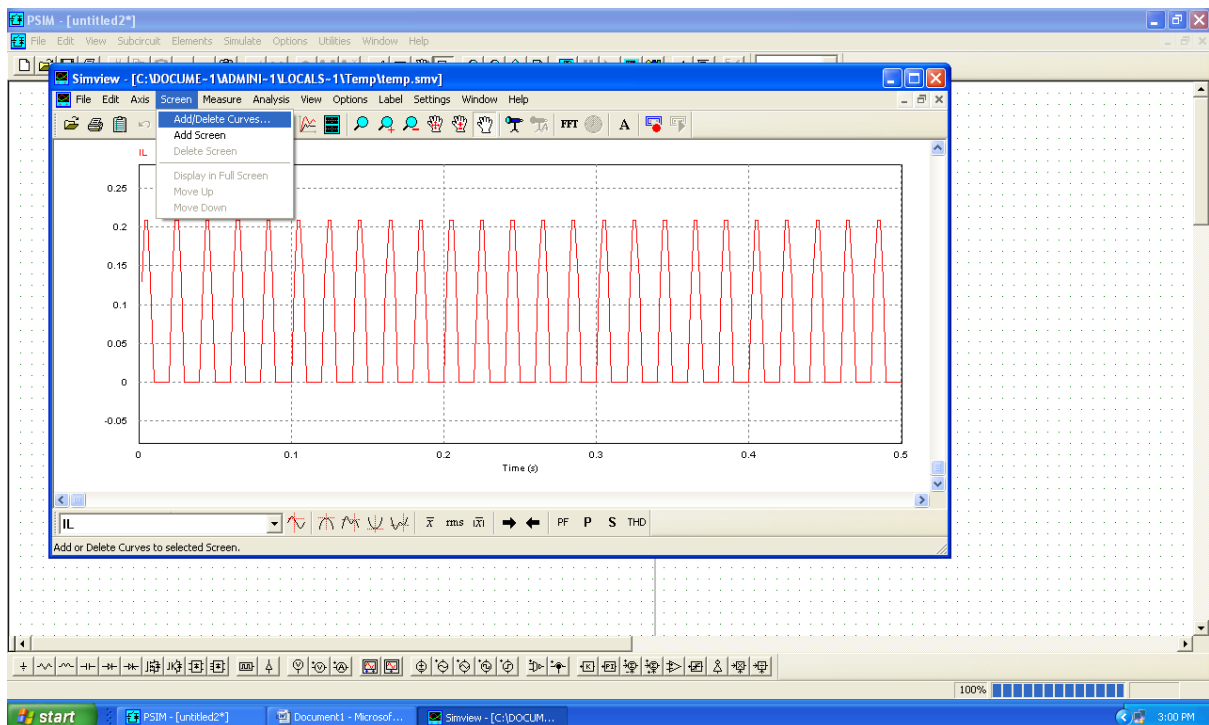

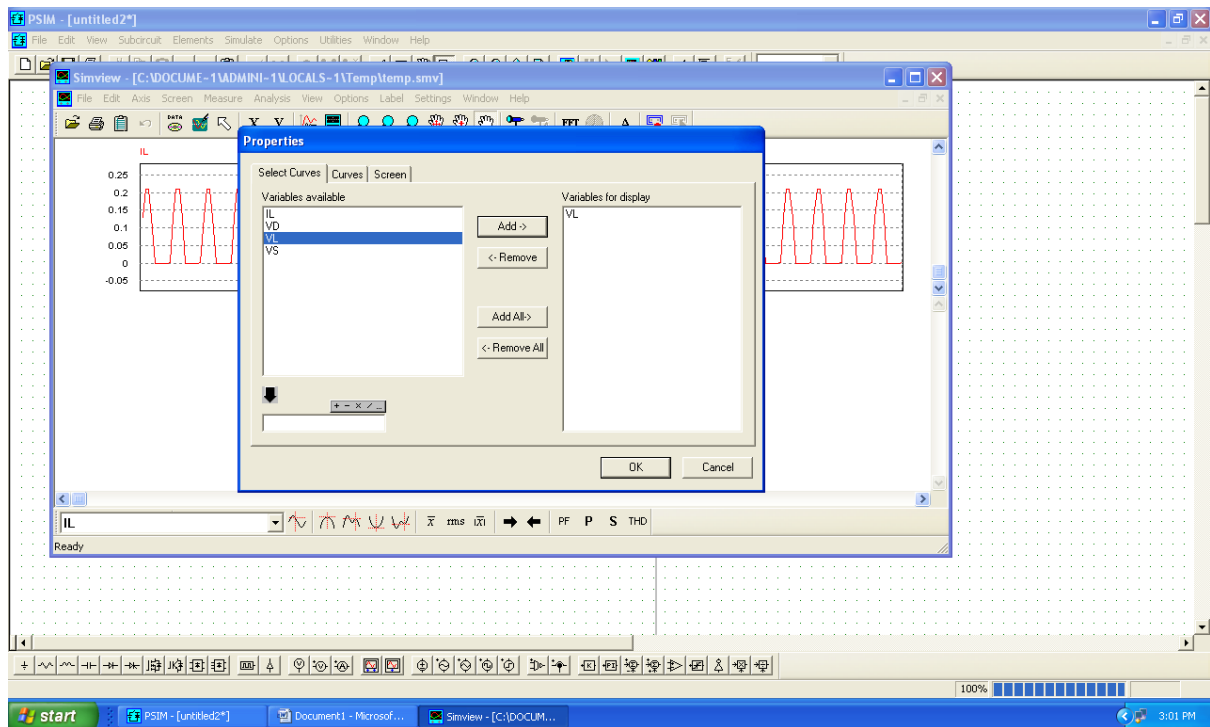



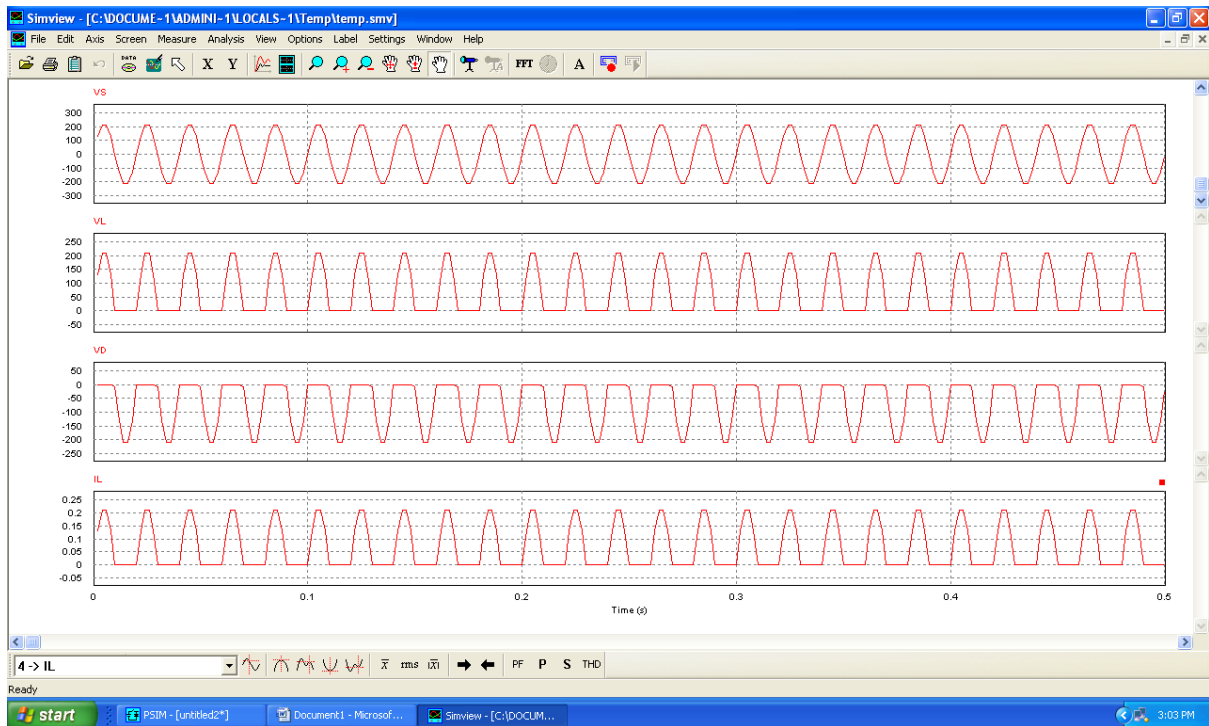
Similarly add all the required variables to analyze the waveforms.



Analysis of waveform by using SimView:

Calculation of Average value:

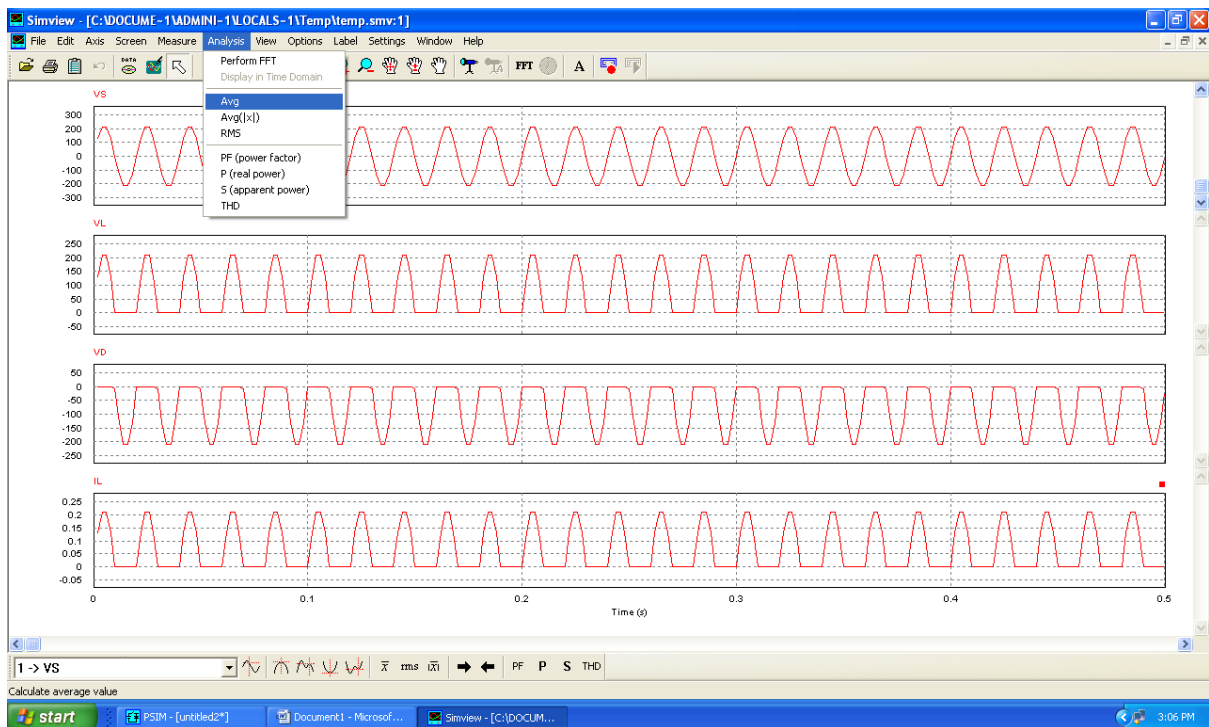
Select “Avg” from “Analysis” icon on task bar.








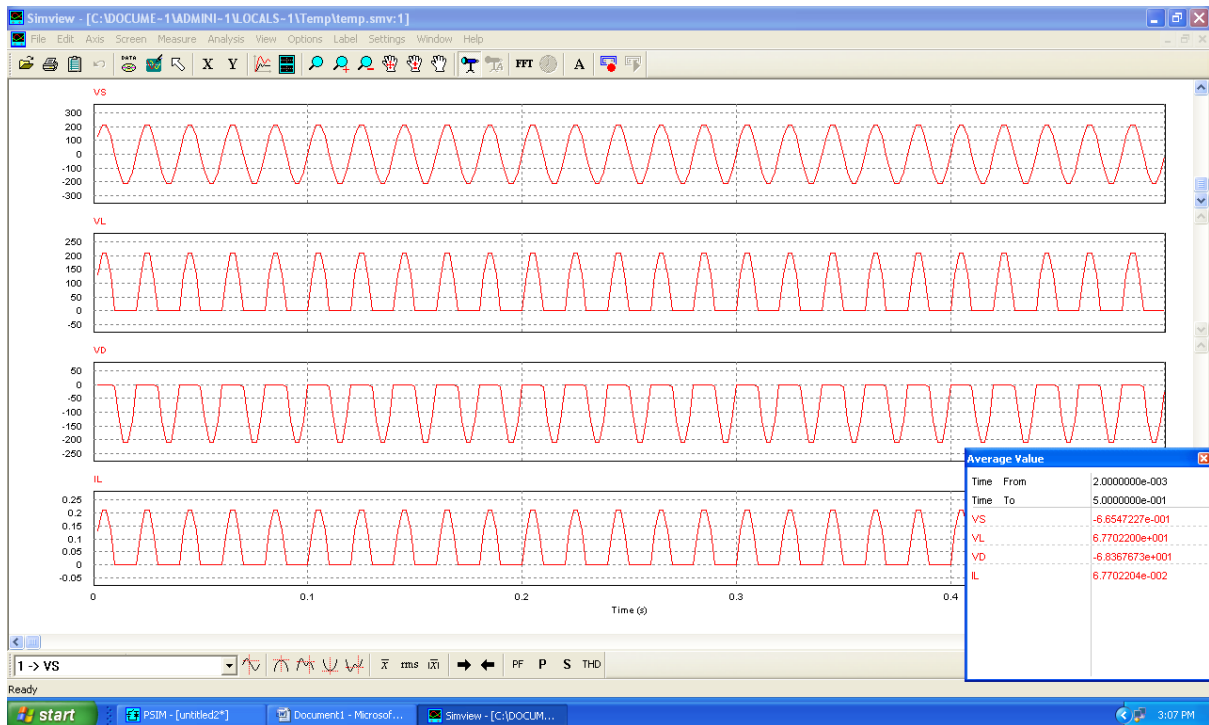On the right bottom of the screen we can observe the average values of according to their lables.




Calculation of RMS value:

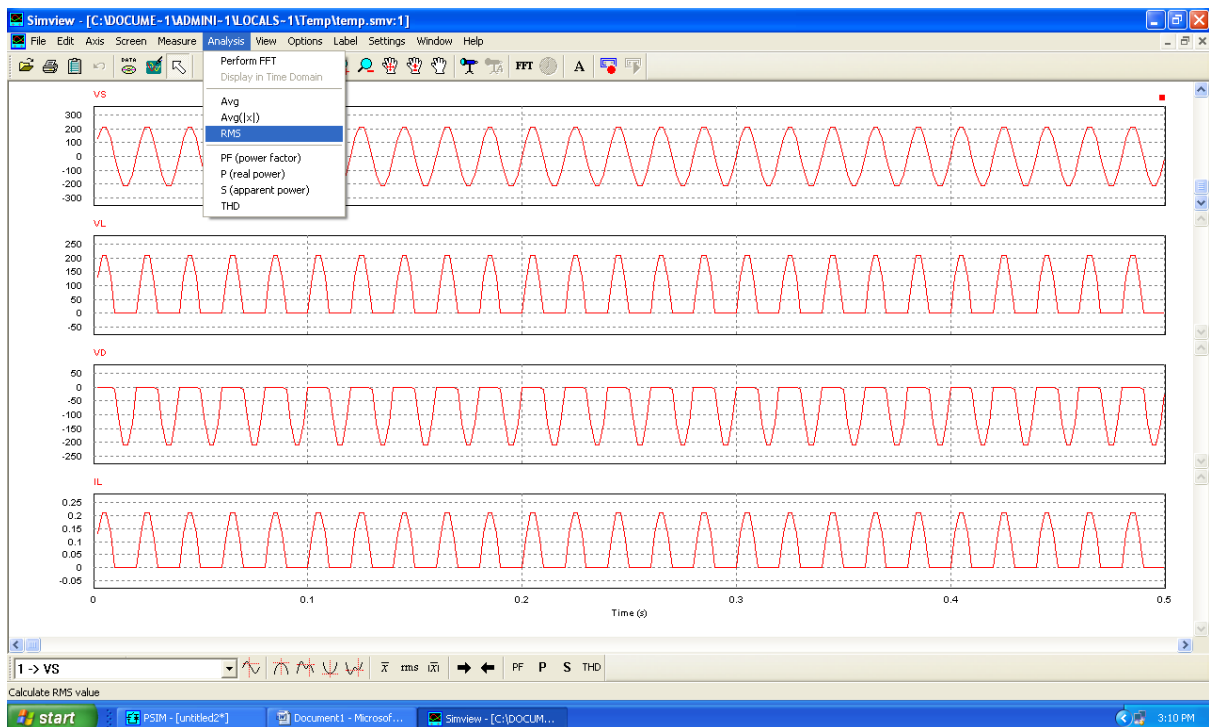Select "RMS" from "Analysis" icon on task bar.





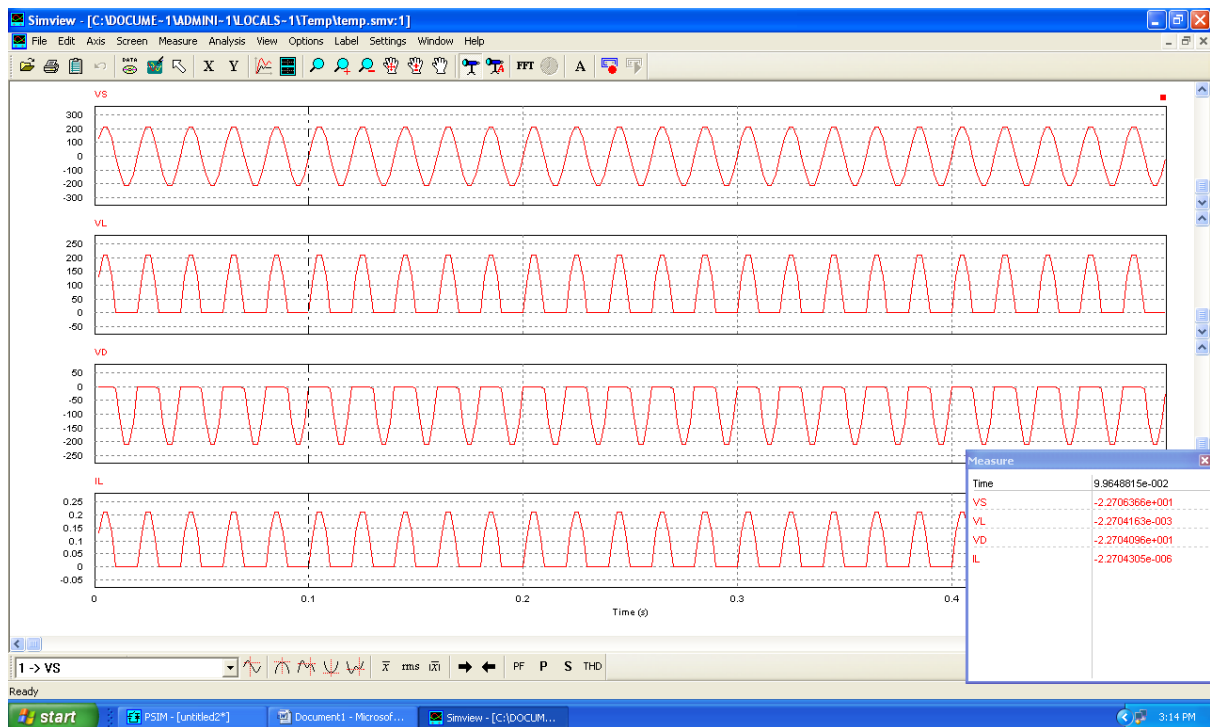
On the right bottom of the screen we can observe the average values of according to their lables.






## CENTER TAPPED FULL WAVE RECTIFIER

### 1) Selection of source

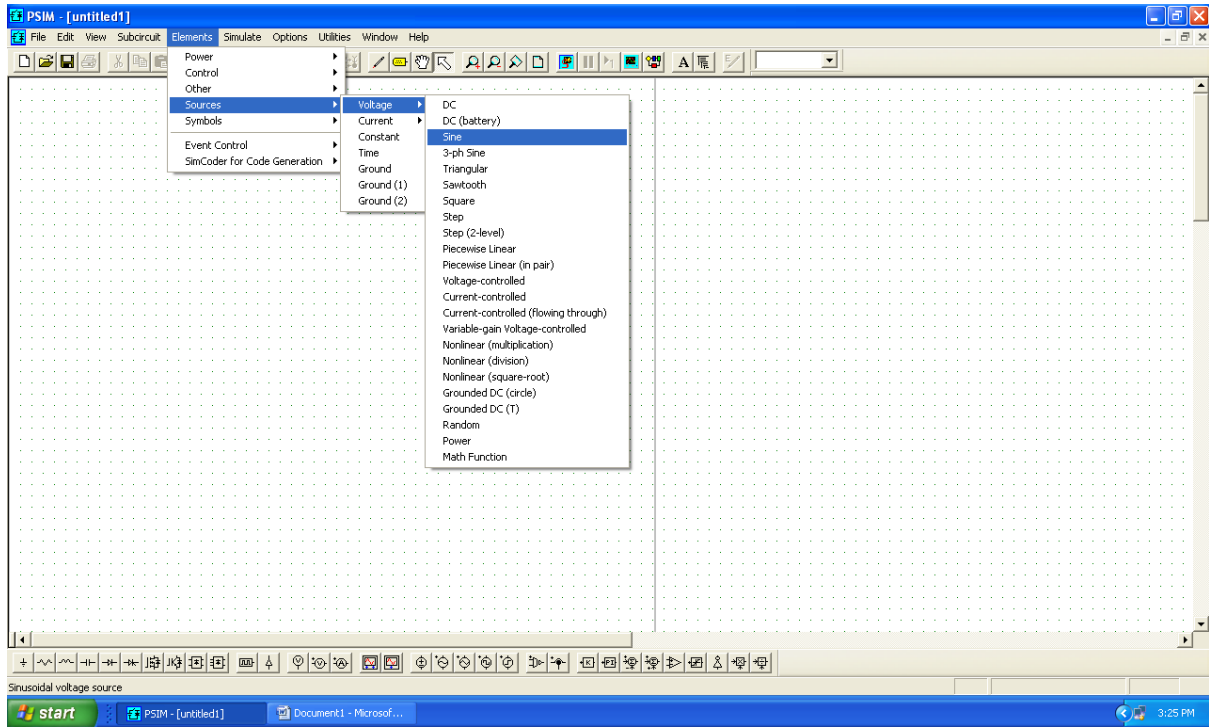


### 2) Selection of transformer

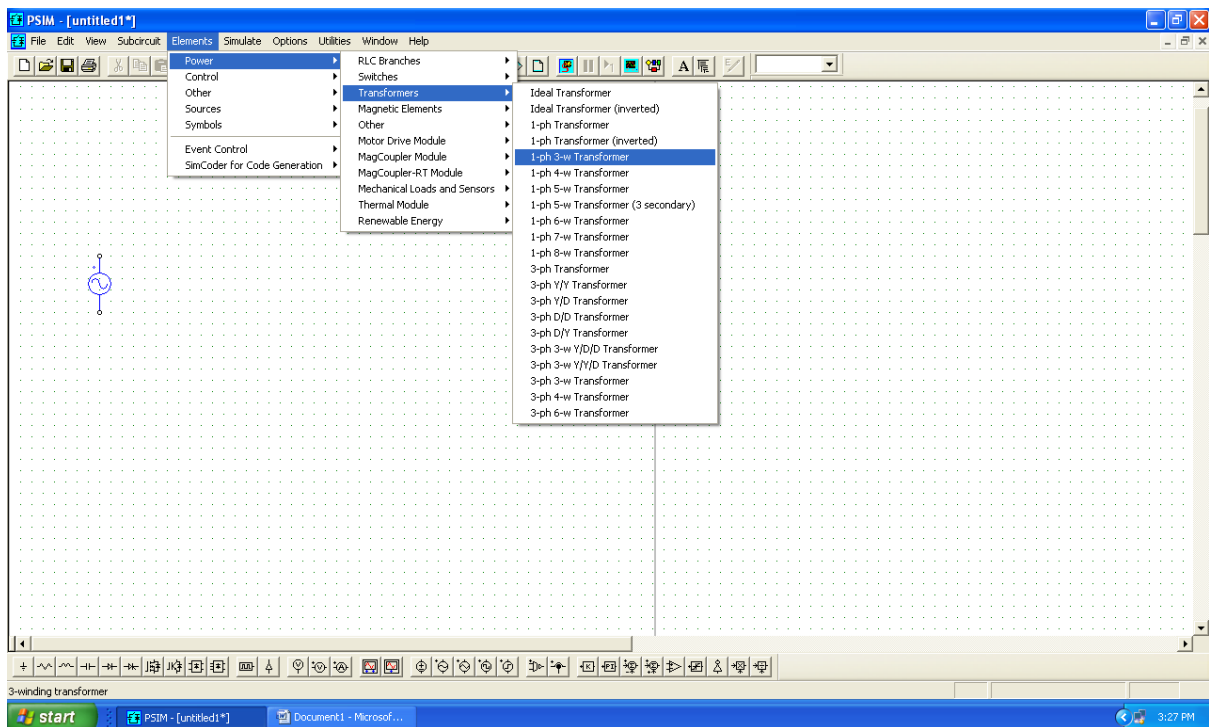




### 3) Selection of volt meter

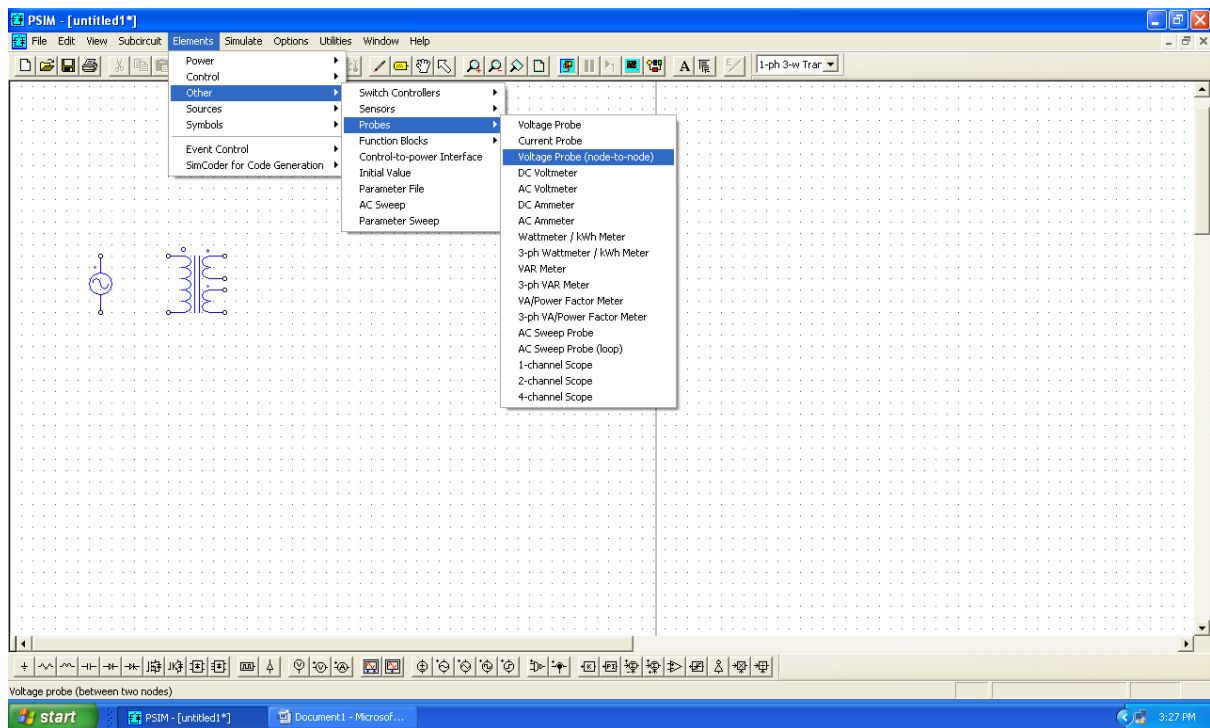


### 4) Selection of ammeter

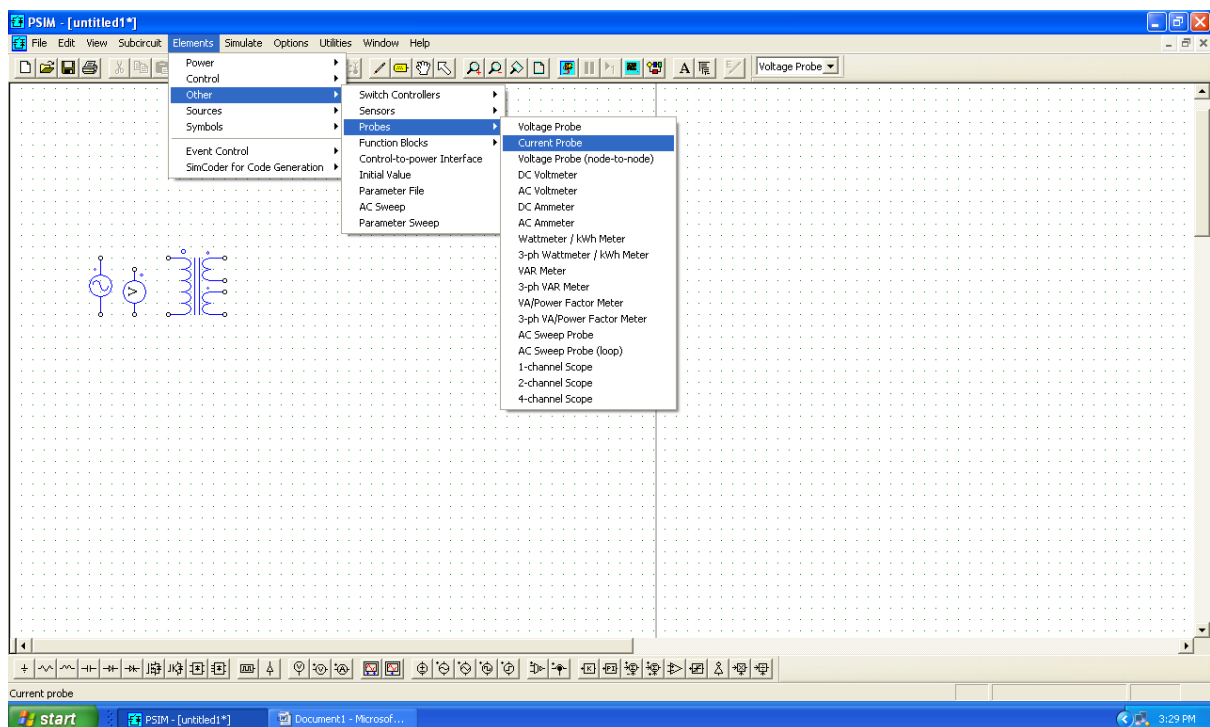




## 5) Selection of diode

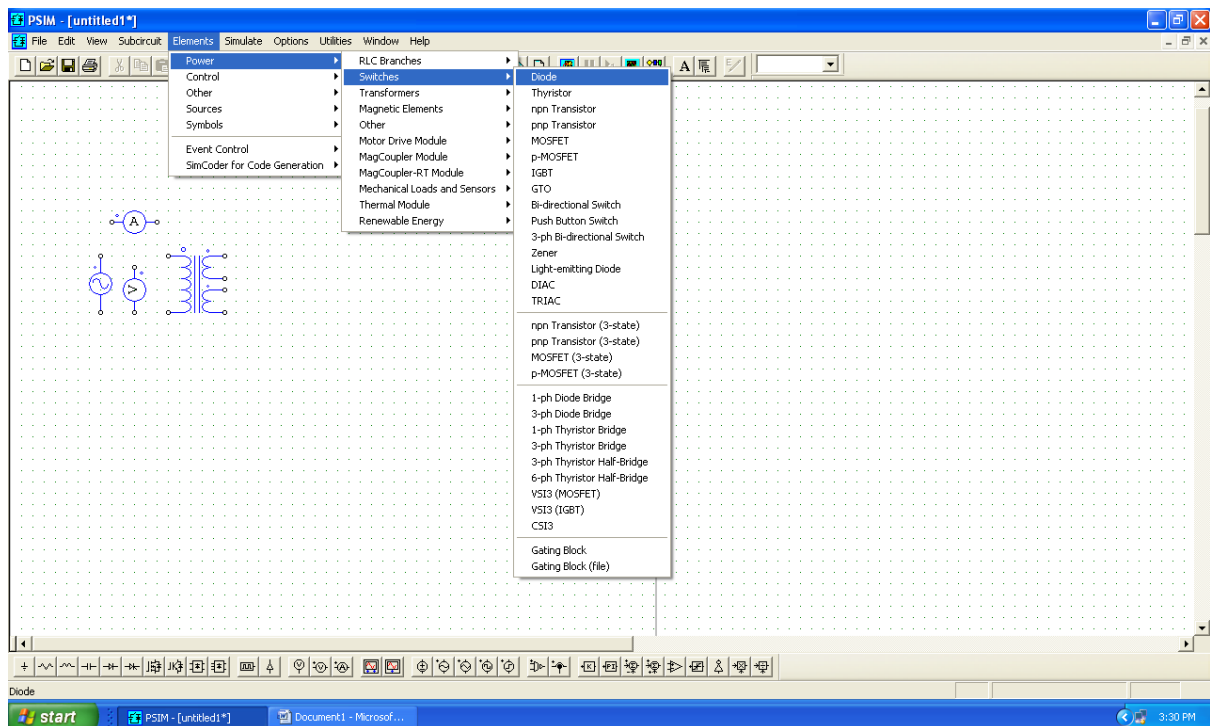


## 6) Selection of resistor

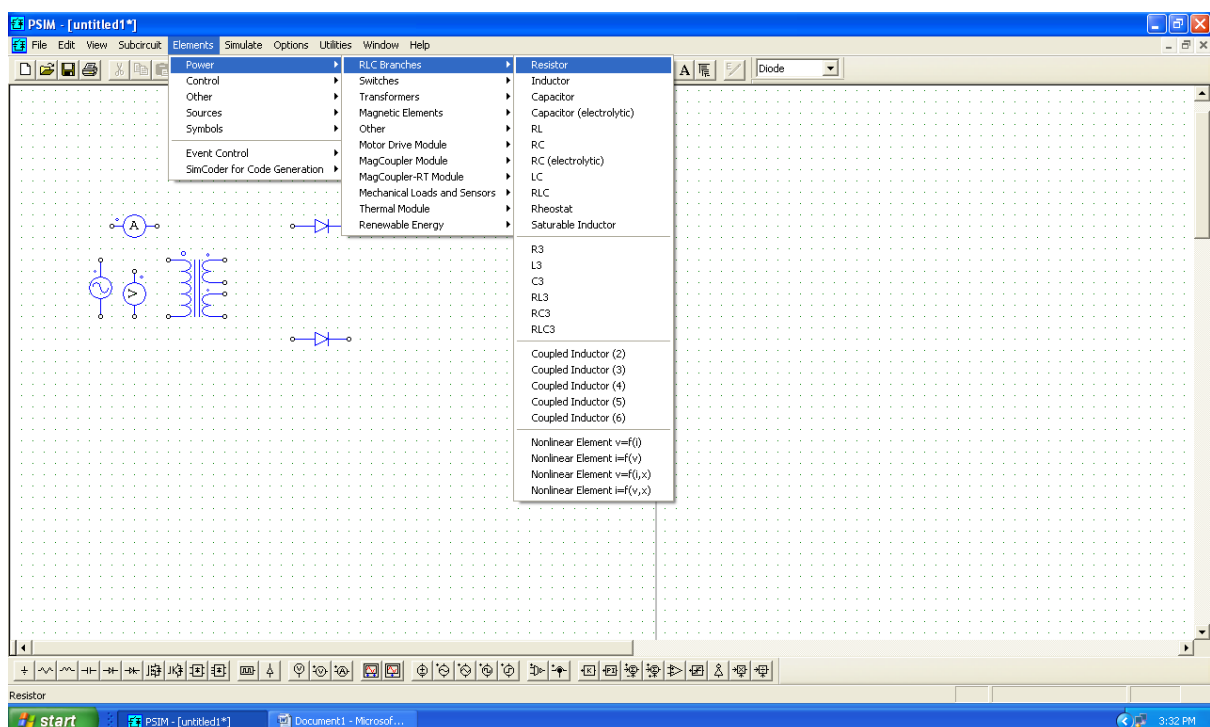




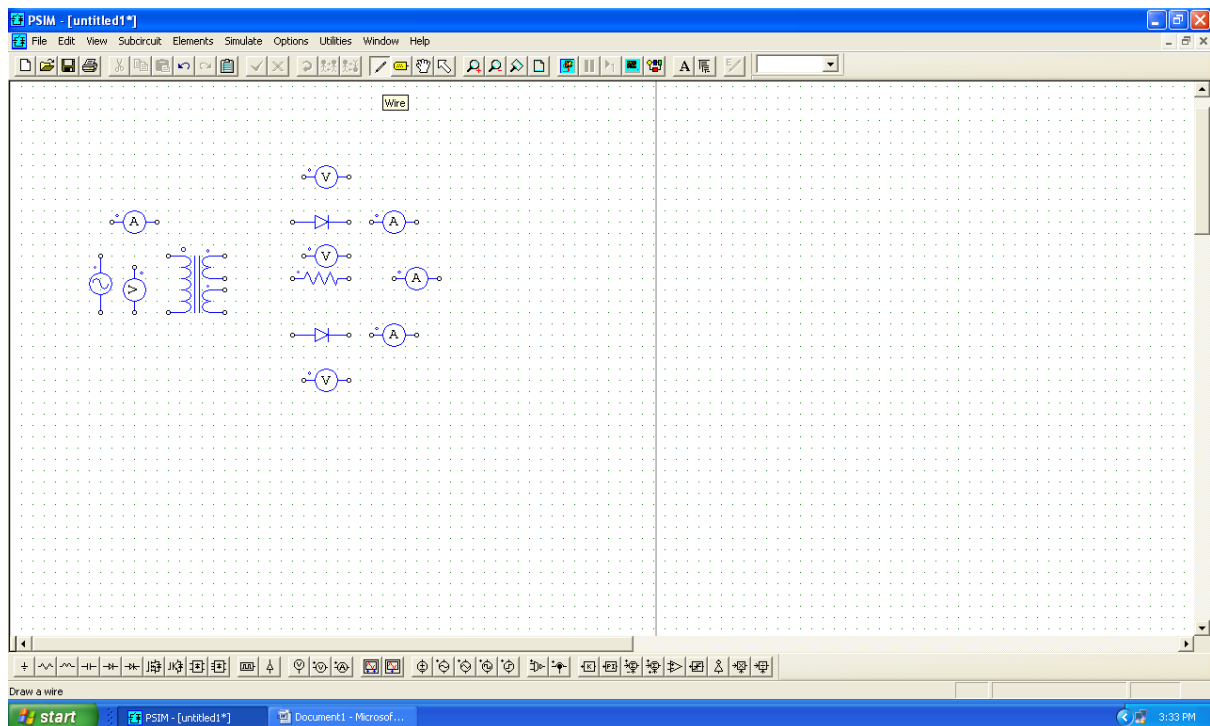7) Select number of elements as shown in below fig




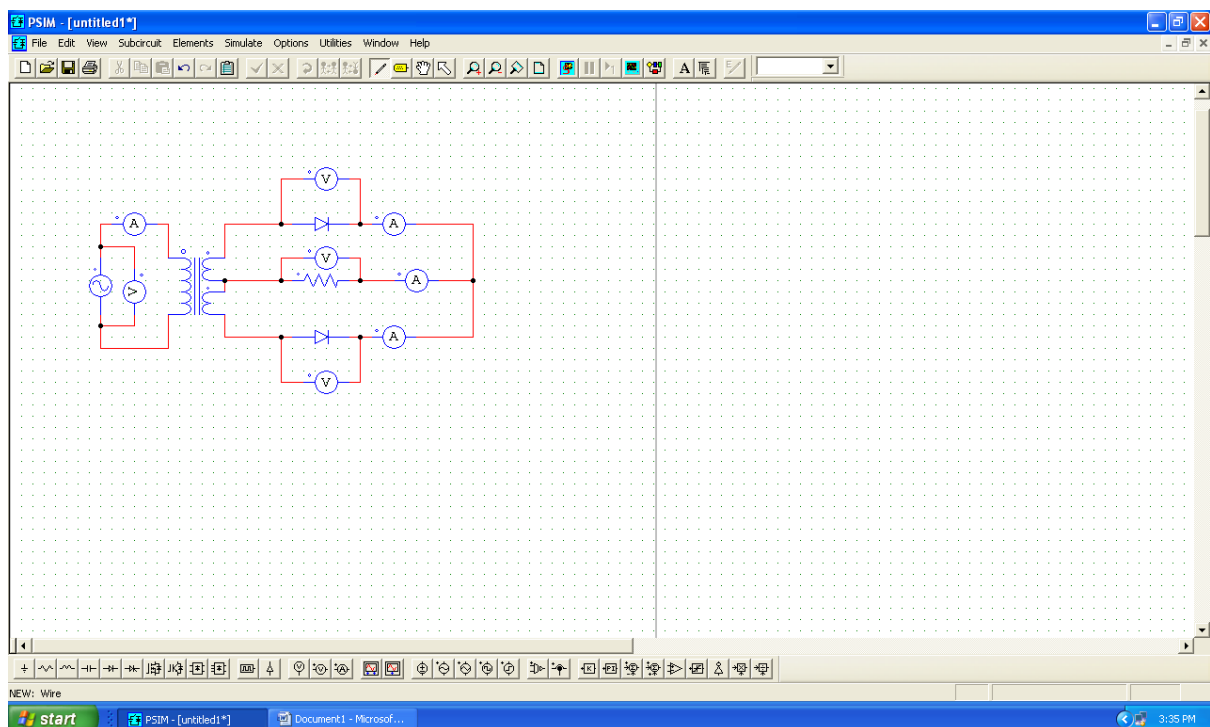8) Connect the elements as shown below using pencil tool






## 9) Add simulation controller

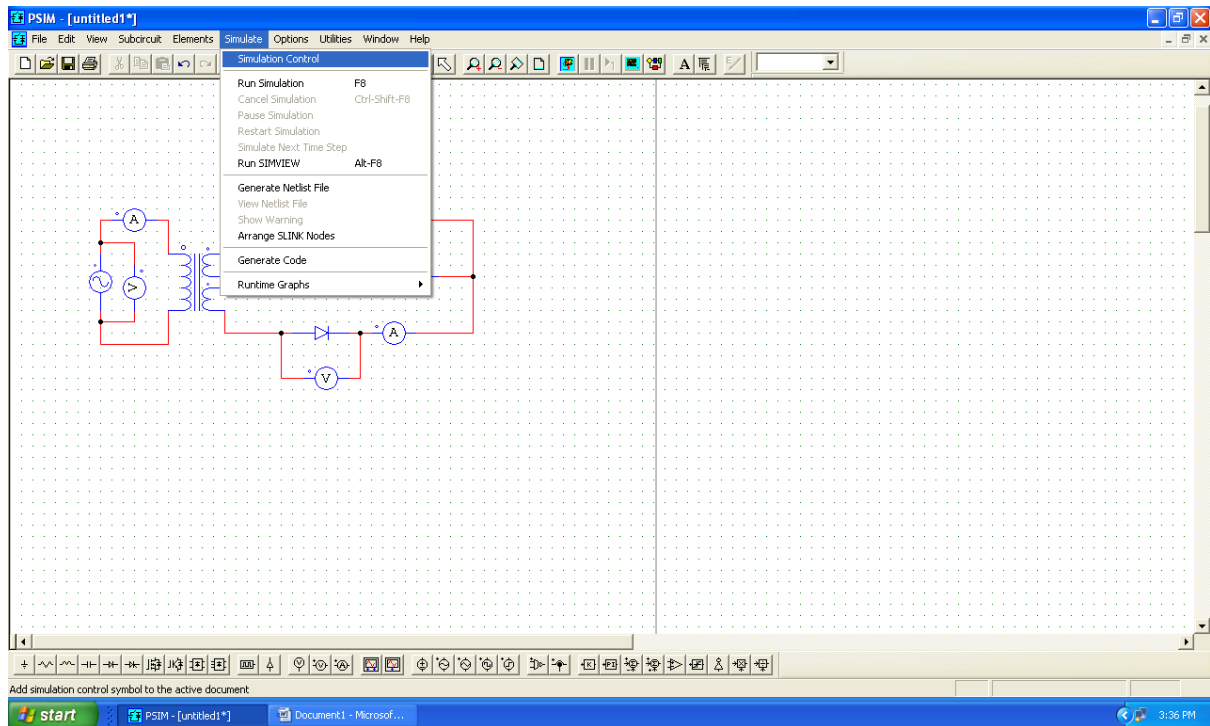


## 10) Put the values as shown below

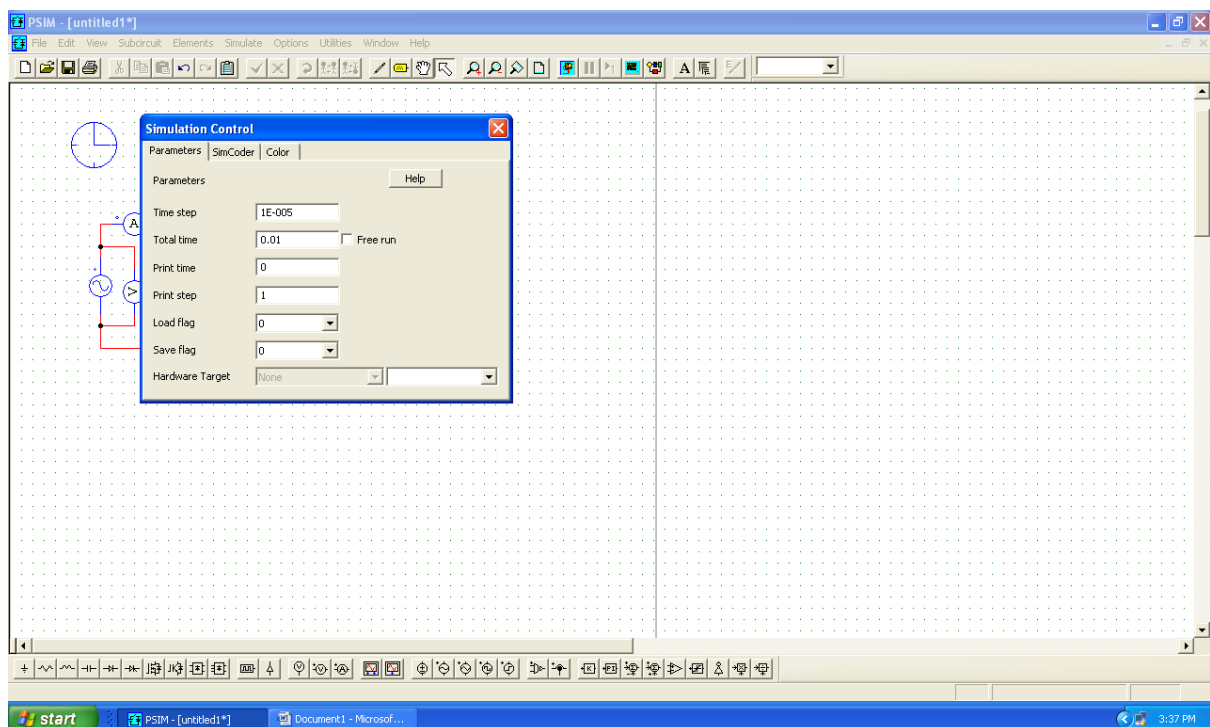




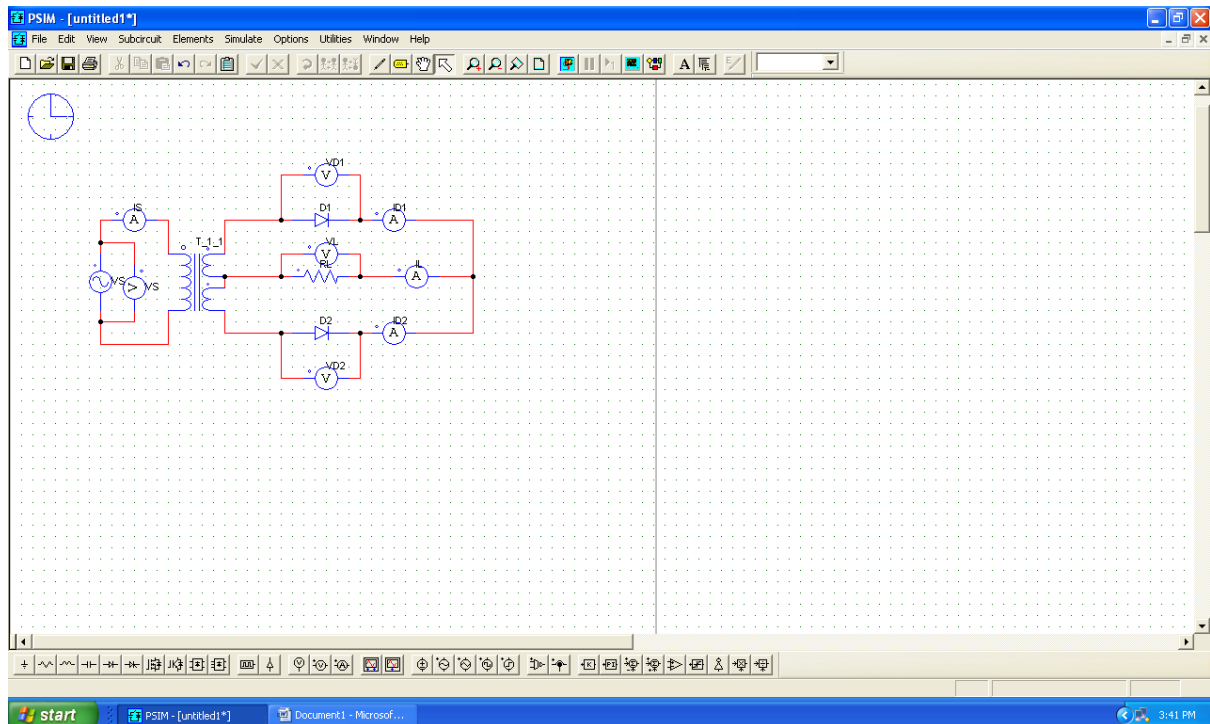11) Give the appropriate name to the every element




12) Run the simulation

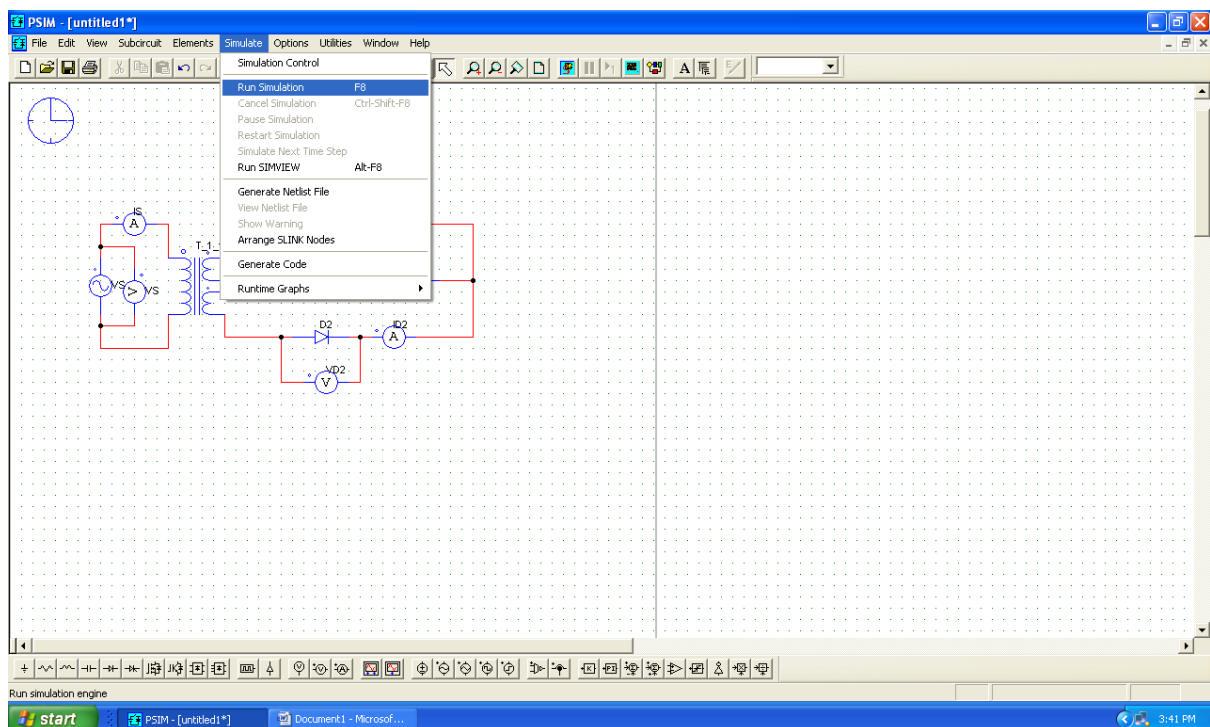






## 13) Select the required

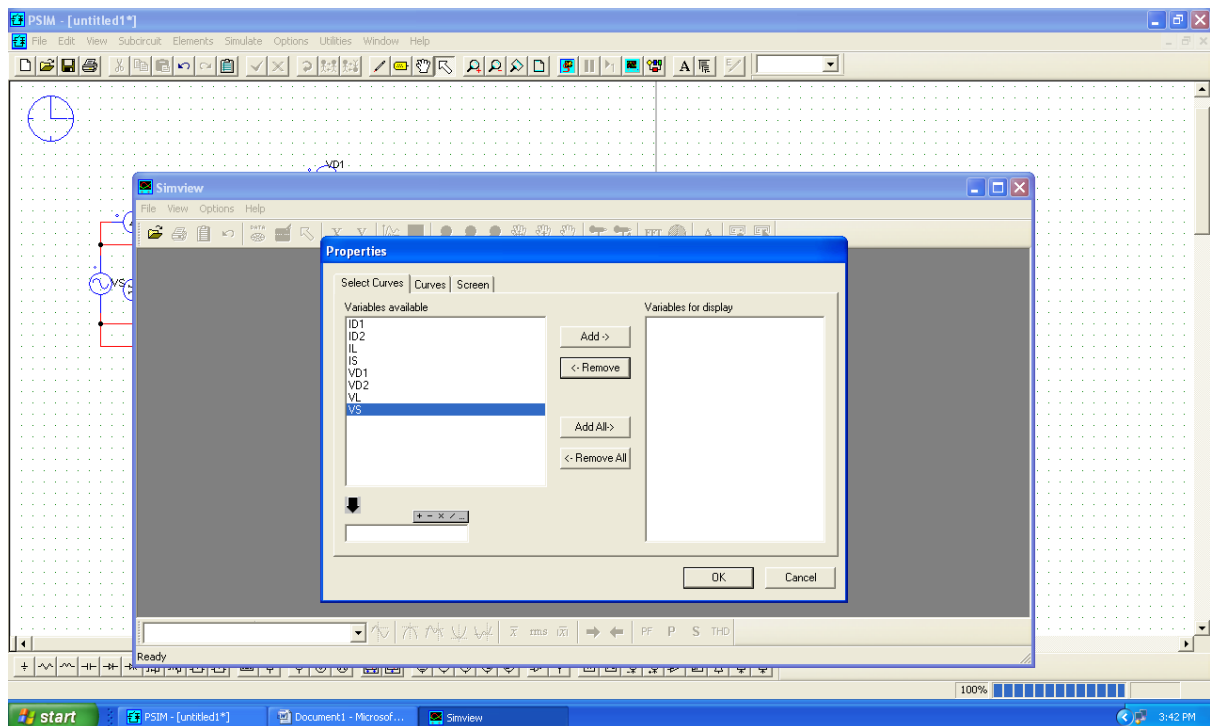

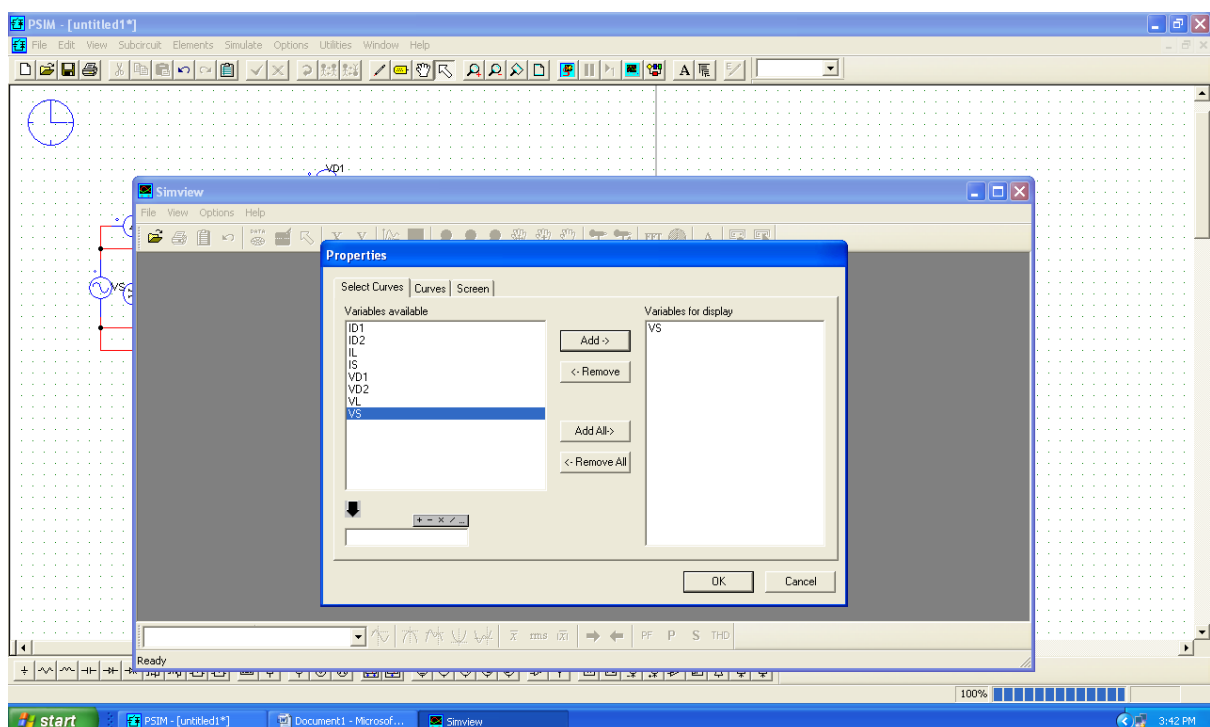
## 14) Select the required element to be measured from the dialogue box







## 15) Source voltage is selected

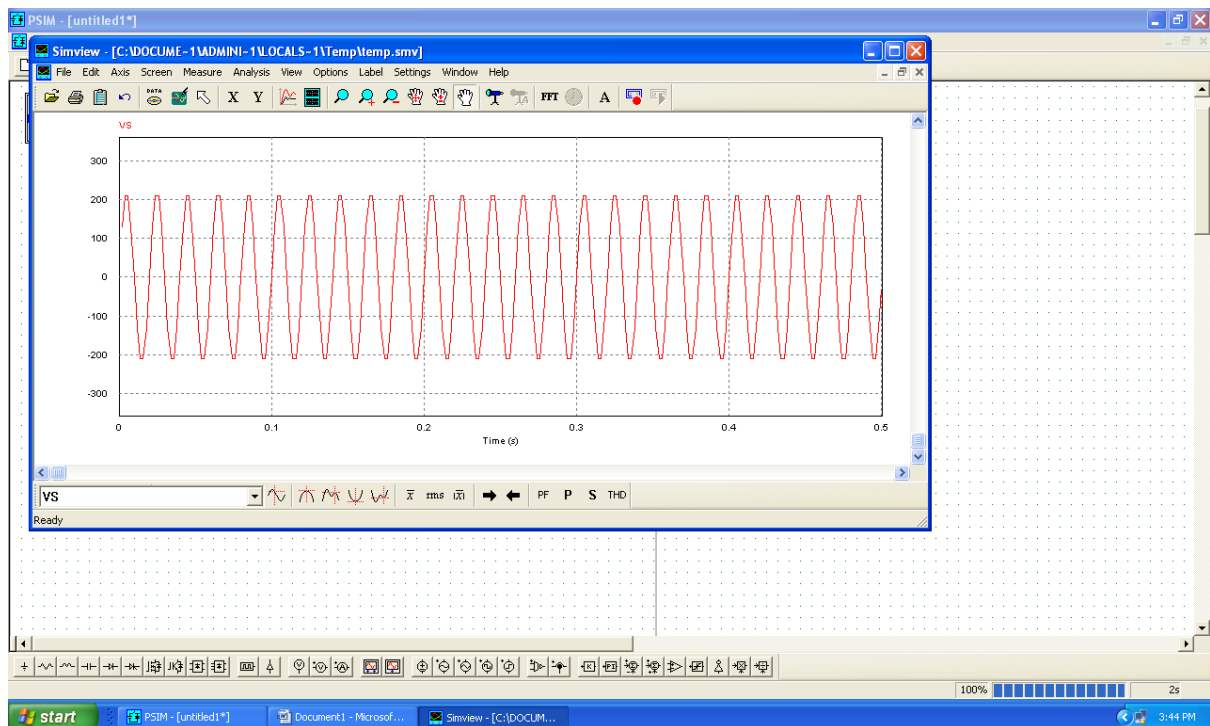


## 16) Addition of other curve

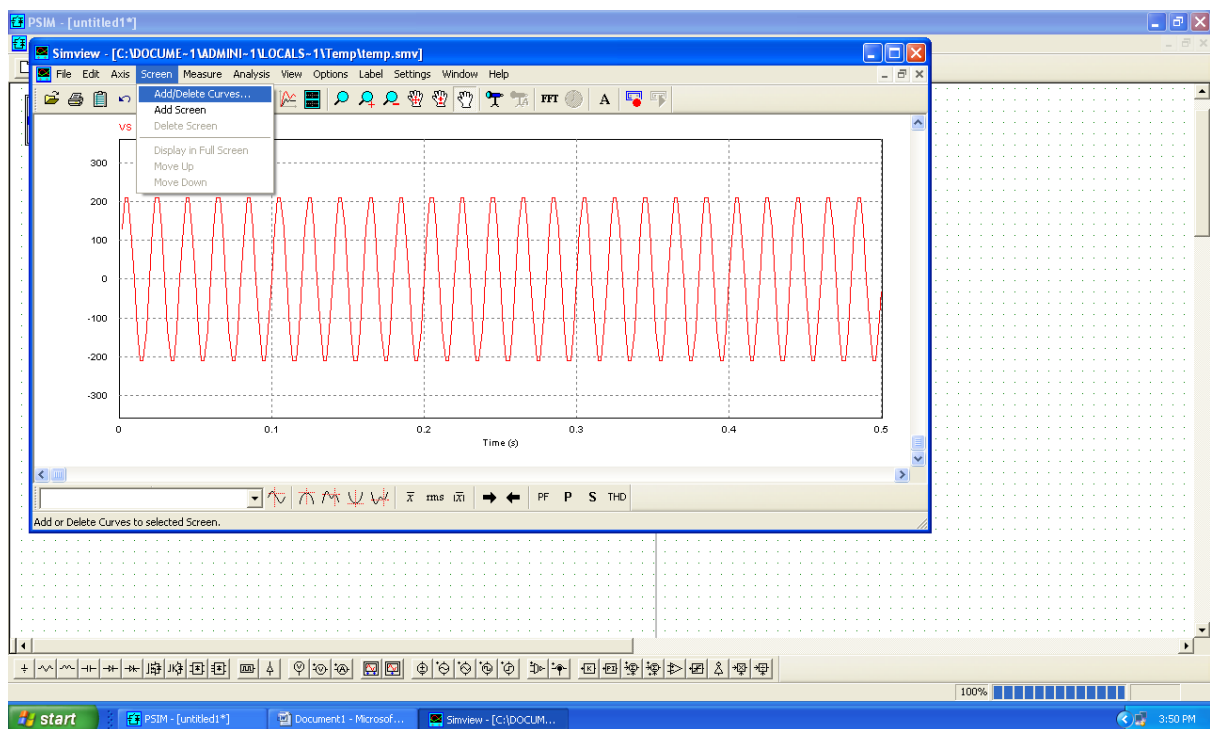

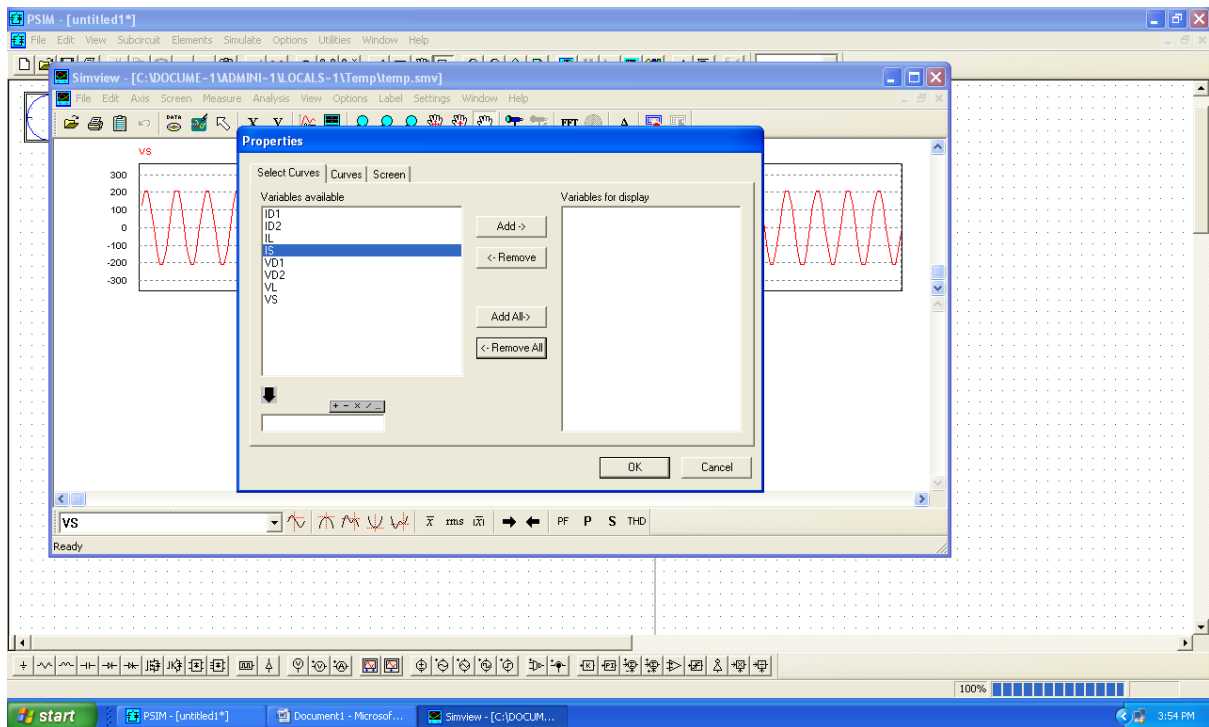

## 17) Voltage and current waveforms

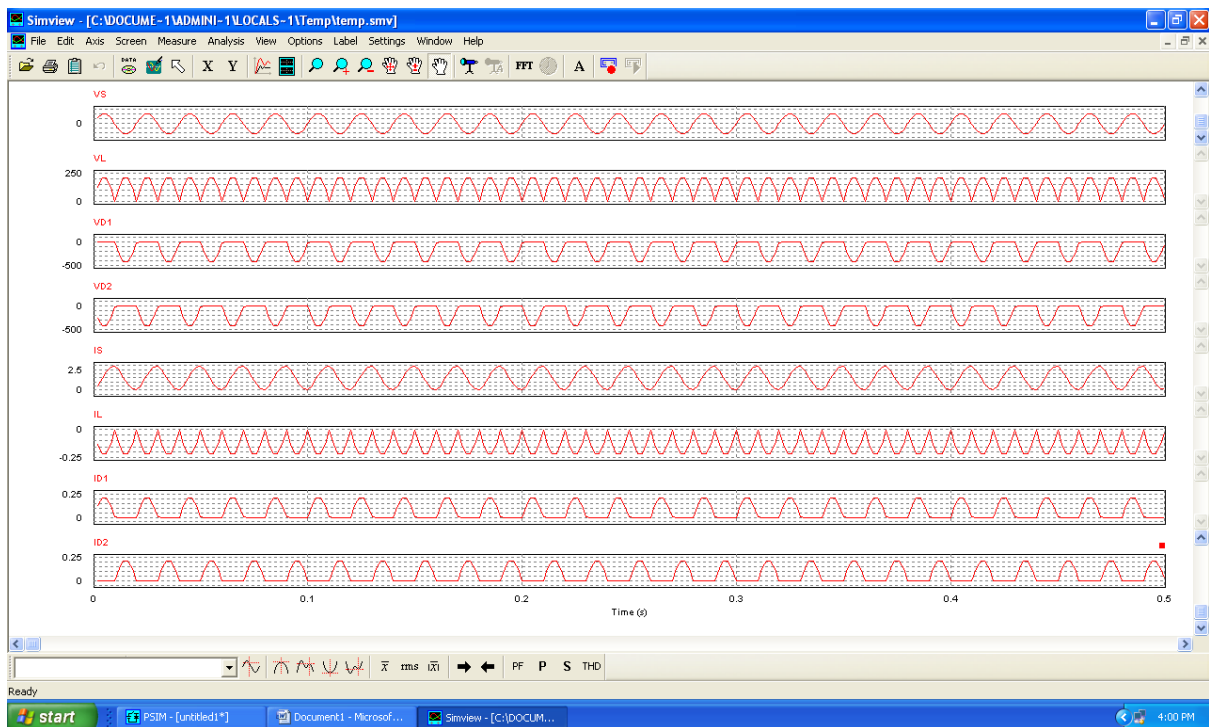





## 2PULSE BRIDGE RECTIFIER WITH R-LOAD

Select the elements as shown above and connect them as shown in below figure with proper labeling

### Circuit diagram

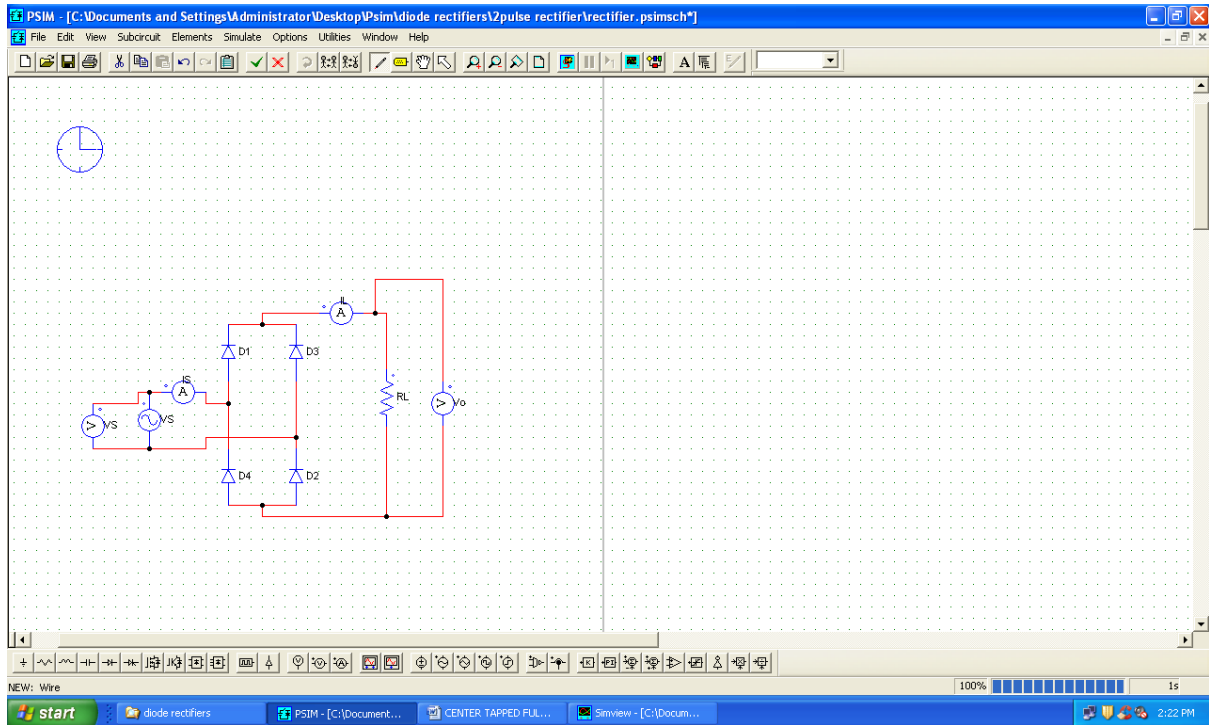

### Voltage and current waveforms

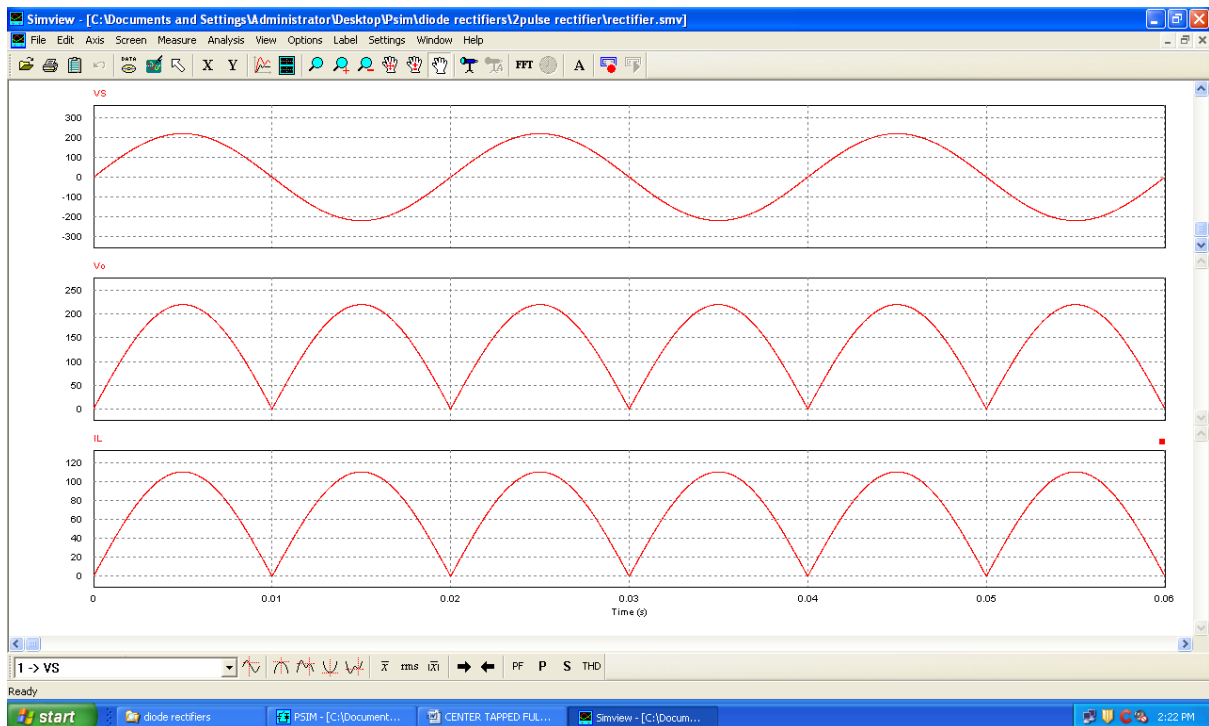





## 2PULSE BRIDGE RECTIFIER WITH RL-LOAD

Select the elements as shown above and connect them as shown in below figure with proper labeling

### Circuit diagram

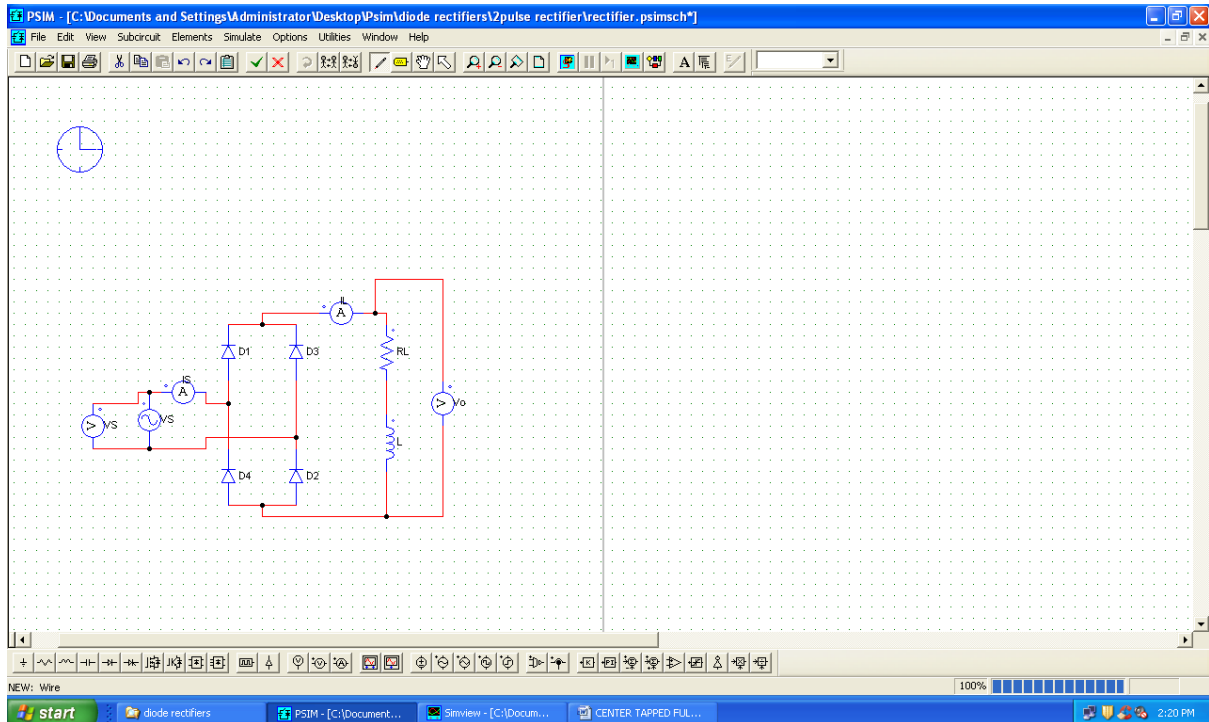

### Voltage and current waveforms

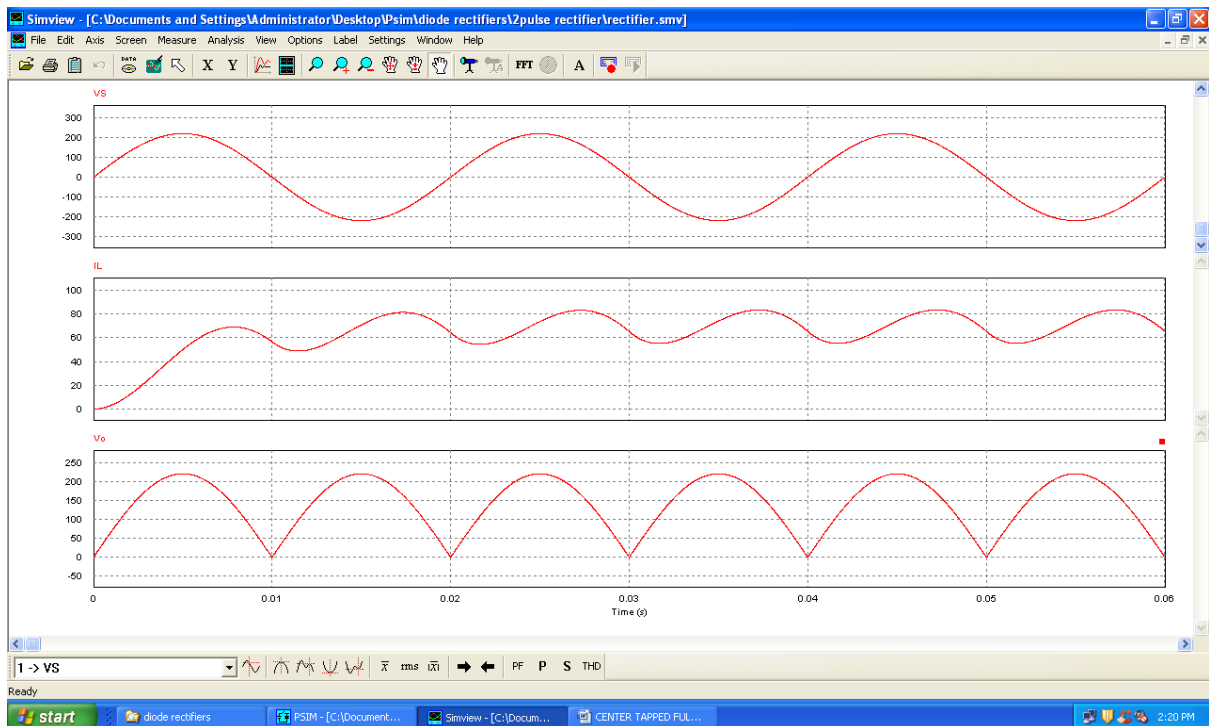





## 2PULSE BRIDGE RECTIFIER WITH RE-LOAD

Select the elements as shown above and connect them as shown in below figure with proper labeling

### Circuit diagram

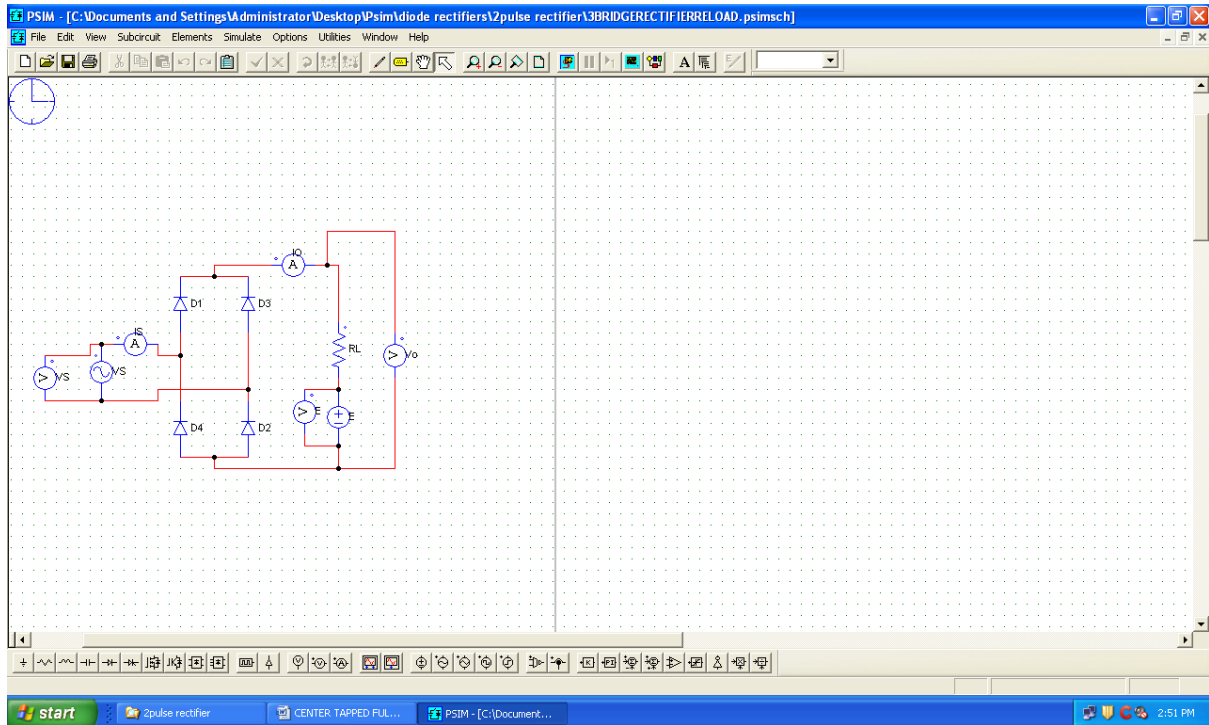

### Voltage and current waveform

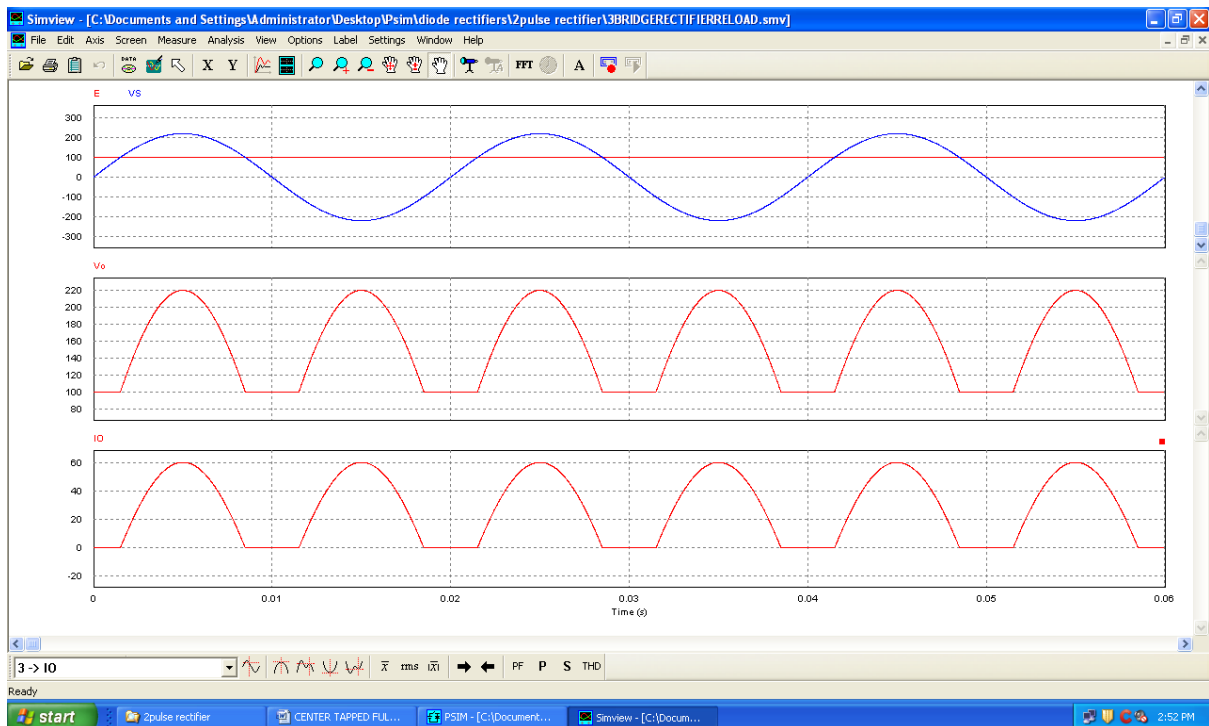





## 2PULSE BRIDGE RECTIFIER WITH RLE-LOAD DISCONTINUOUS CONDUCTION

Select the elements as shown above and connect them as shown in below figure with proper labeling

### Circuit diagram

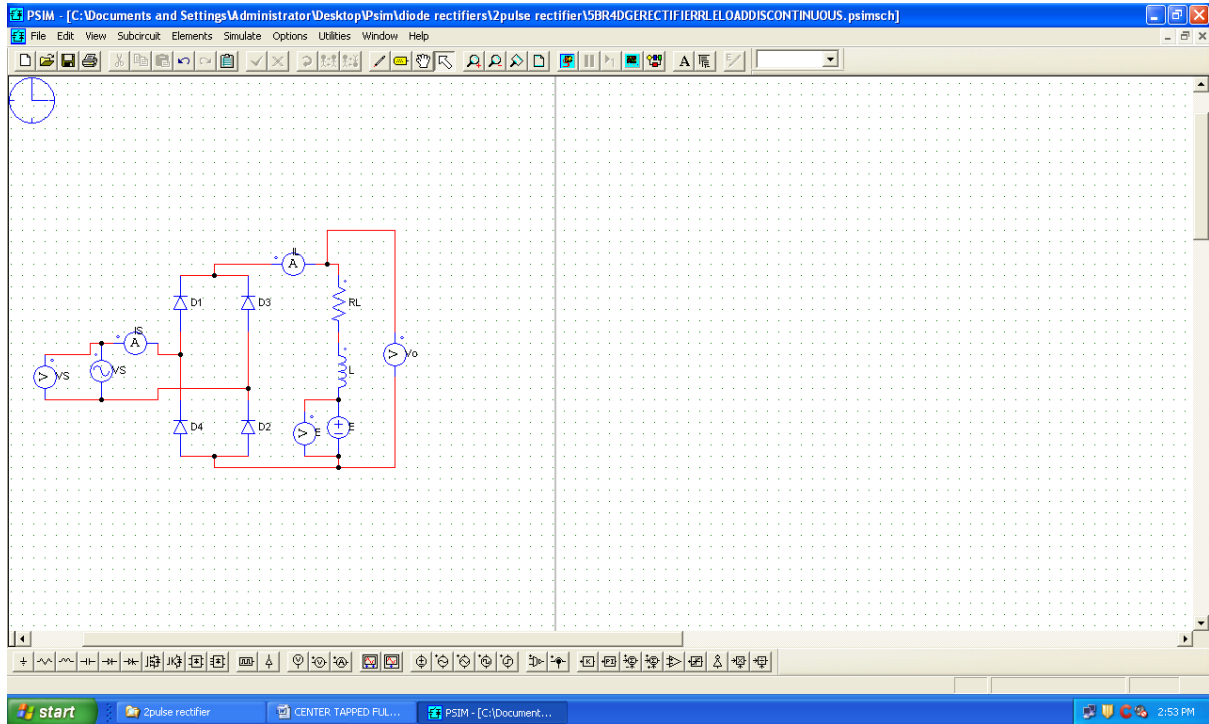

### Voltage and current waveforms

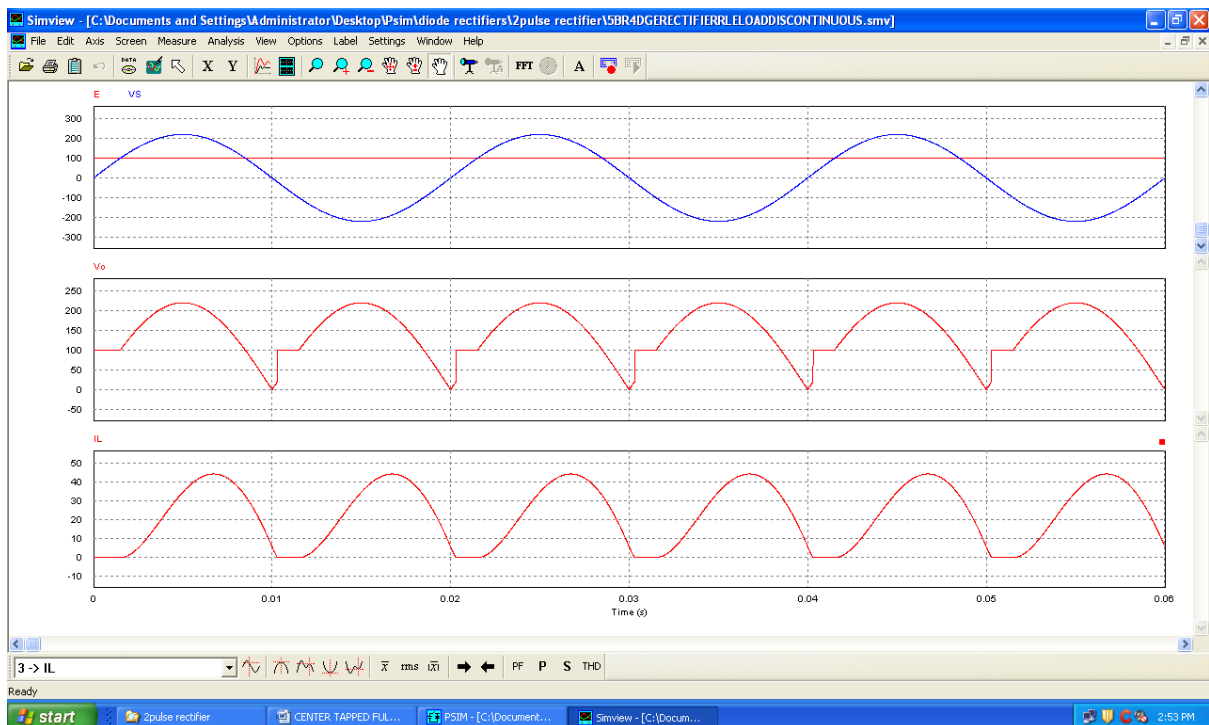





## 2PULSE BRIDGE RECTIFIER WITH RLE-LOAD CONTINUOUS CONDUCTION

Select the elements as shown above and connect them as shown in below figure with proper labeling

### Circuit diagram

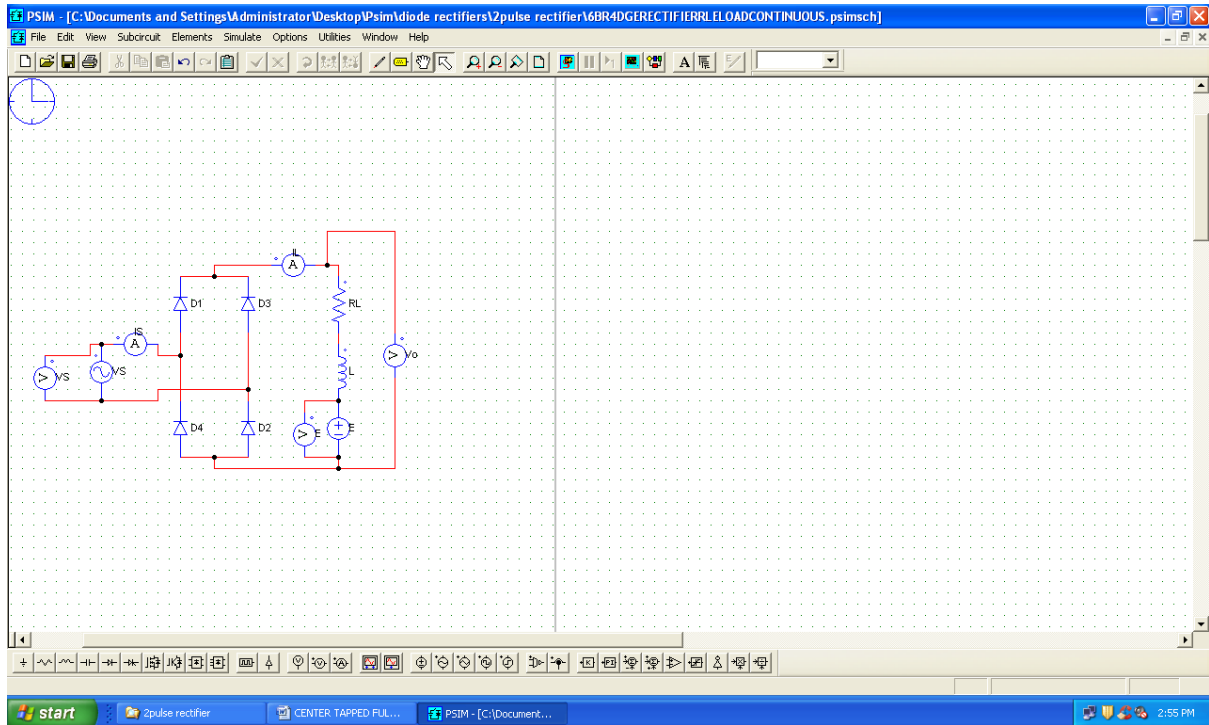

### Voltage and current waveforms

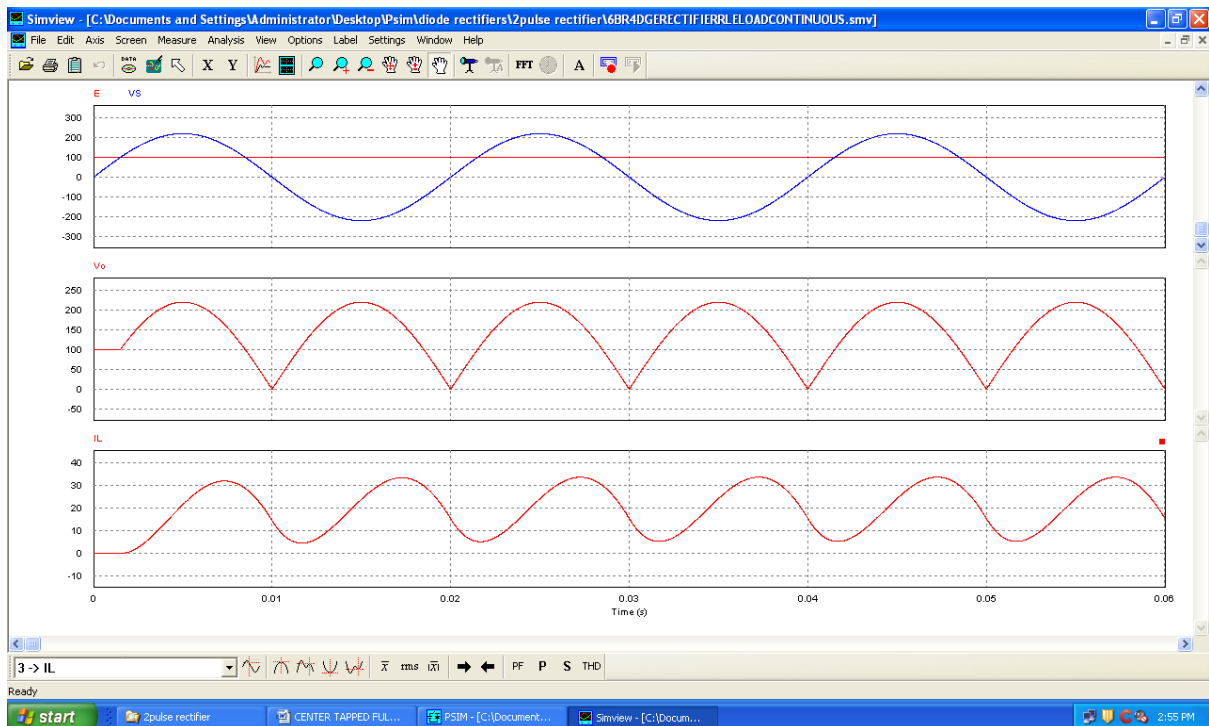







## 2PULSE BRIDGE RECTIFIER WITH RL-LOAD WITH FREE WHEELING DIODE

Select the elements as shown above and connect them as shown in below figure with proper labeling

### Circuit diagram

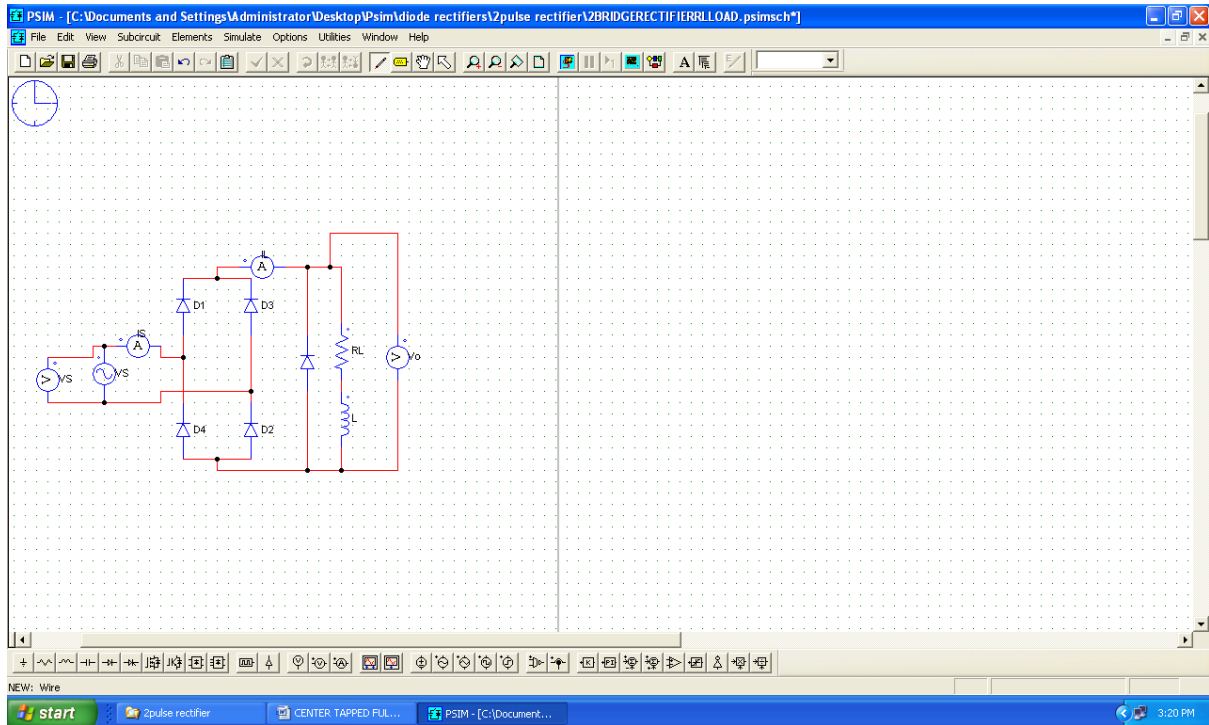

### Voltage and current waveforms

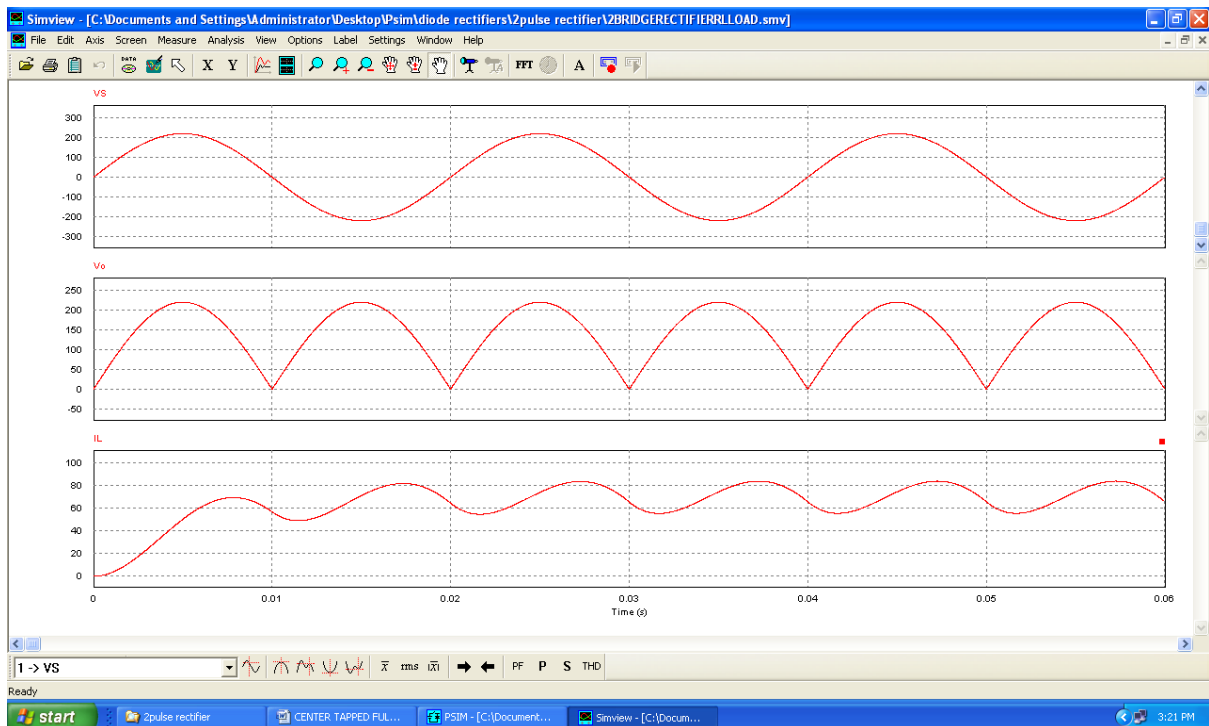





## 2PULSE BRIDGE RECTIFIER WITH RLE-LOAD WITH FREE WHEELING DIODE

Select the elements as shown above and connect them as shown in below figure with proper labeling

### Circuit diagram

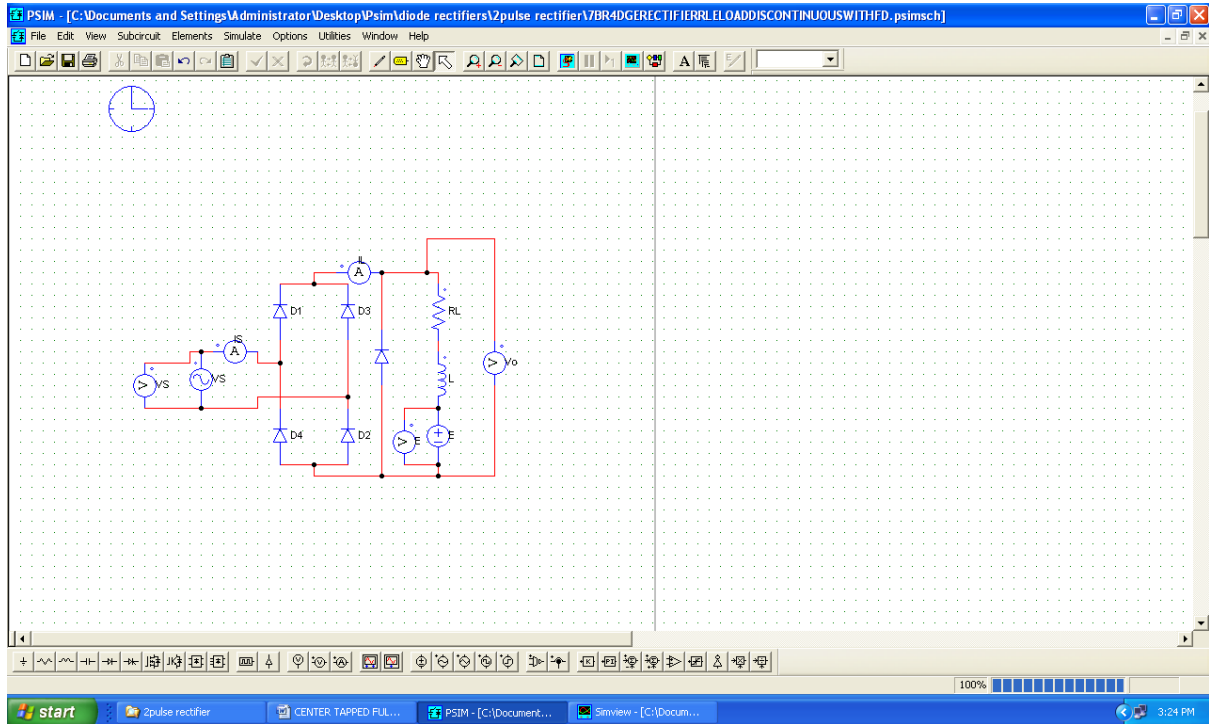



### Voltage and current waveforms

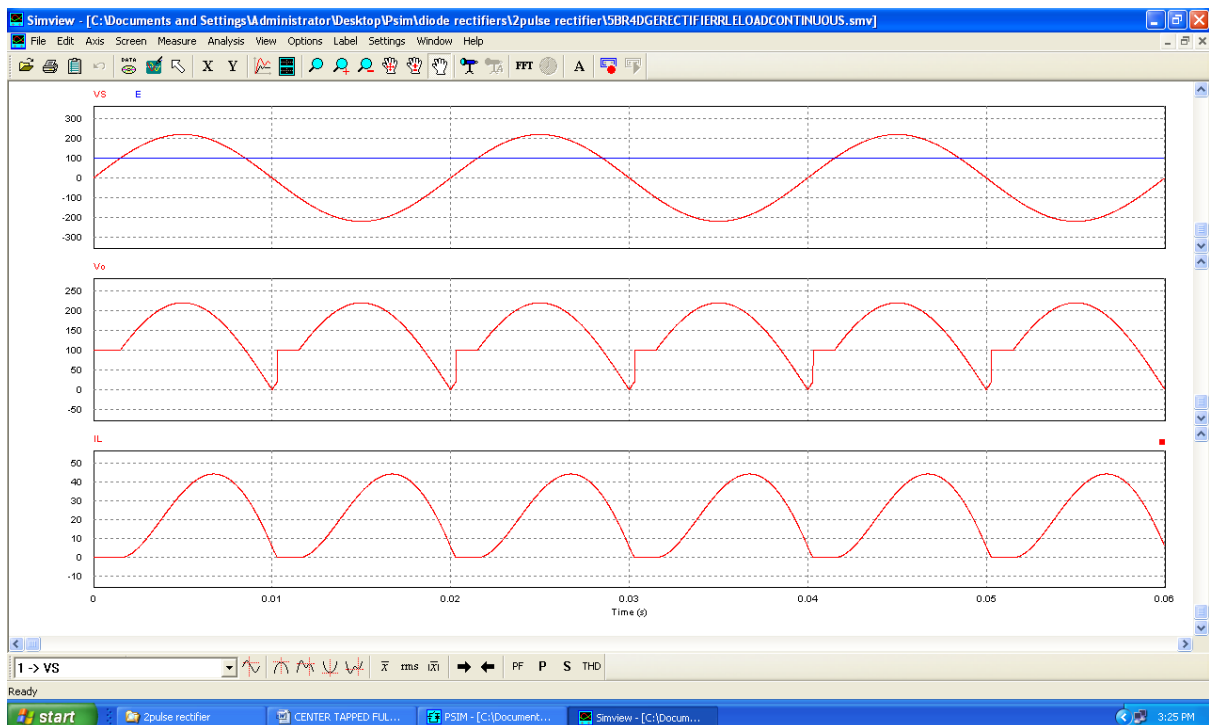




## Controlled rectifier

Select the thyristor

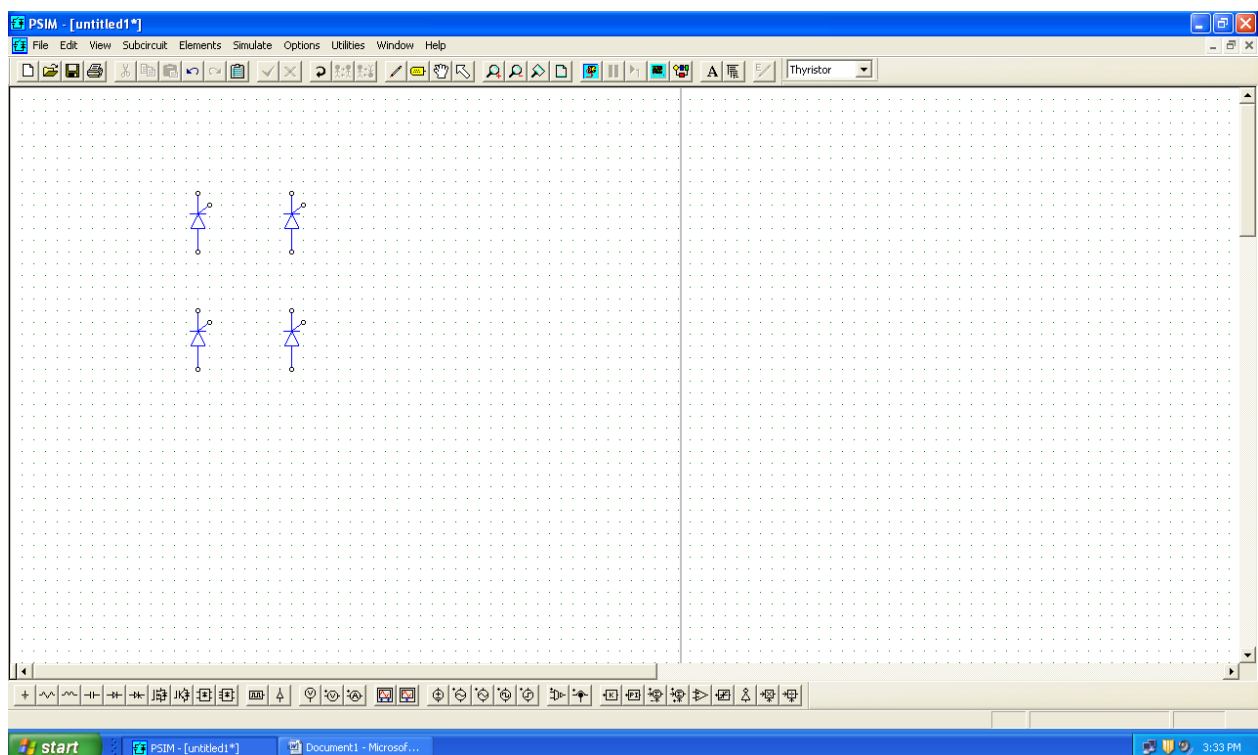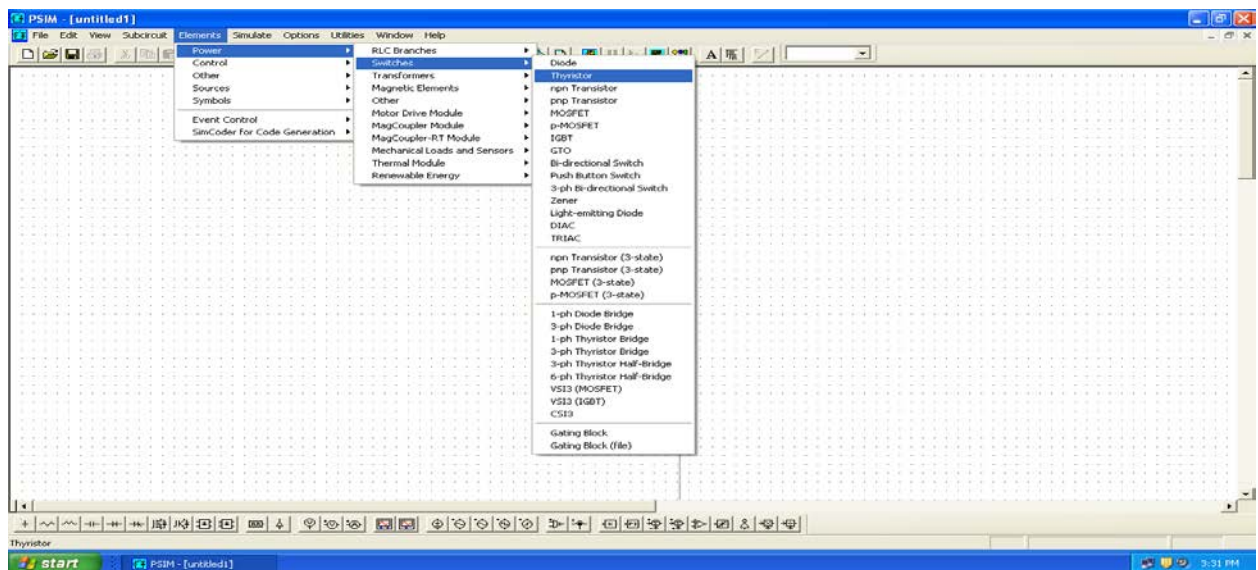



Select the source

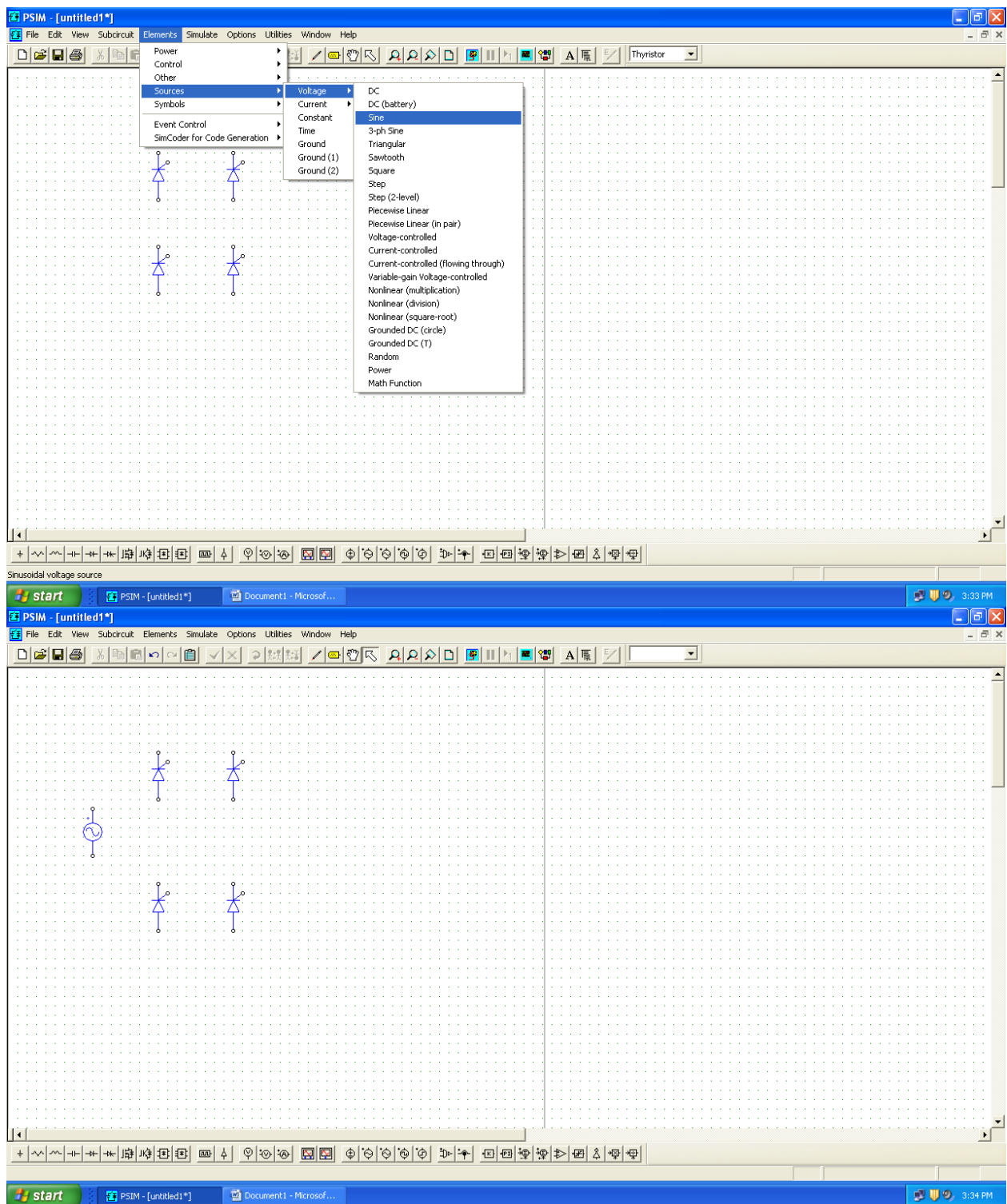



## Select the gating block

The screenshot displays the P-SIM software interface. The 'Elements' menu is open, and the 'Switches' sub-menu is selected. The 'Gating Block' option is highlighted in the list. The circuit diagram on the left shows a power source connected to two thyristors. The bottom status bar indicates the time is 3:35 PM.

PSIM - [untitled1\*]

File Edit View Subcircuit Elements Simulate Options Utilities Window Help

Power

- Control
- Other
- Sources
- Symbols

Event Control

SimCoder for Code Generation

RLC Branches

- Switches
- Transformers
- Magnetic Elements
- Other
- Motor Drive Module
- MagCoupler Module
- MagCoupler-RT Module
- Mechanical Loads and Sensors
- Thermal Module
- Renewable Energy

Diode

- Thyristor
- npn Transistor
- pnp Transistor
- MOSFET
- p-MOSFET
- IGBT
- GTO
- Bi-directional Switch
- Push Button Switch
- 3-ph Bi-directional Switch
- Zener
- Light-emitting Diode
- DIAC
- TRIAC

npn Transistor (3-state)

pnp Transistor (3-state)

MOSFET (3-state)

p-MOSFET (3-state)

1-ph Diode Bridge

3-ph Diode Bridge

1-ph Thyristor Bridge

3-ph Thyristor Bridge

3-ph Thyristor Half-Bridge

6-ph Thyristor Half-Bridge

VS13 (MOSFET)

VS13 (IGBT)

CS13

Gating Block

Gating Block (file)

Gating block for switch(es)

start PSIM - [untitled1\*] Document1 - Microsof...

PSIM - [untitled1\*]

File Edit View Subcircuit Elements Simulate Options Utilities Window Help


Gating Block

start PSIM - [untitled1\*] Document1 - Microsof...

3:35 PM




## Select the RL load

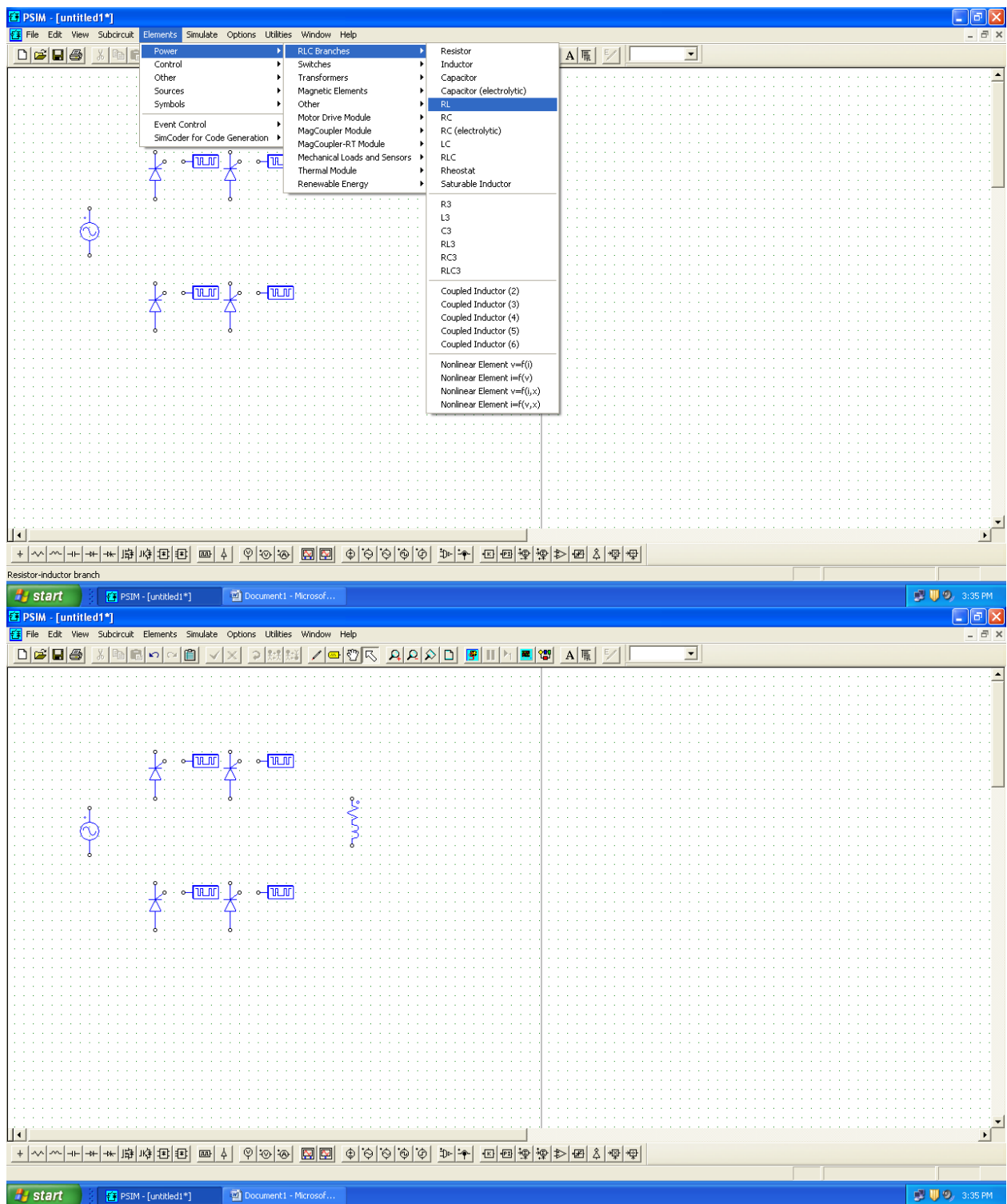




Select the volt meter

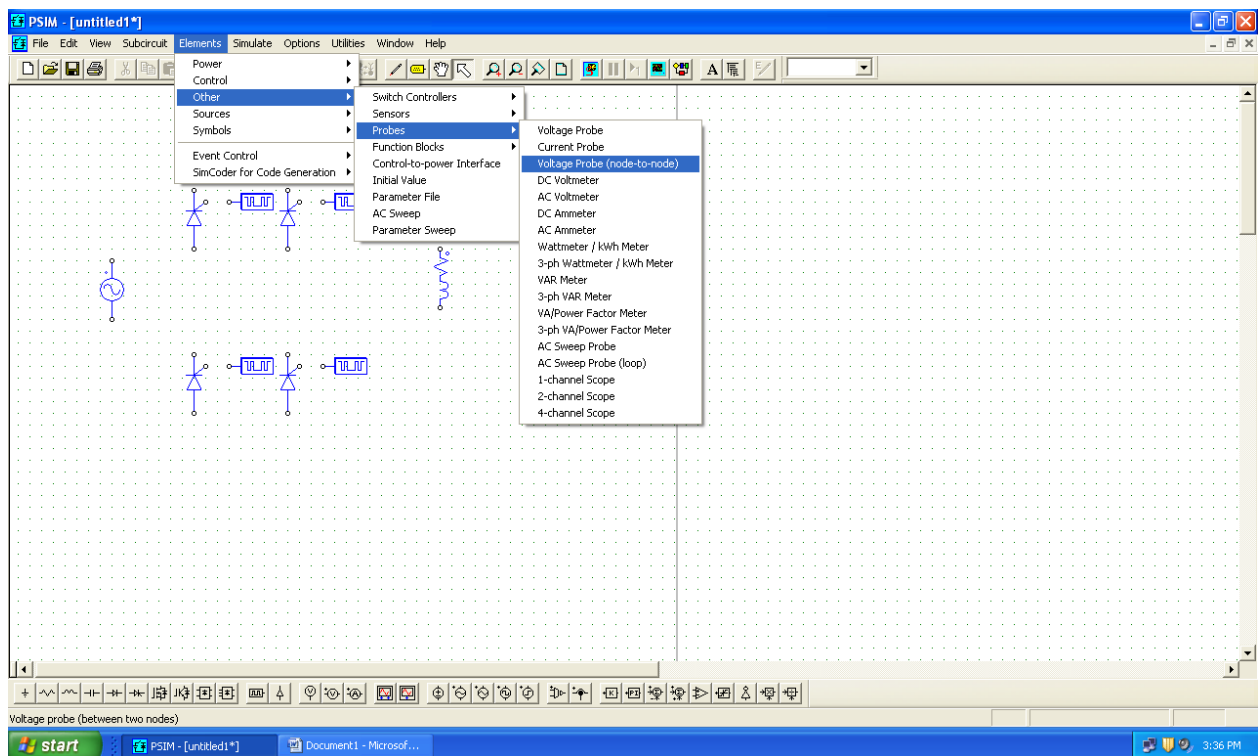


Select the ammeter

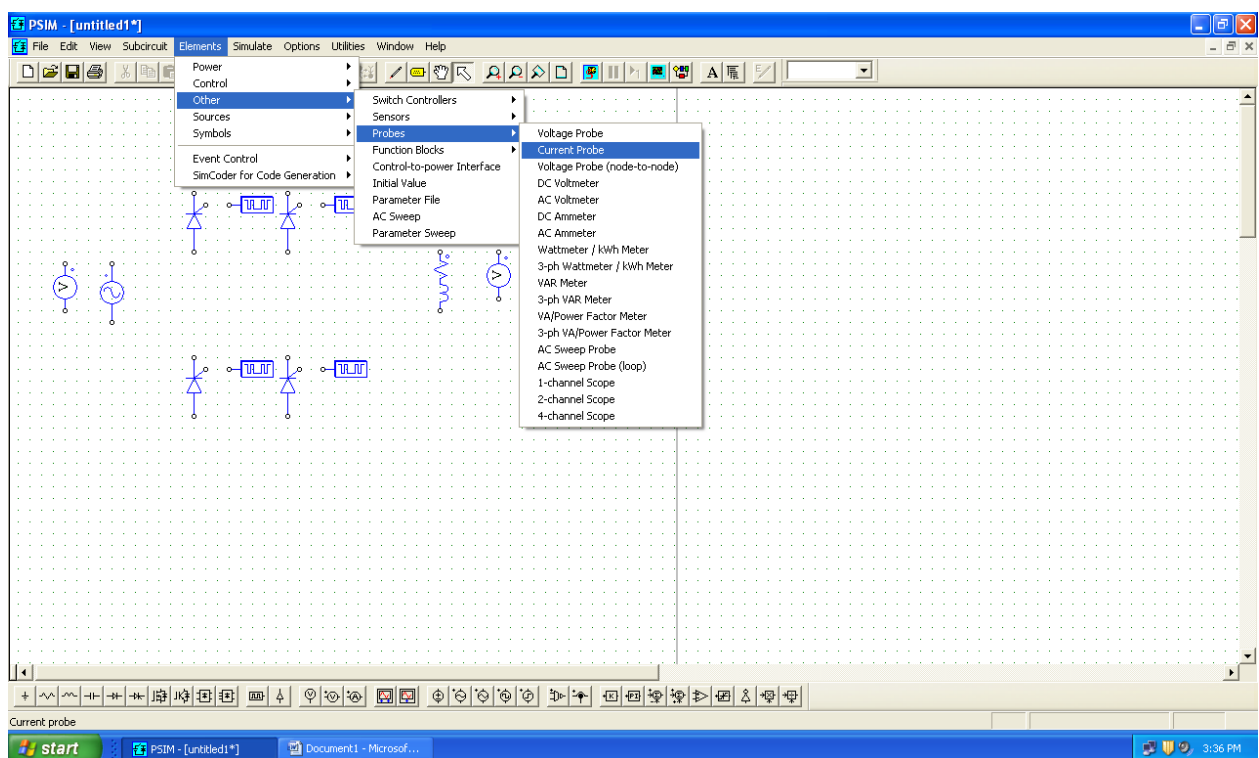




Connect the circuit using wiring tool

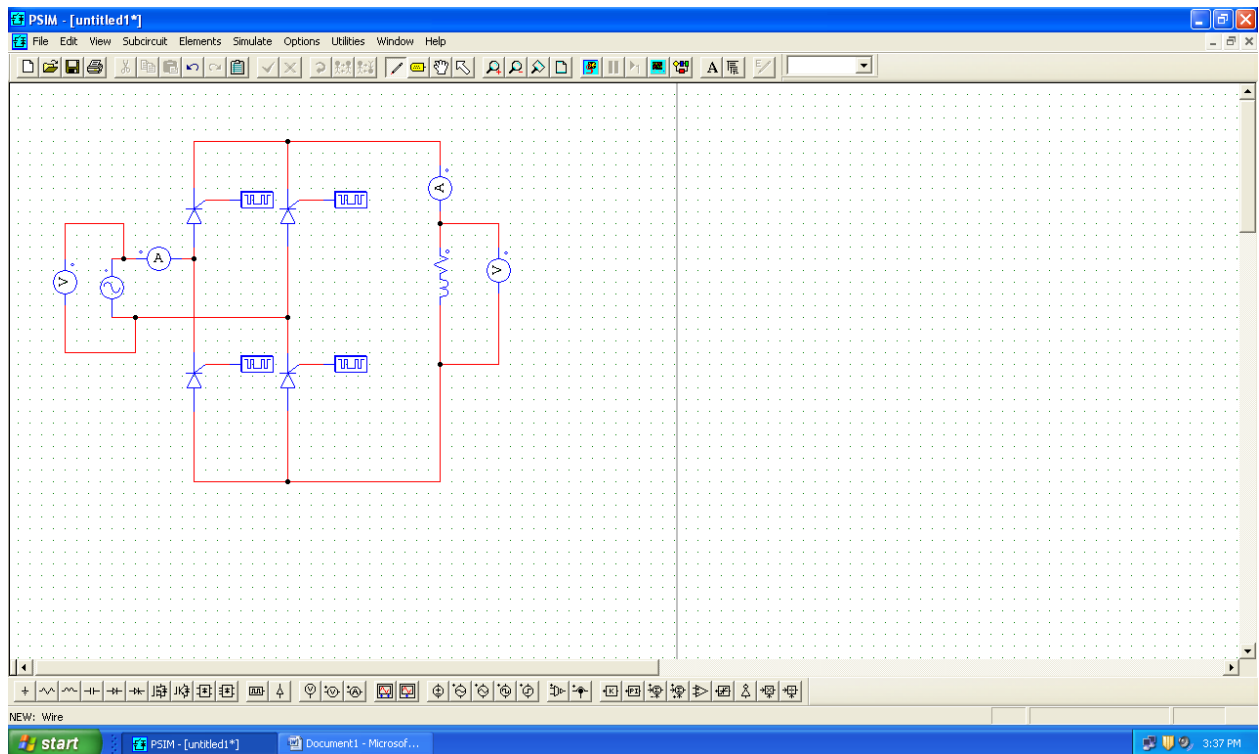



Give the proper label


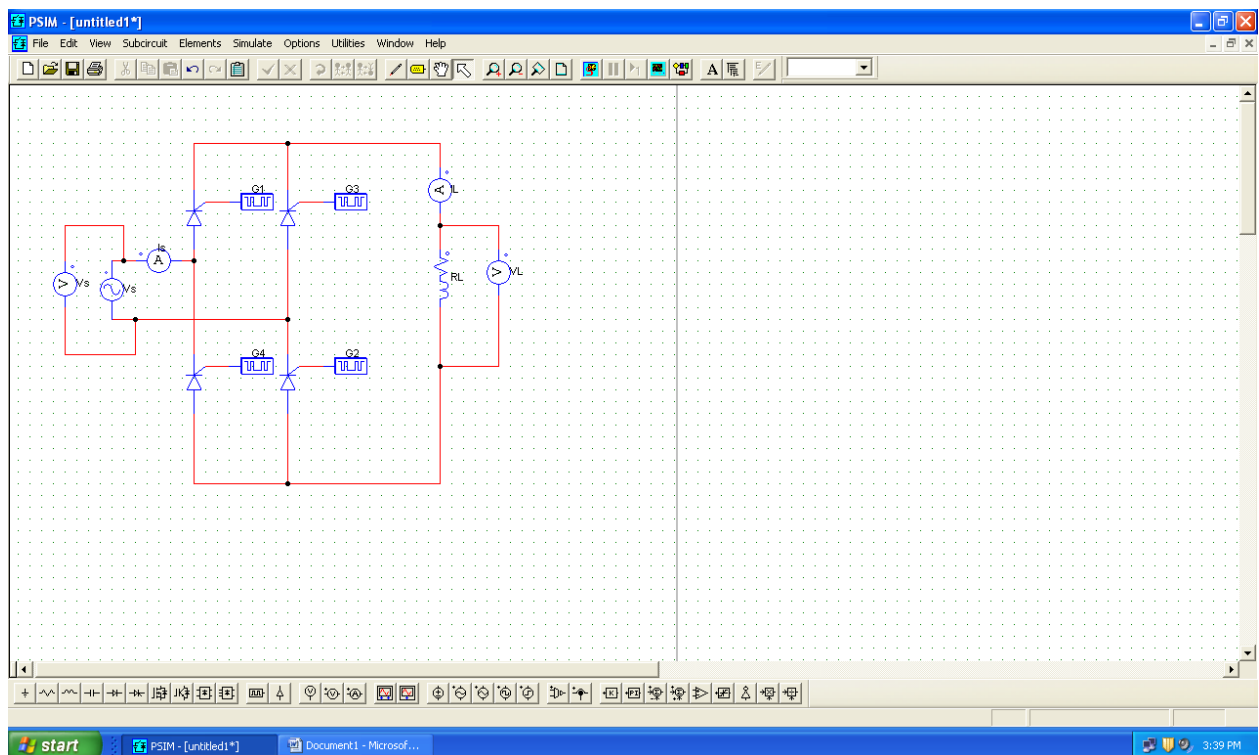






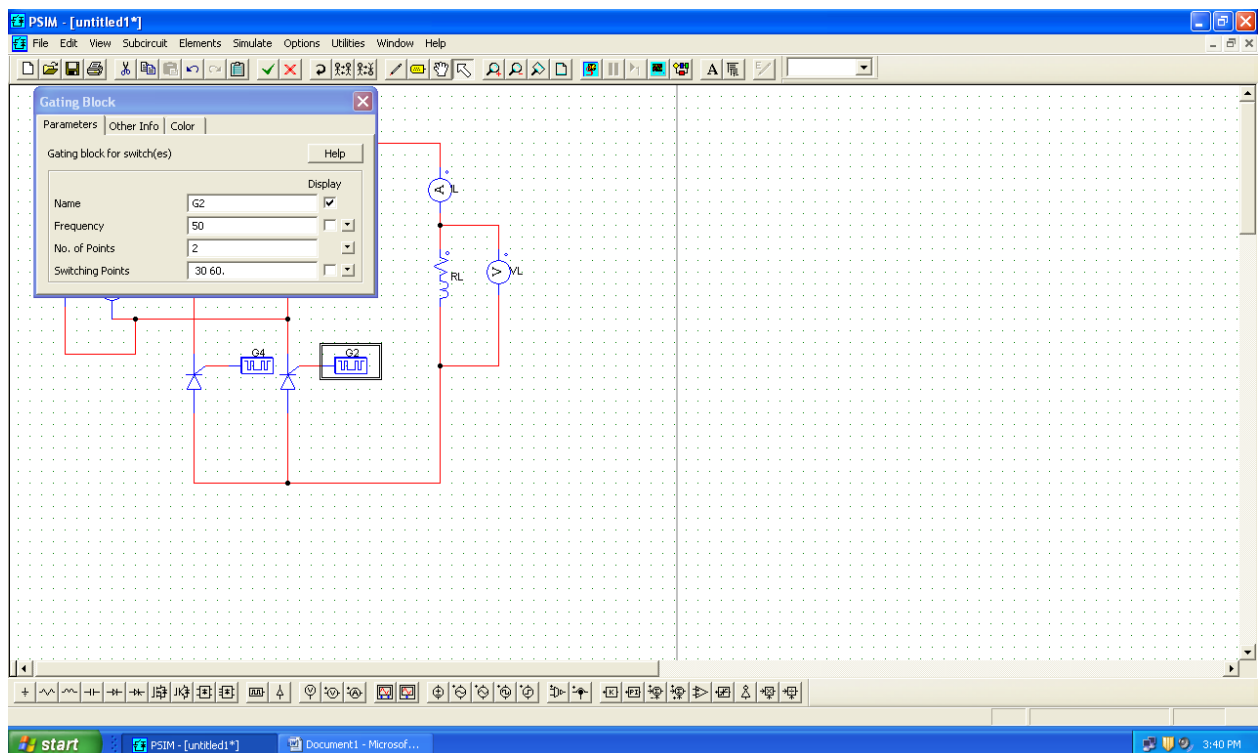
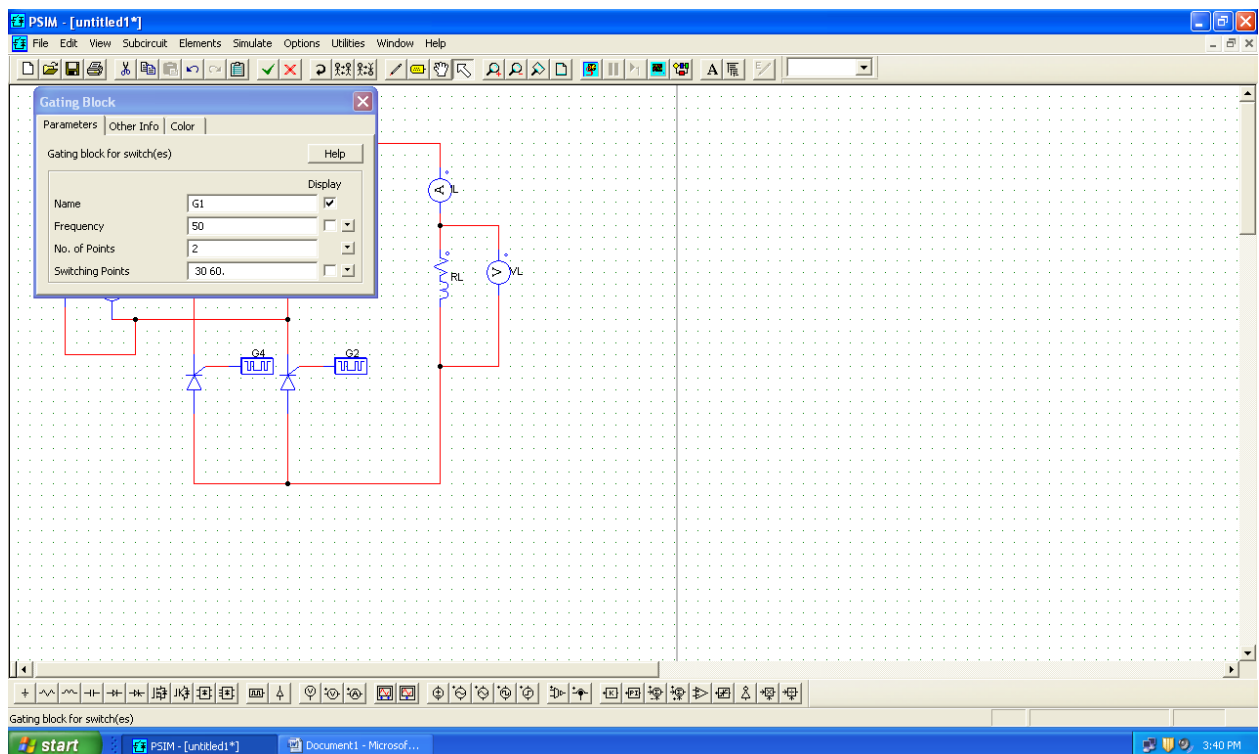
Give the gating block parameters as shown below



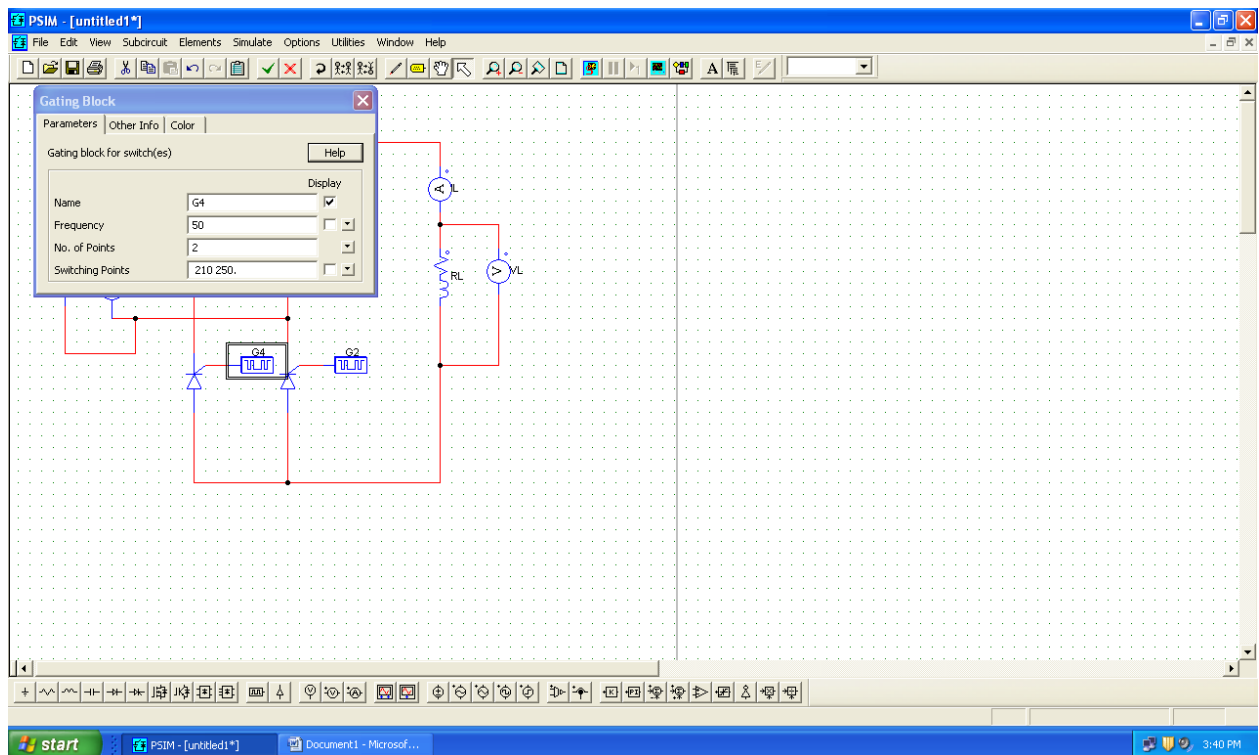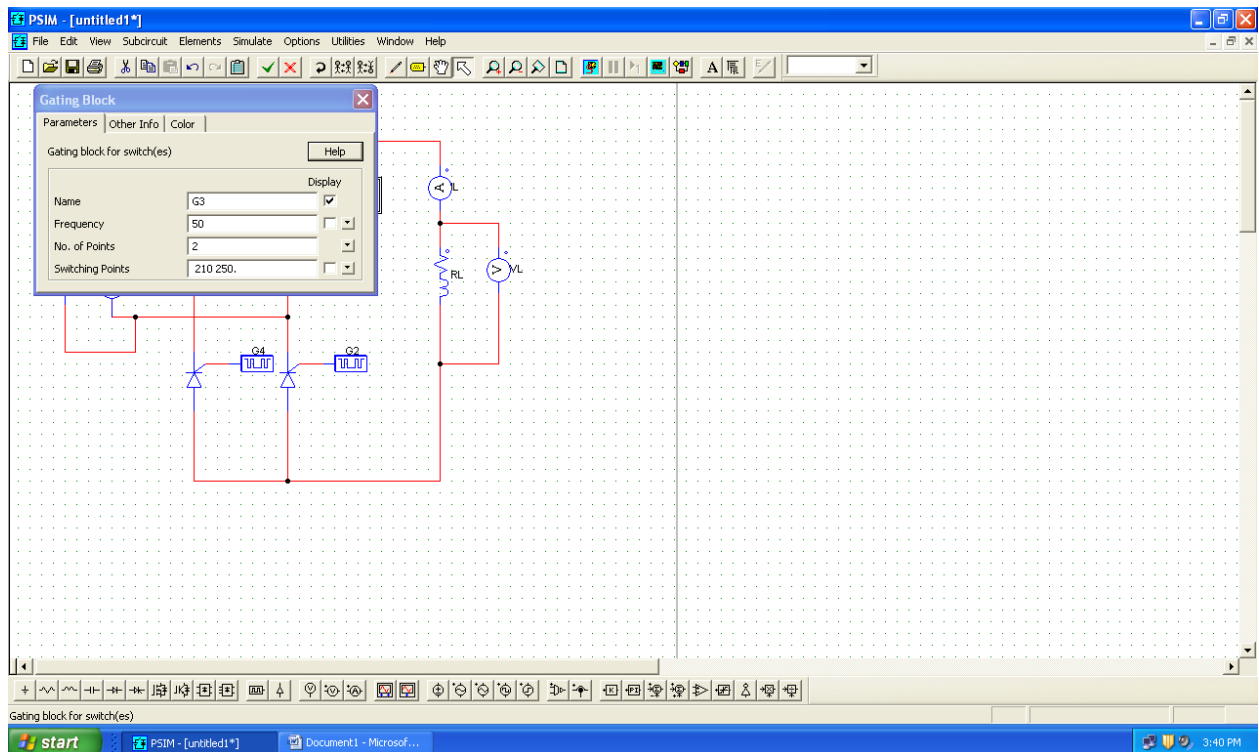




## Select the simulation control

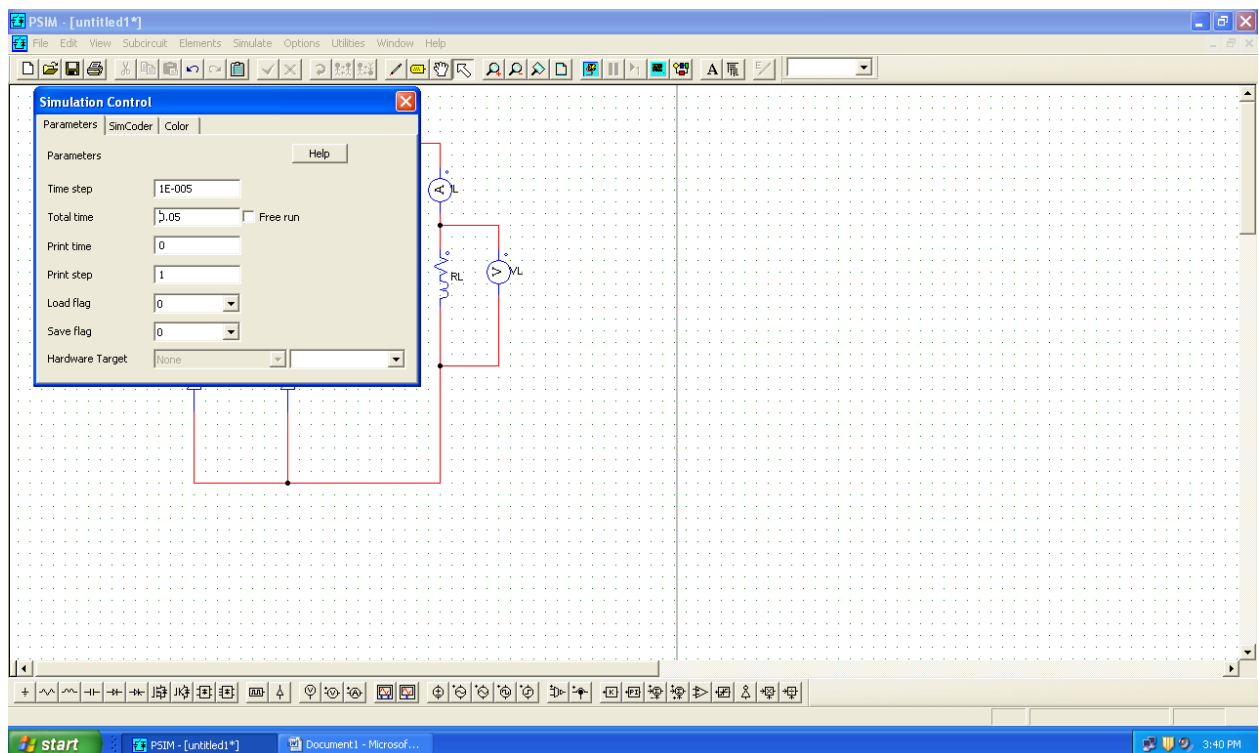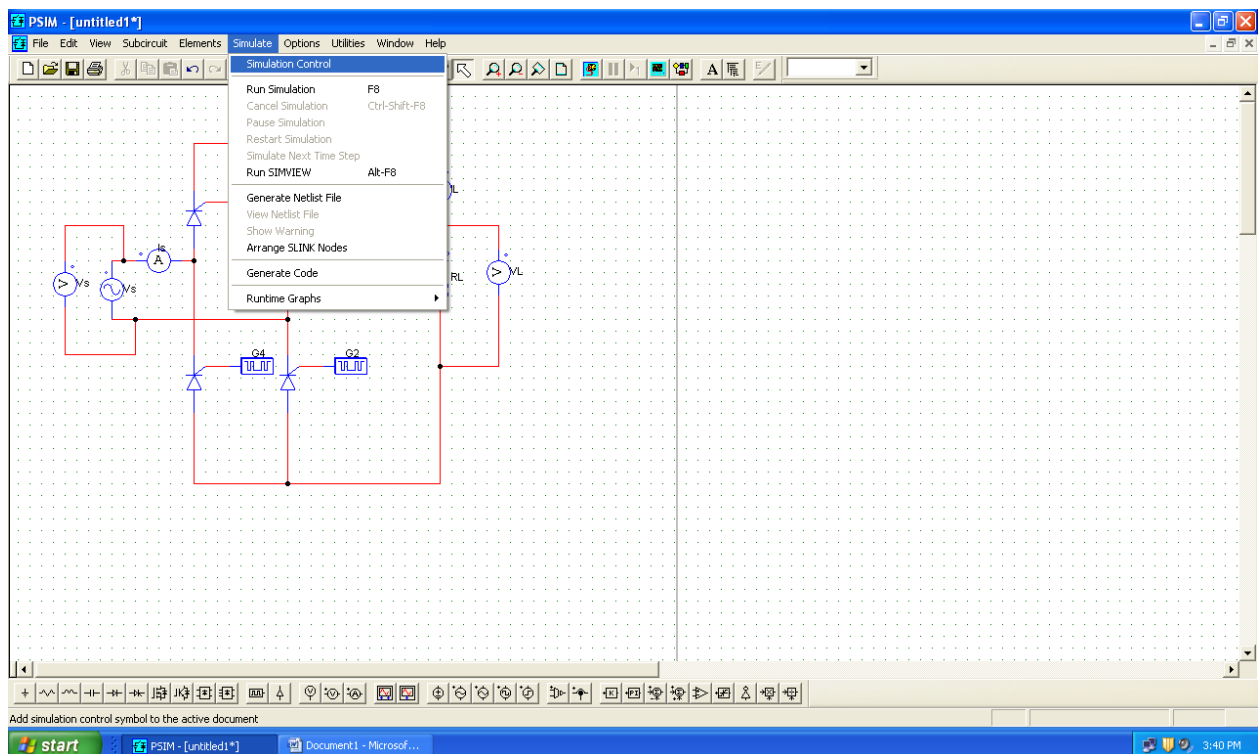




## Output waveforms

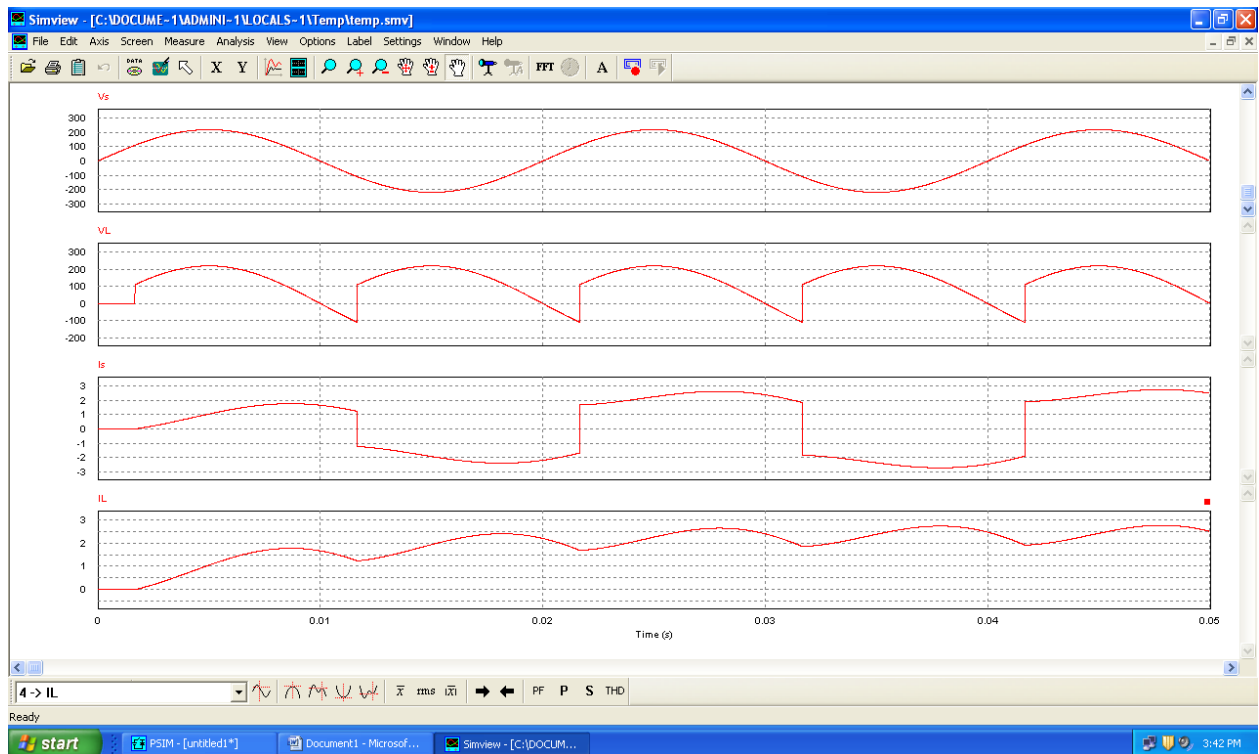




## RECTIFIER WITH FREE WHEELING DIODE

### Circuit diagram

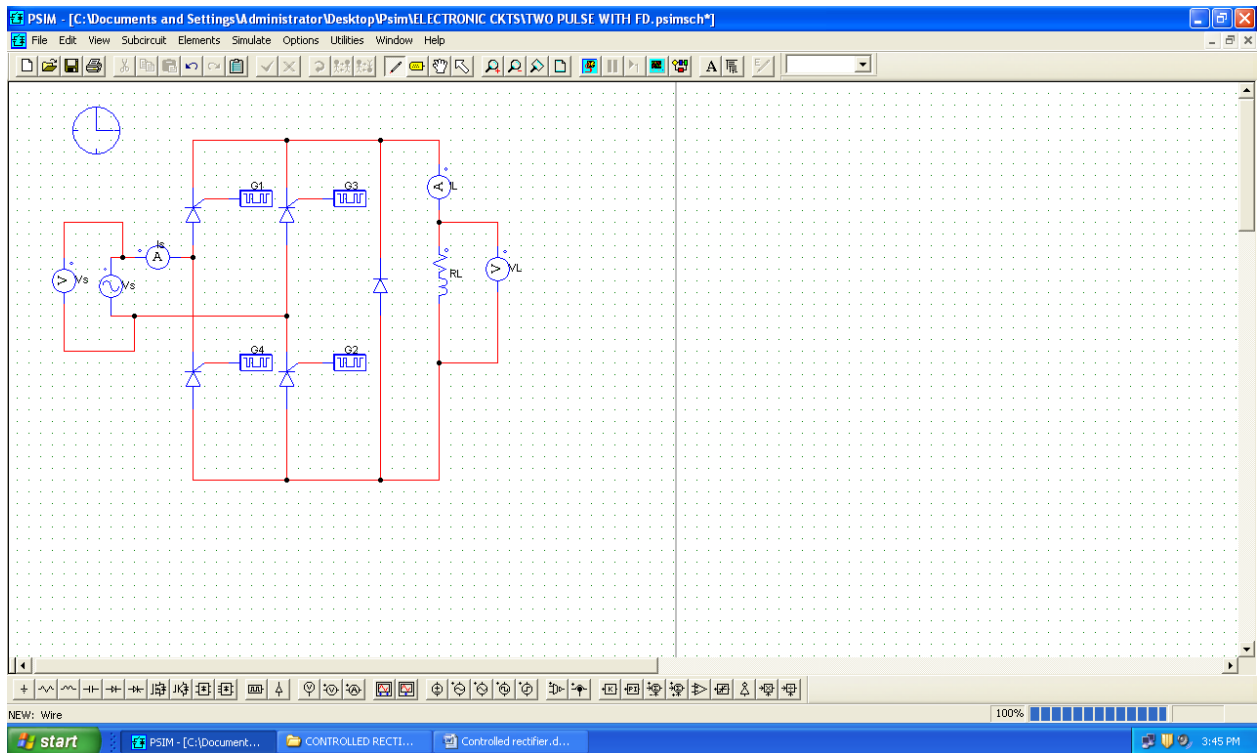


### Output waveforms

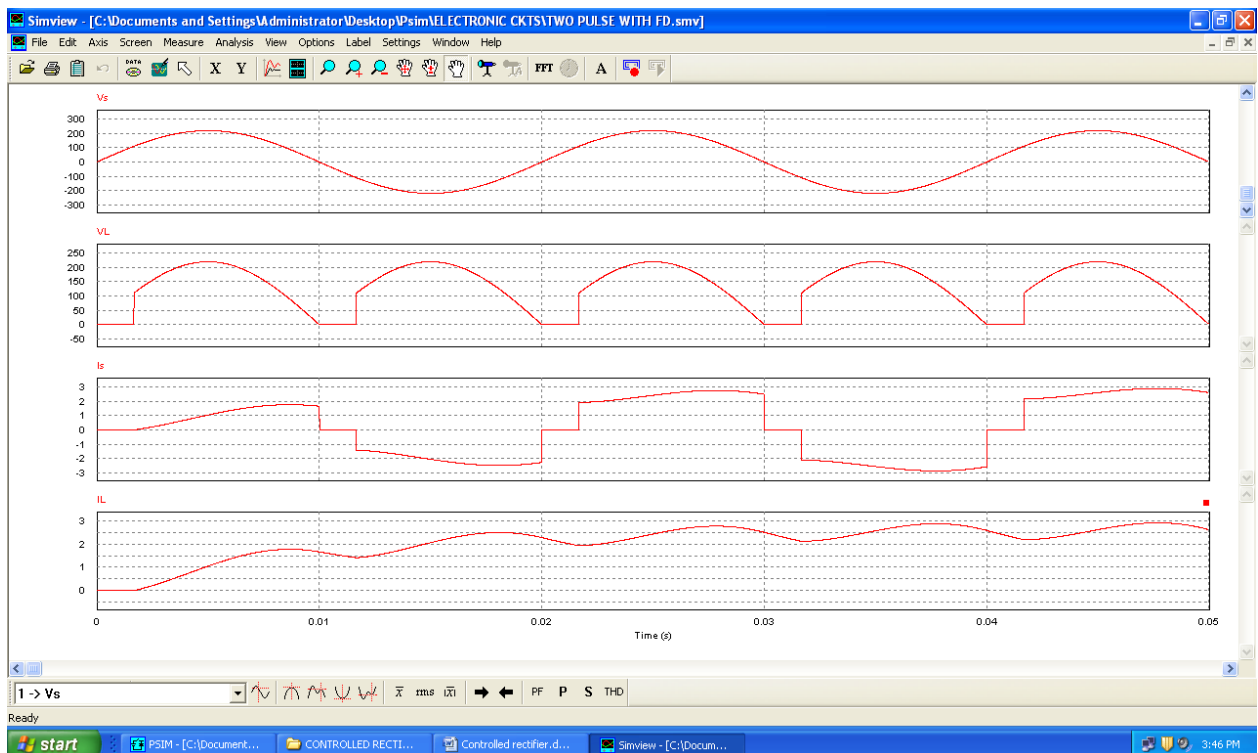




## THREE PULSE RECTIFIER

SELECTION OF 3-PHASE AC VOLTAGE SOURCE:

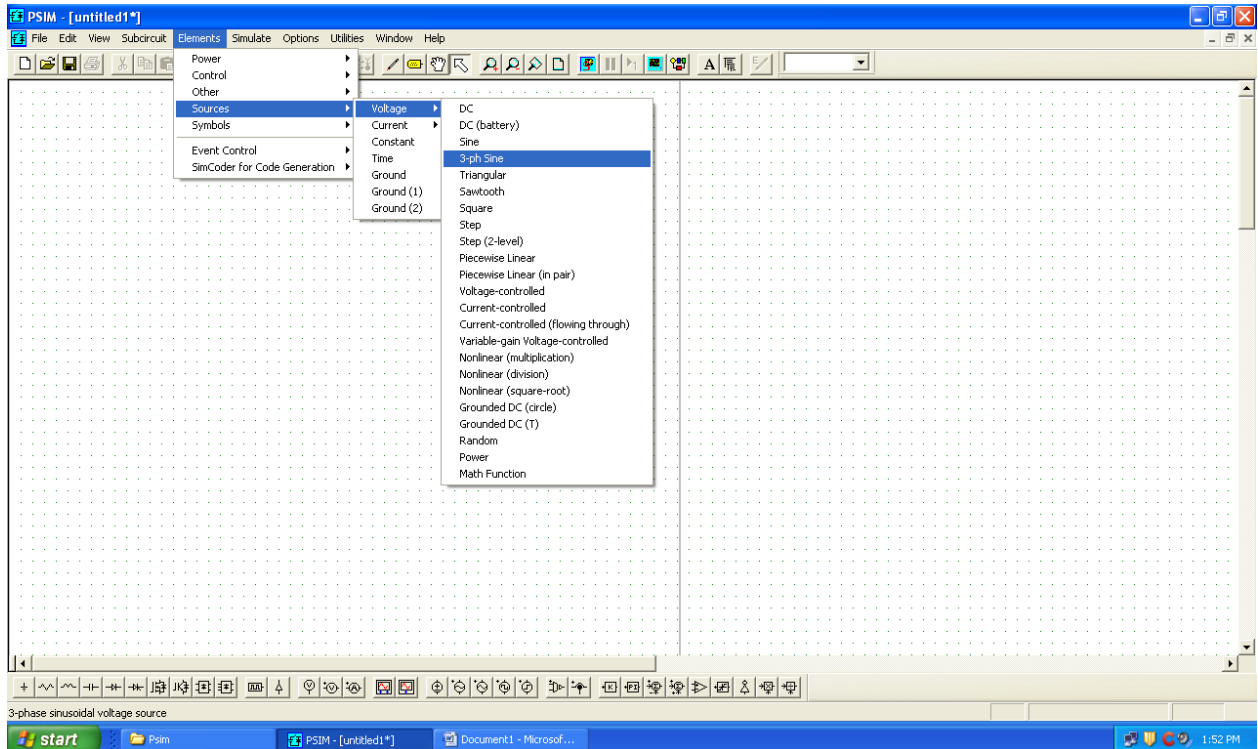


SELECTION OF DIODE:

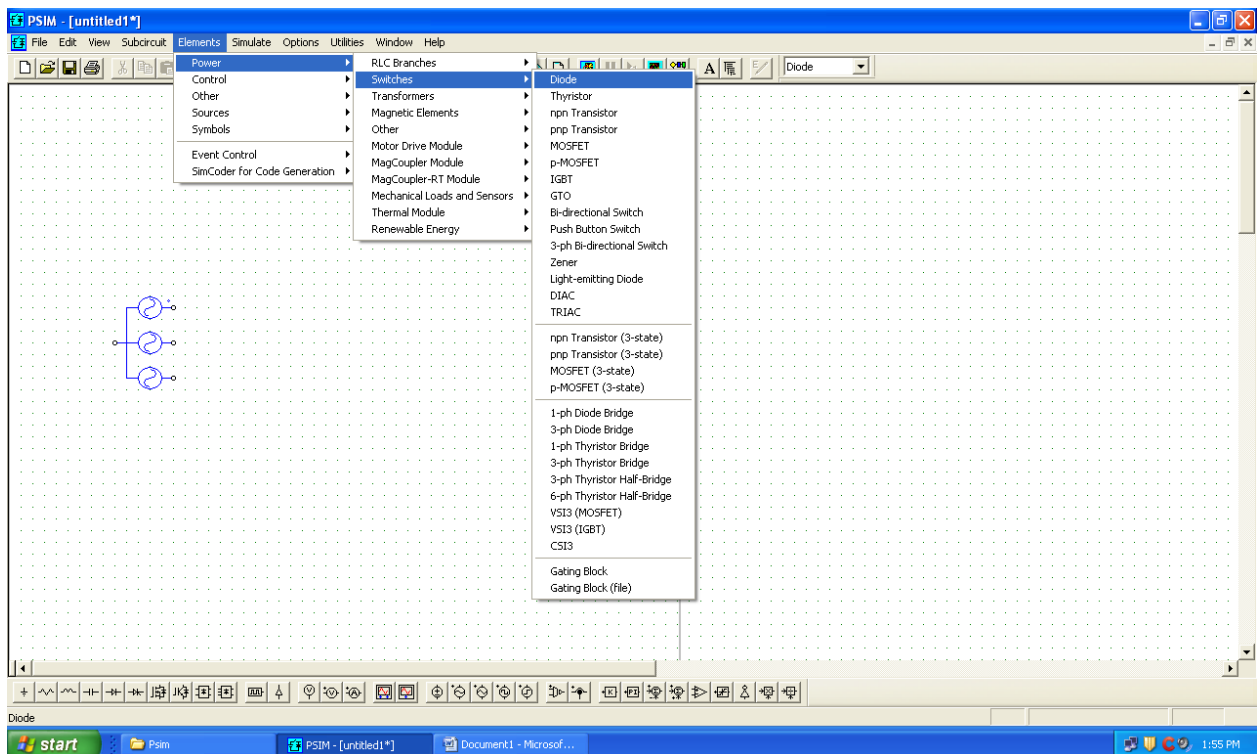




## SELECTION OF THE LOAD RESISTANCE:

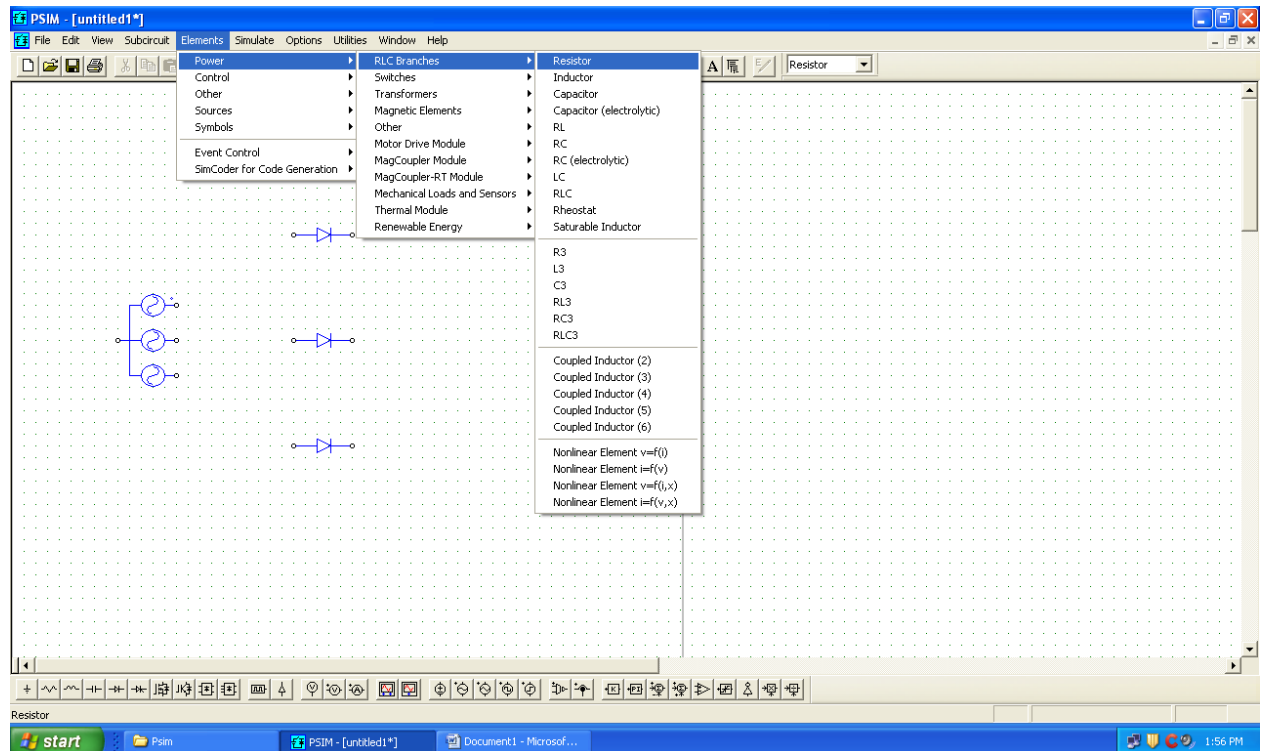


## SELECTION OF VOLTMETERS:

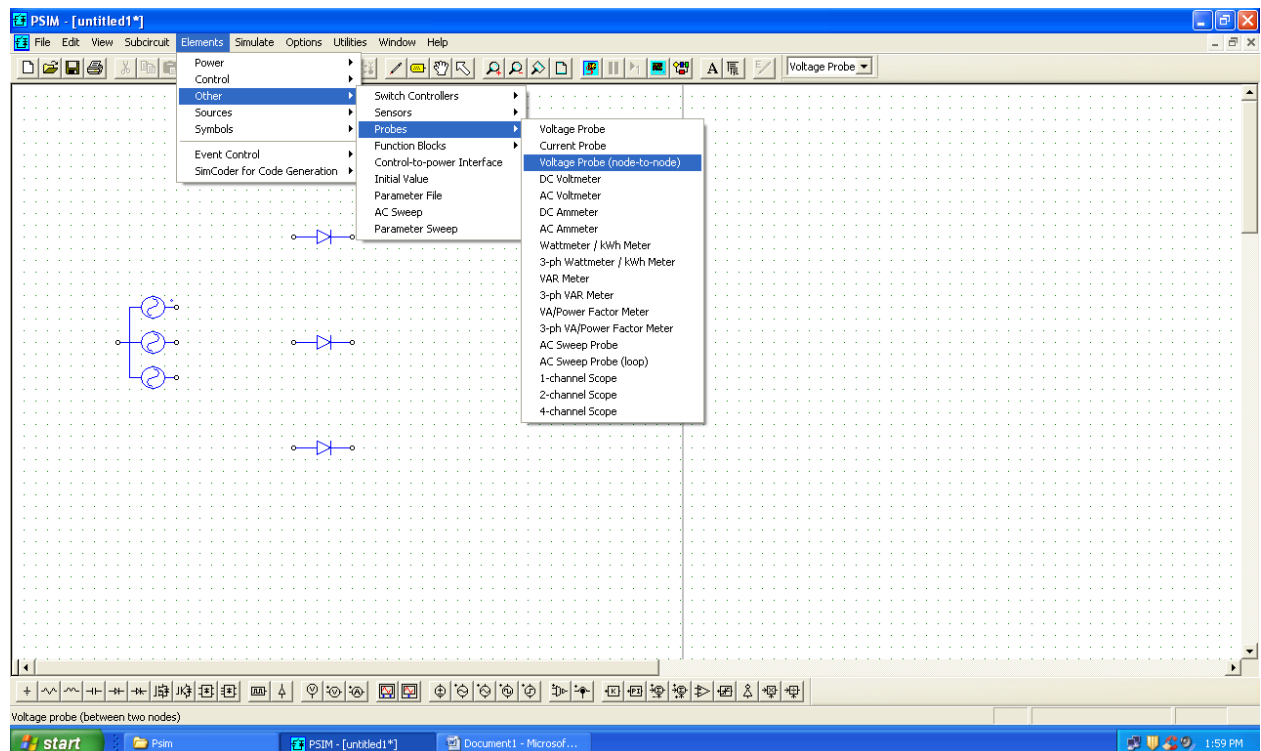




## SELECTION OF AMMETERS:

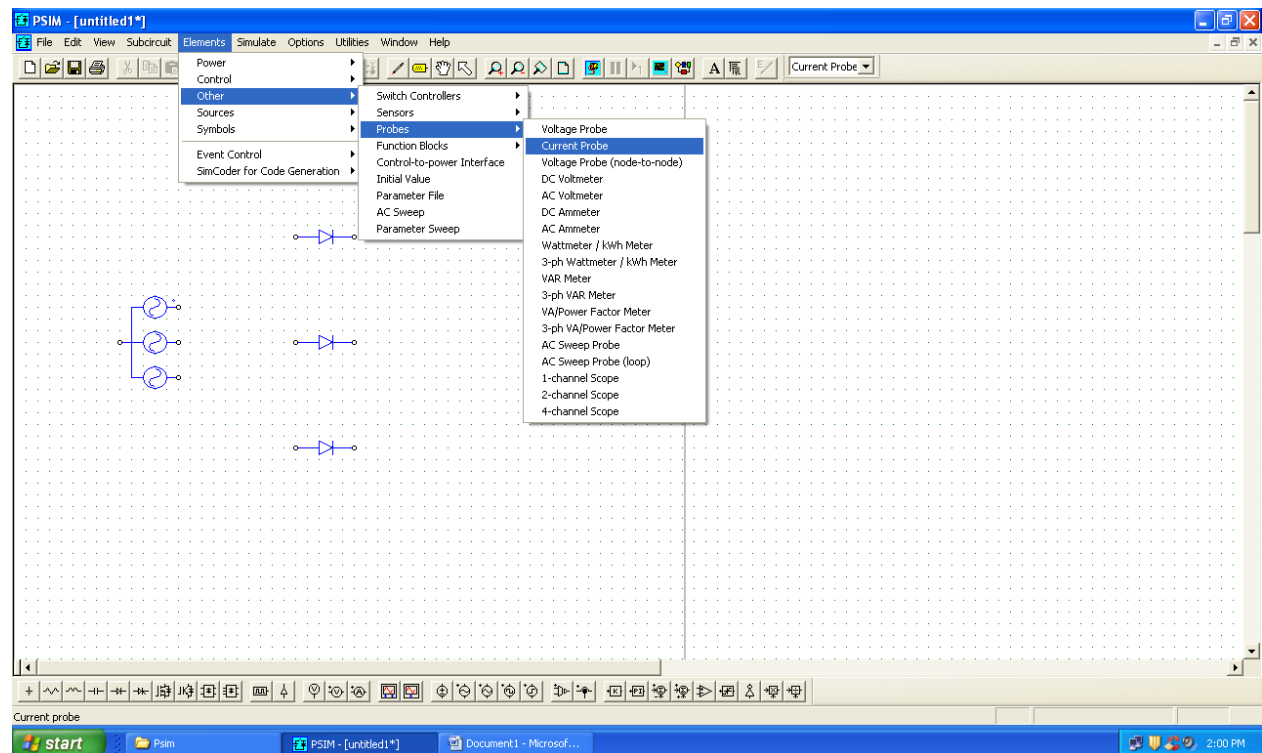


## CONNECTING THE ELEMENTS:

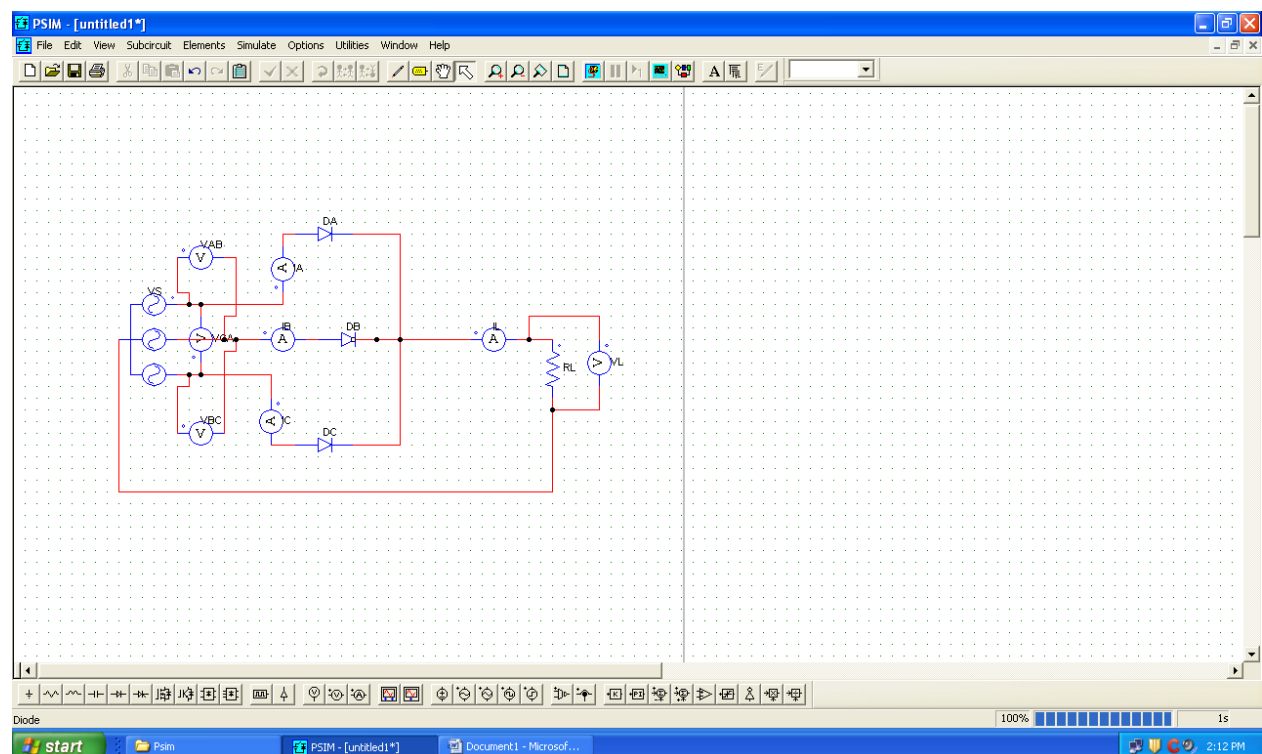






## SELECTION OF THE GROUND:

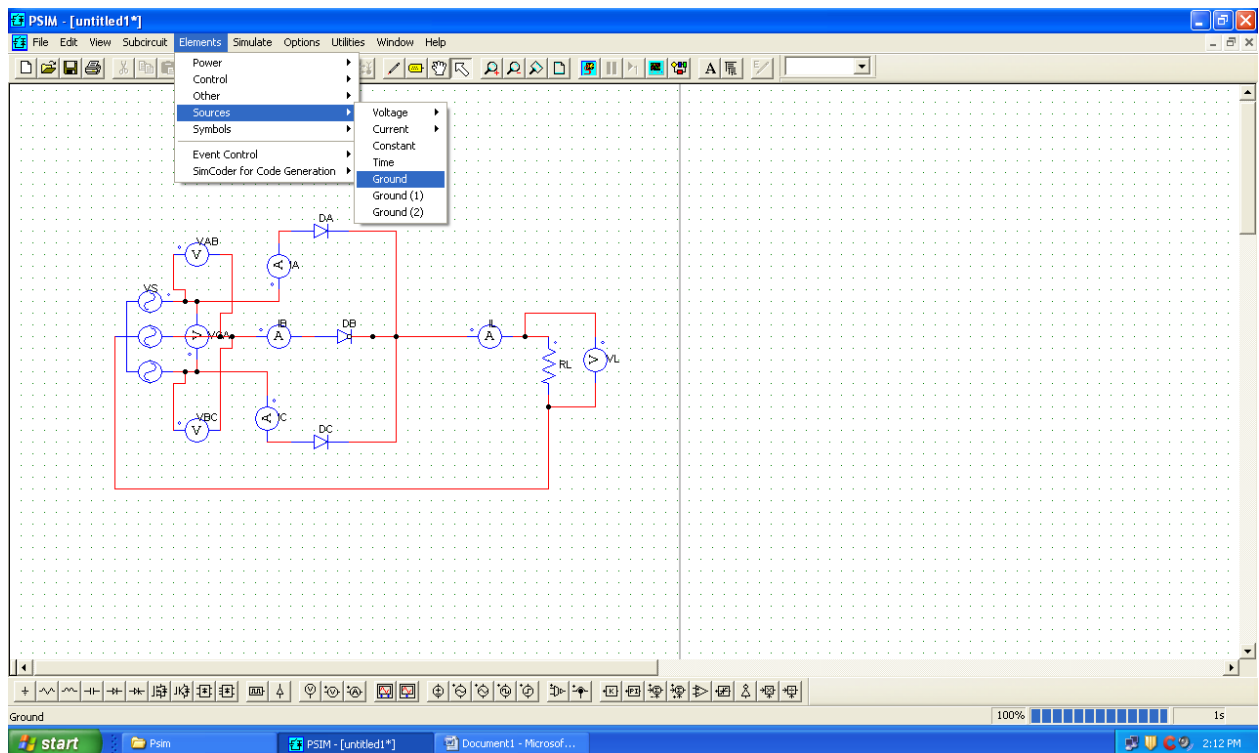


## FINAL CIRCUIT:

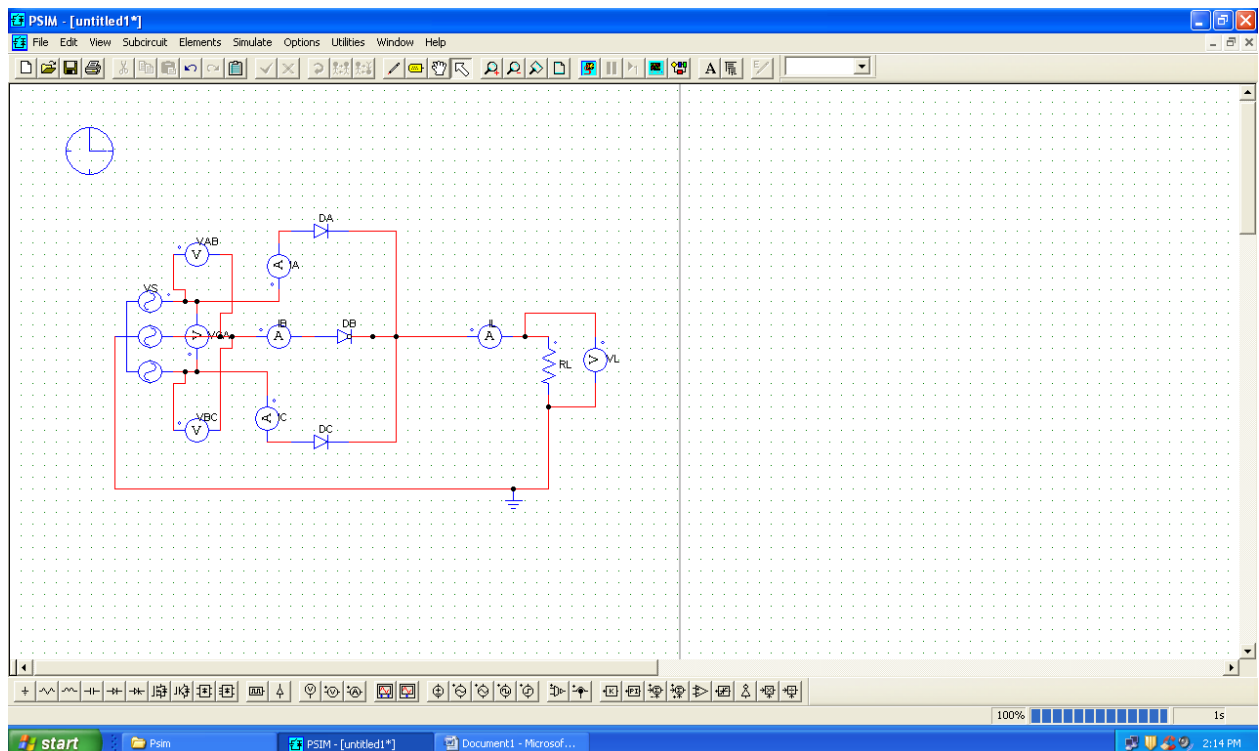



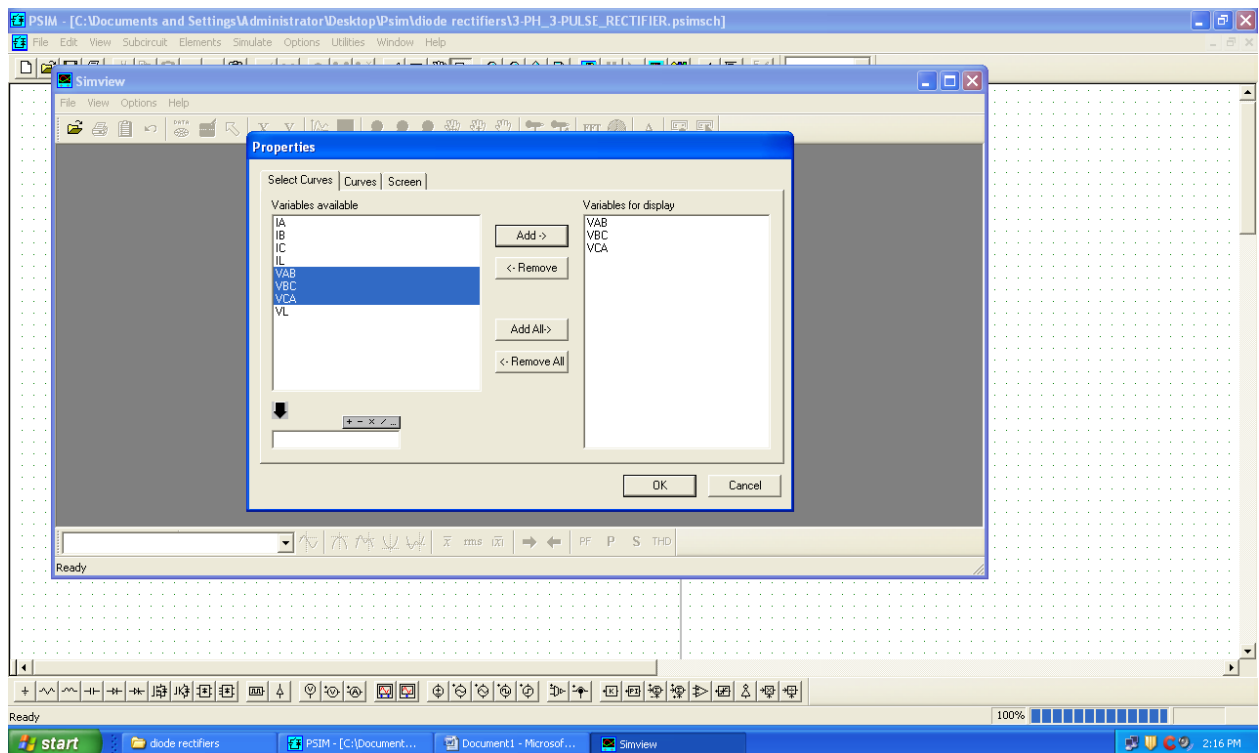
## SELECTING THE VARIABLES FOR OUTPUT WAVEFORMS:




## 3-PH SOURCE VOLTAGE WAVEFORMS:

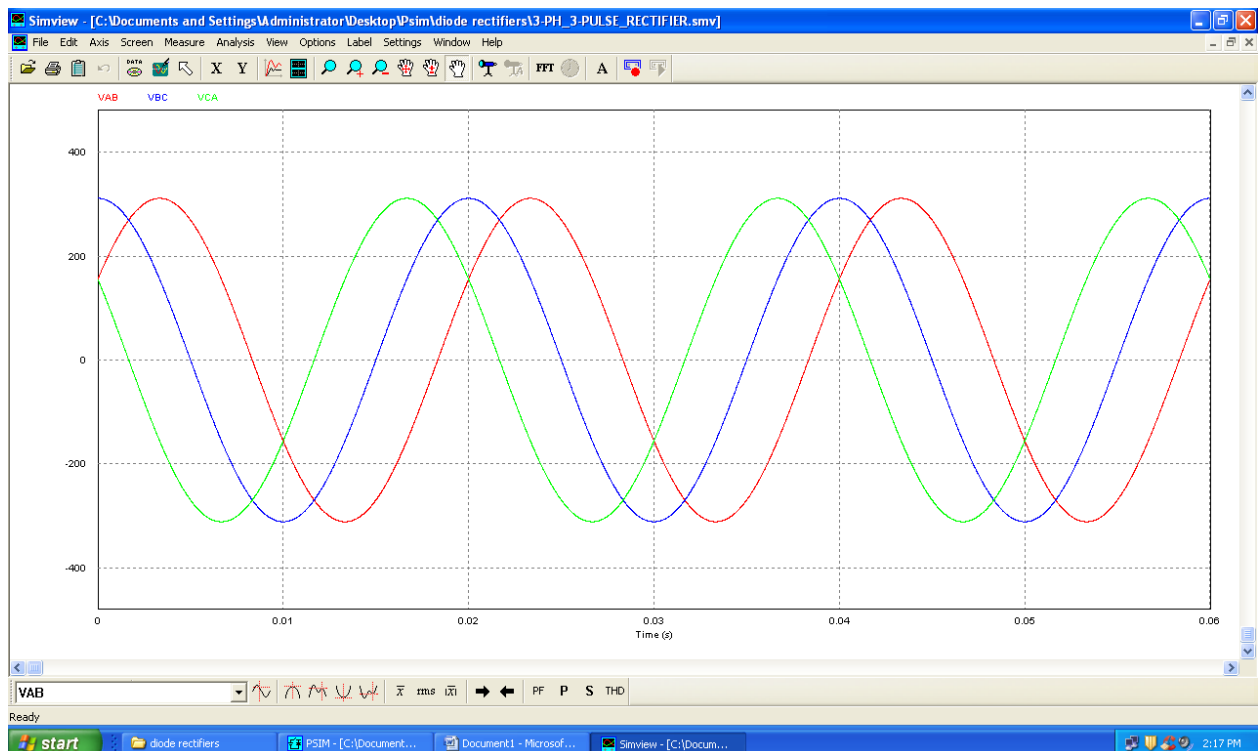



## OUTPUT WAVEFORMS OF ALL VARIABLES:

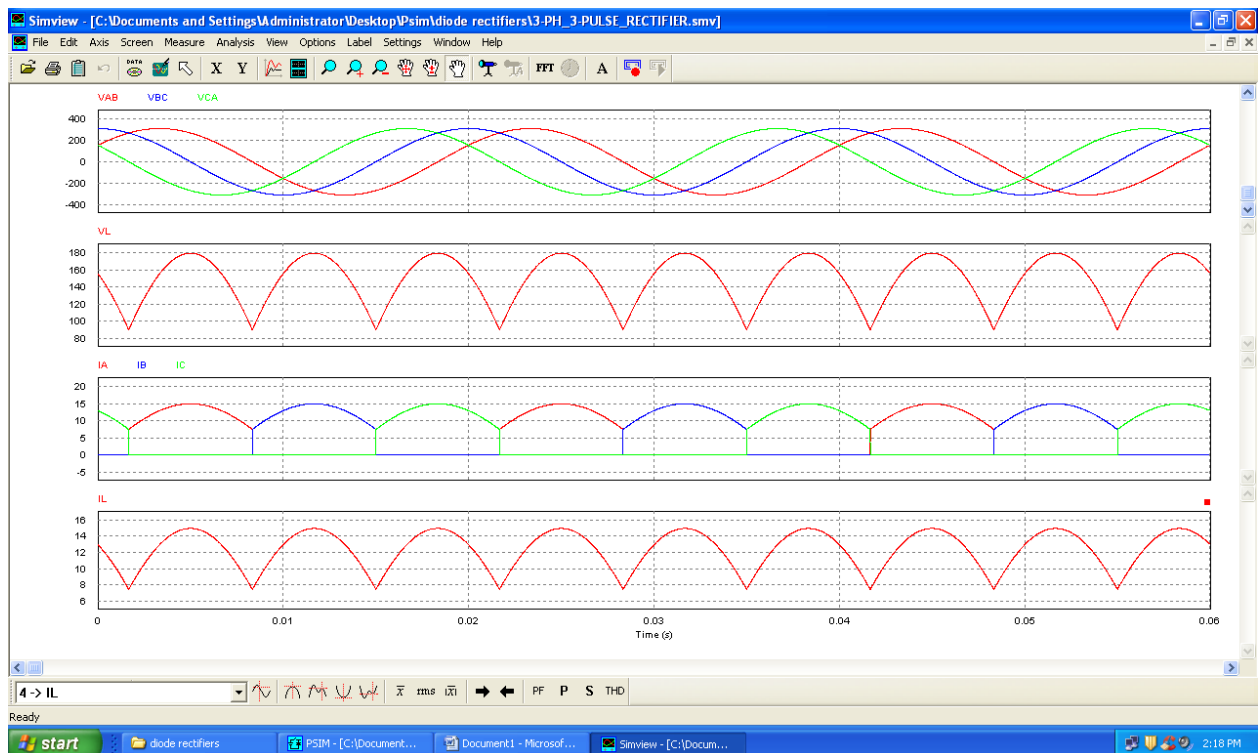





## SIX PULSE RECTIFIER

Select the elements as shown above and connect them as shown in below figure with proper labeling

### Circuit diagram

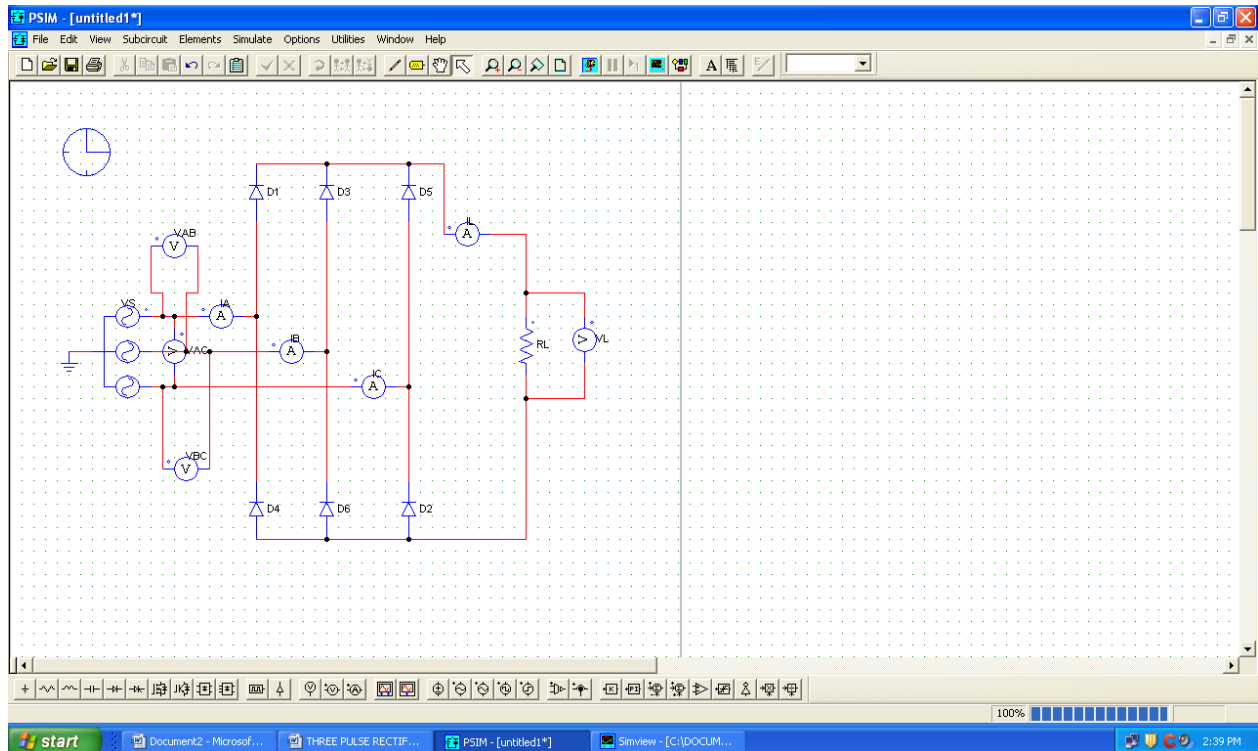


### OUTPUT WAVEFORMS:

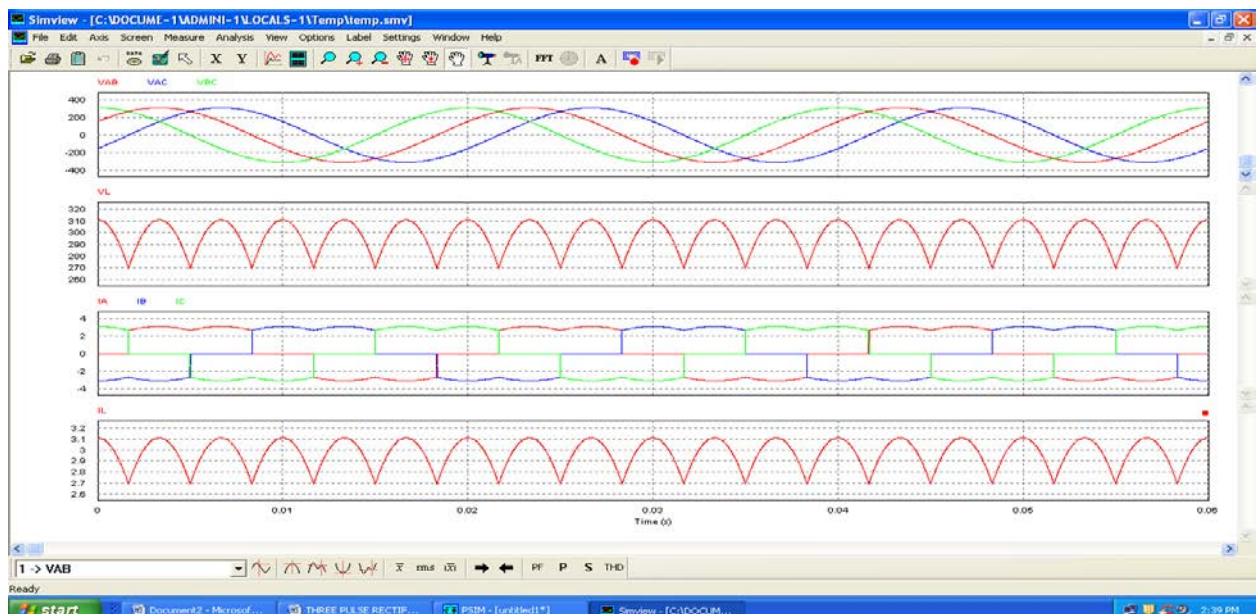




## TWELVE PULSE RECTIFIER

SELECTING THE 3-PHASE Y-Y TRANSFORMER:

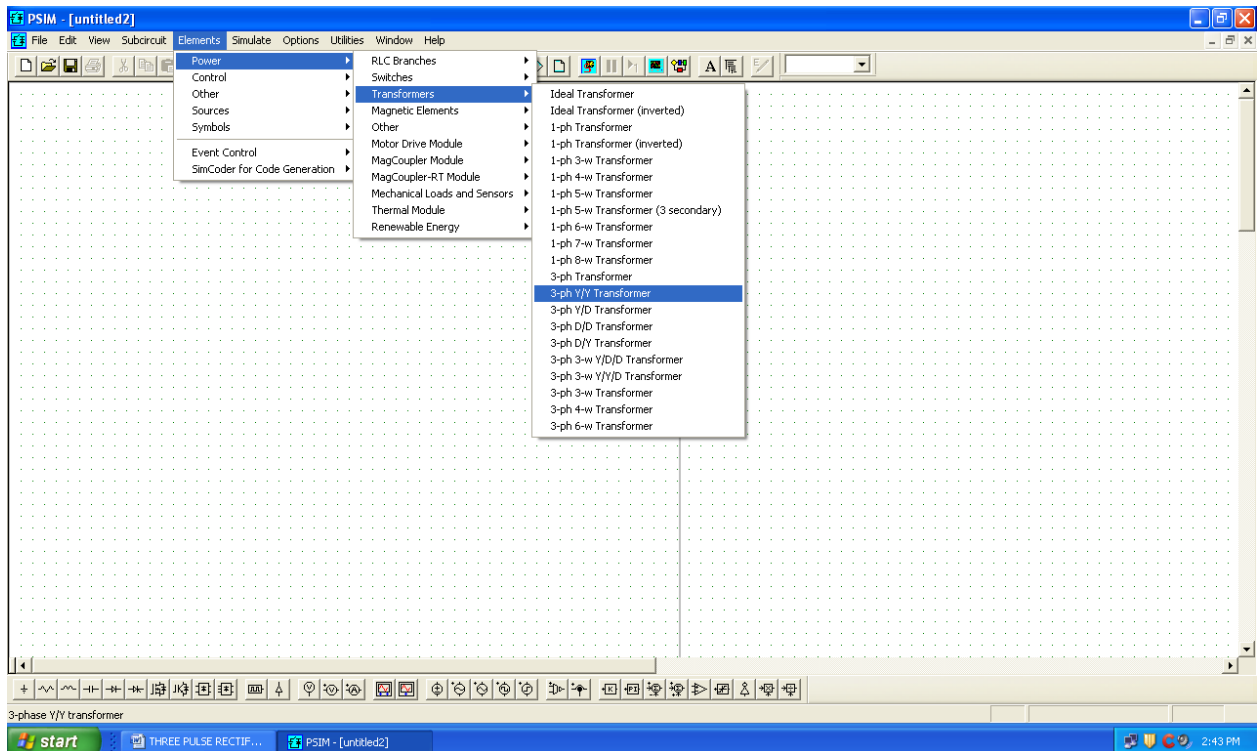


SELECTING THE 3-PHASE Y-Δ TRANSFORMER:

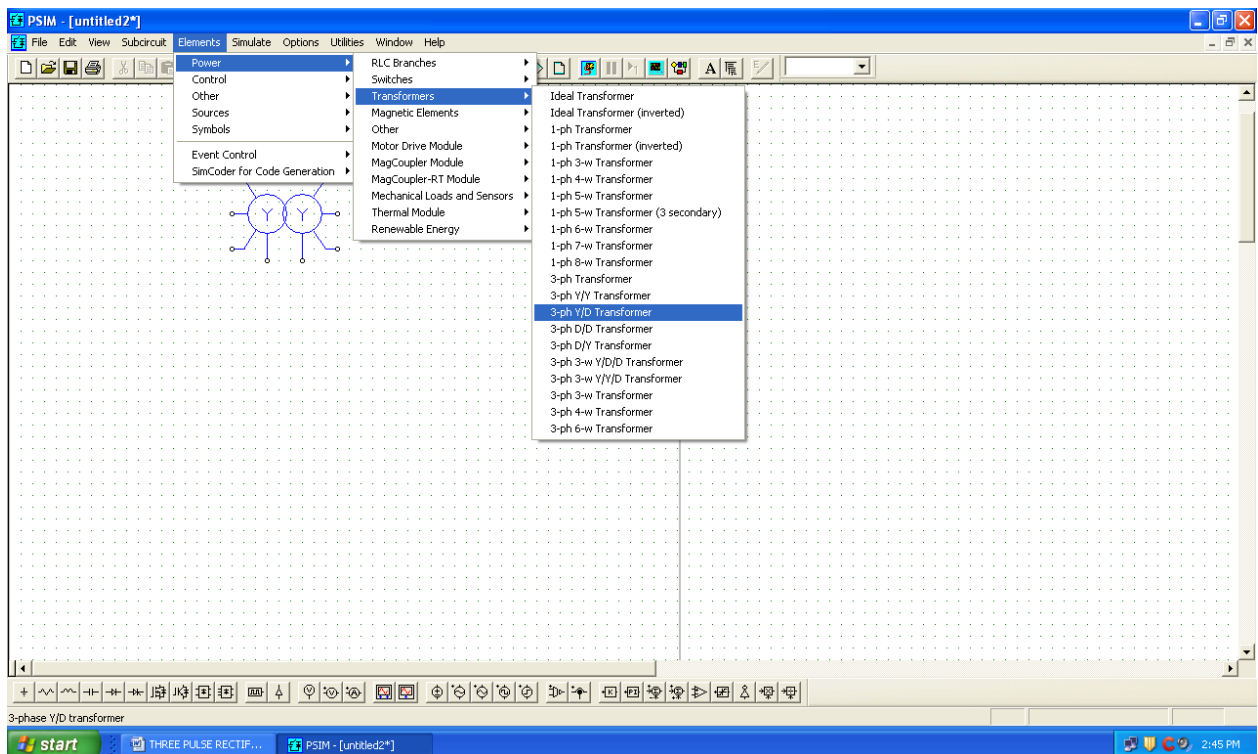




Select the remaining elements as shown above and connect them as shown in below figure with proper labeling

CIRCUIT DIAGRAM:

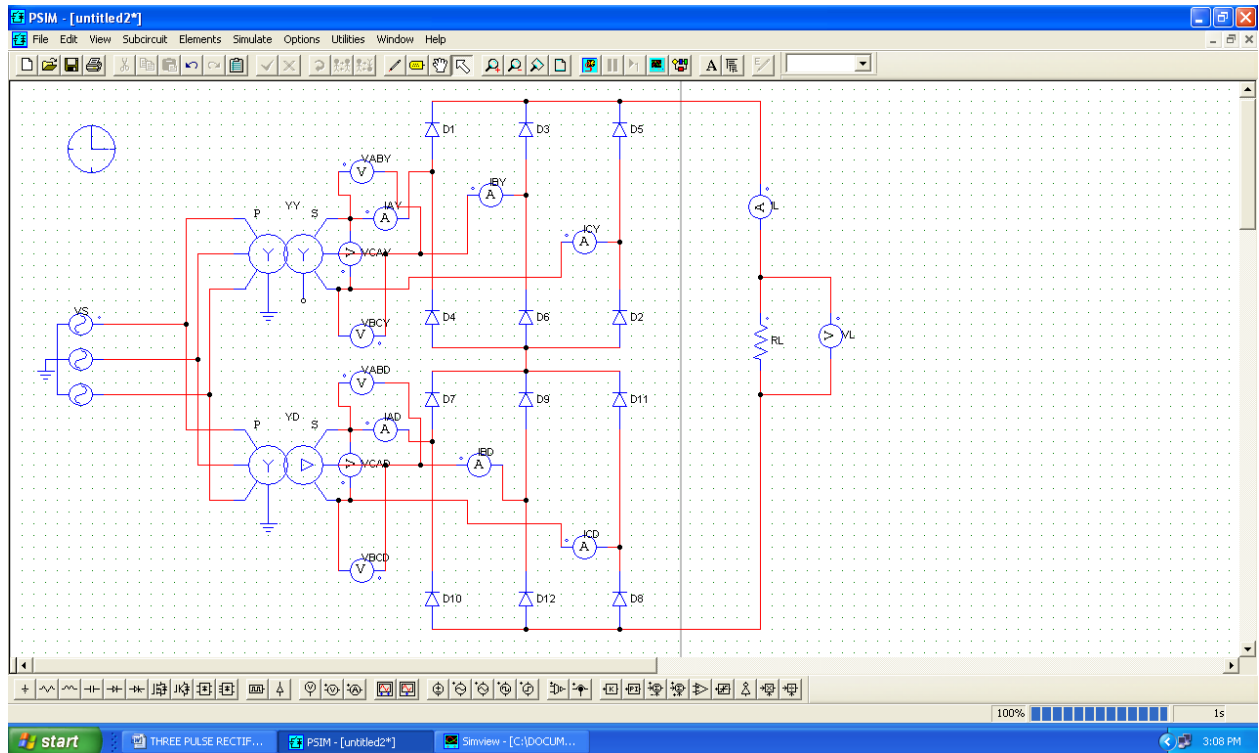

OUTPUT WAVEFORMS:

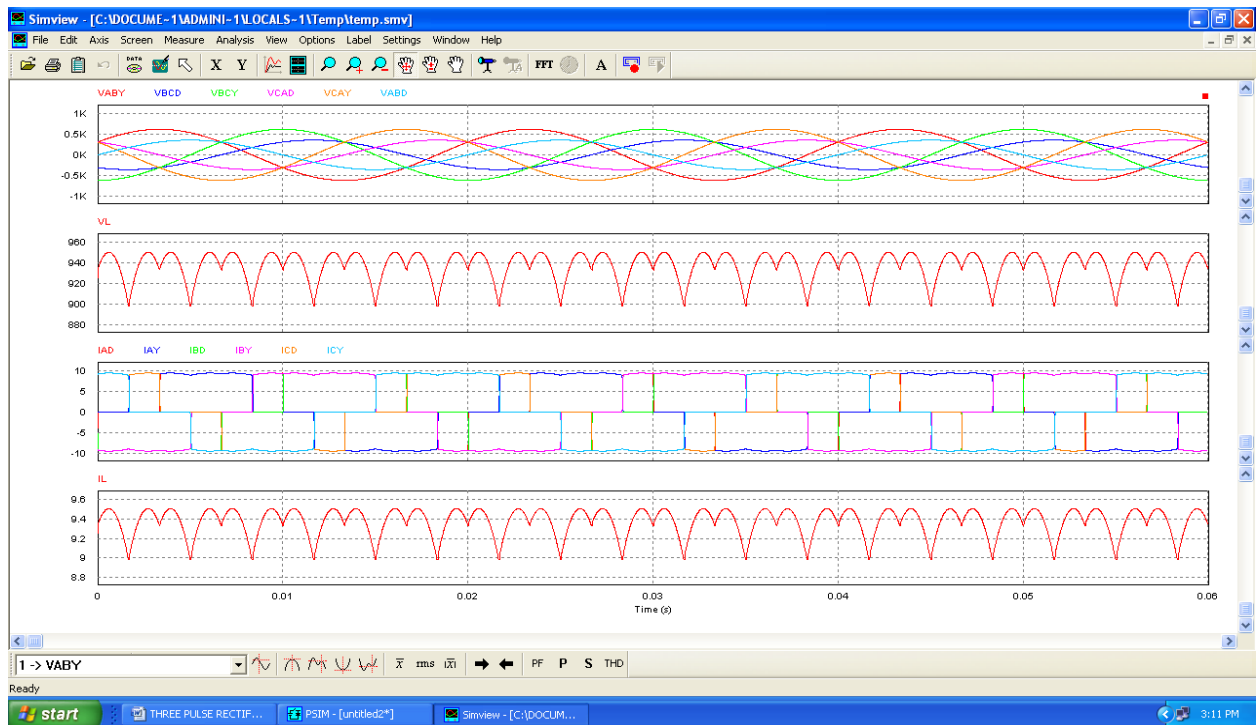





## Dc to Dc converters

### Buck converter

Selection of DC source

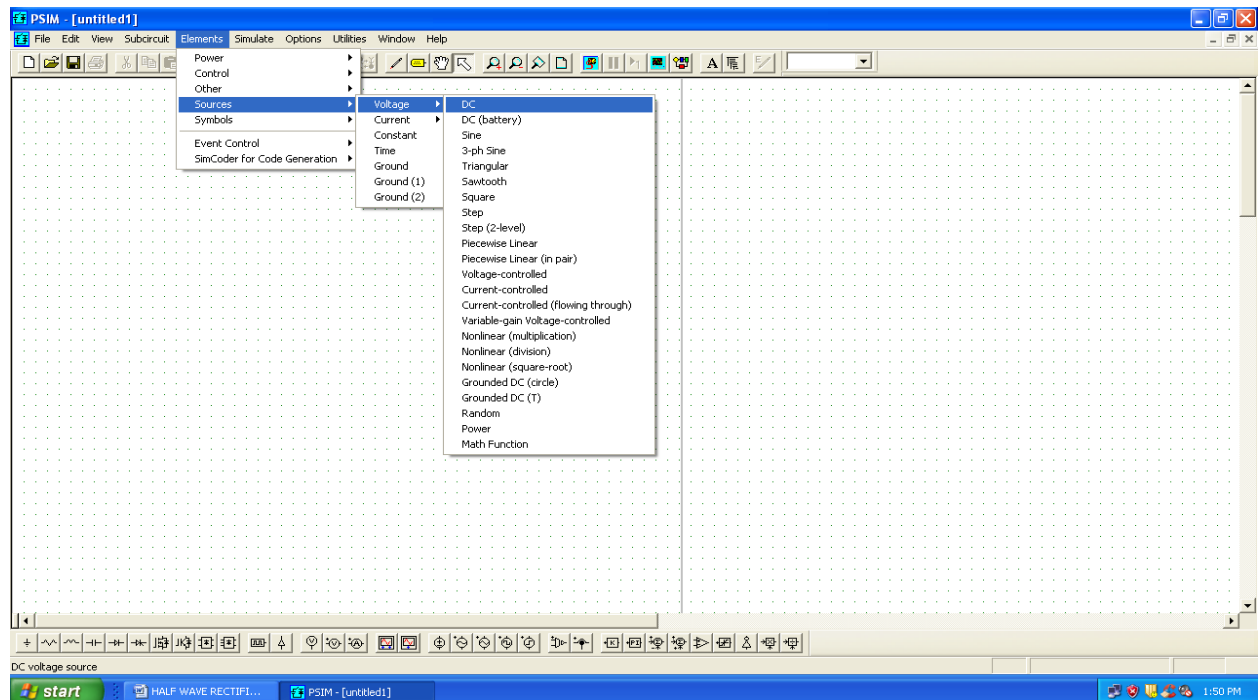


Selection of mosfet

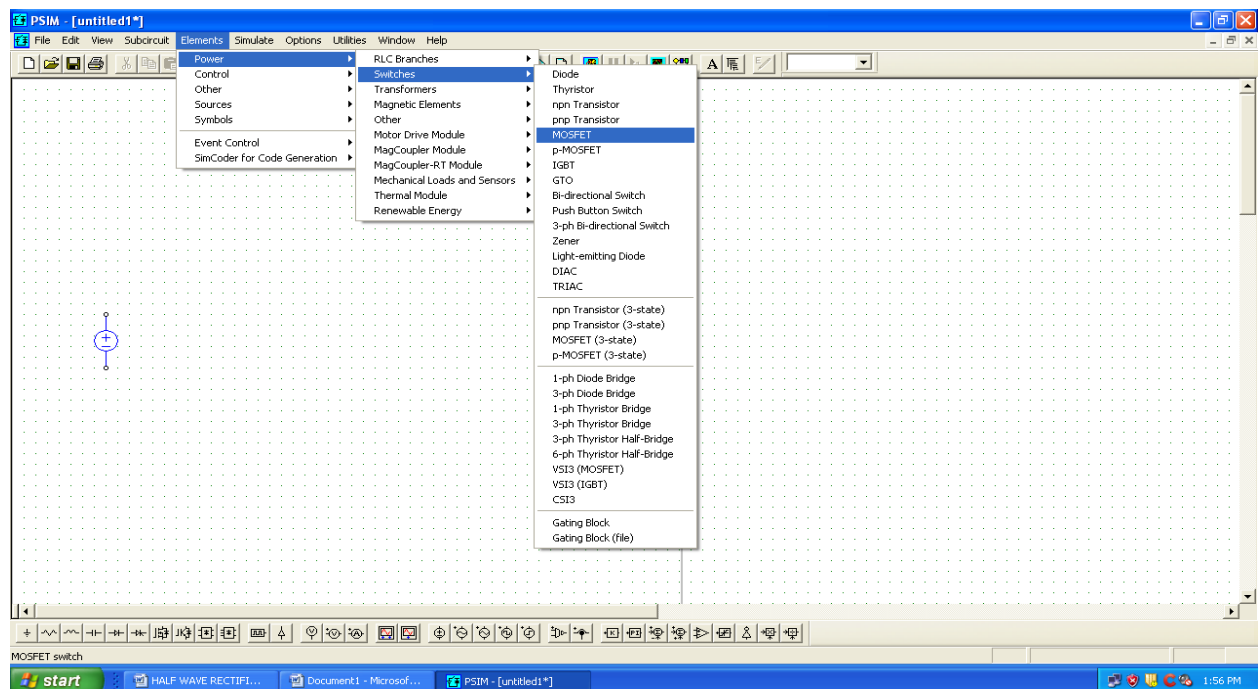






## Selection of diode

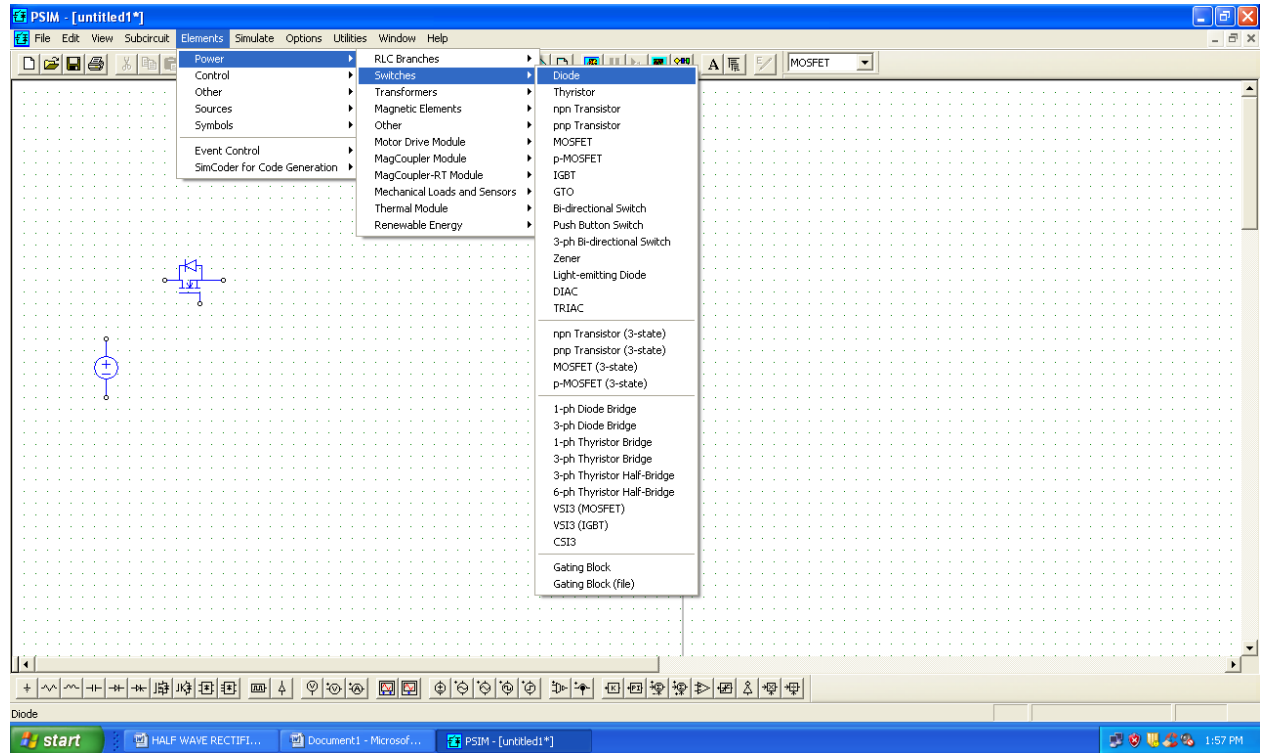


## Selection of Inductor

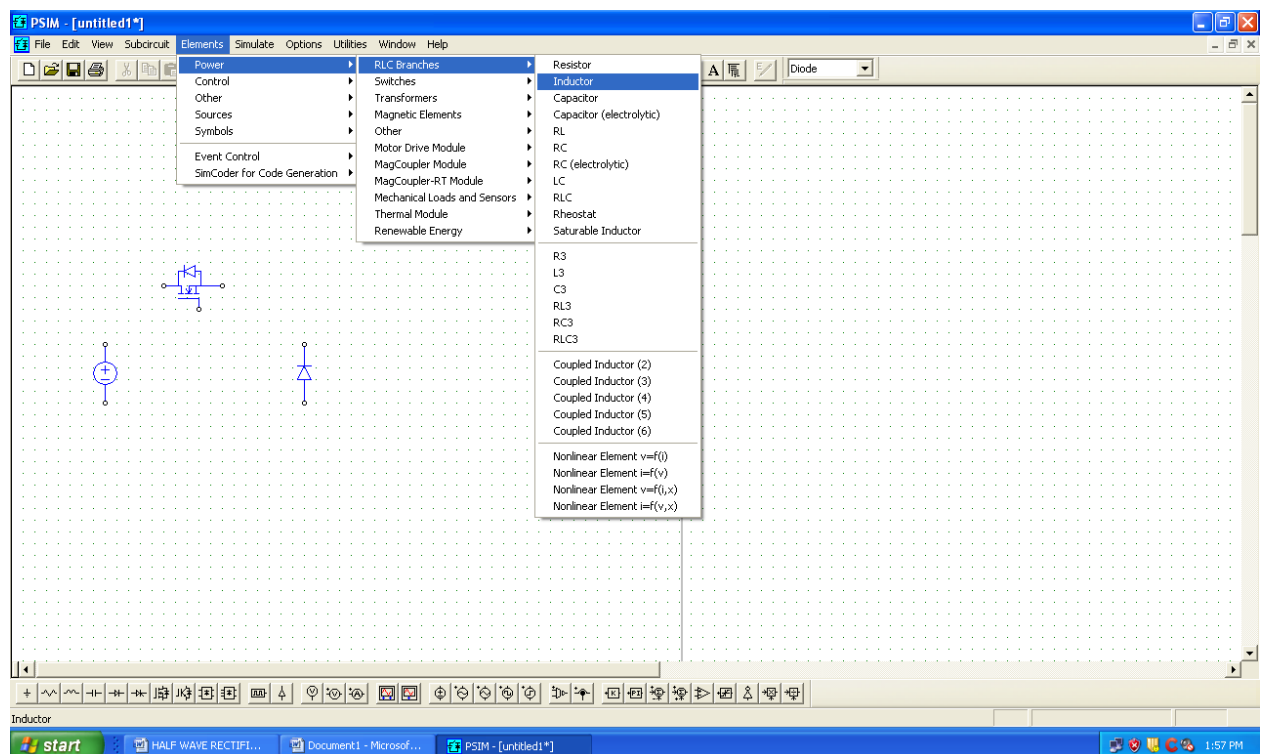




## Selection of Capacitor

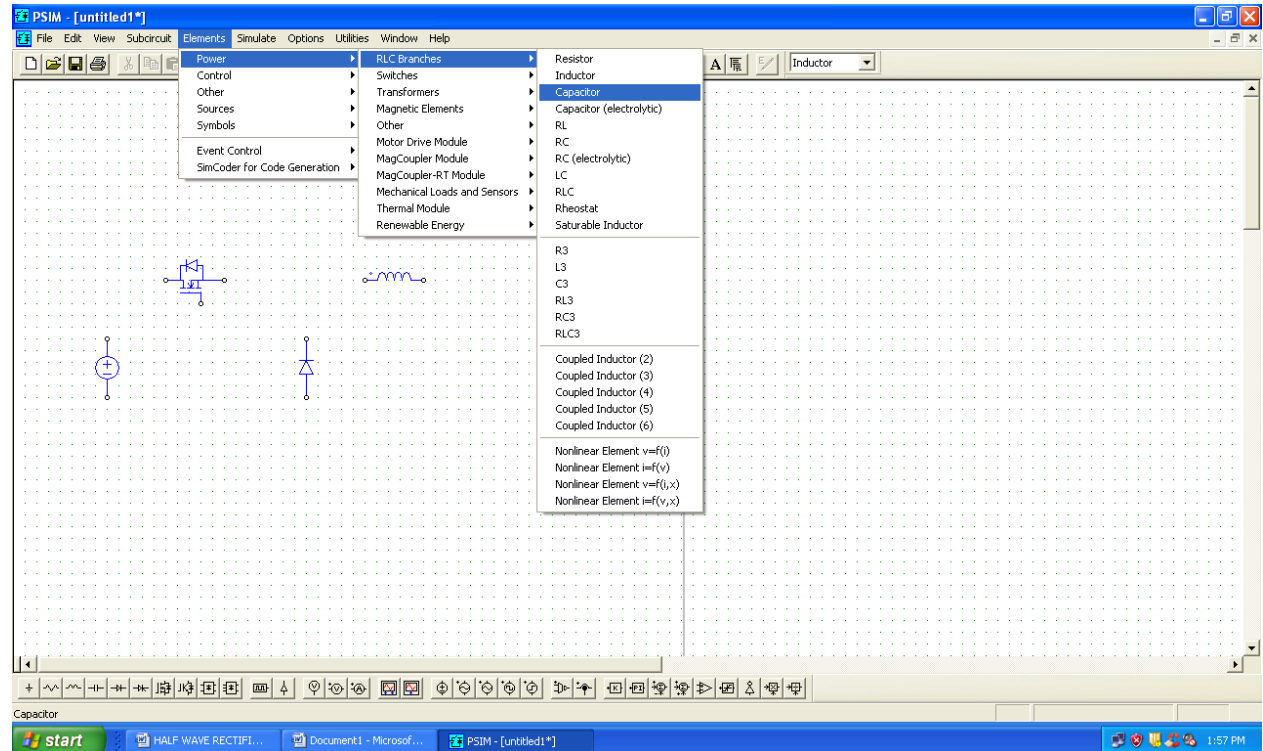


## Selection of Resistor

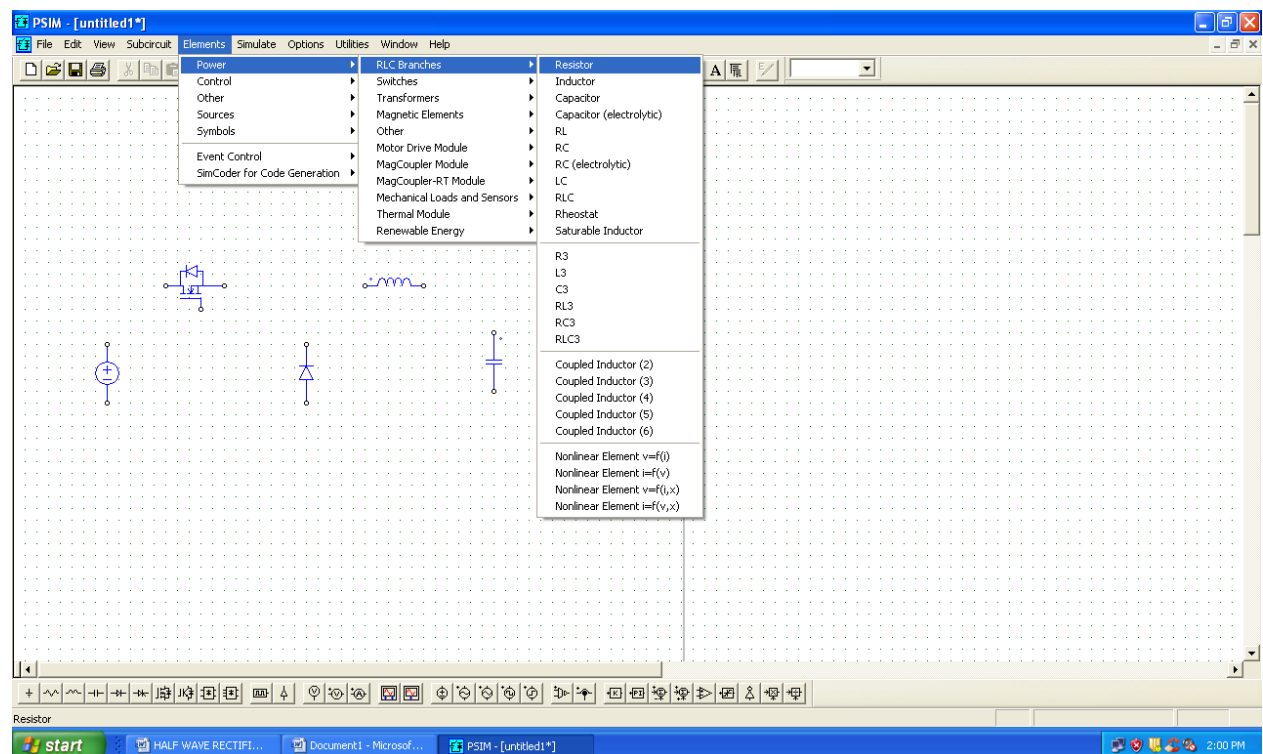




## Selection of ammeter

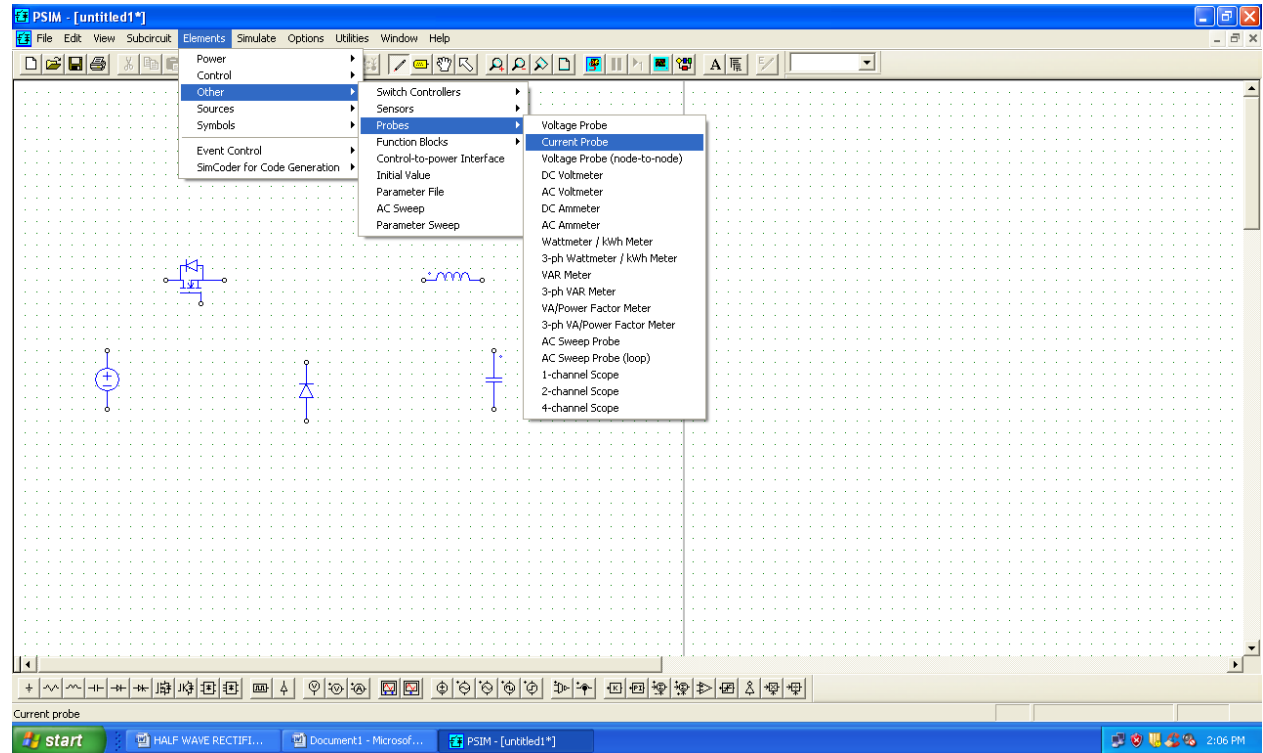


## Selection of volt meter

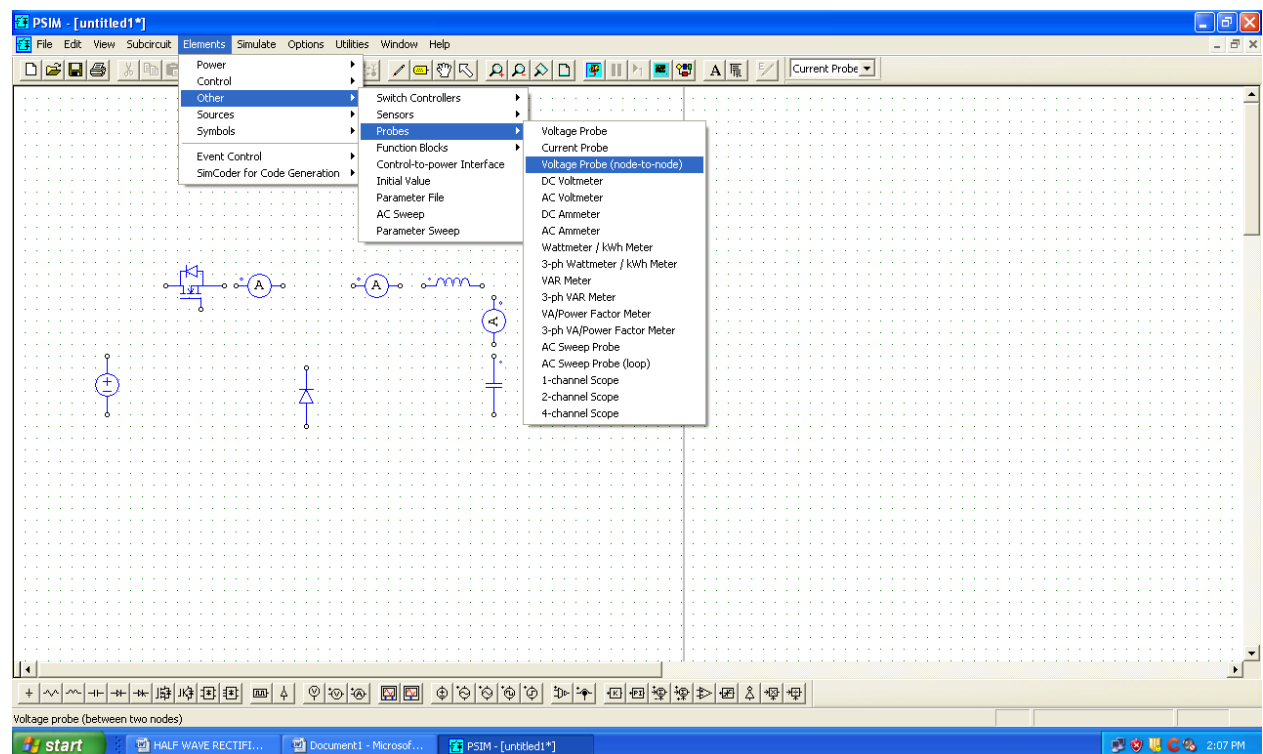




## Selection of gating block

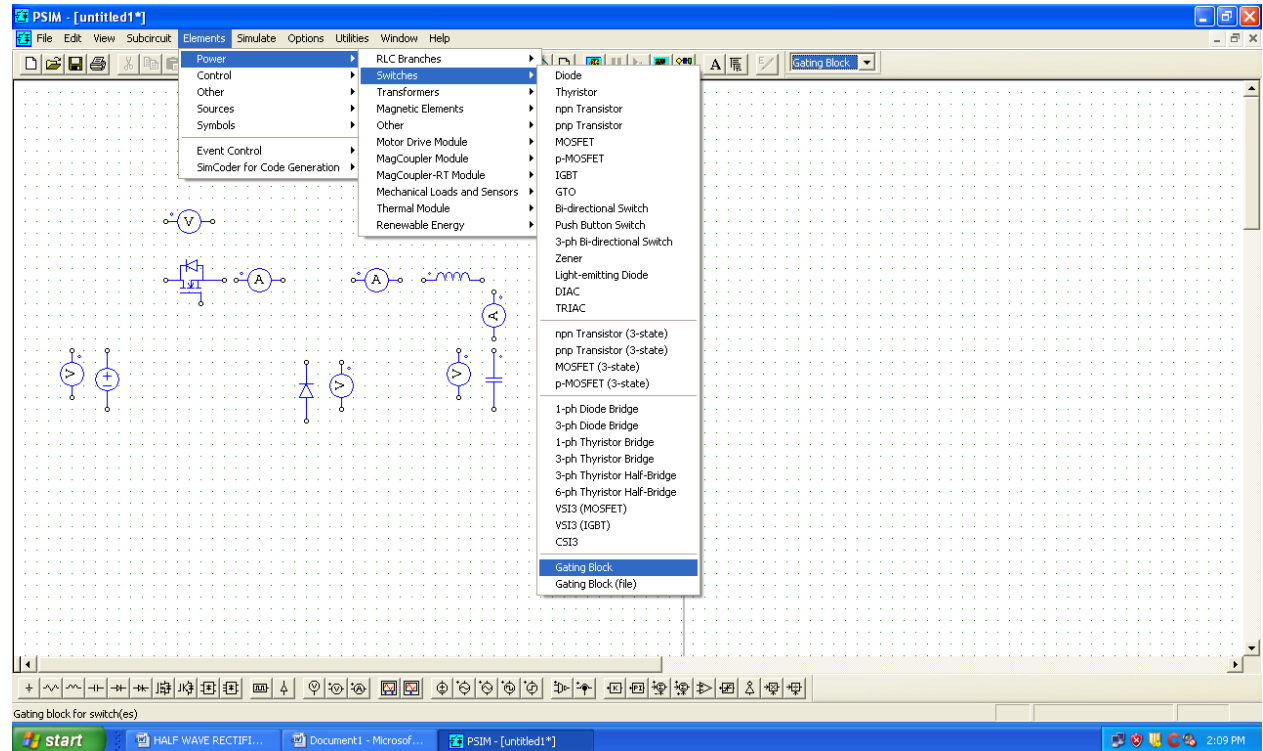

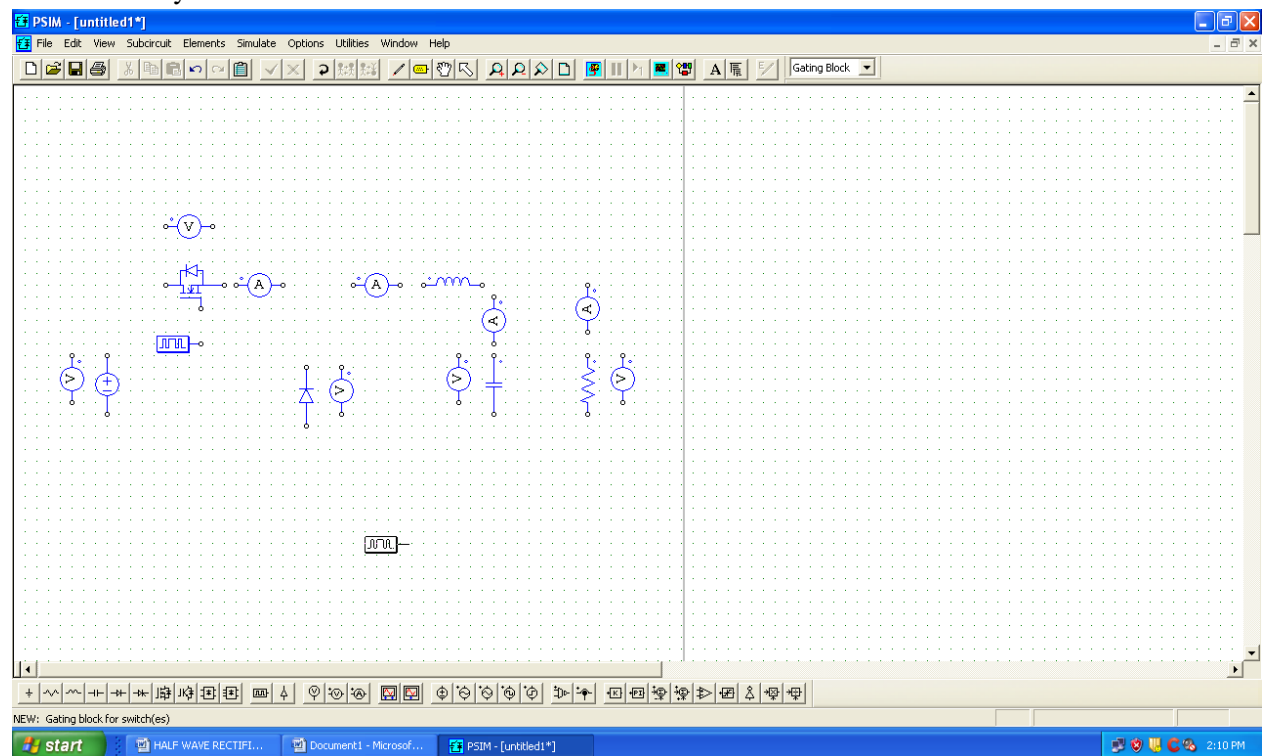
## Select as many elements as shown below






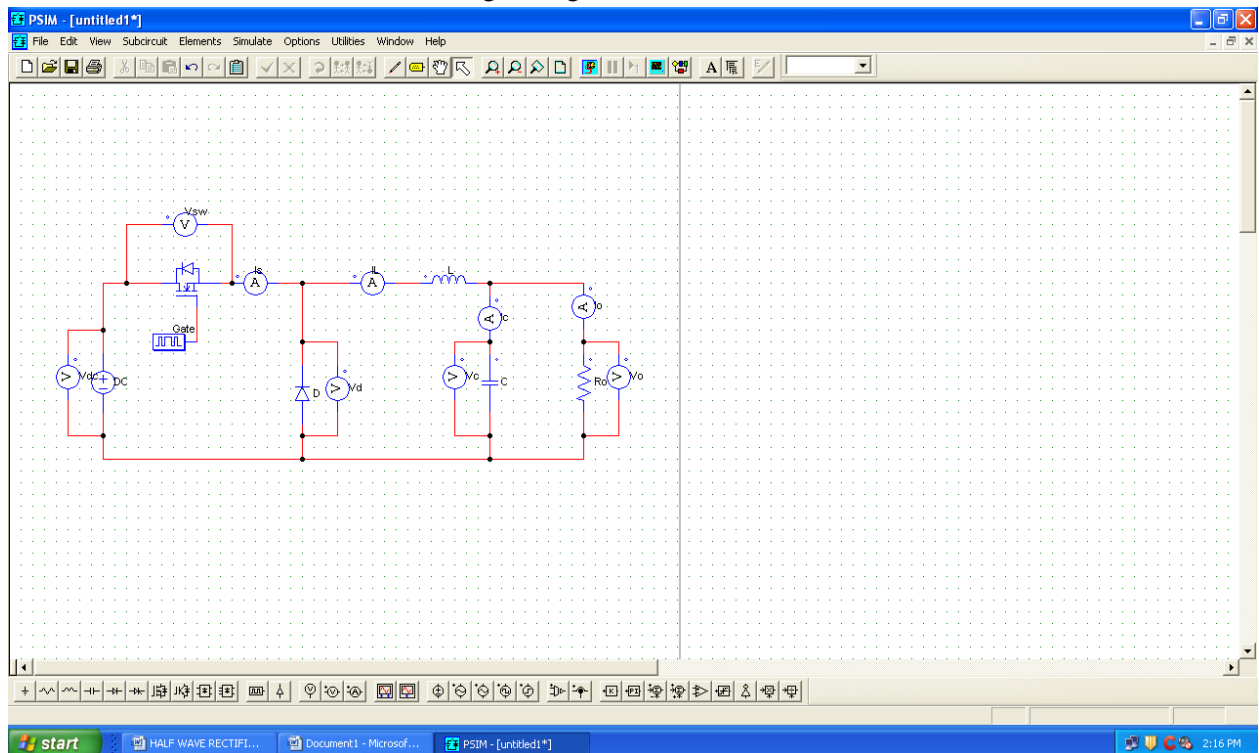Connect the circuit as shown below using wiring tool




Give the inductor value=1mh

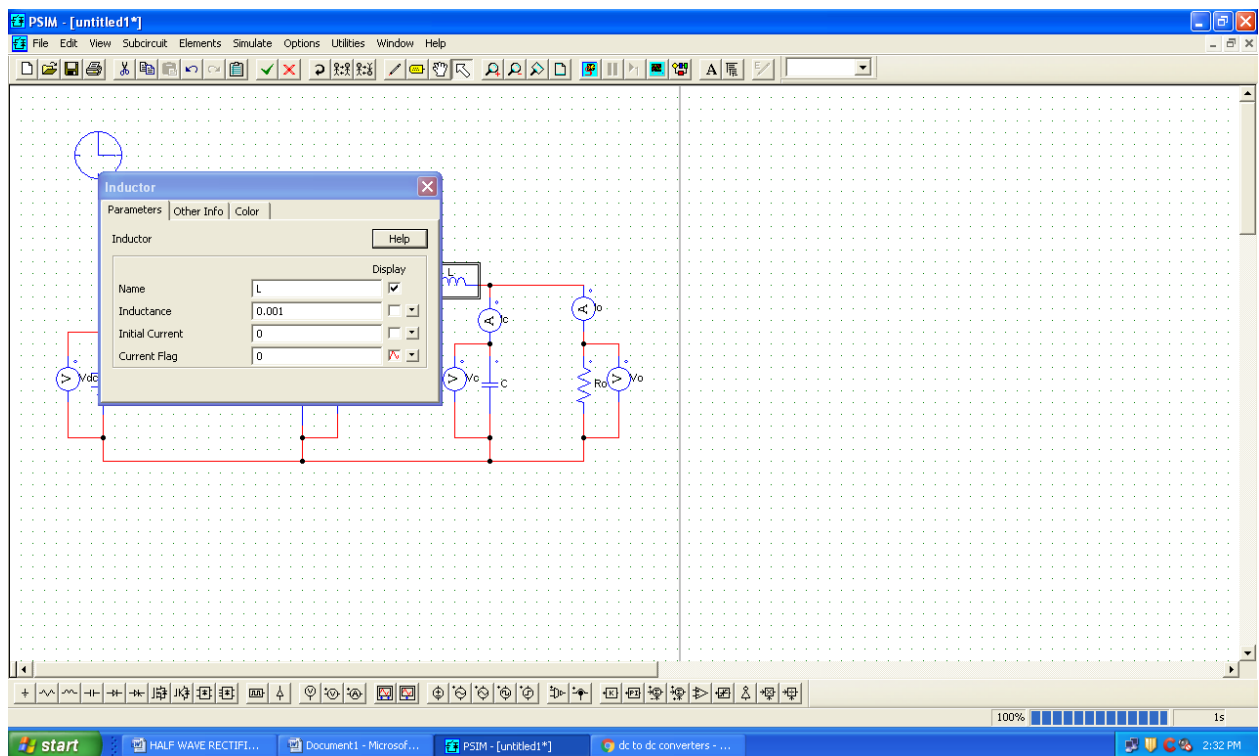




Give the capacitor value=30micro F

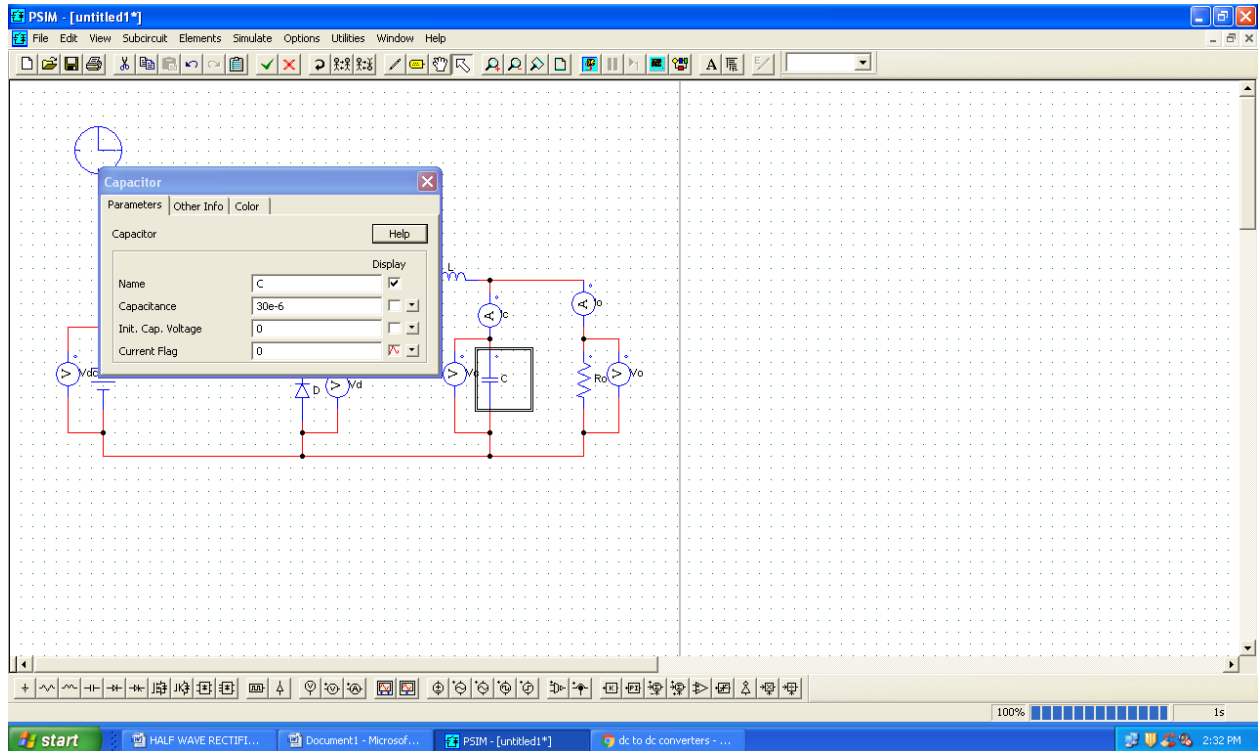


Give the resistor value=50ohm

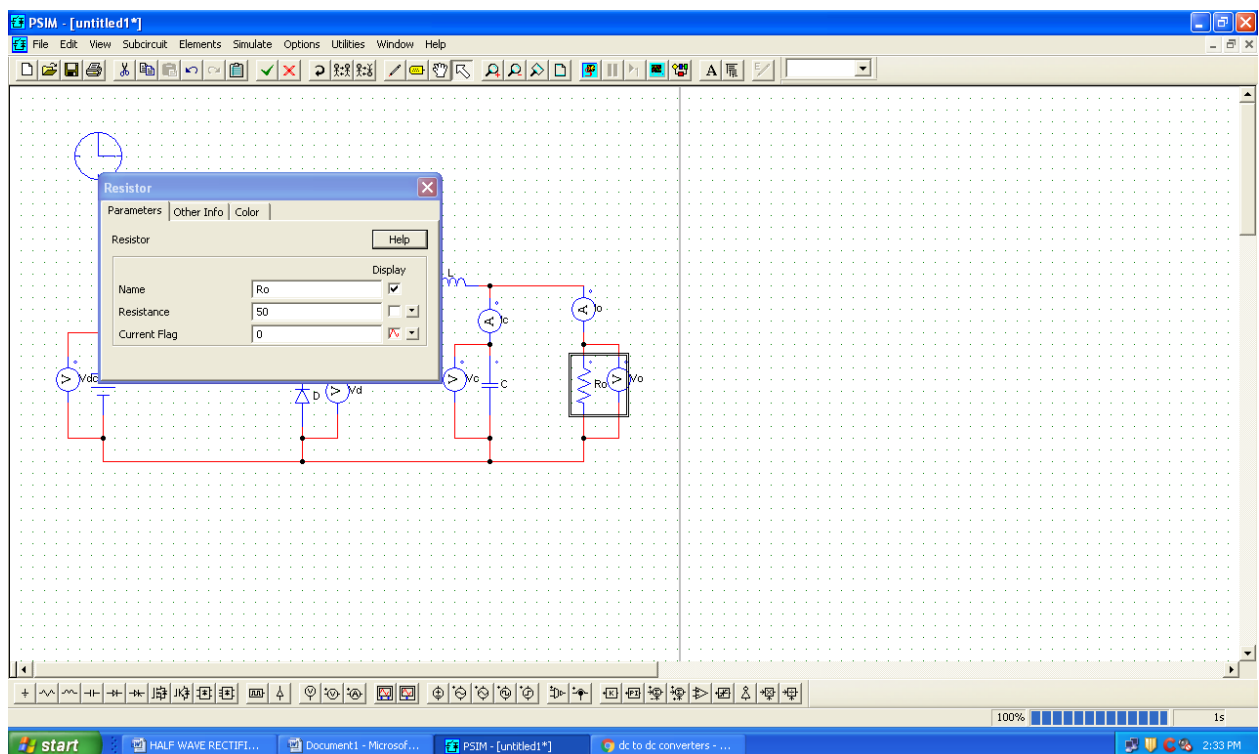




Give the dc source value=50V

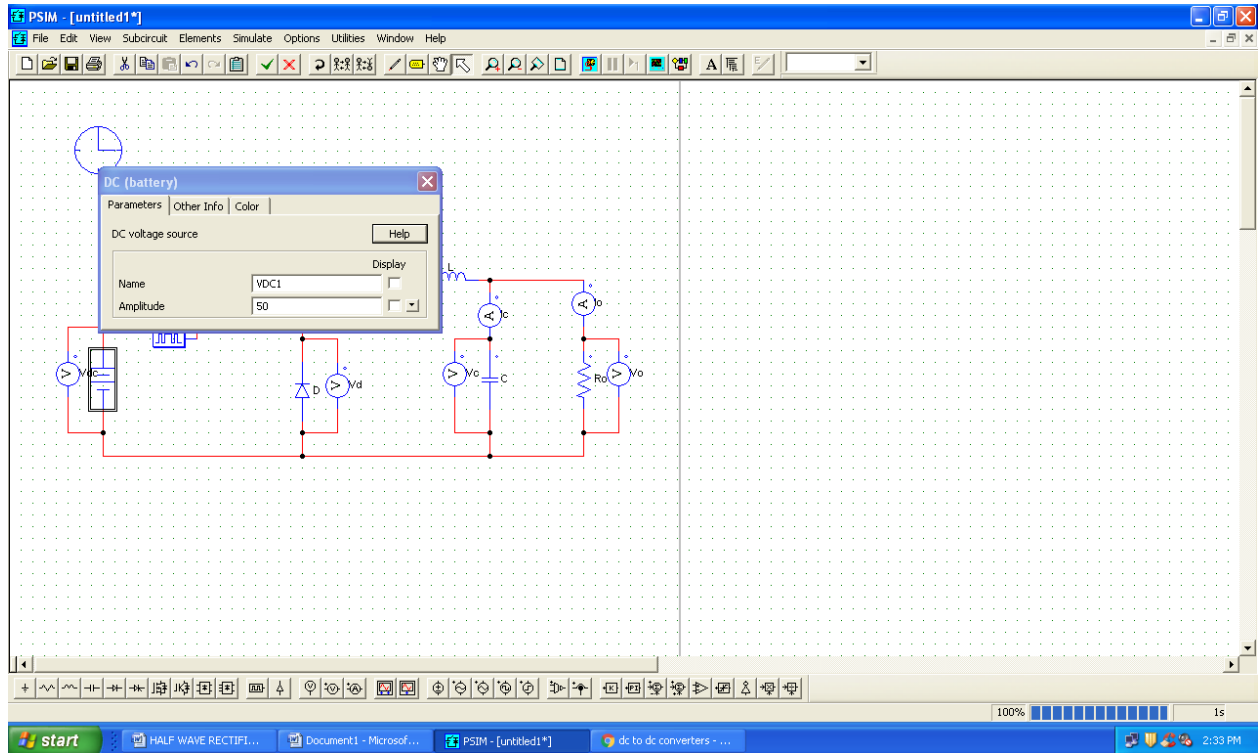


Select simulation control

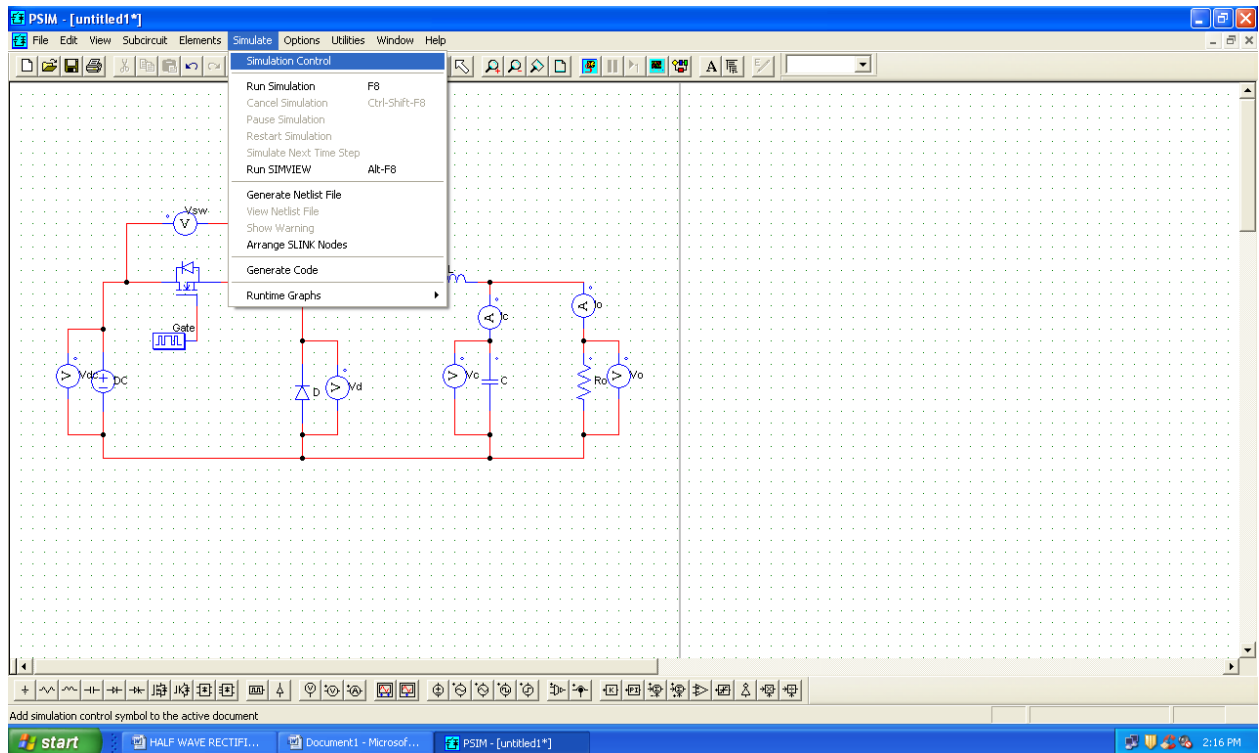




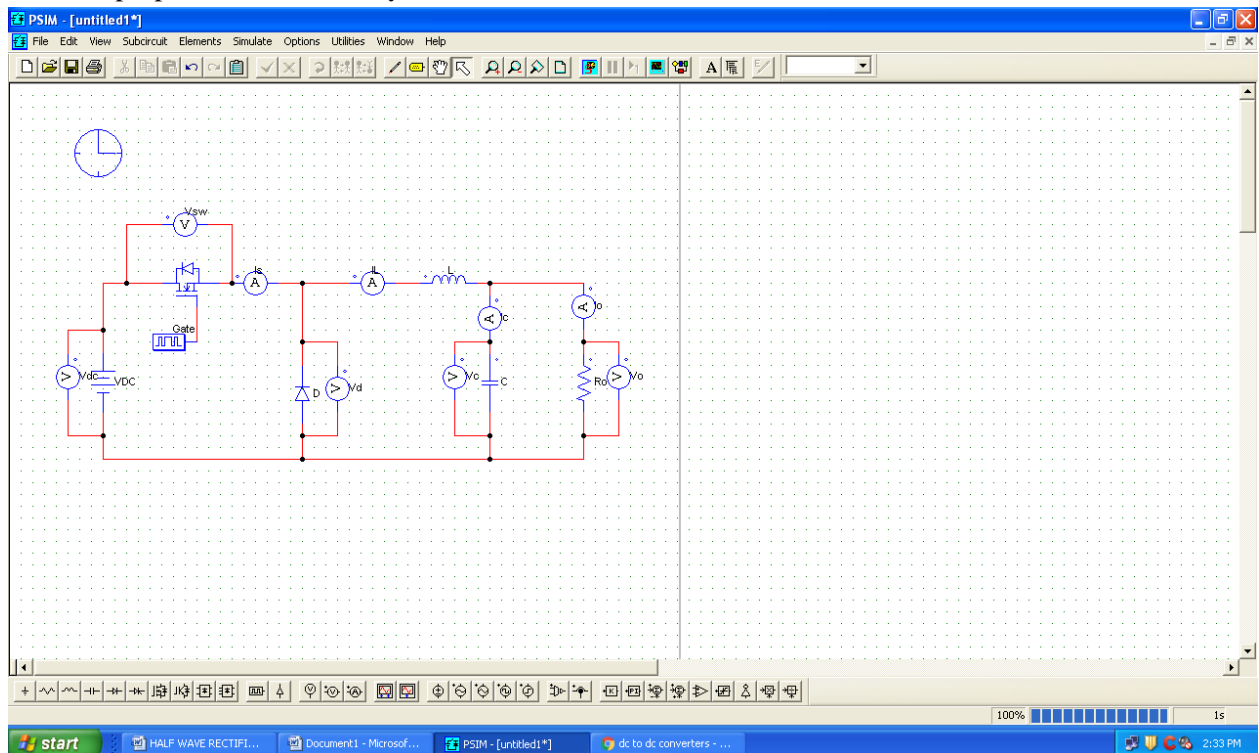Give the proper label to the every element



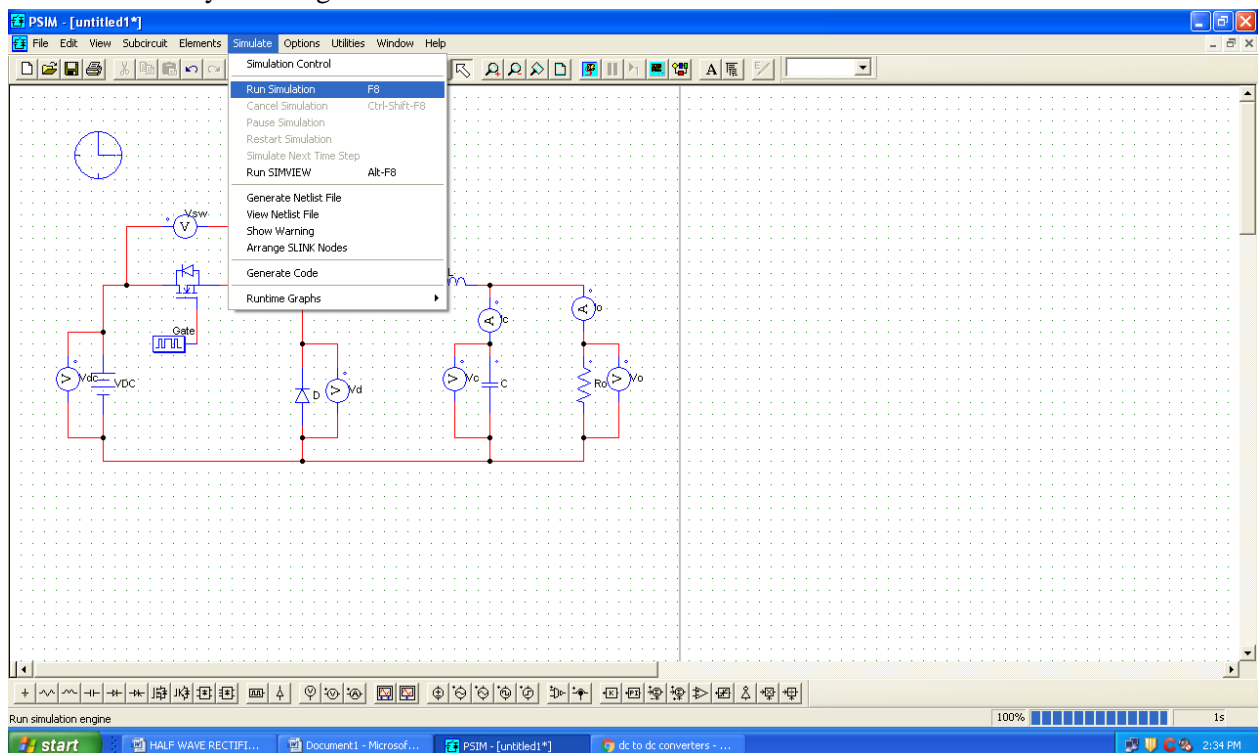
Run the circuit by selecting run simulation








## Voltage waveforms

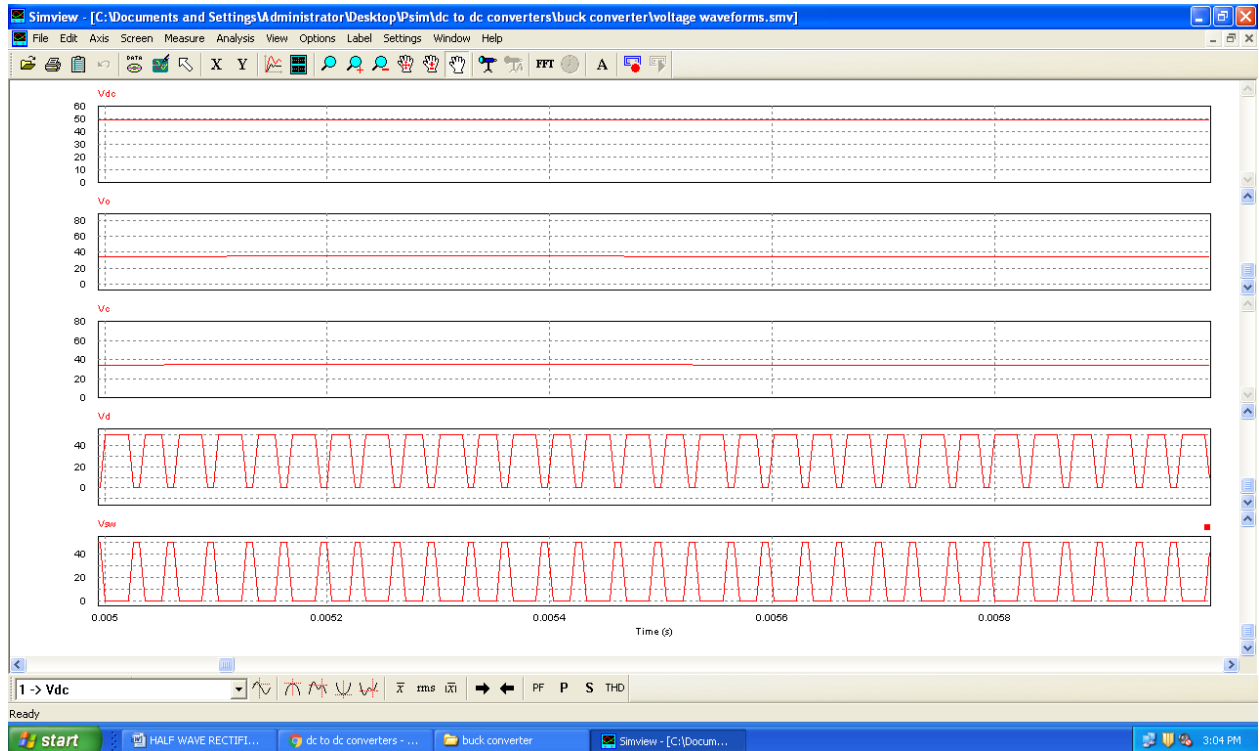

## Current waveforms

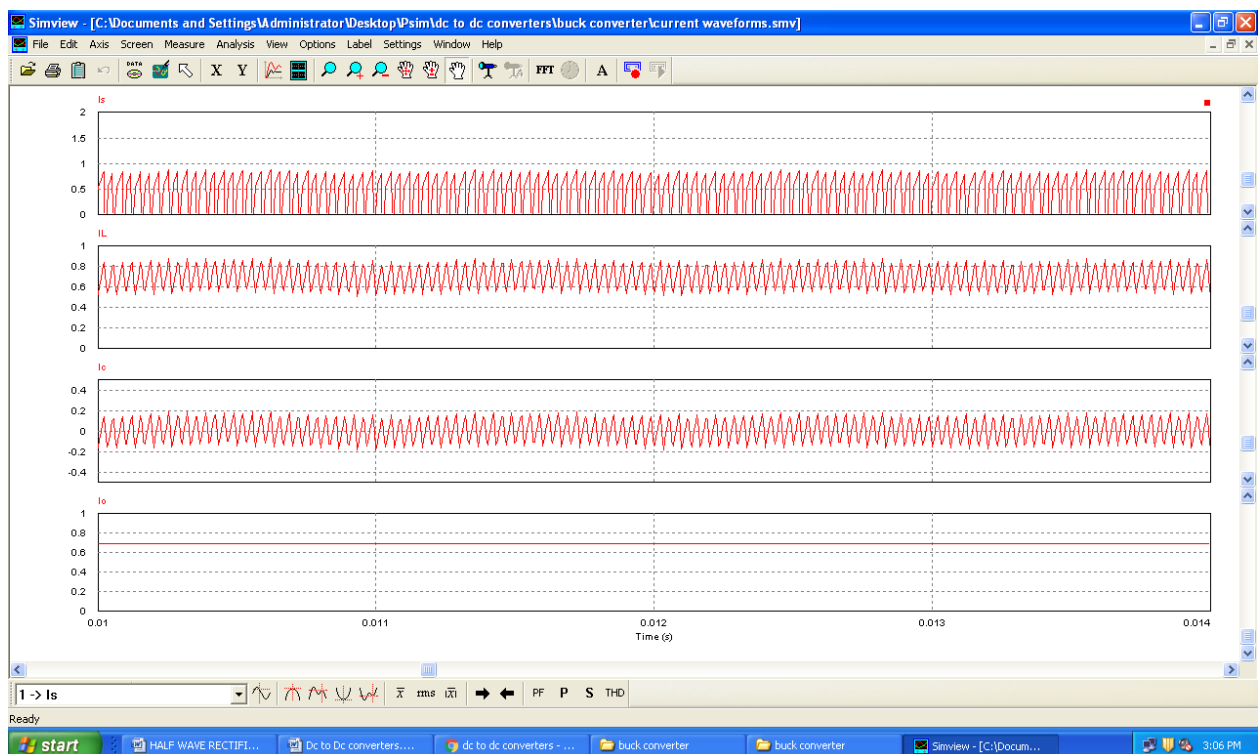





## Boost converter

Select the elements as shown above and connect them as shown in below figure with proper labeling

### Circuit diagram

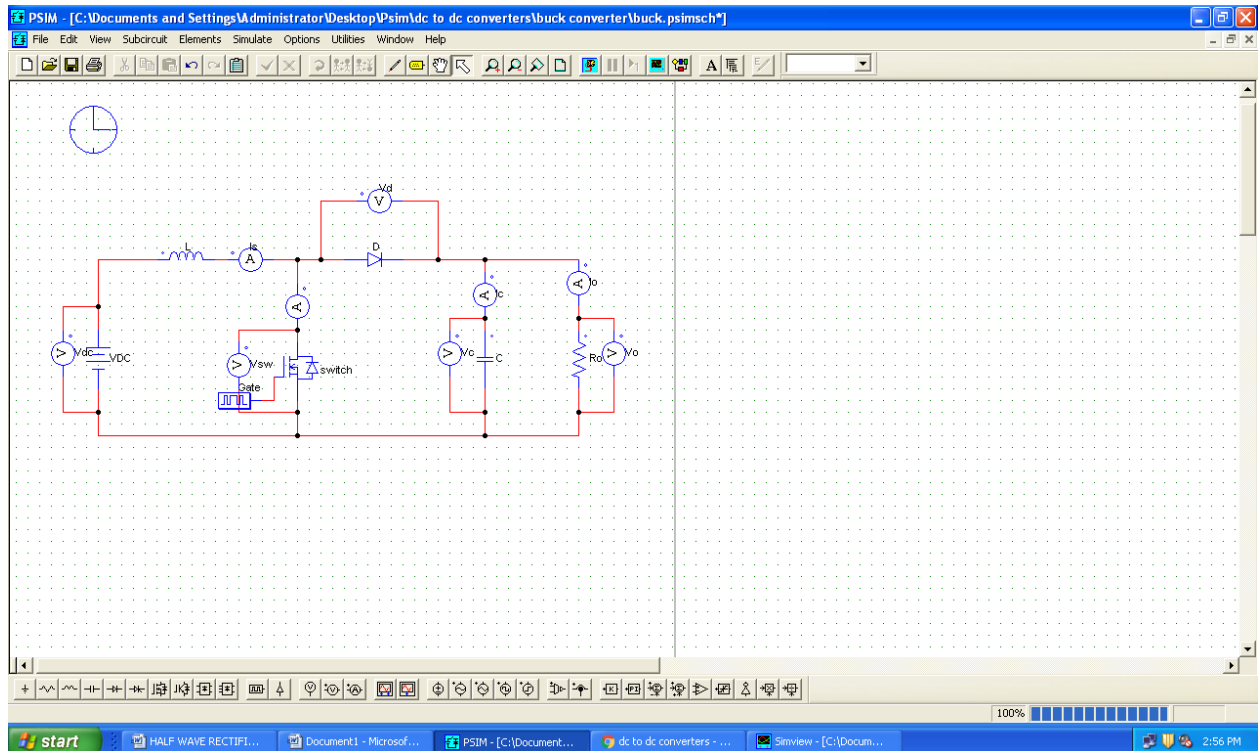


### Voltage waveforms

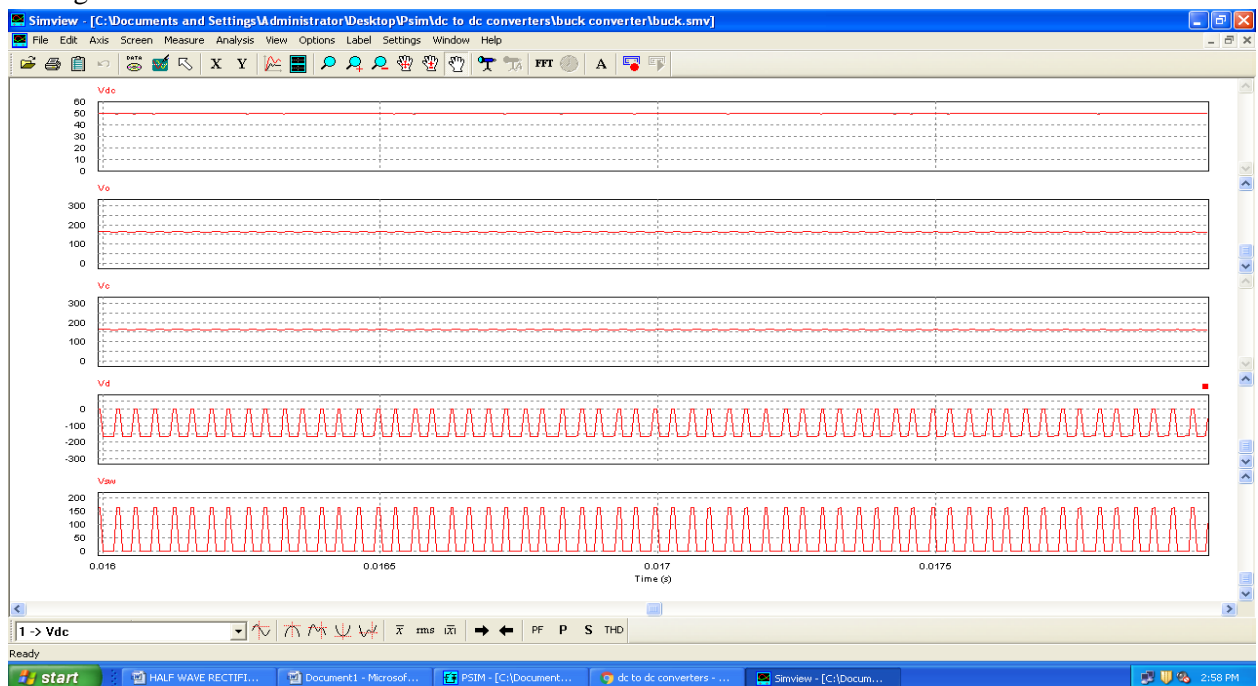



## Current waveforms

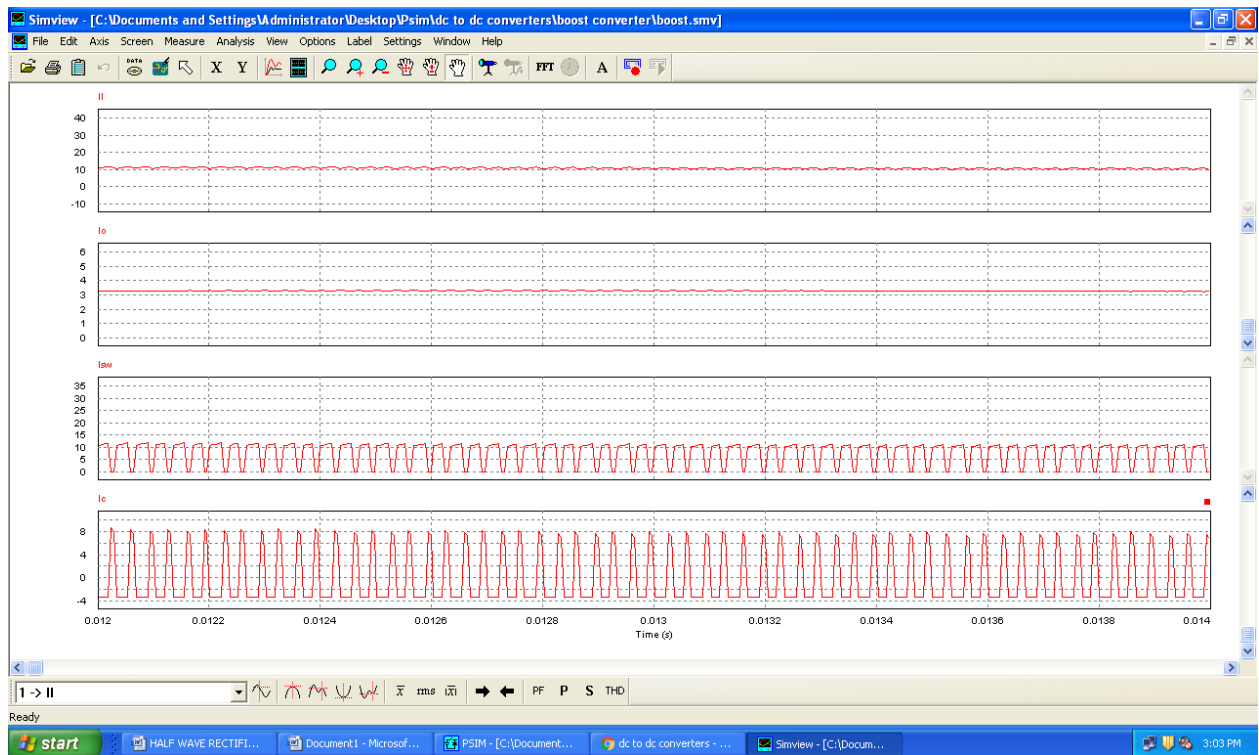





## Buck-Boost converter

Select the elements as shown above and connect them as shown in below figure with proper labeling

### Circuit diagram

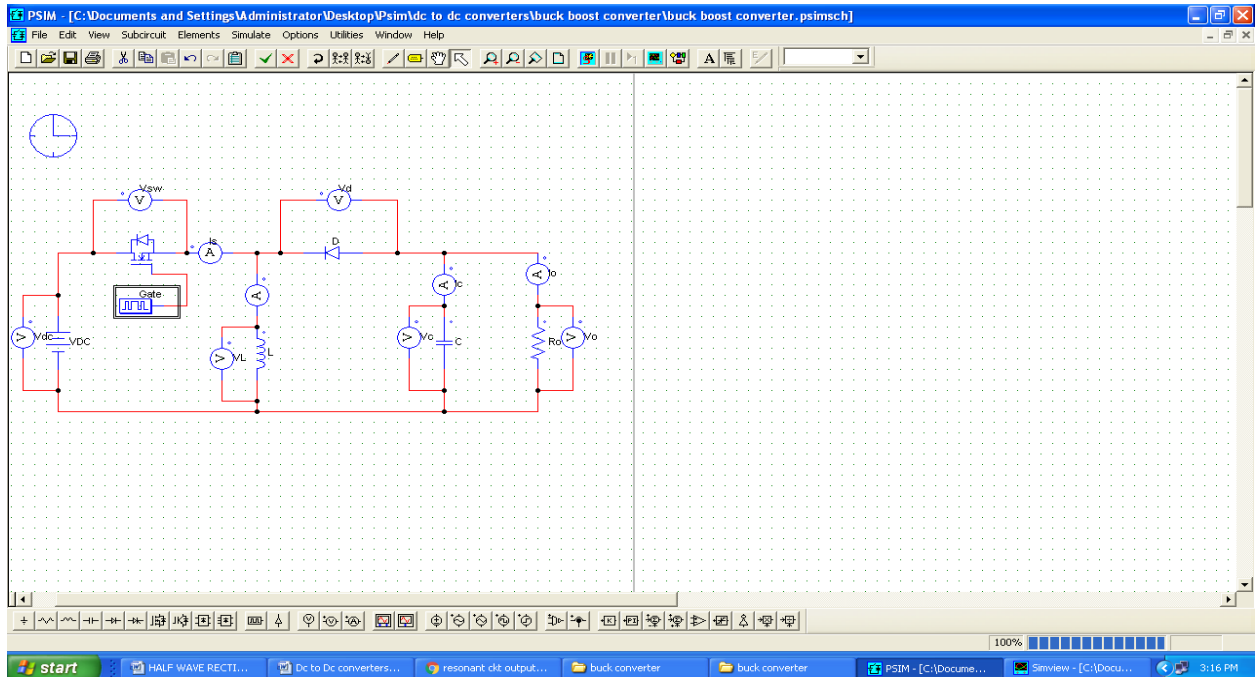


### Voltage waveforms

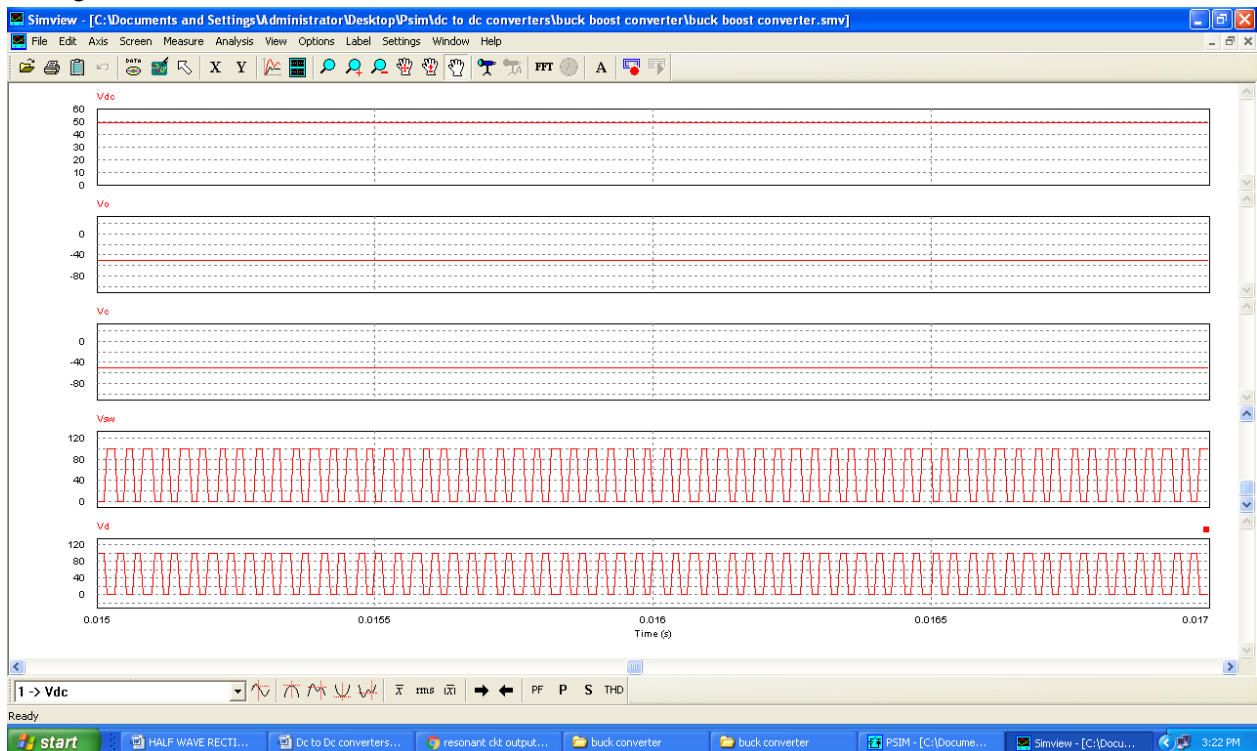



## Current waveforms

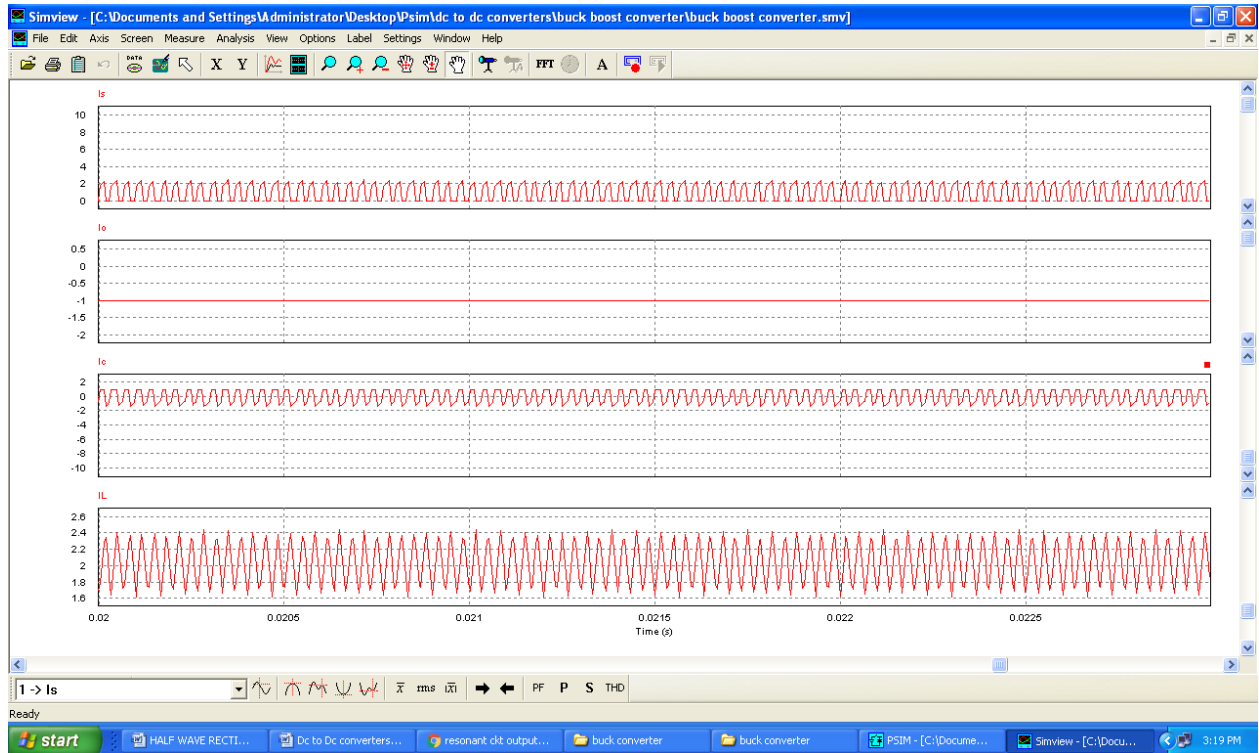





## Inverters

### Single phase inverter

Select the  
source

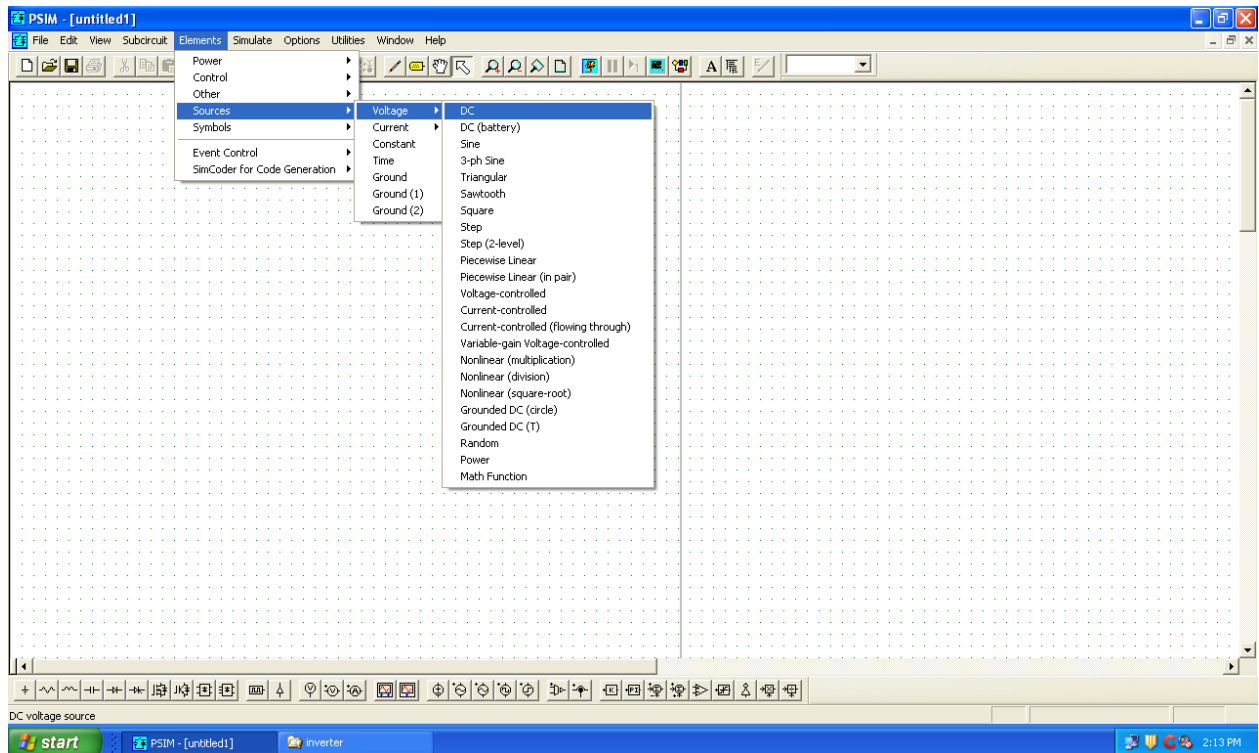


Select the mosfet

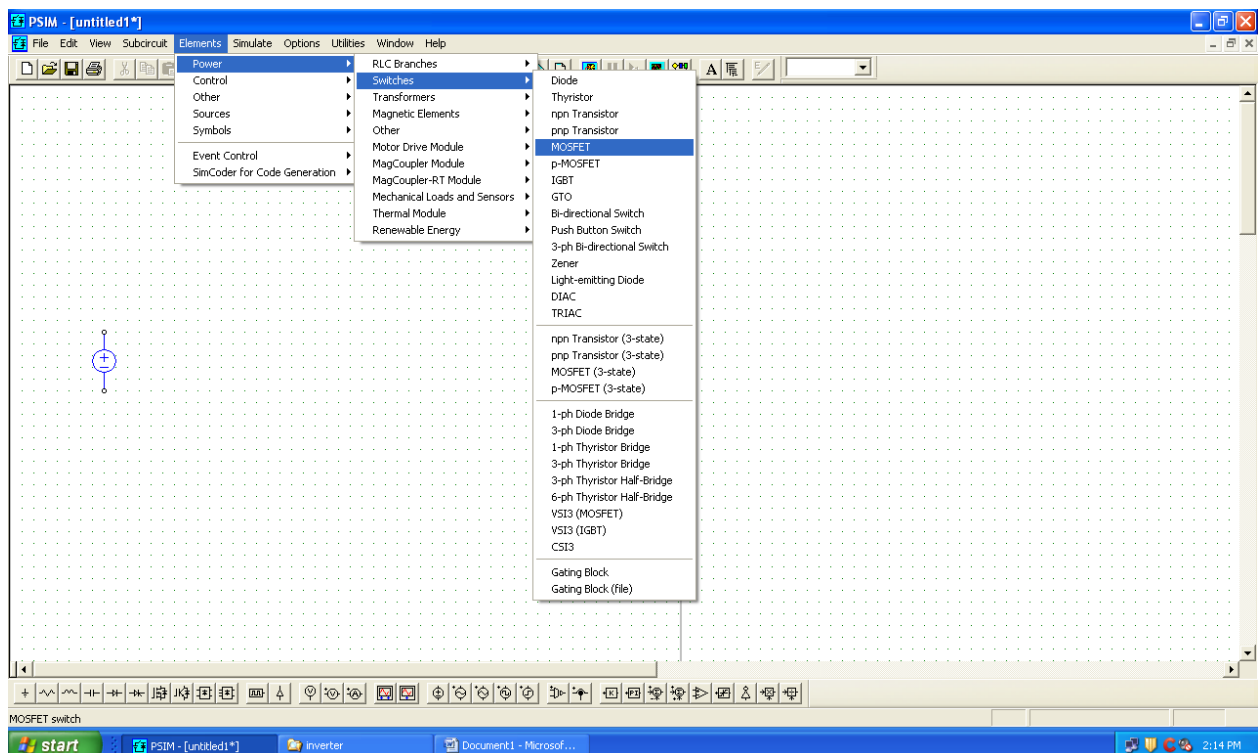




Select the resistor

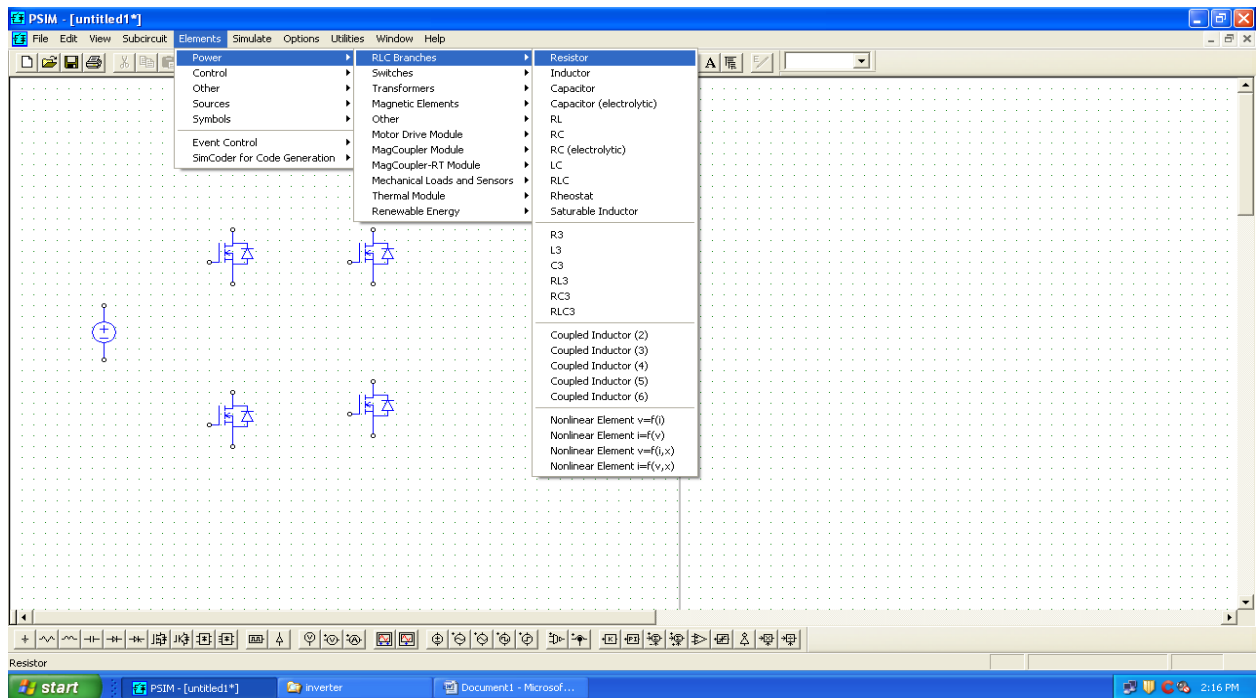


Select the ammeter

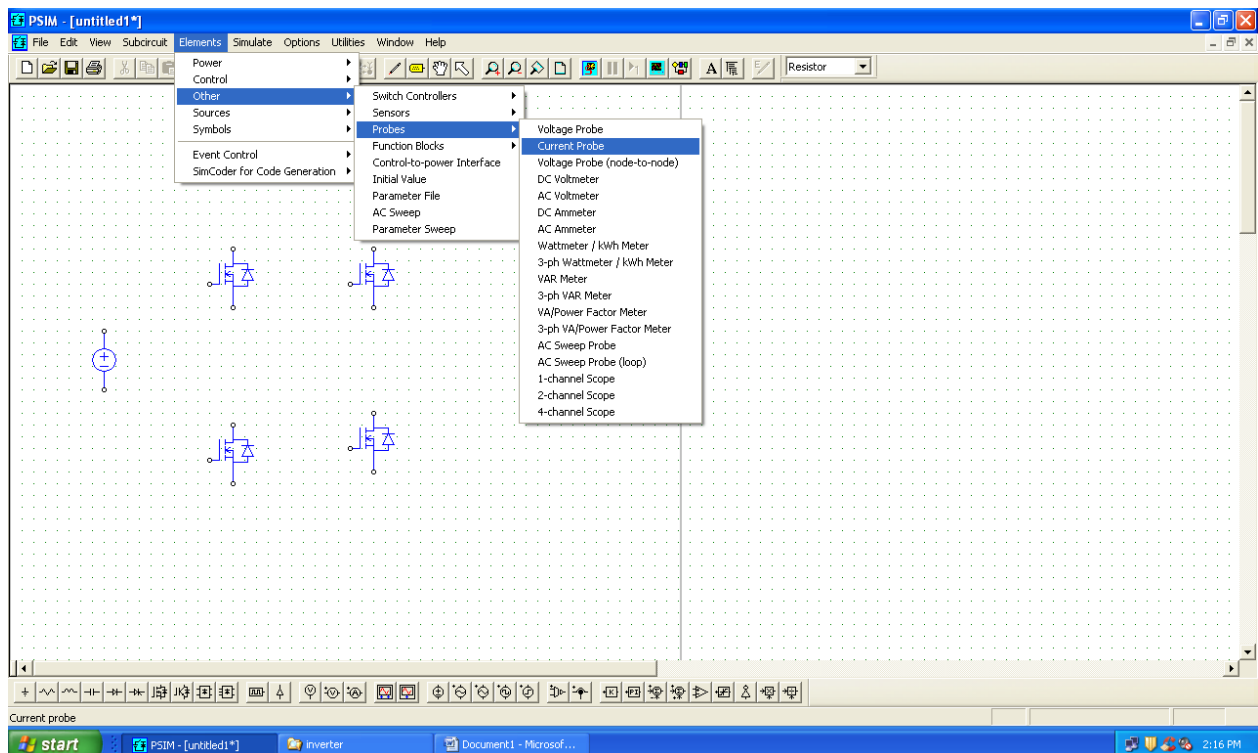




Select the volt meter

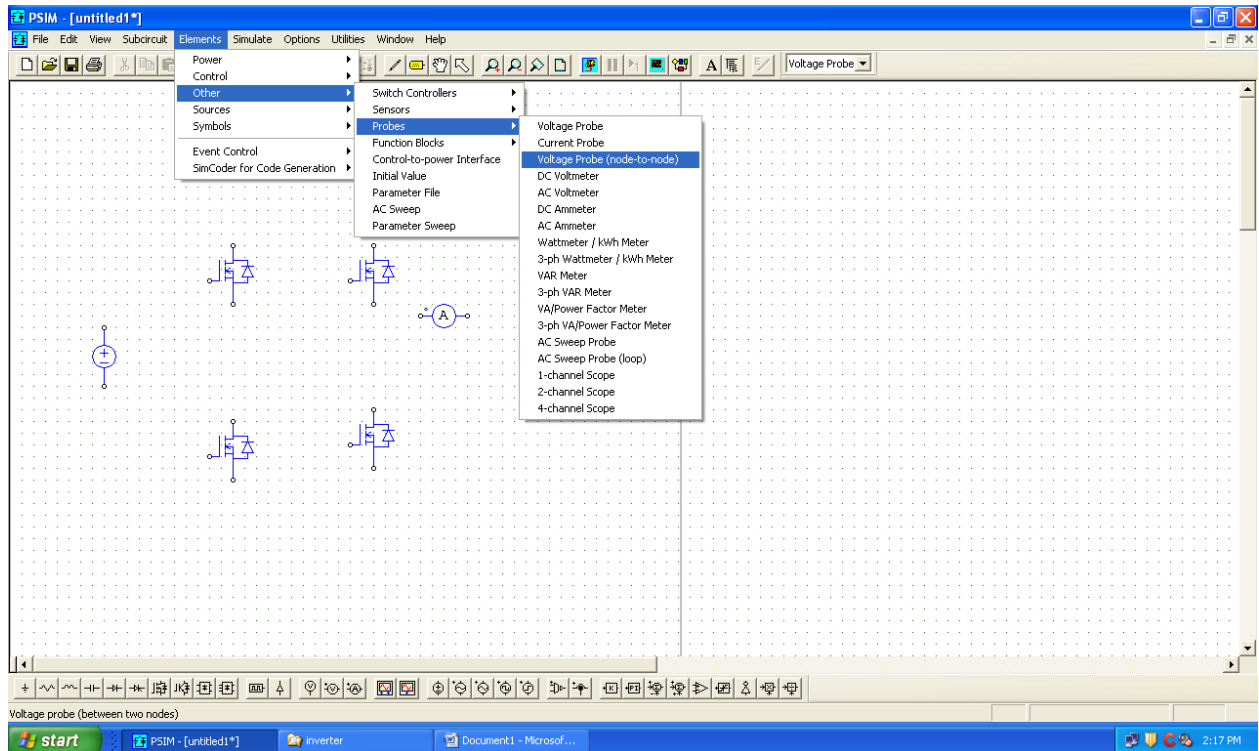


Select the gating block

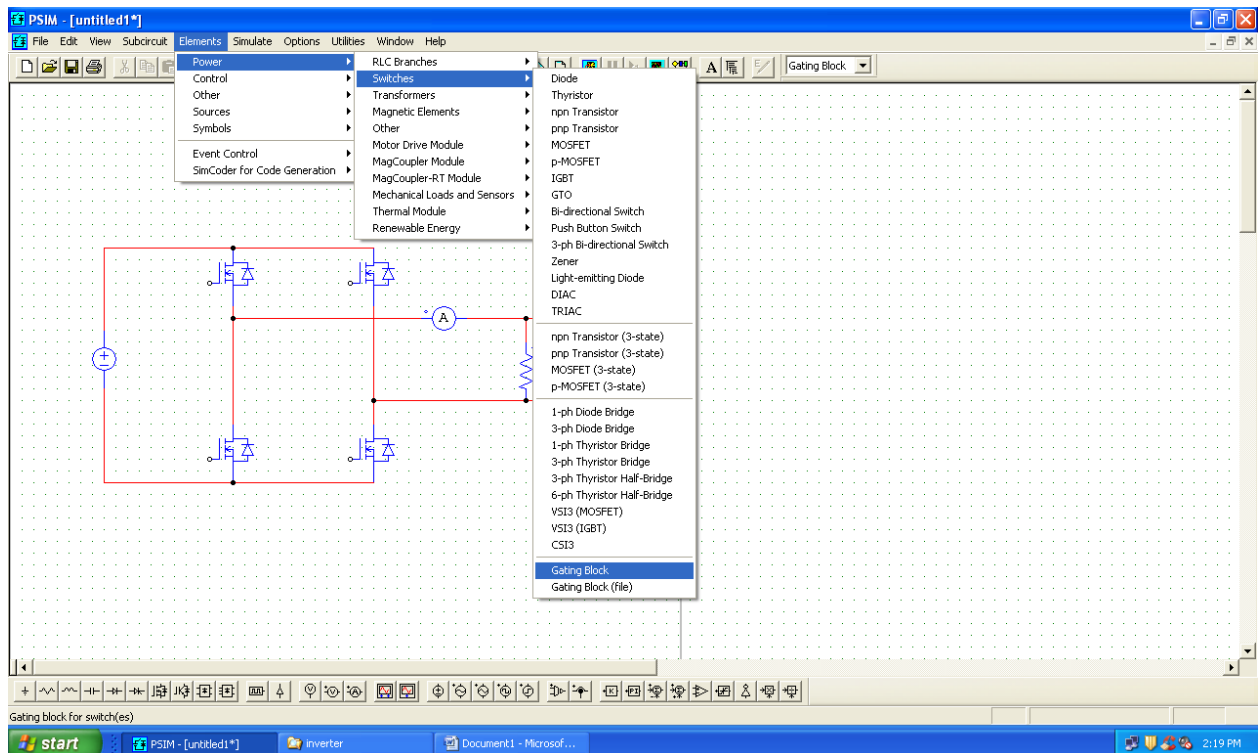







Connect the circuit by using wiring tool

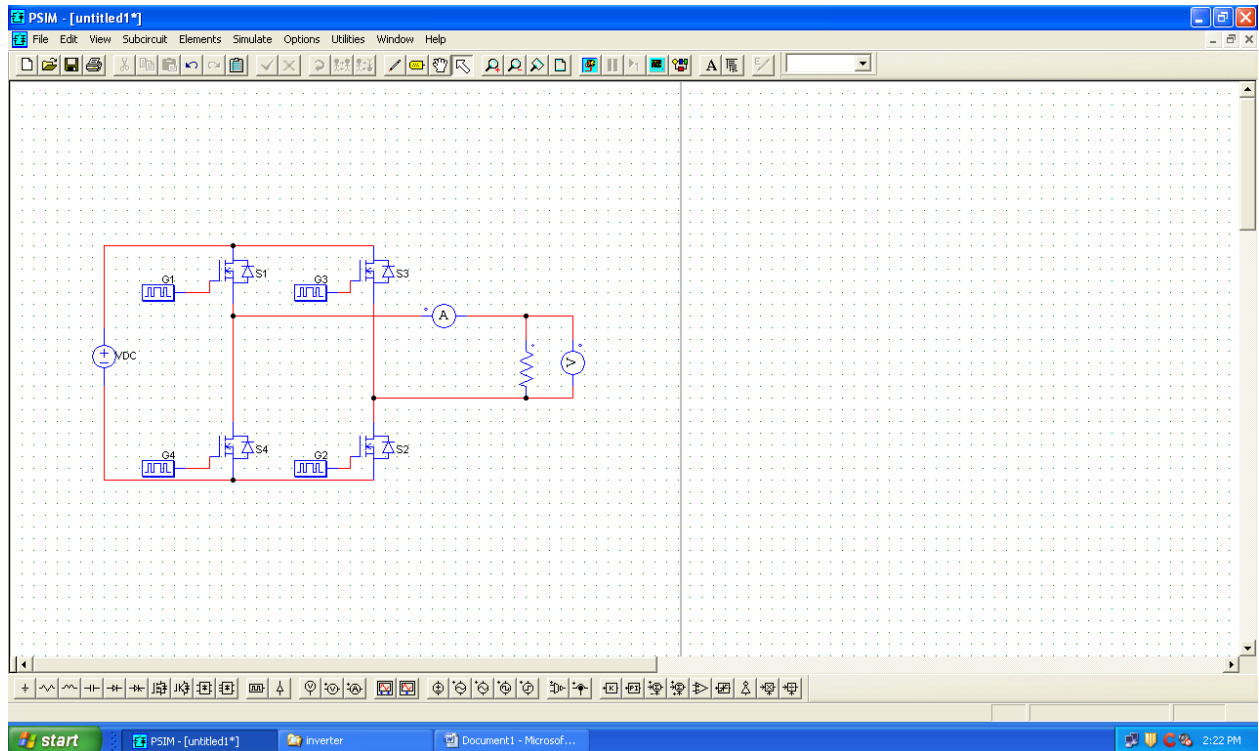


Select simulation control

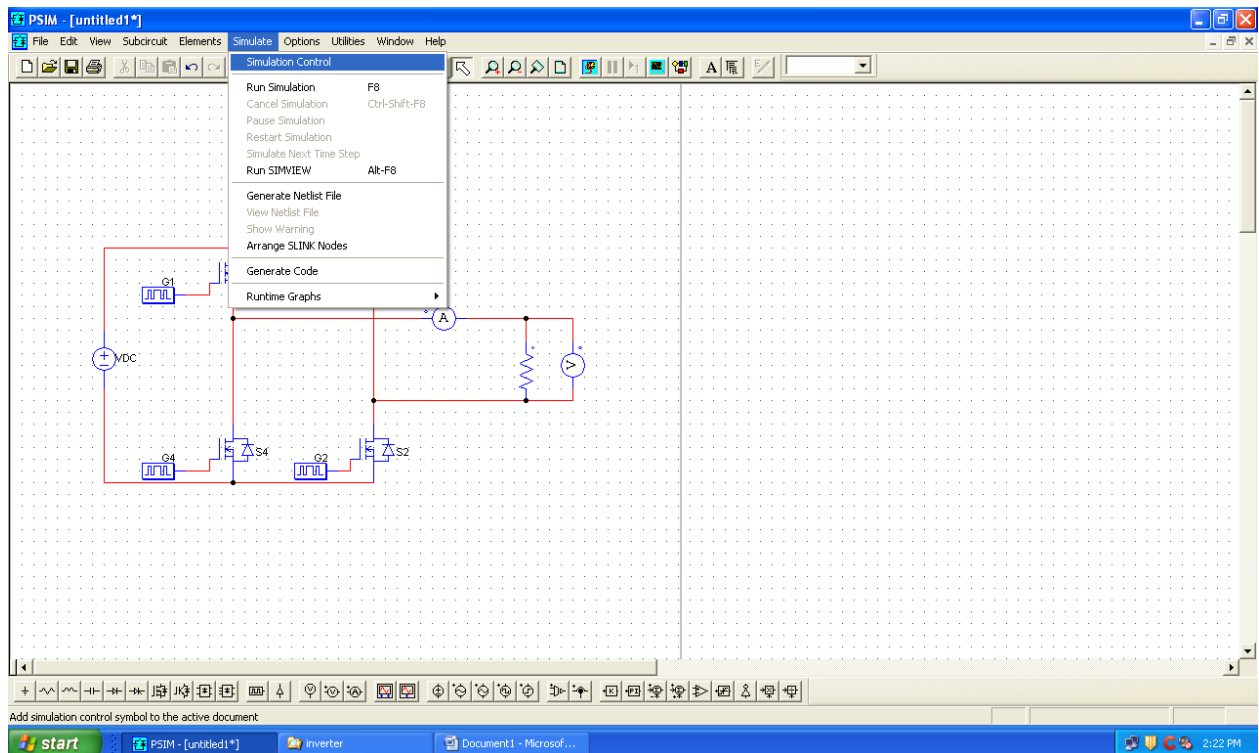

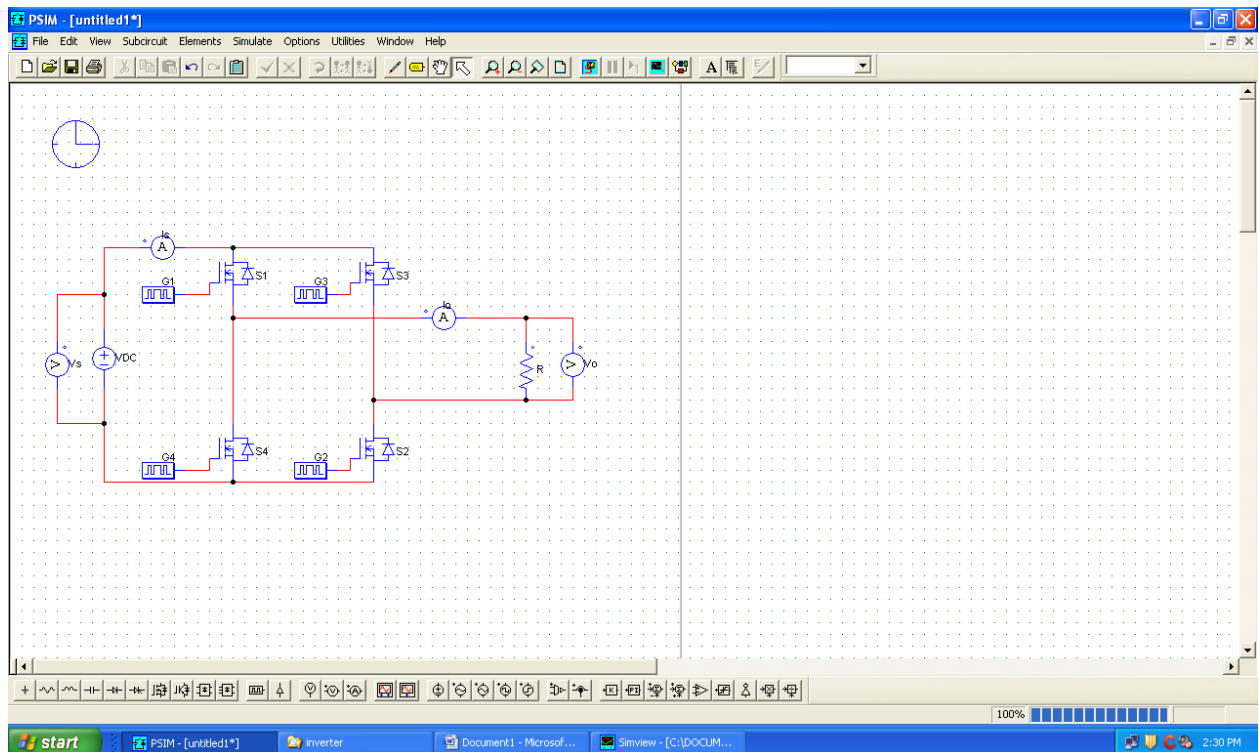


## Output waveforms

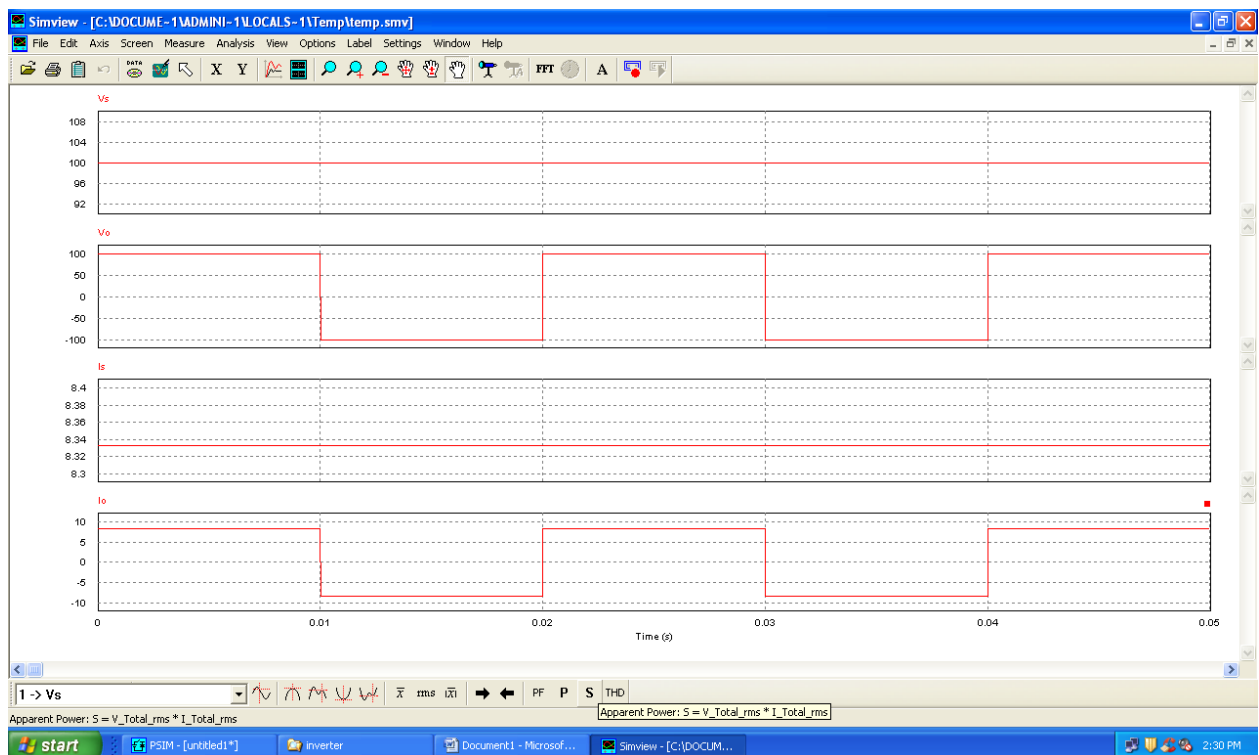





## 3-phase inverter

Select the dc source

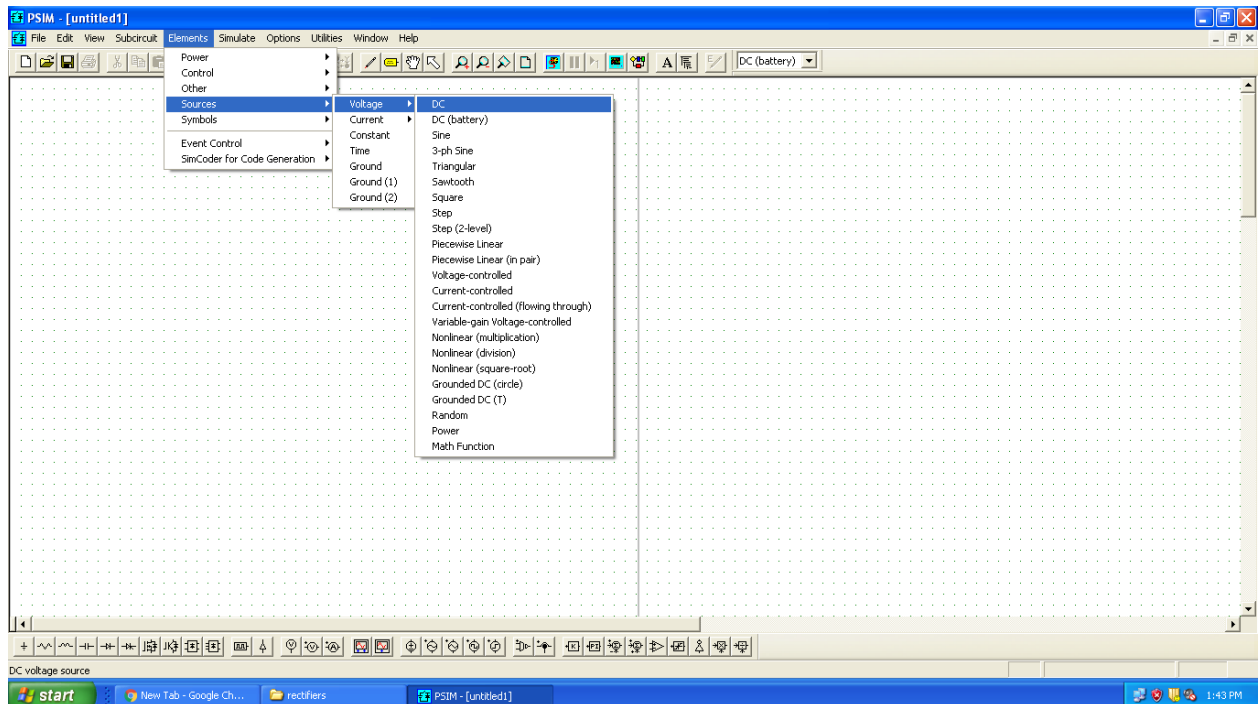



Select the Mosfet

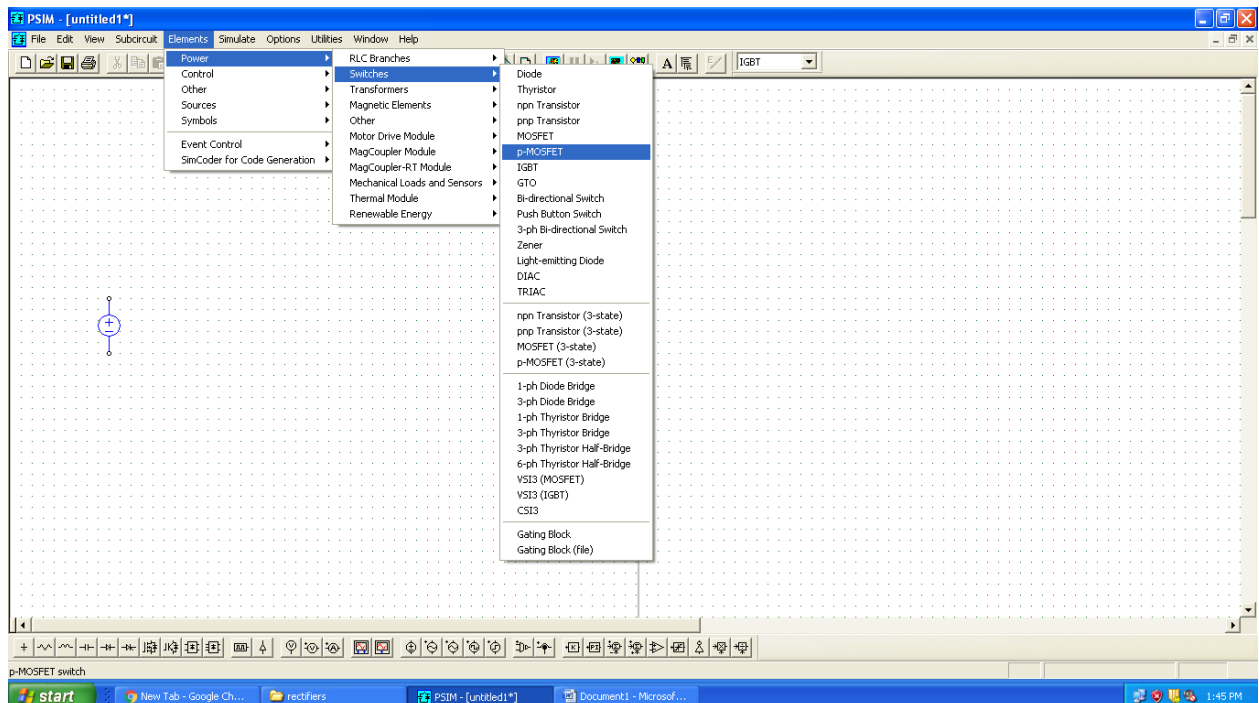

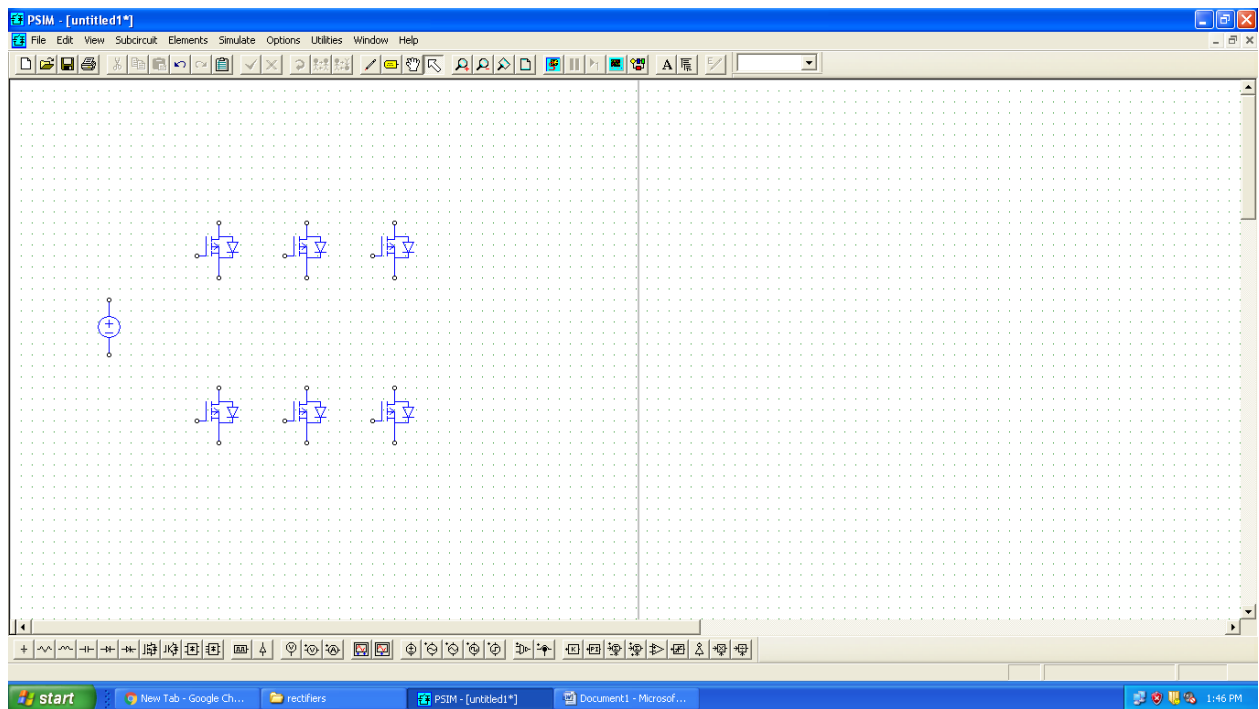



Select 3-phase R-load

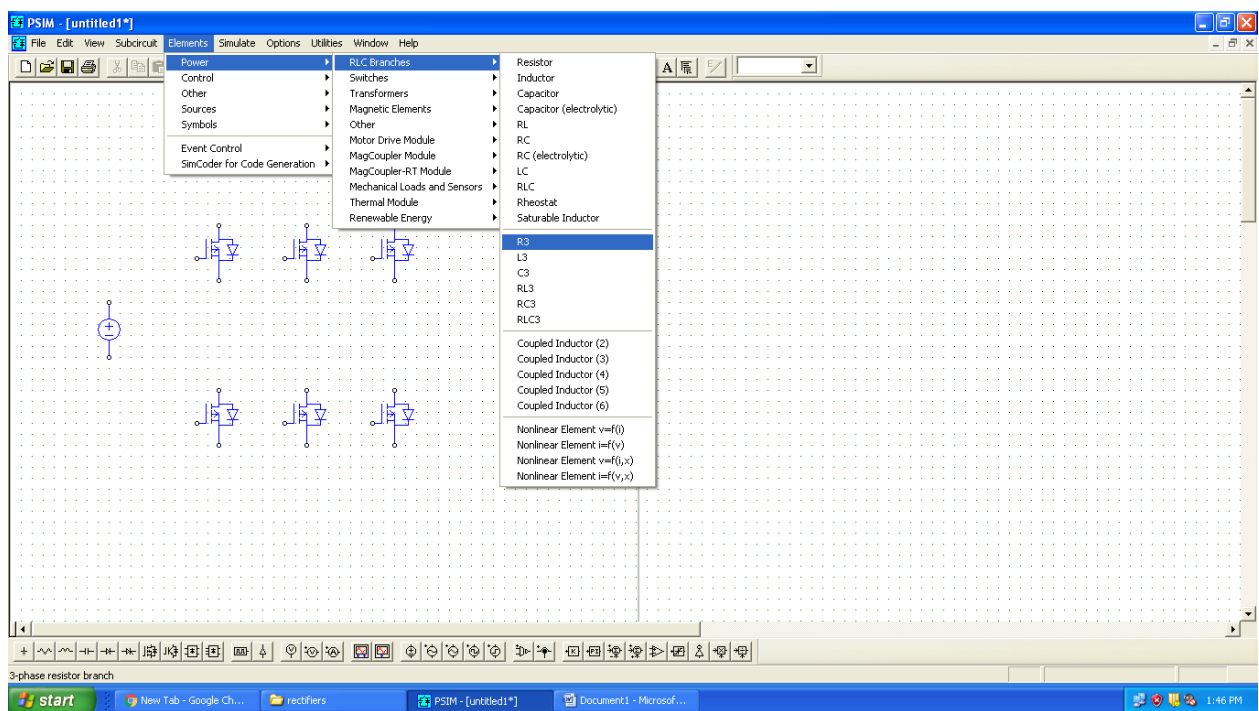

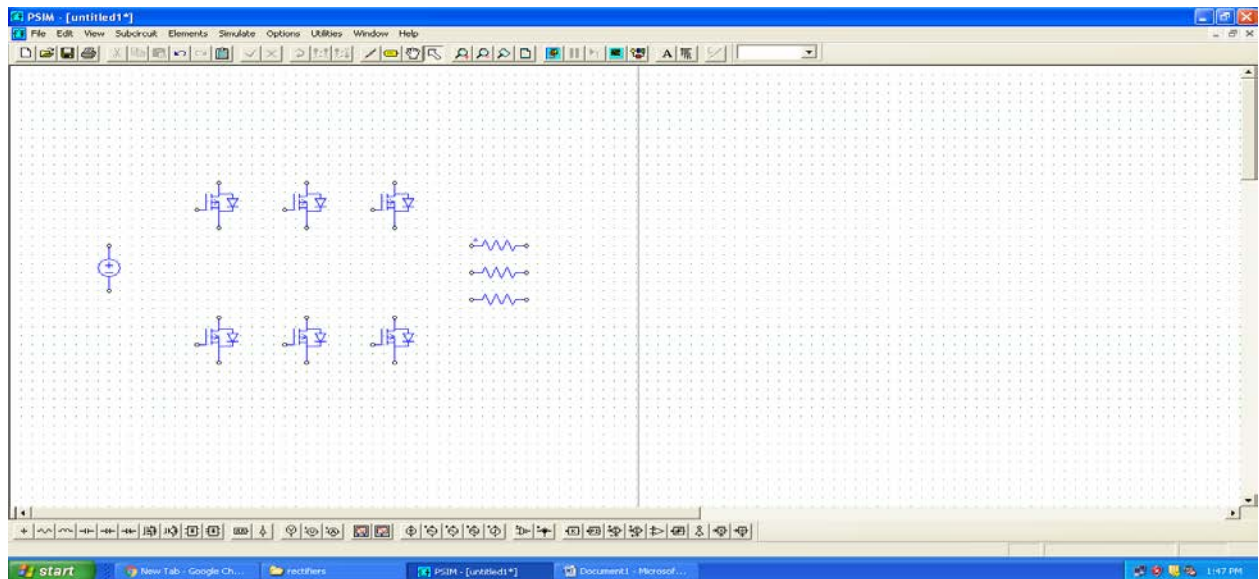


Select gating block

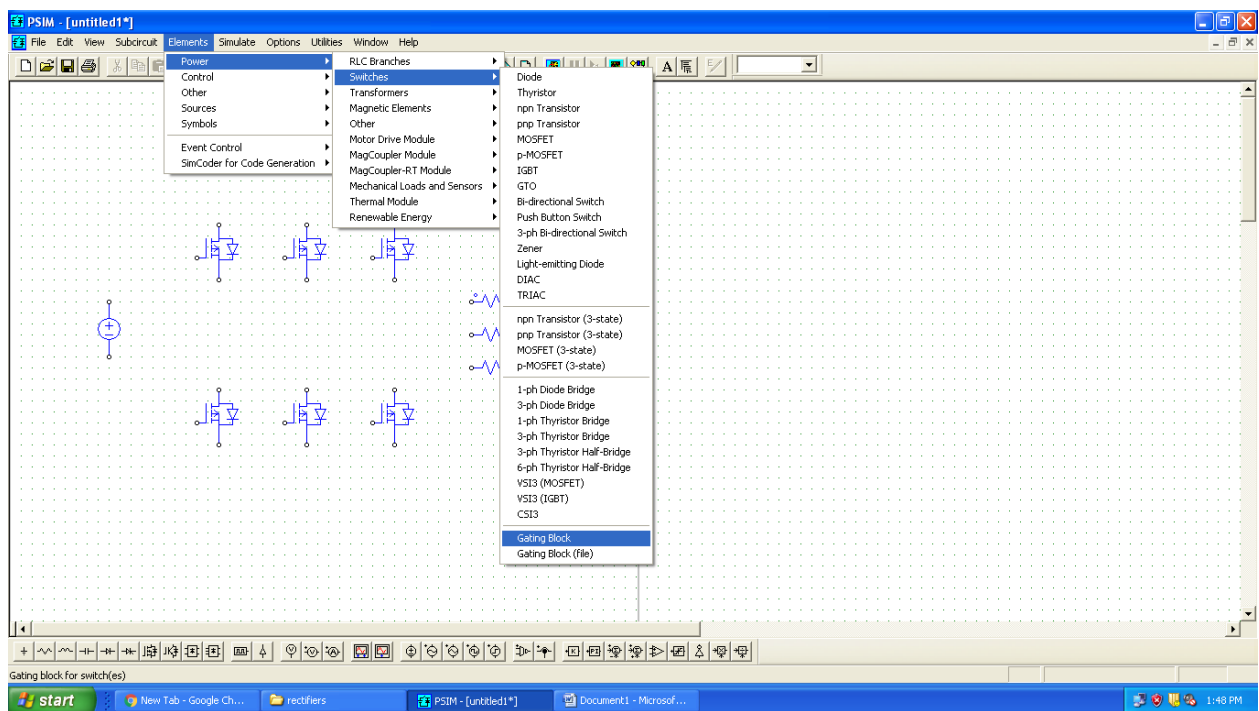


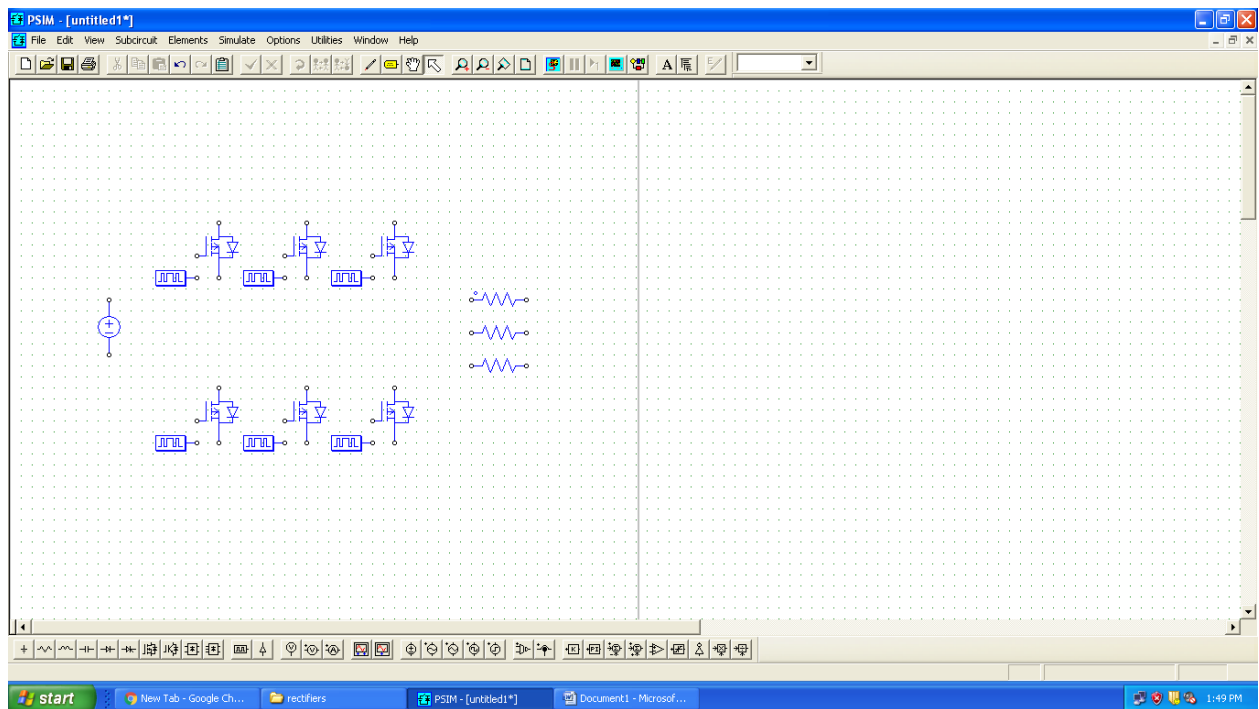


Select volt meter

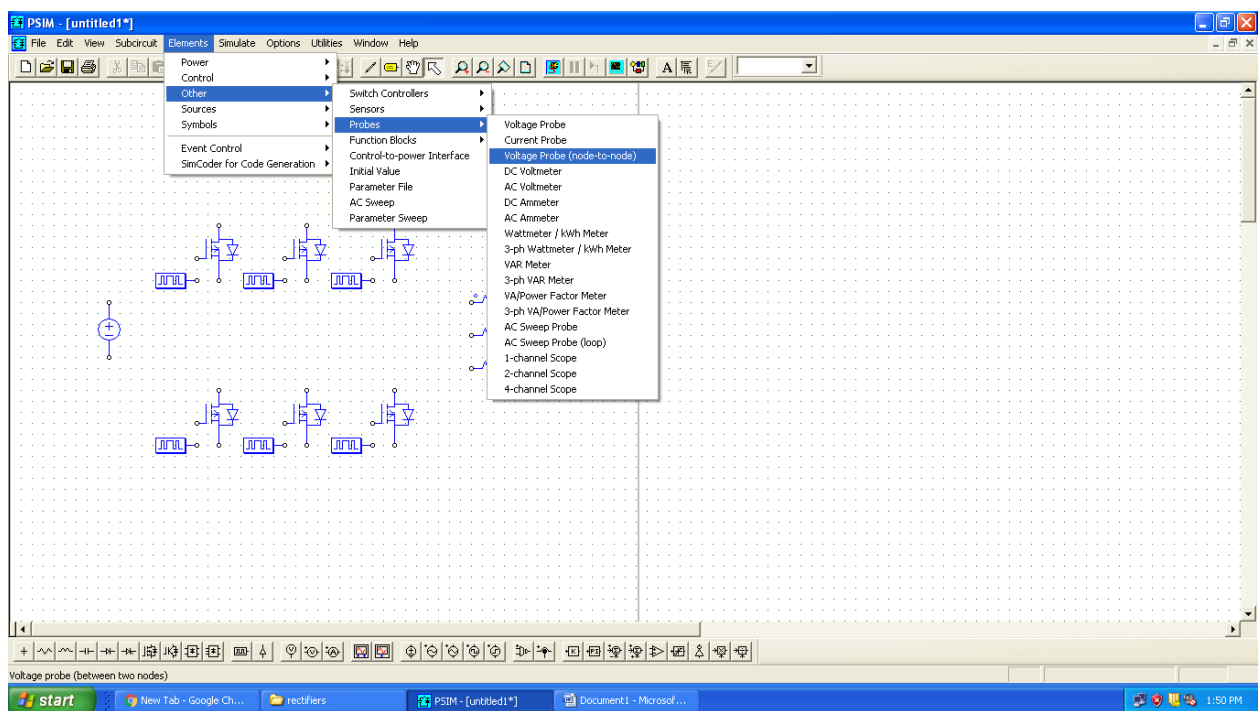



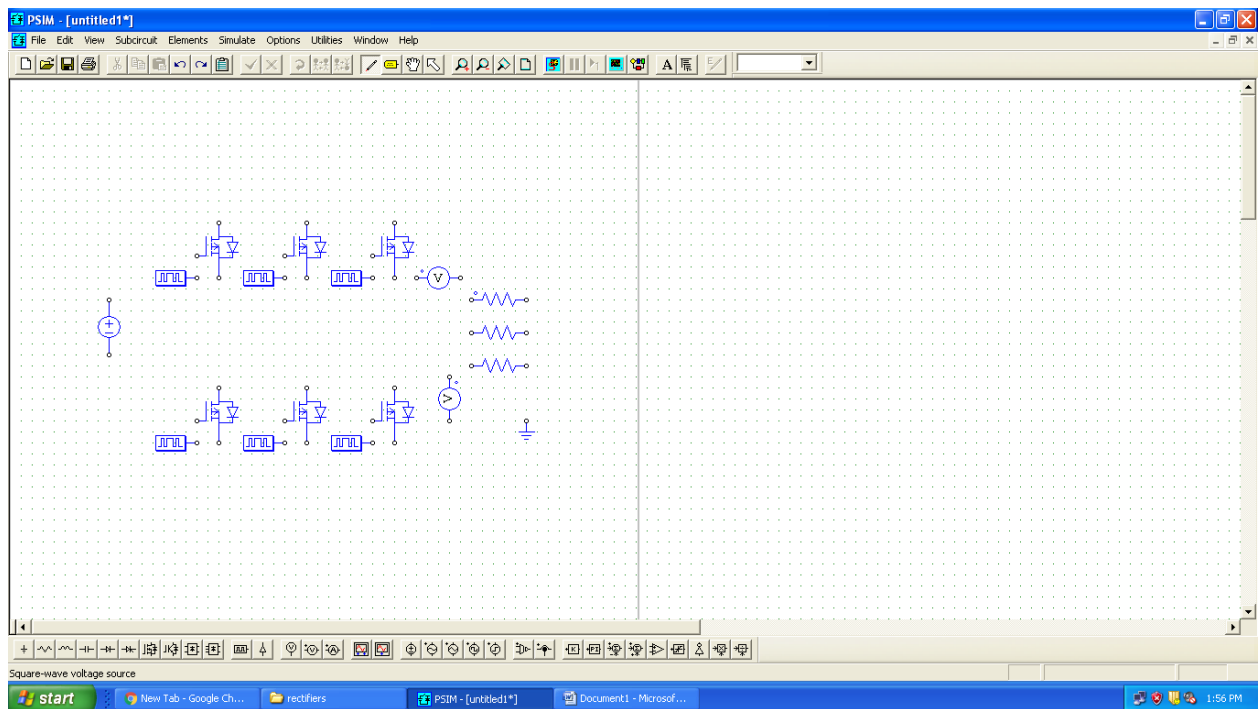



Connect the circuit by using wiring tool

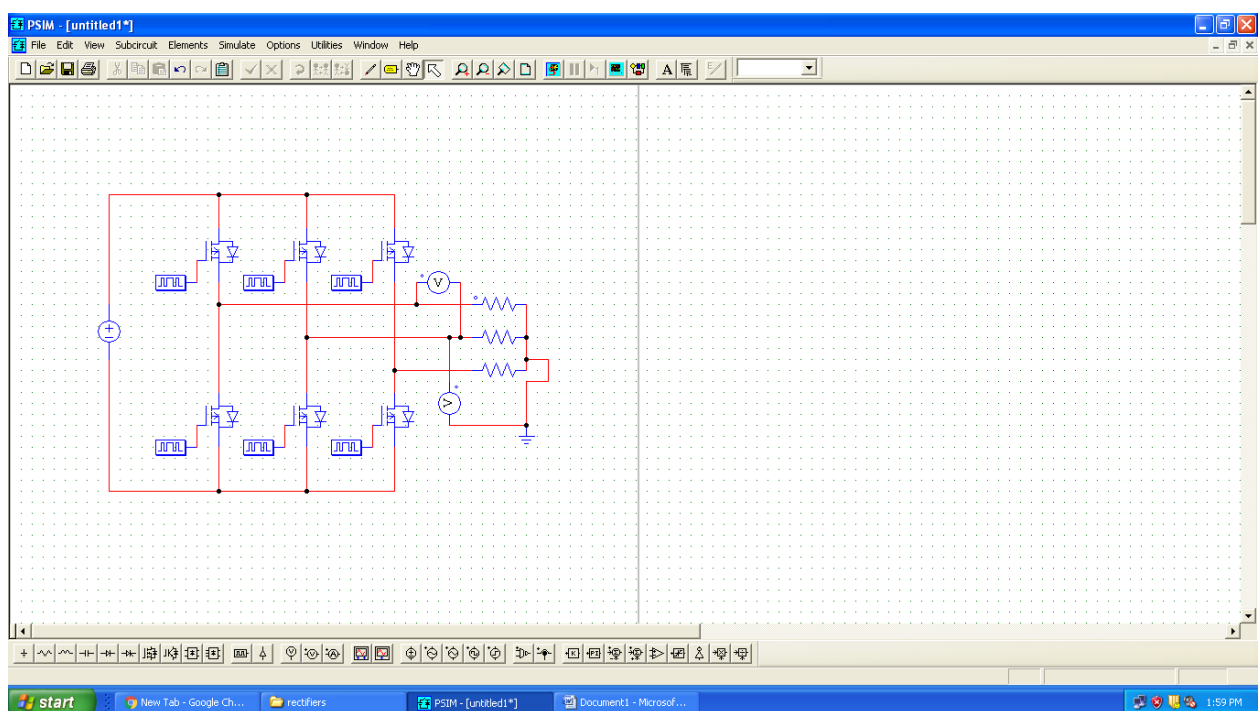







Select the simulation control

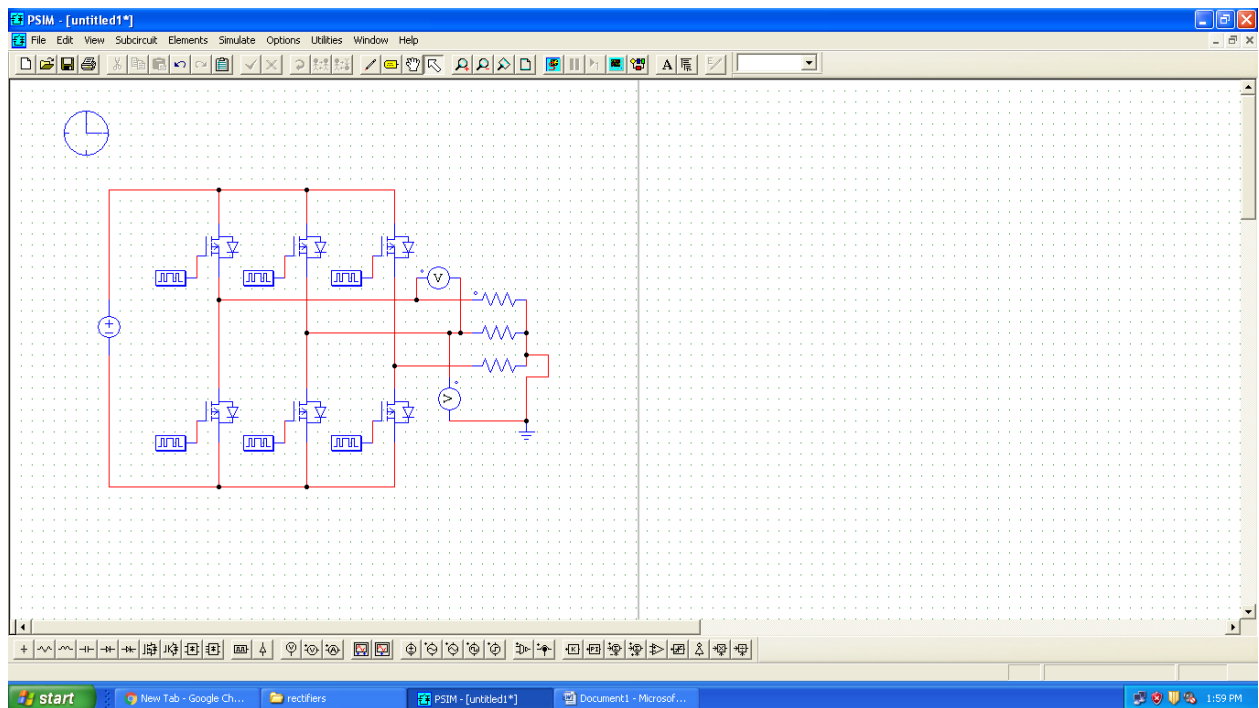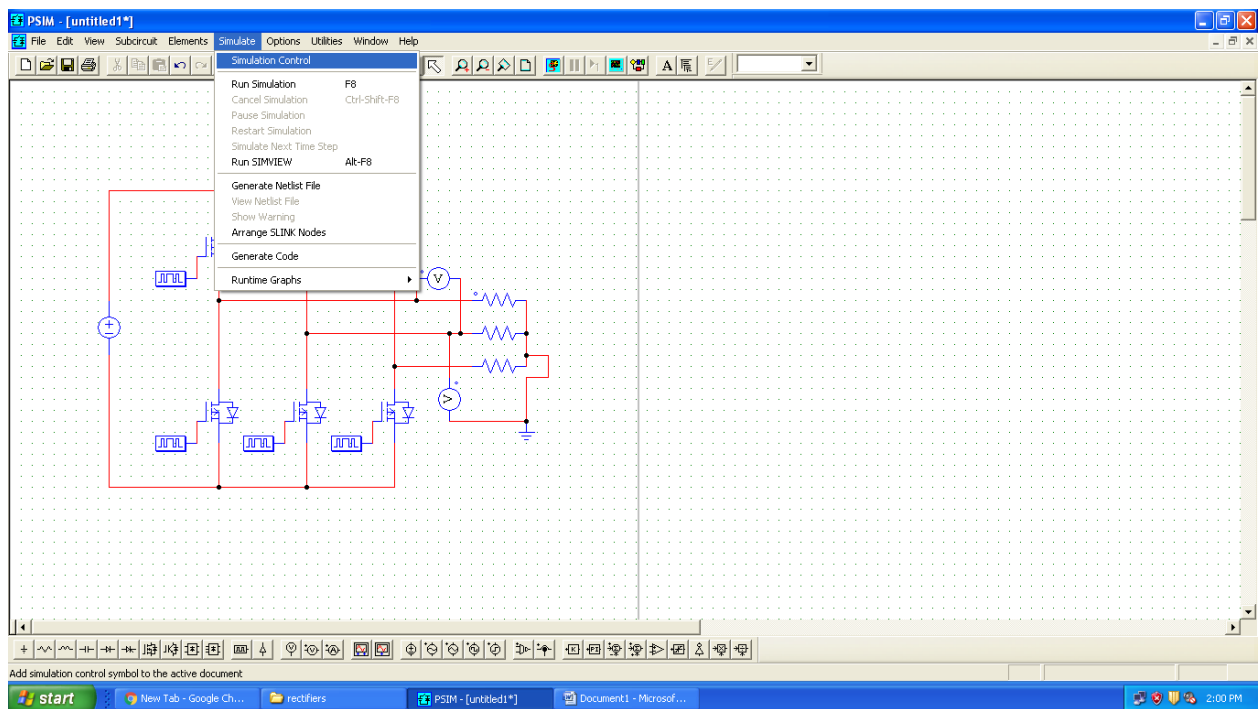


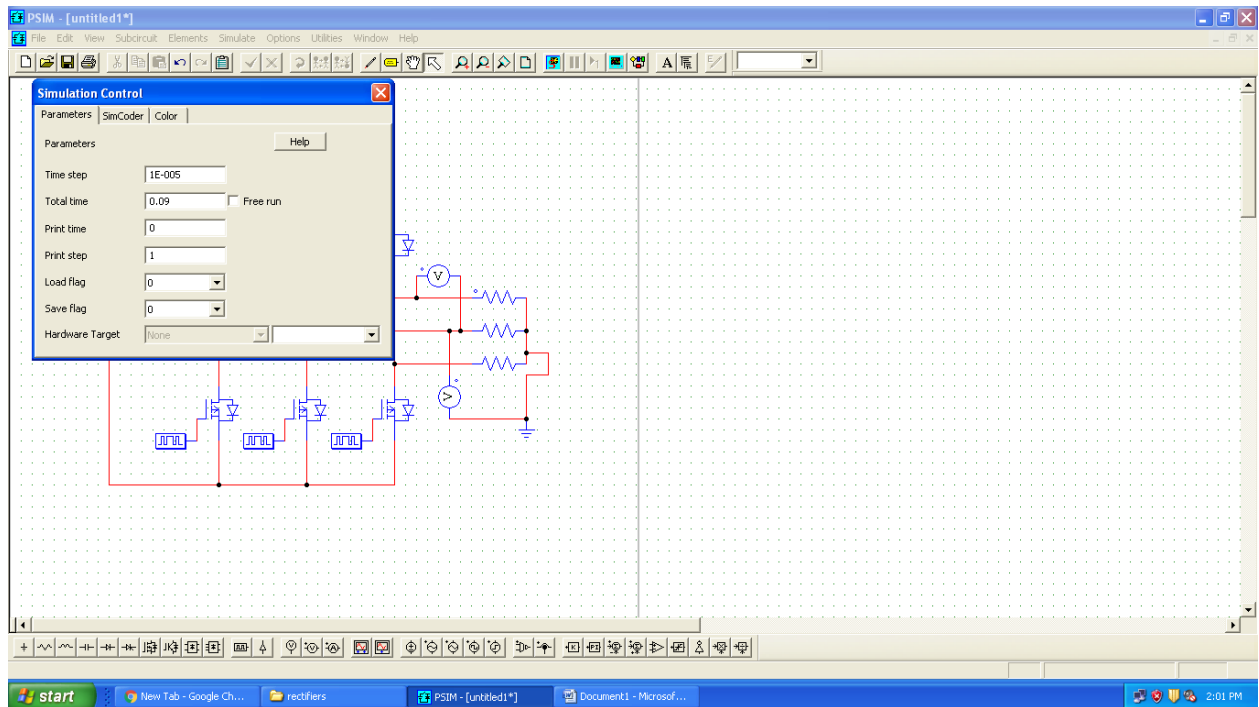




Give the proper labling


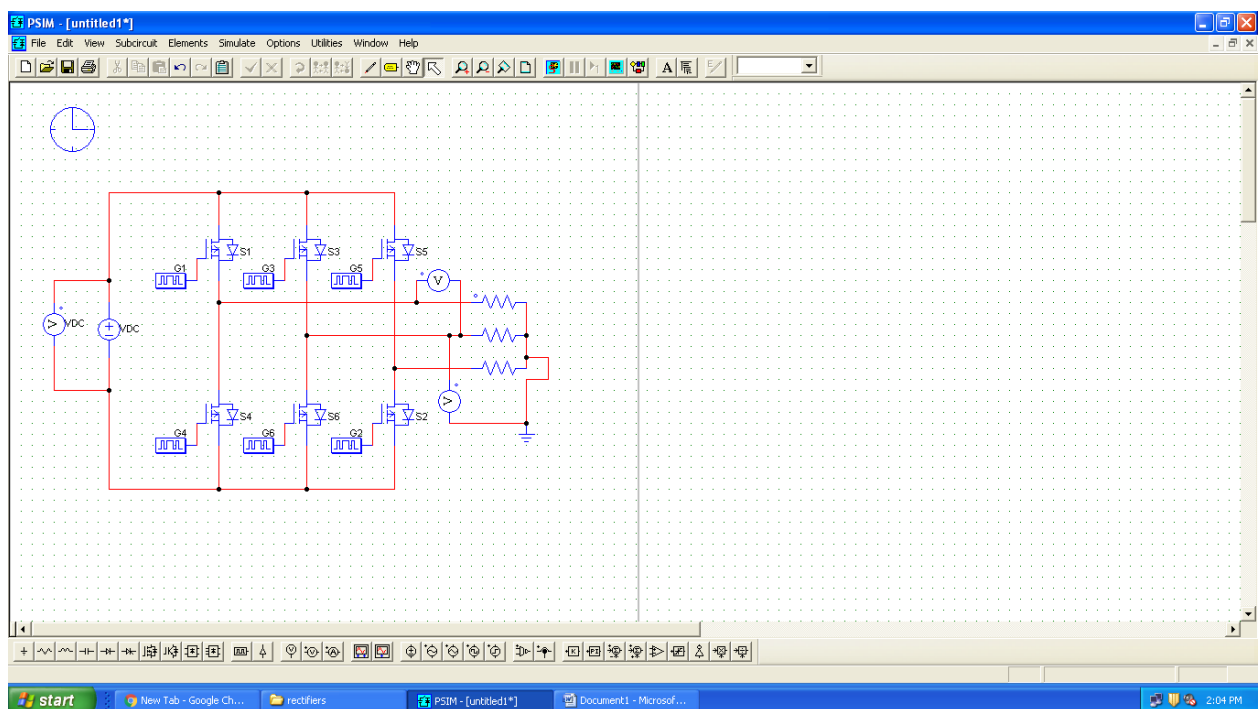




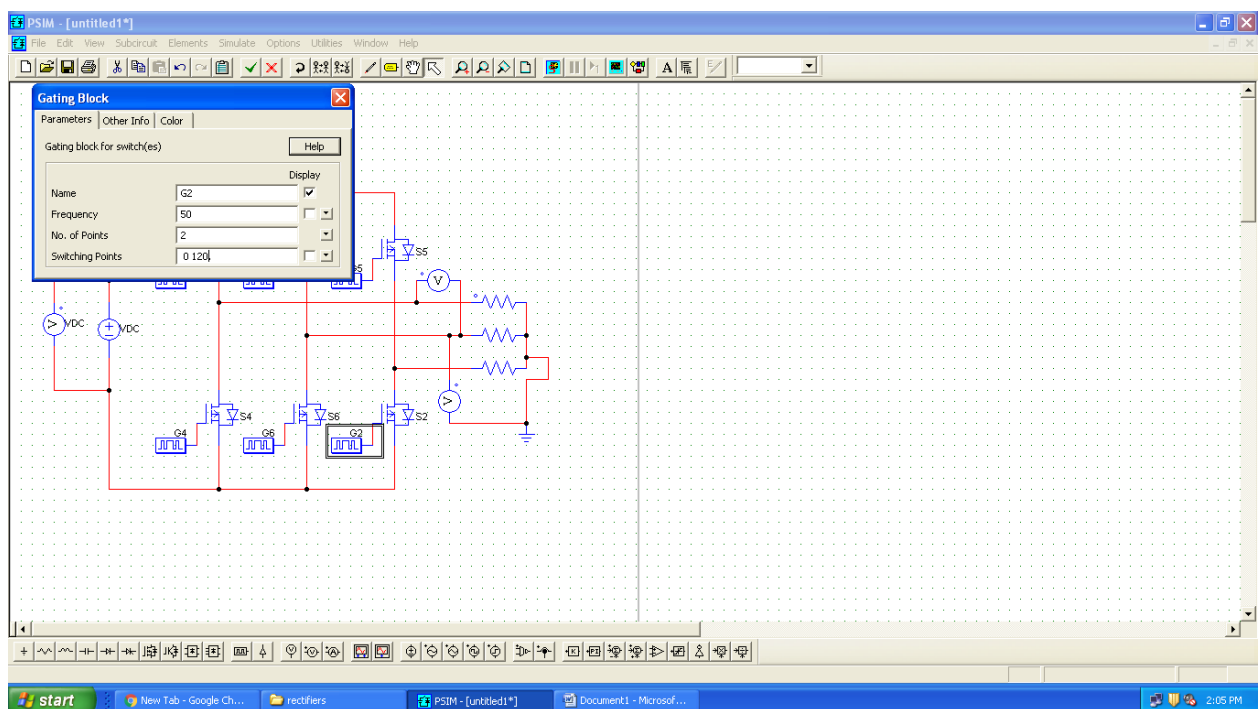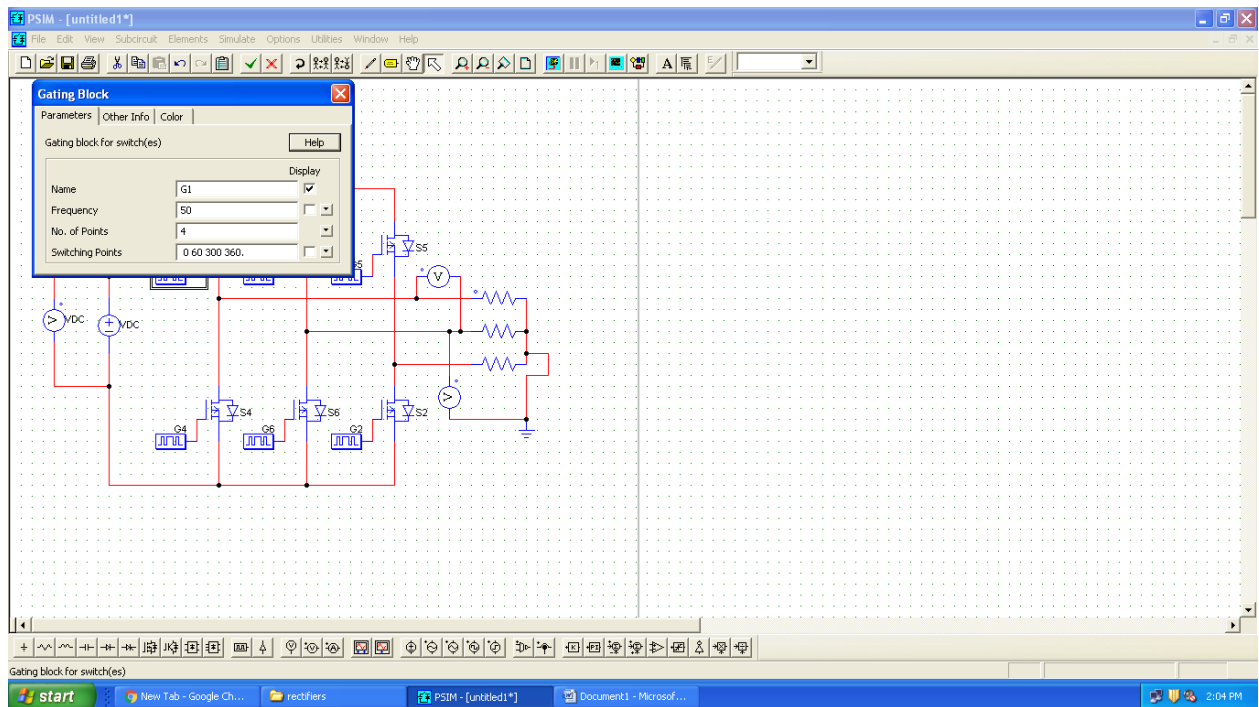Give all the gating parameters as shown below




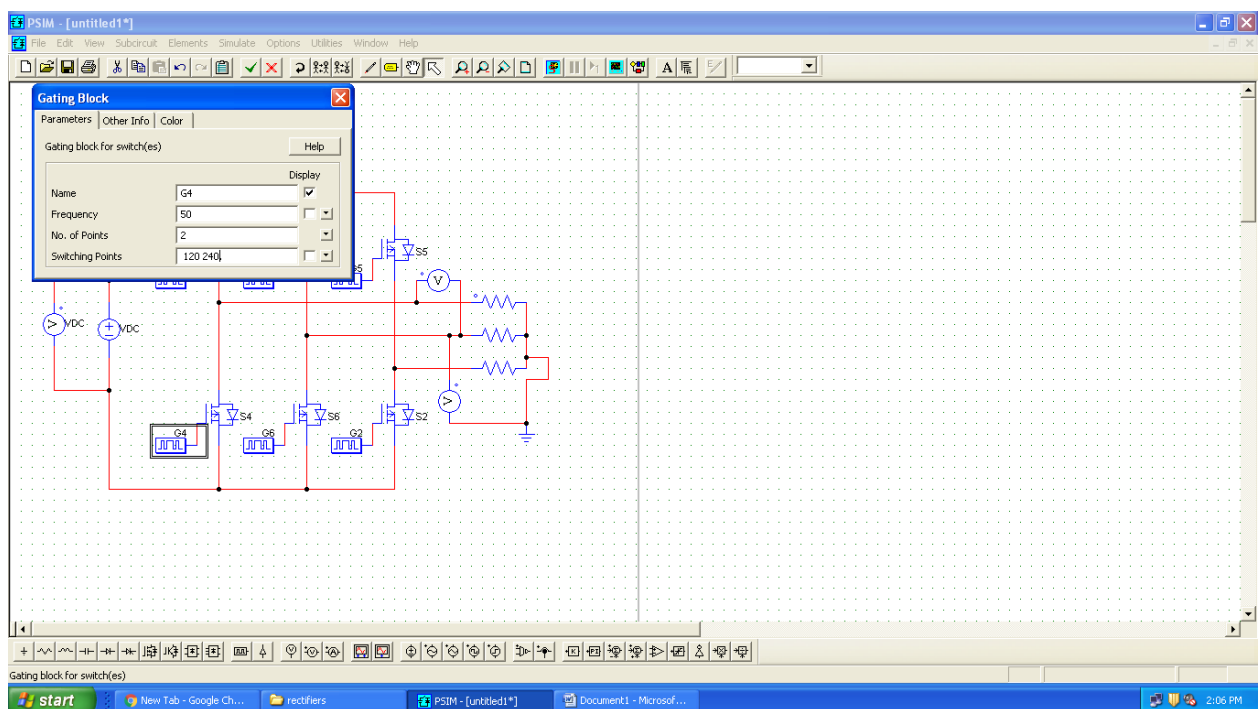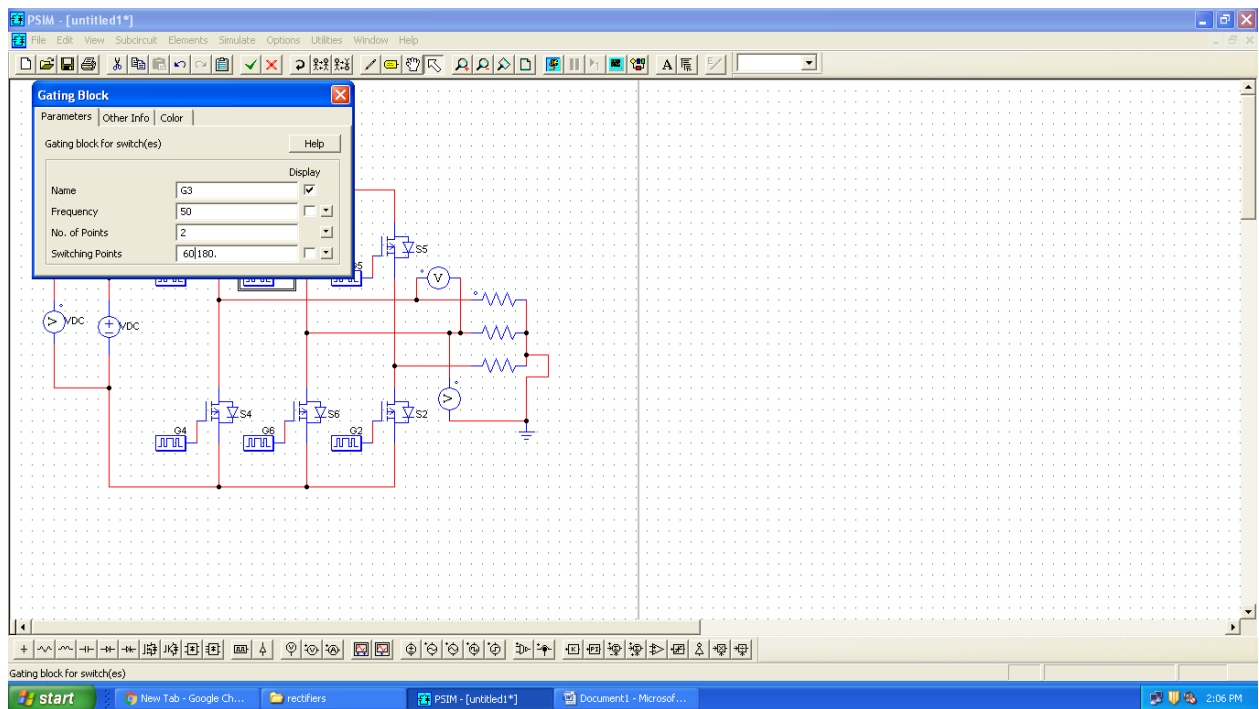

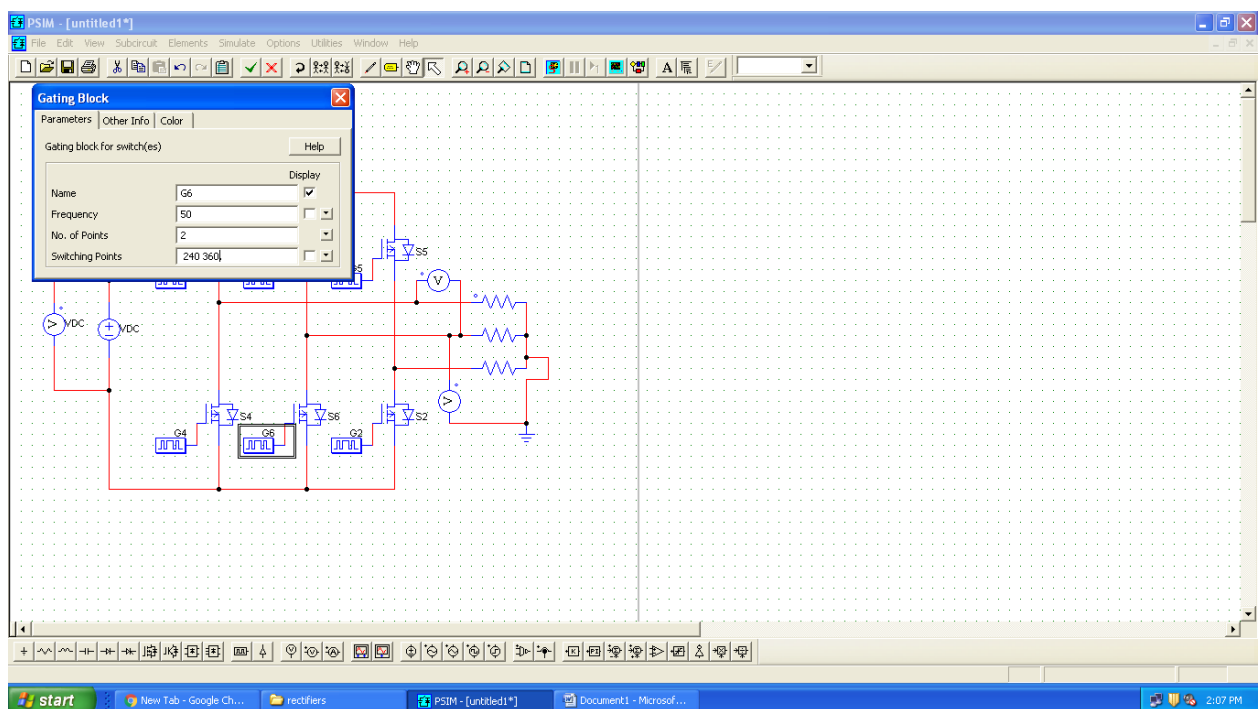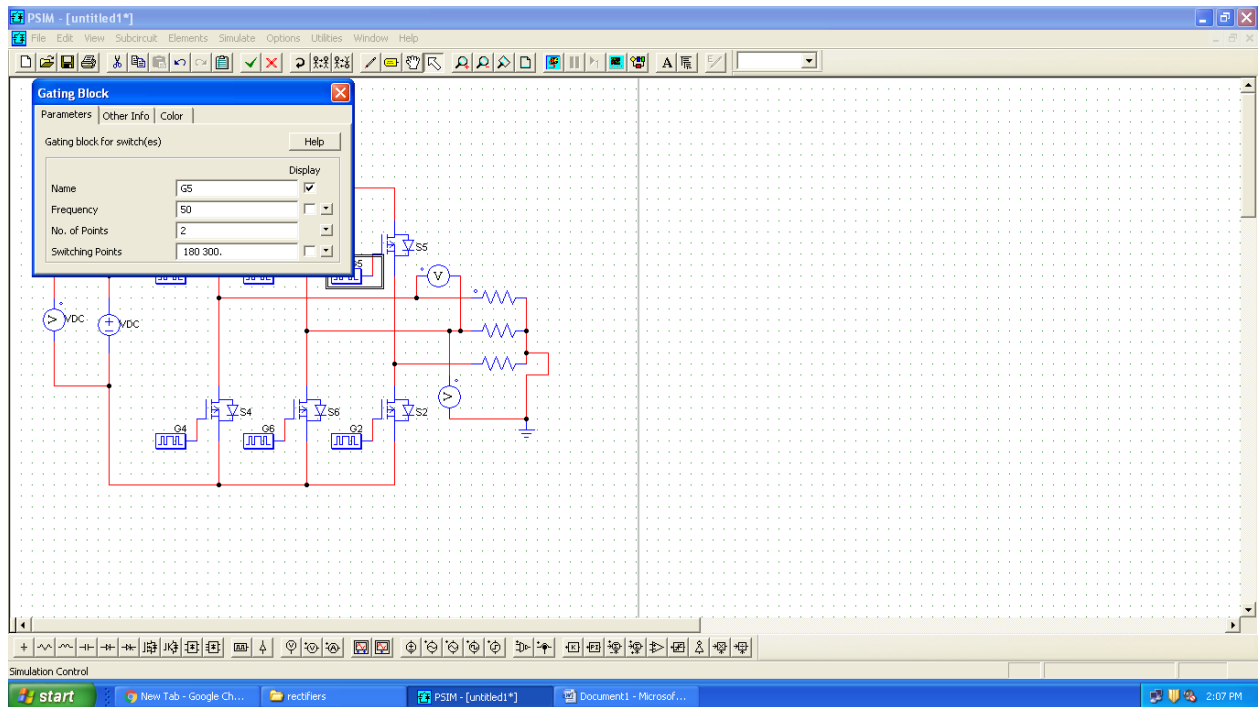




## Circuit diagram

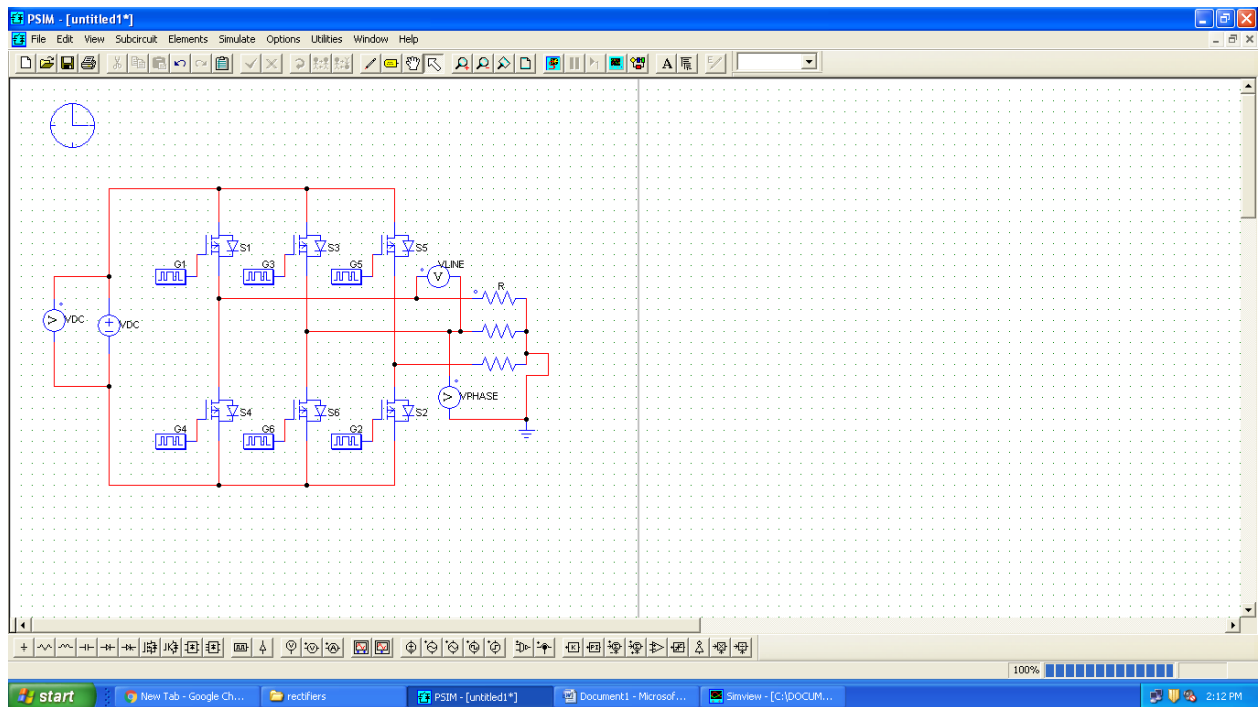



## Output waveforms

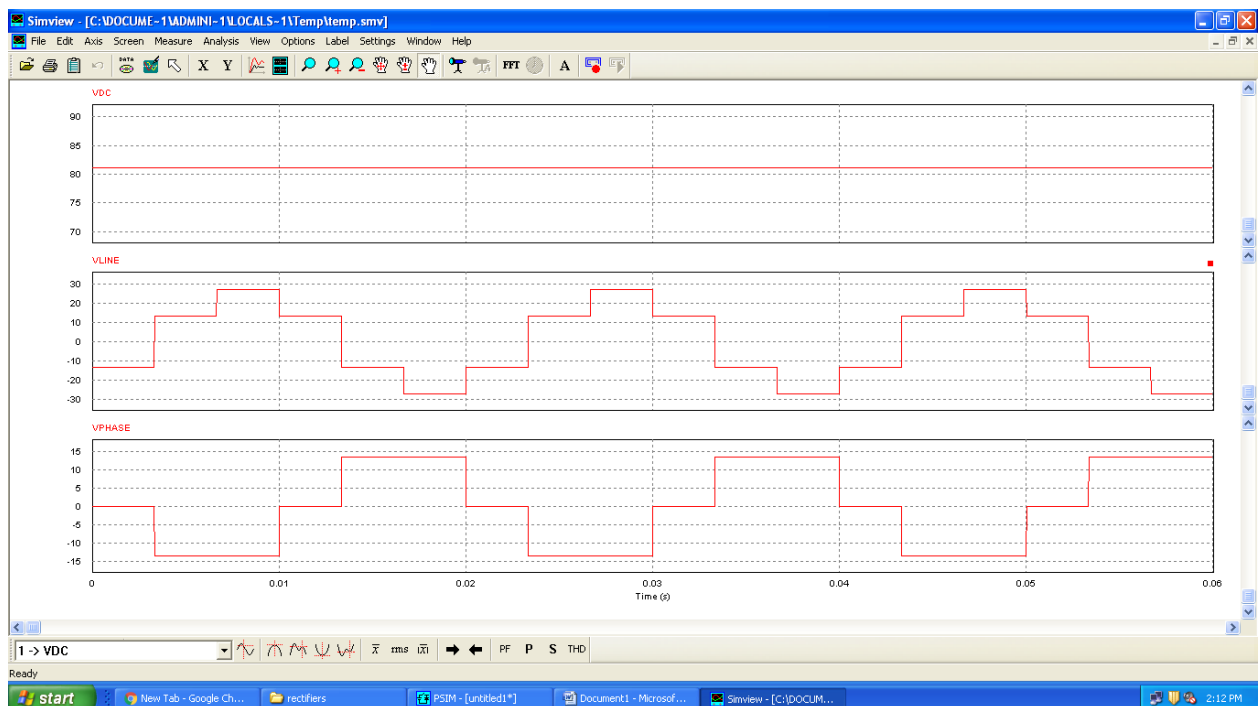





## Cycloconverter

select the thyristor

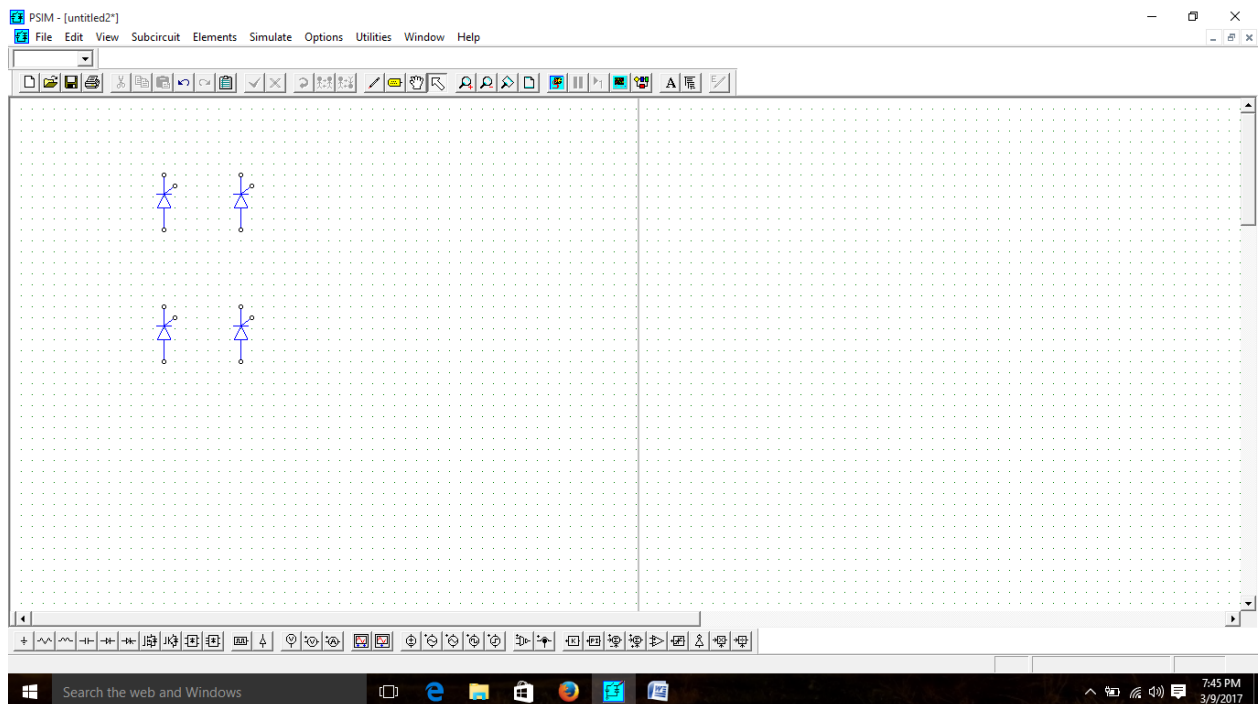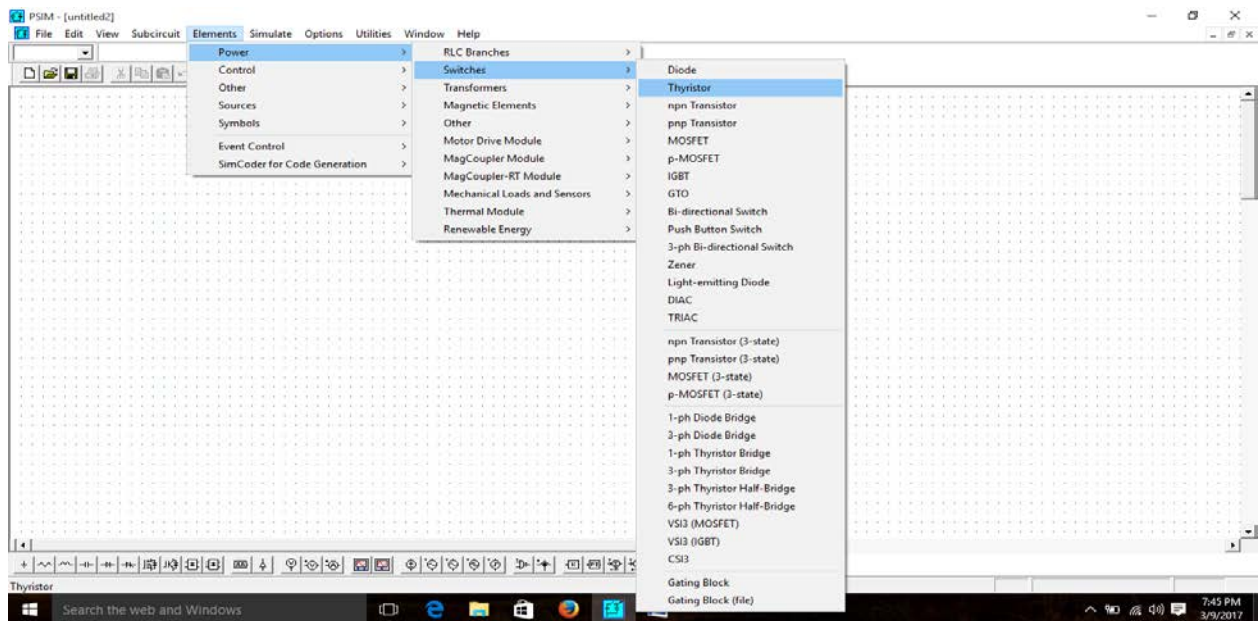


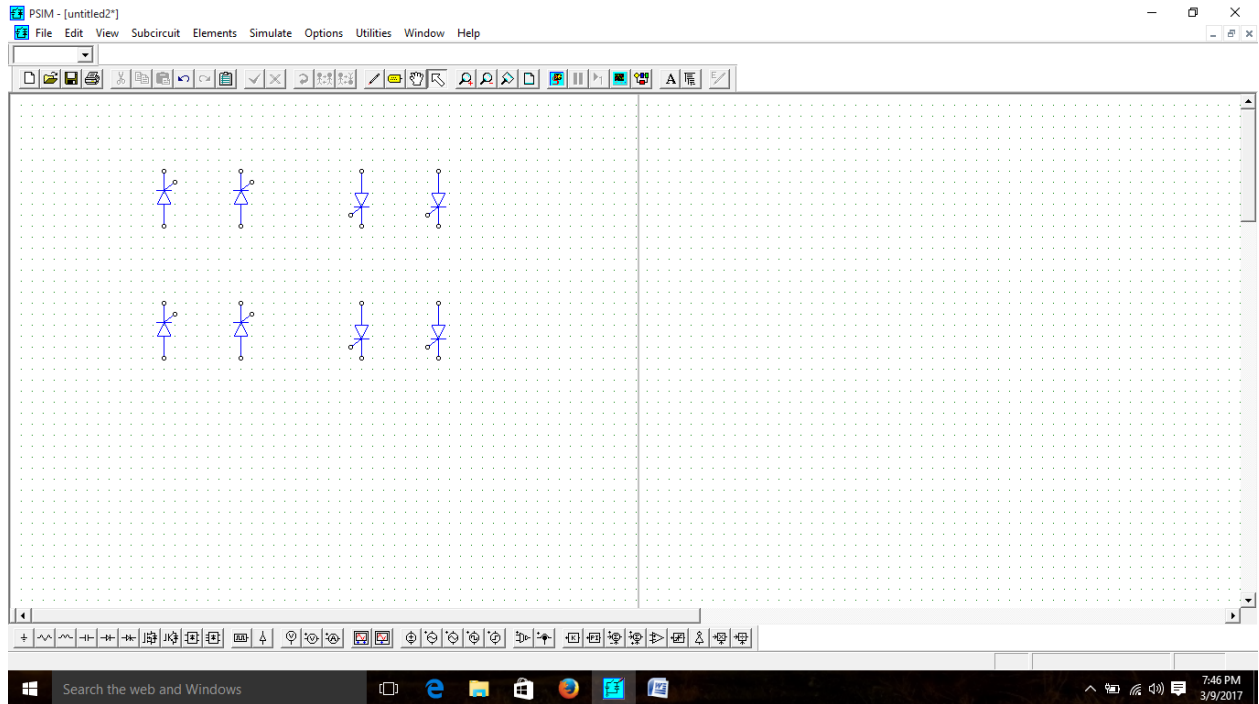


## Select voltage source

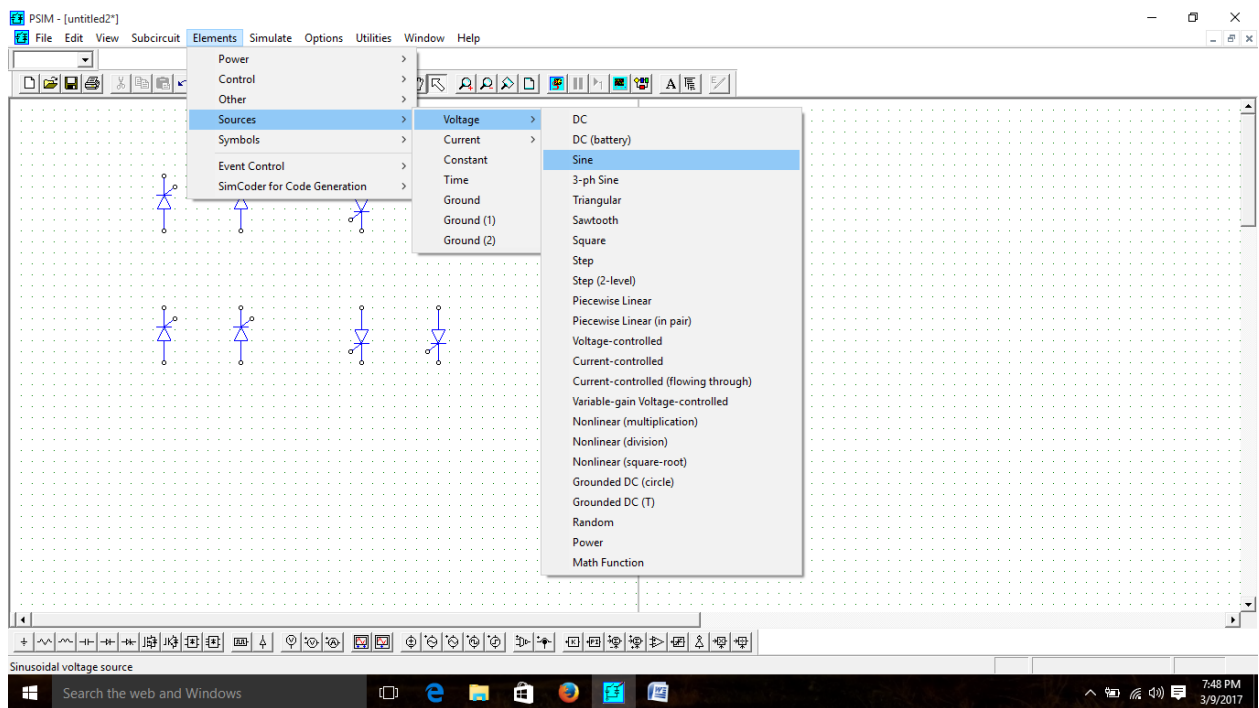




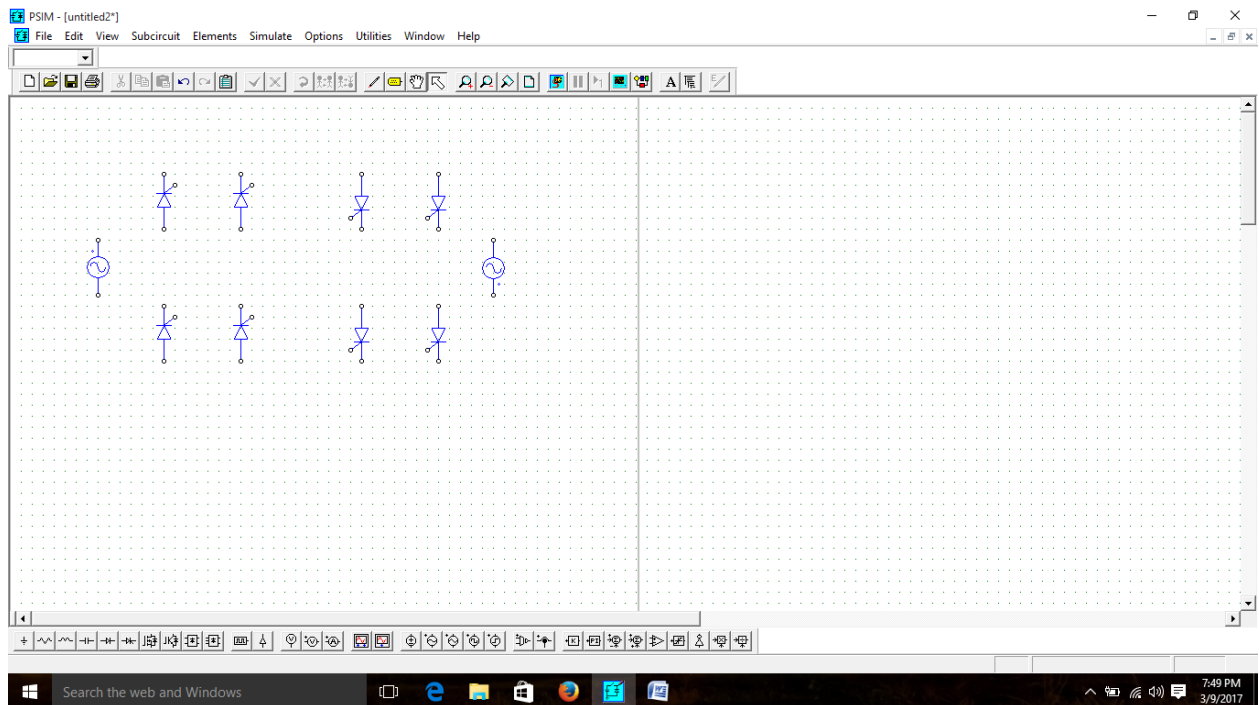



Select the resistor

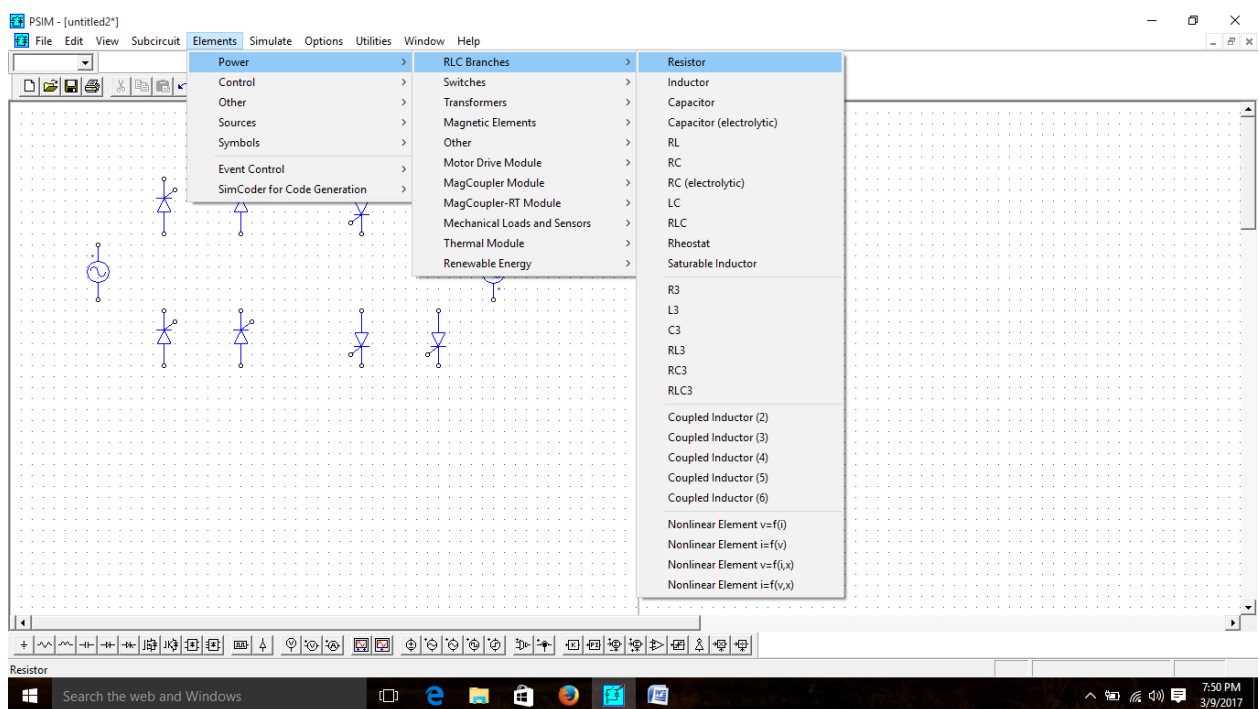

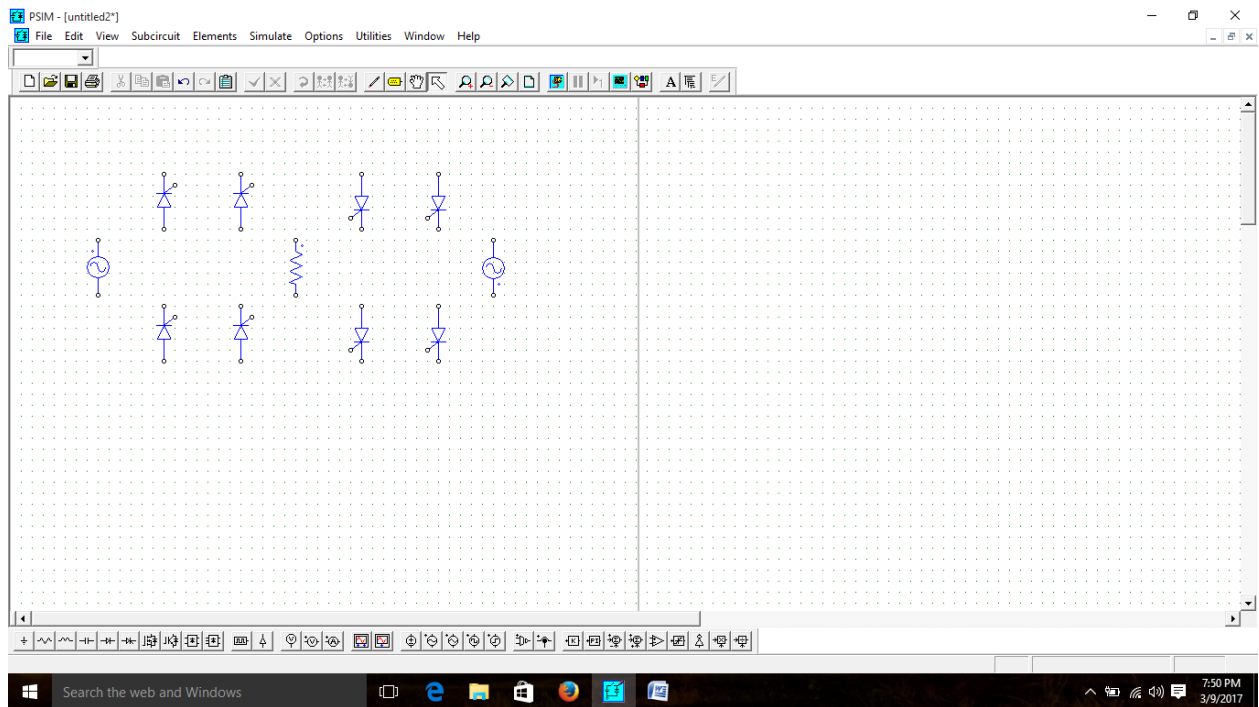



Select the volt meter

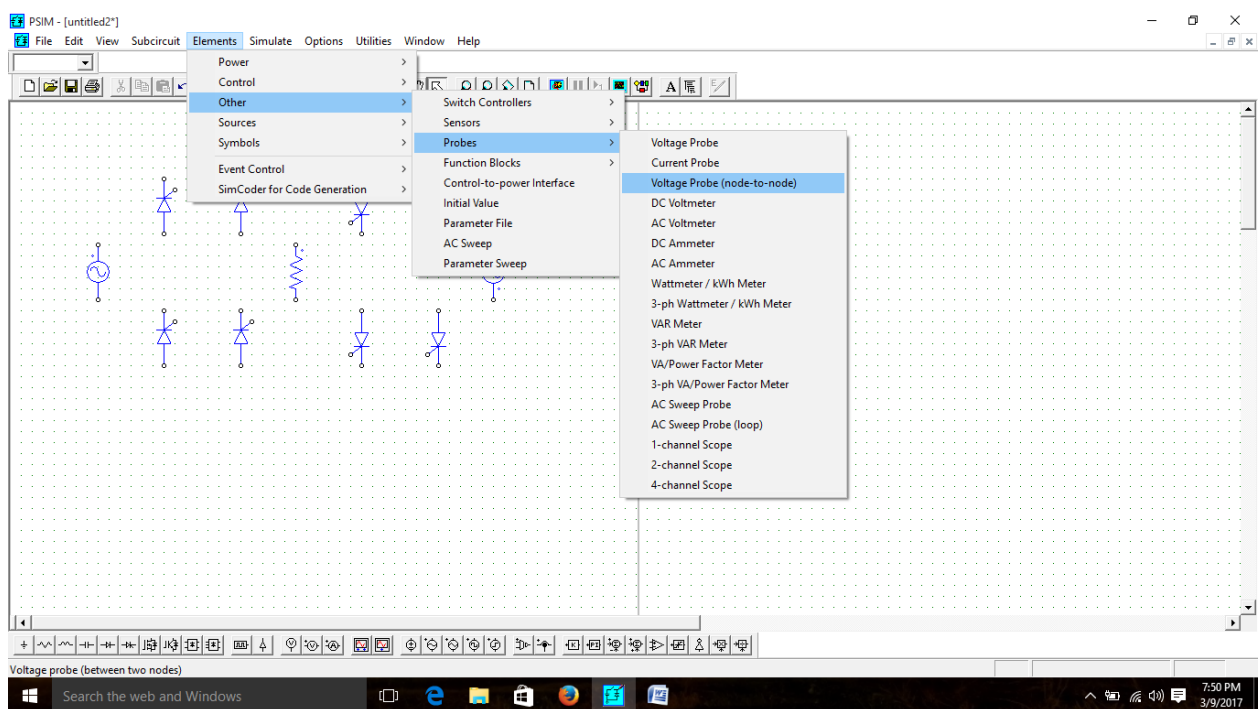

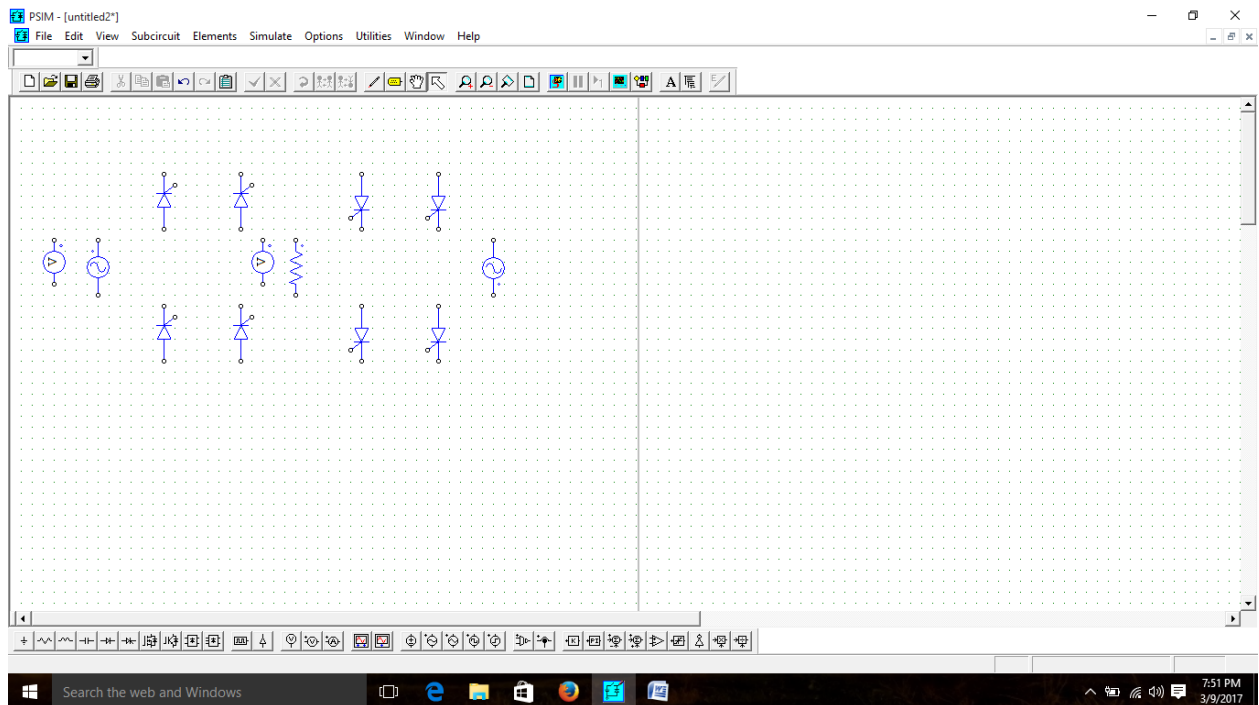


Select the gating block

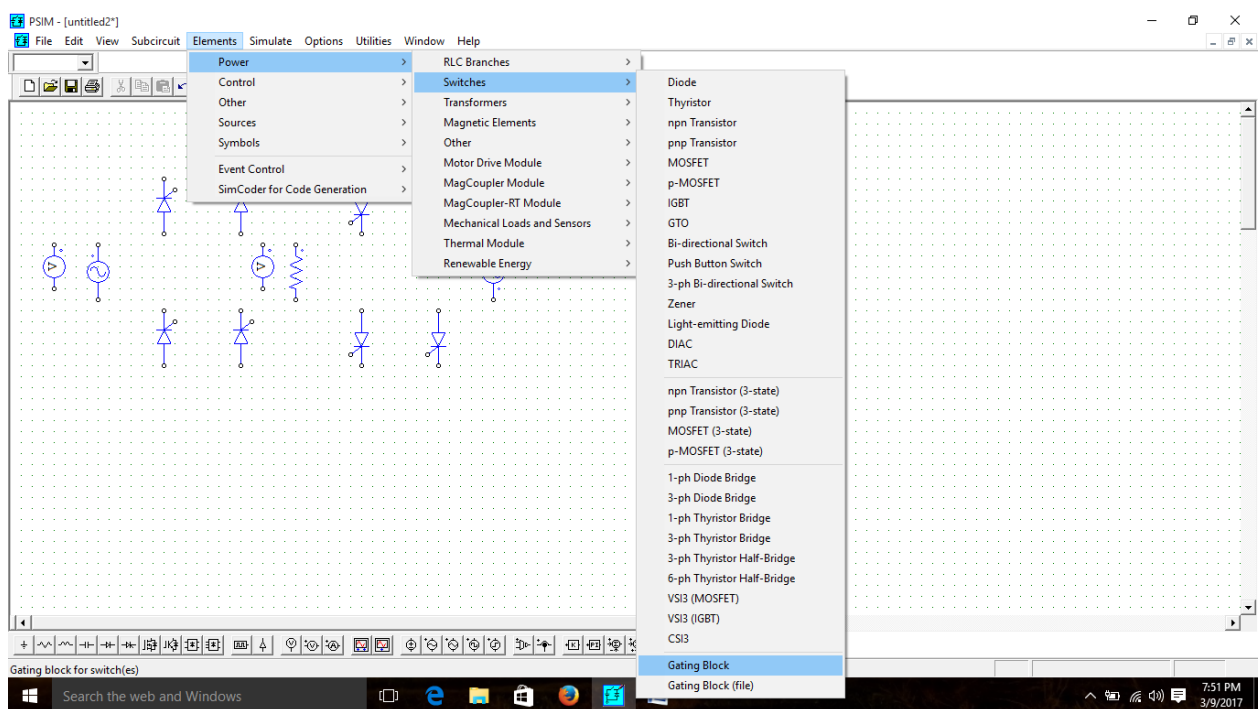

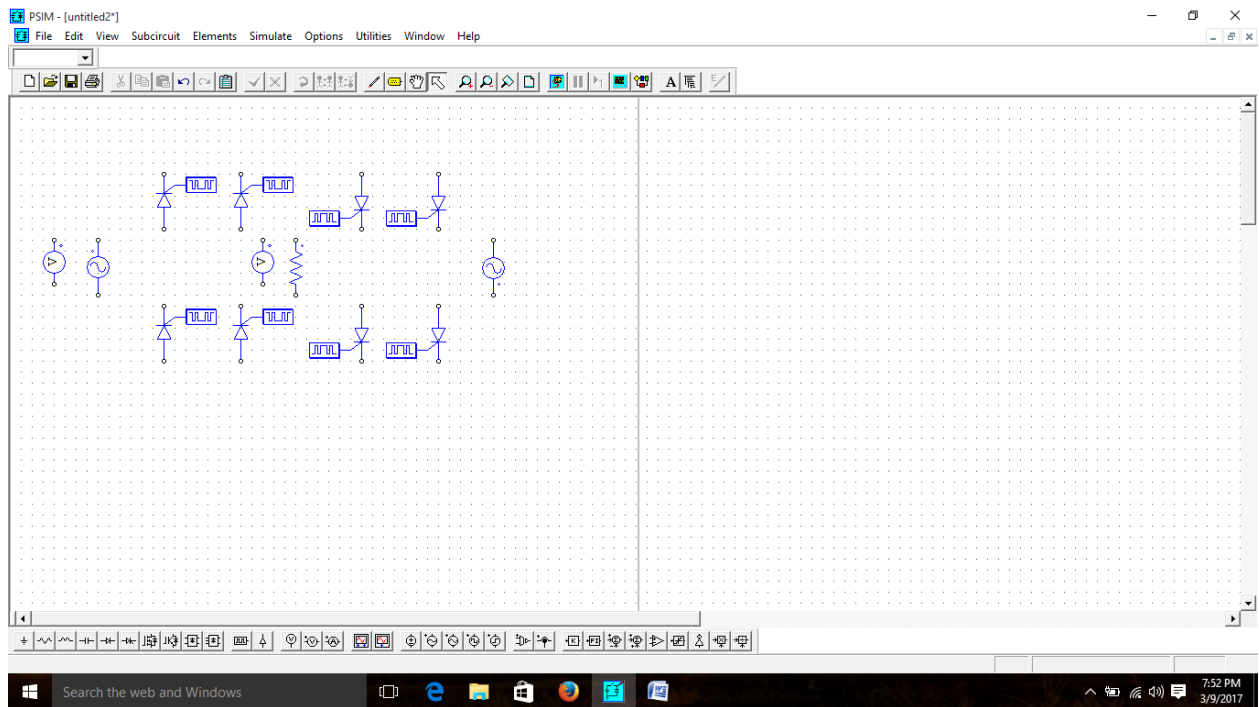


Select the wire for conning elements

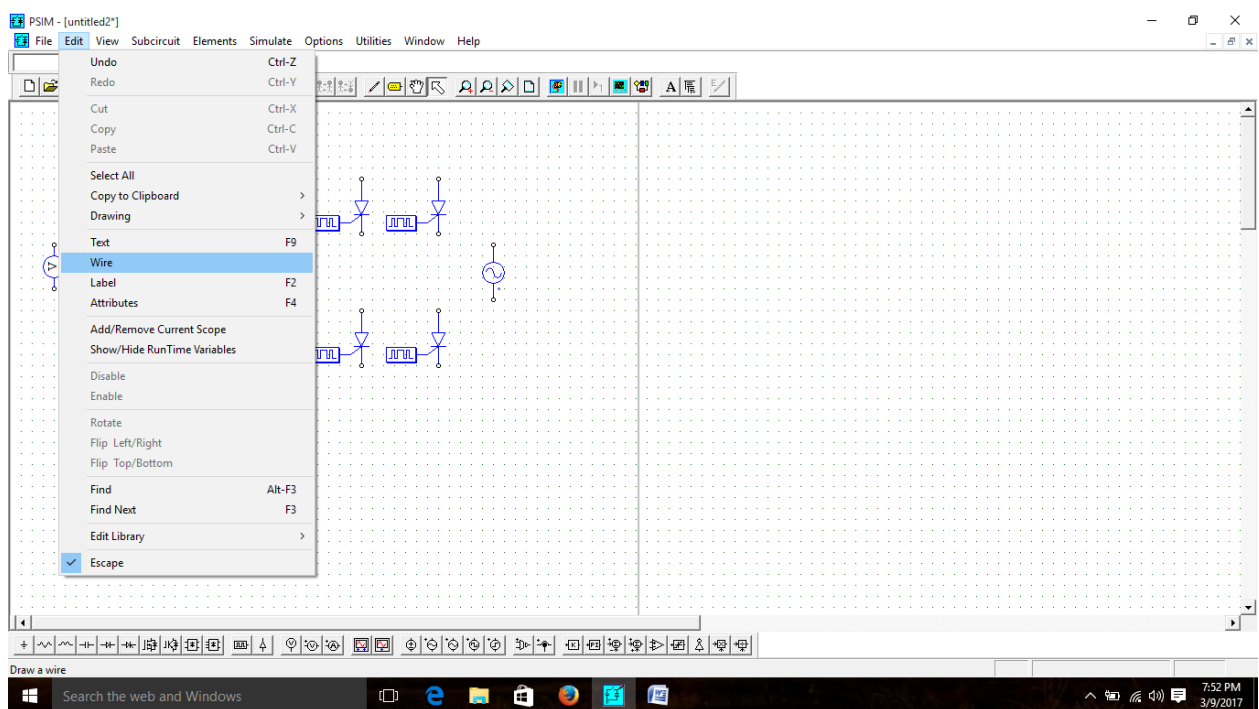







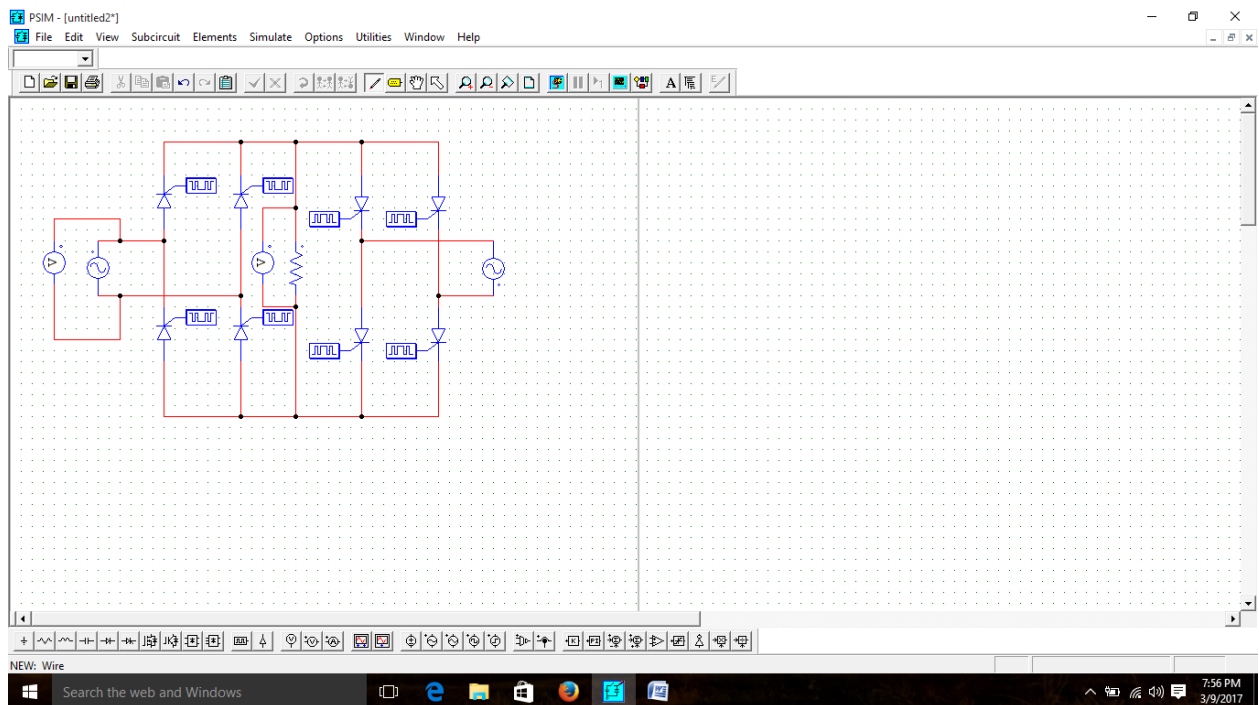
Connect all the elements using wiring tool




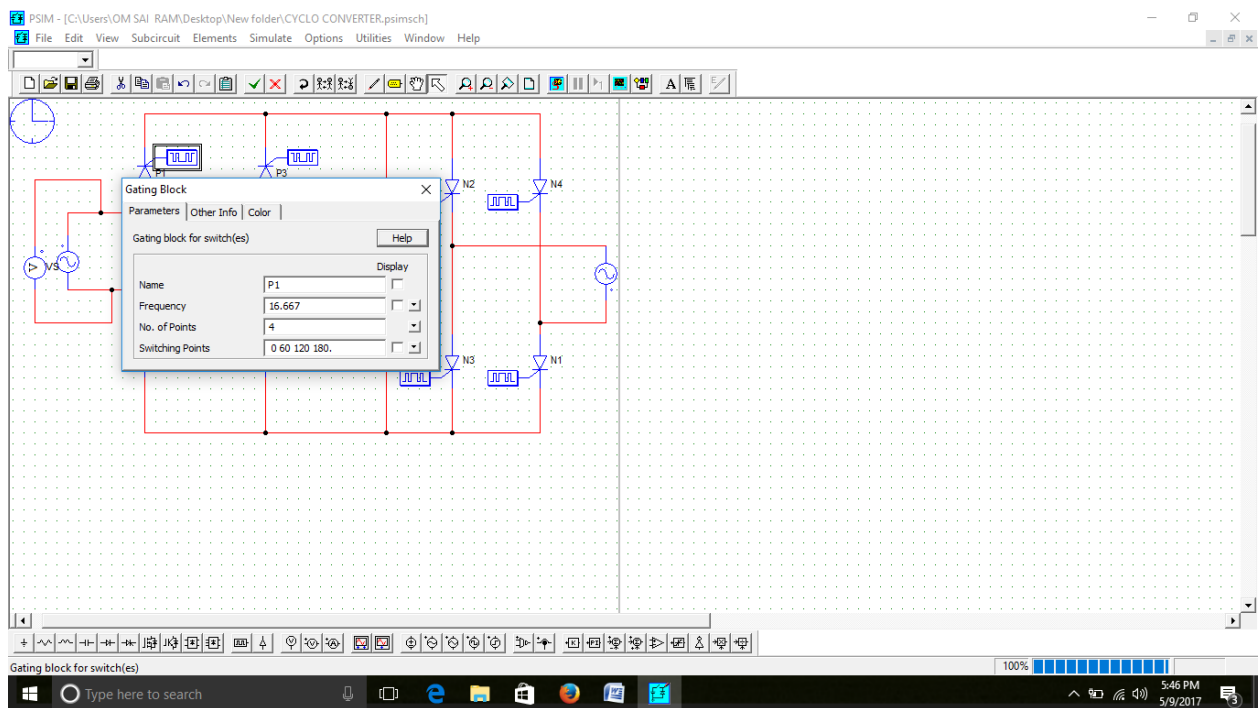Give the gating block parameters for all 8 gating blocks




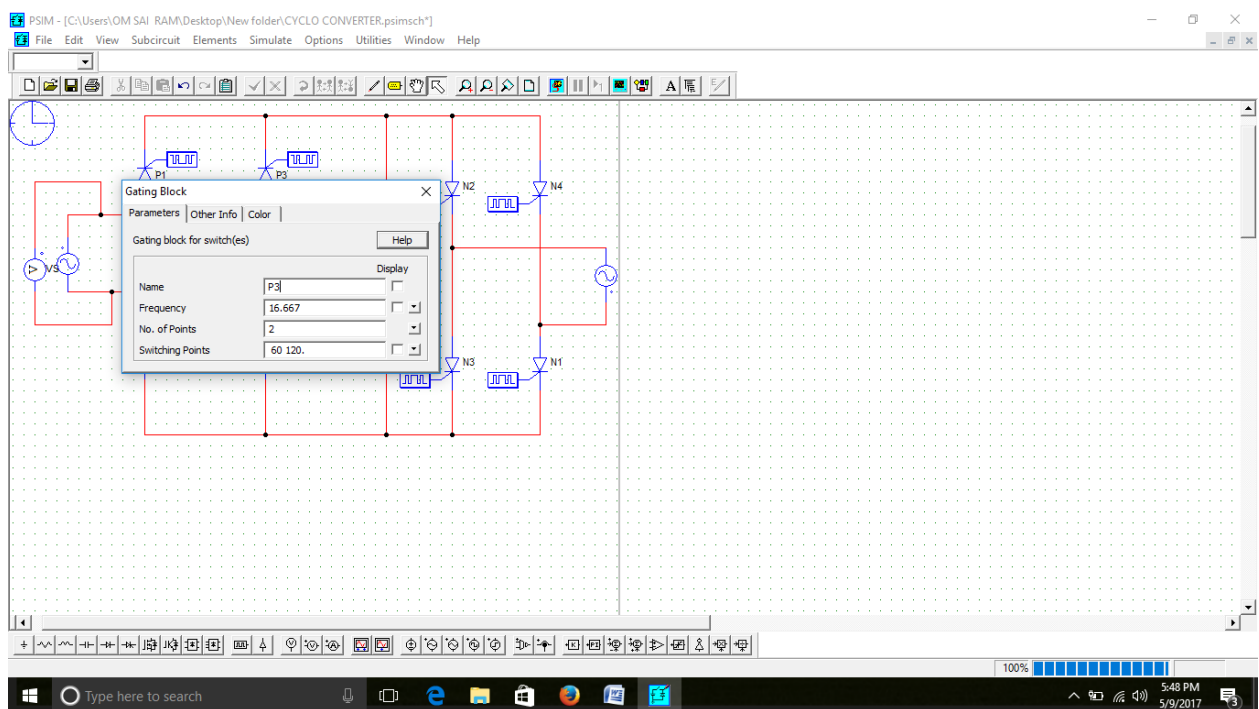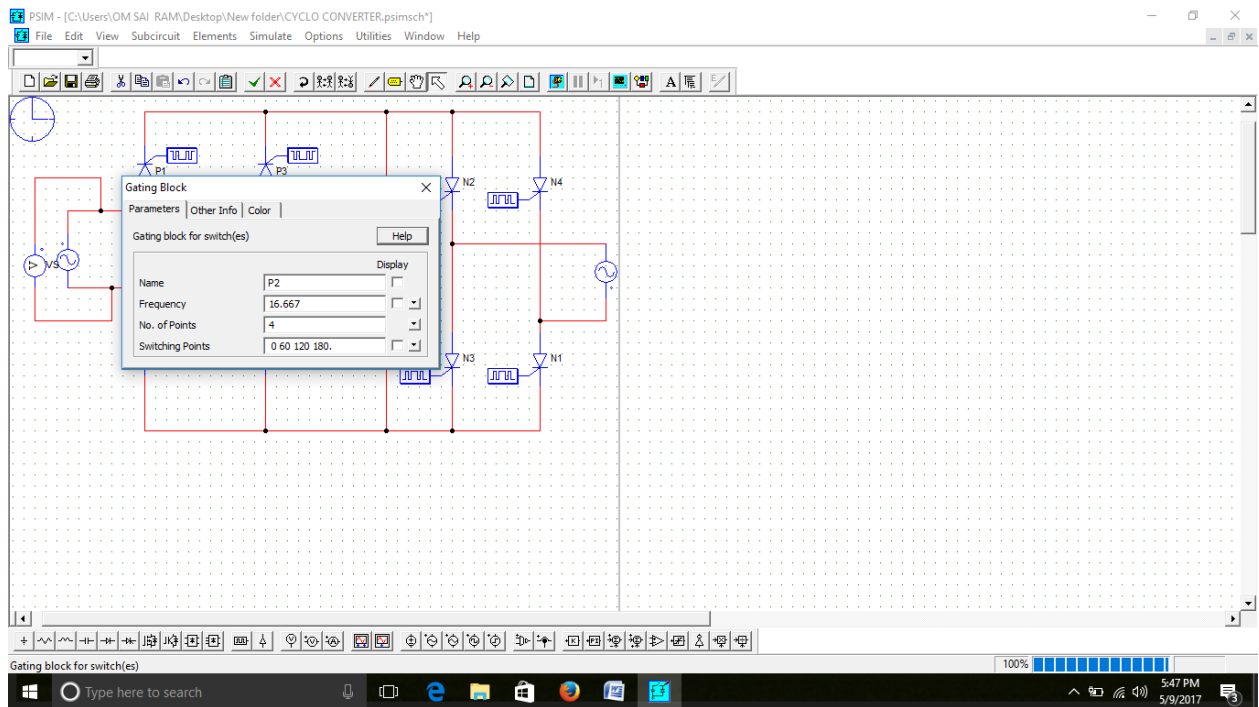

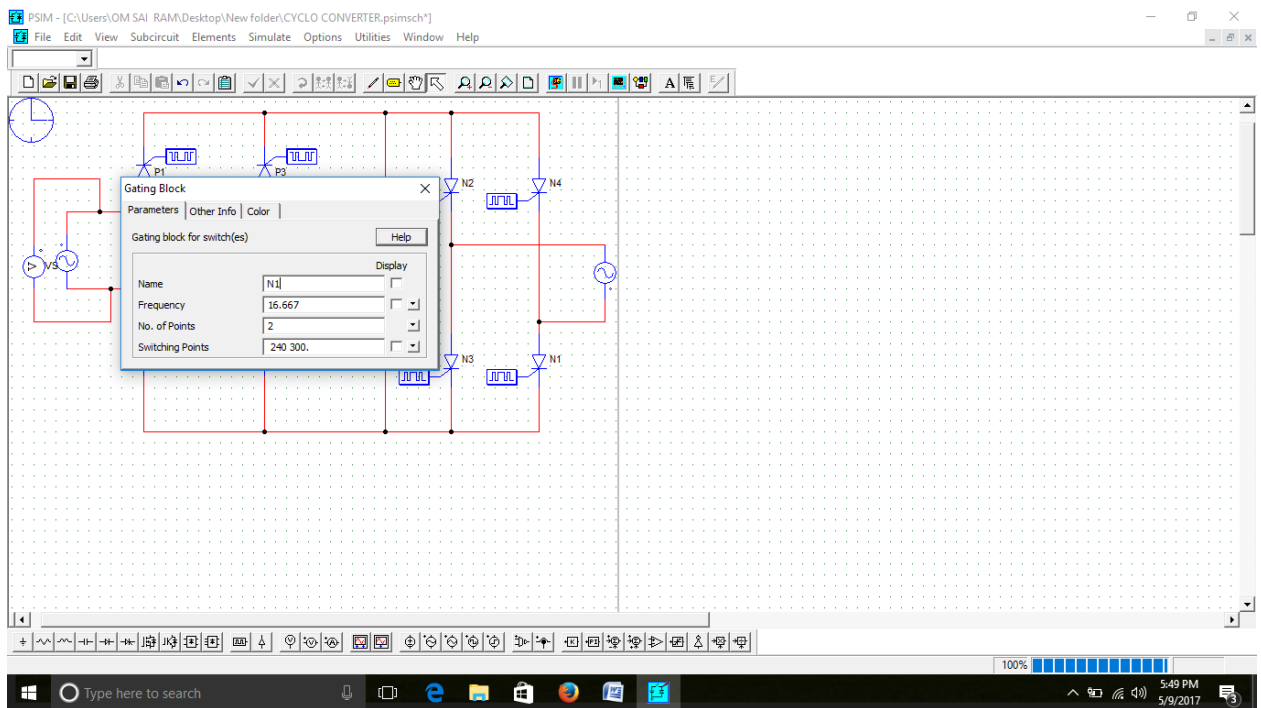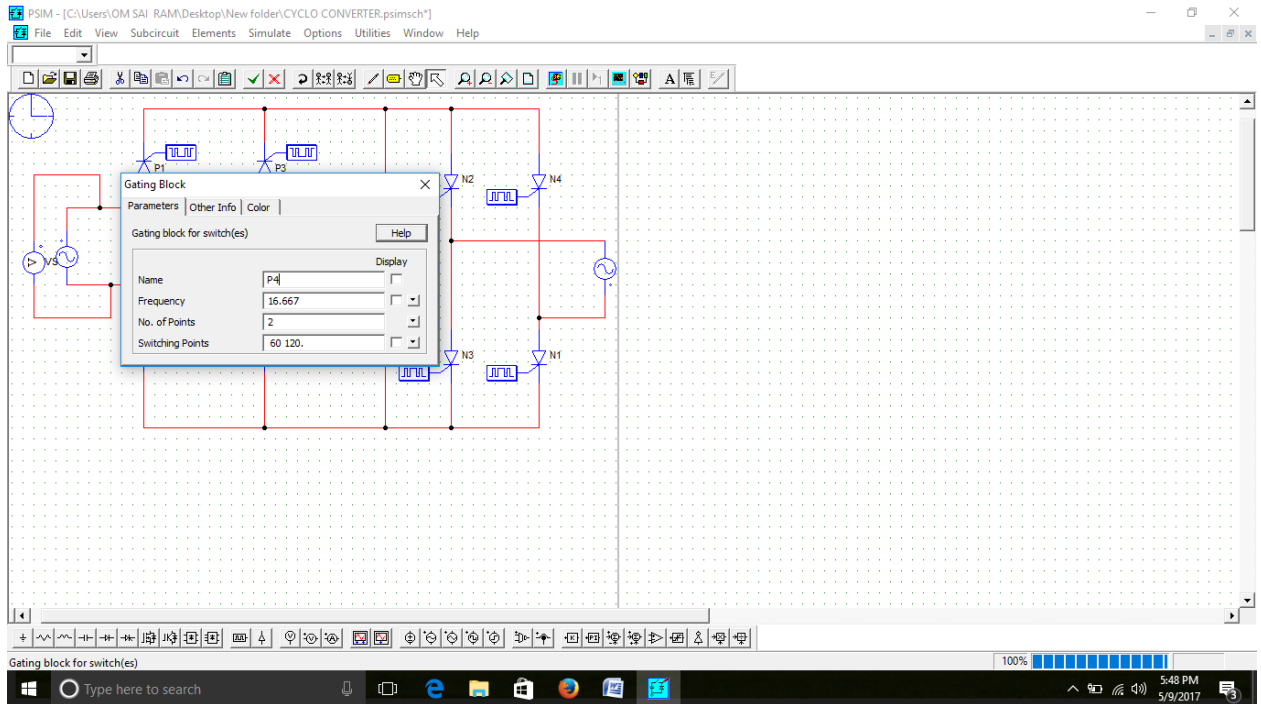



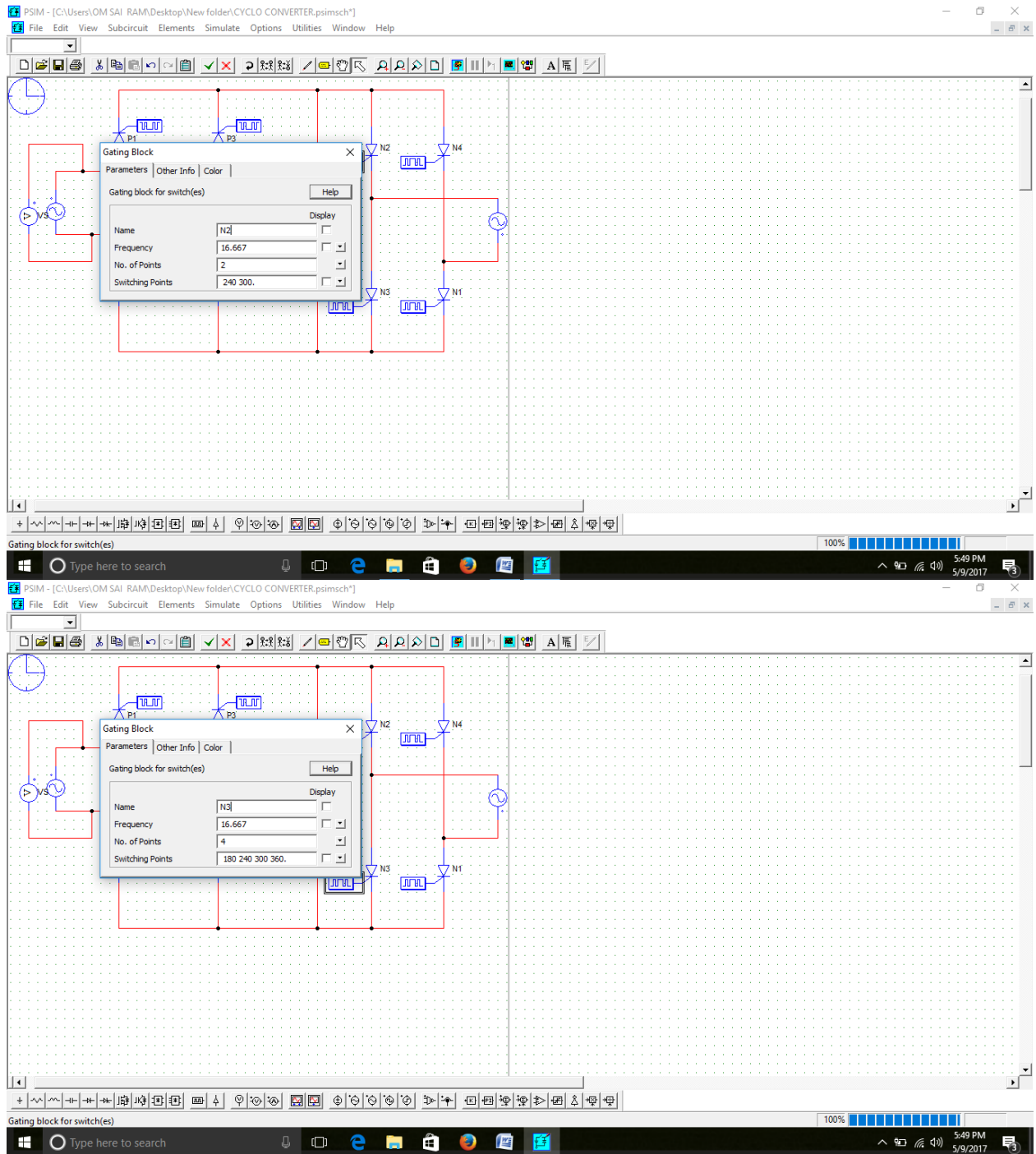





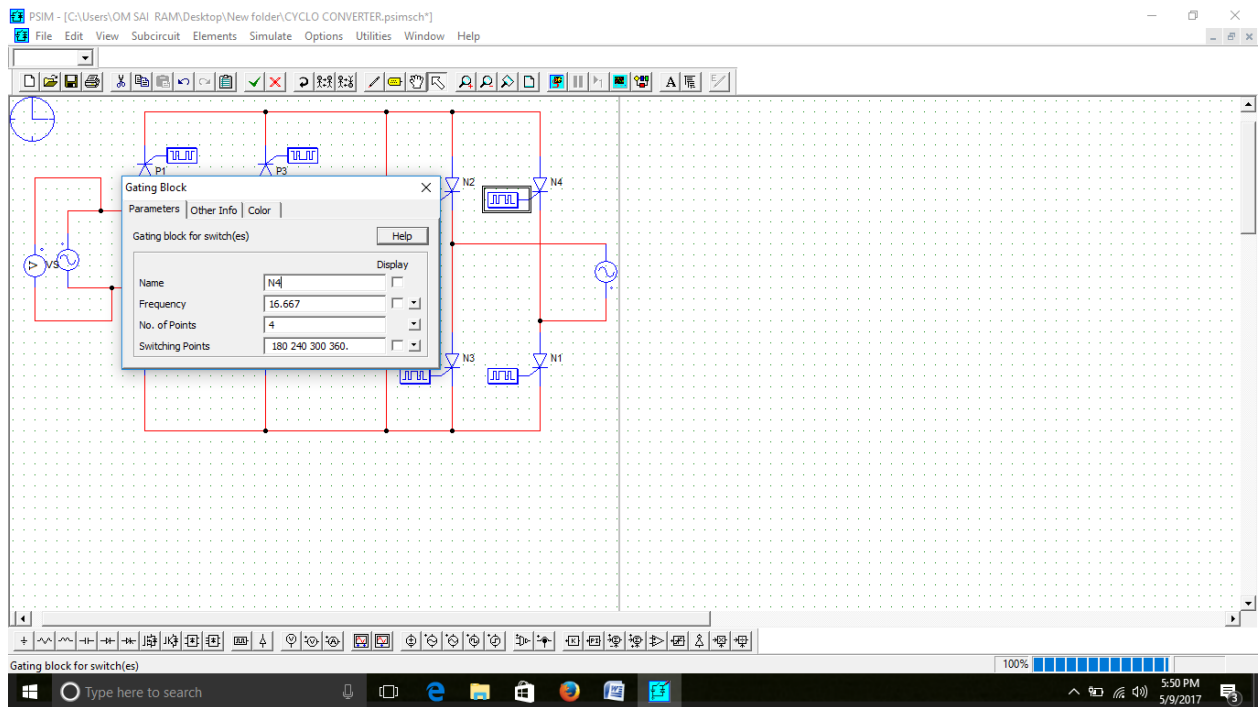


## Select the simulation control

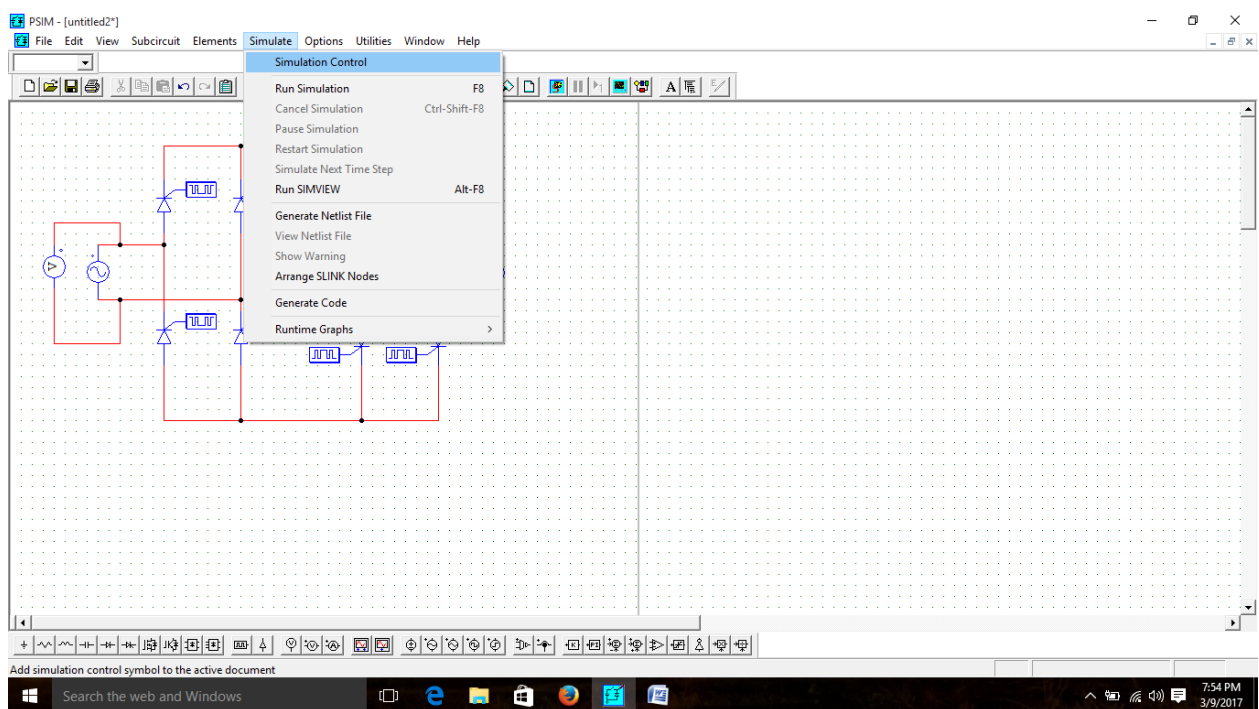

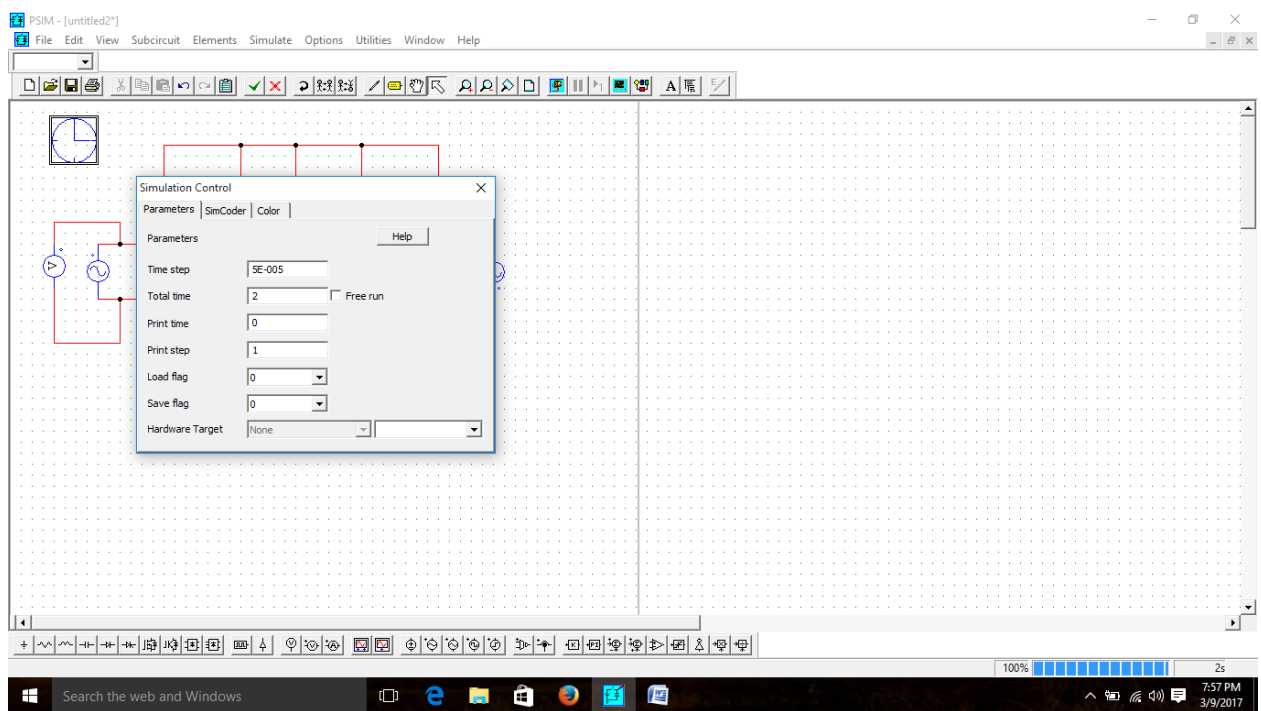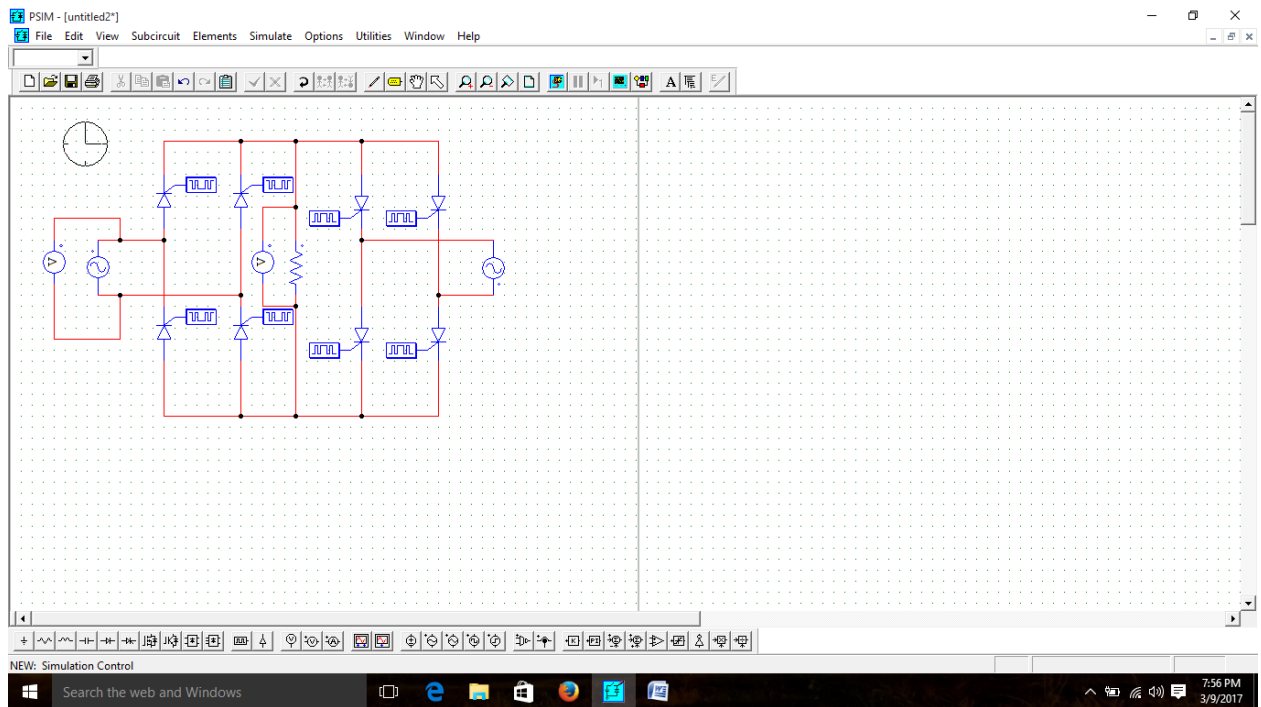

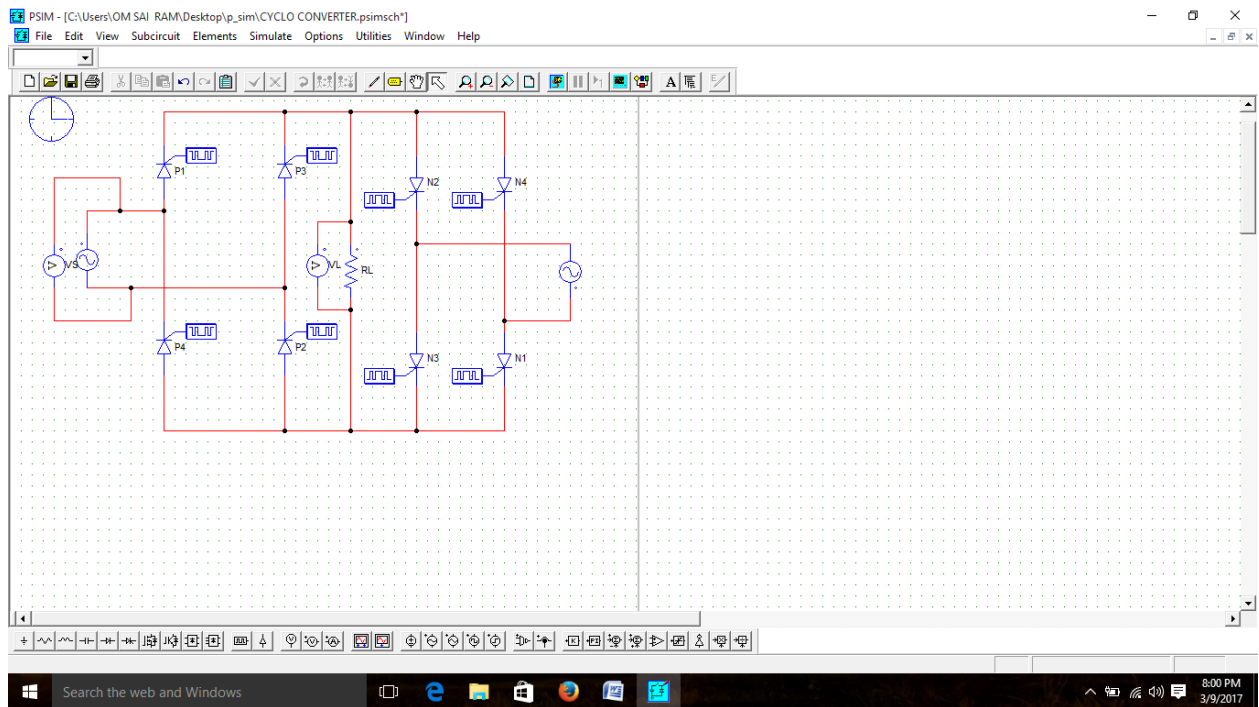


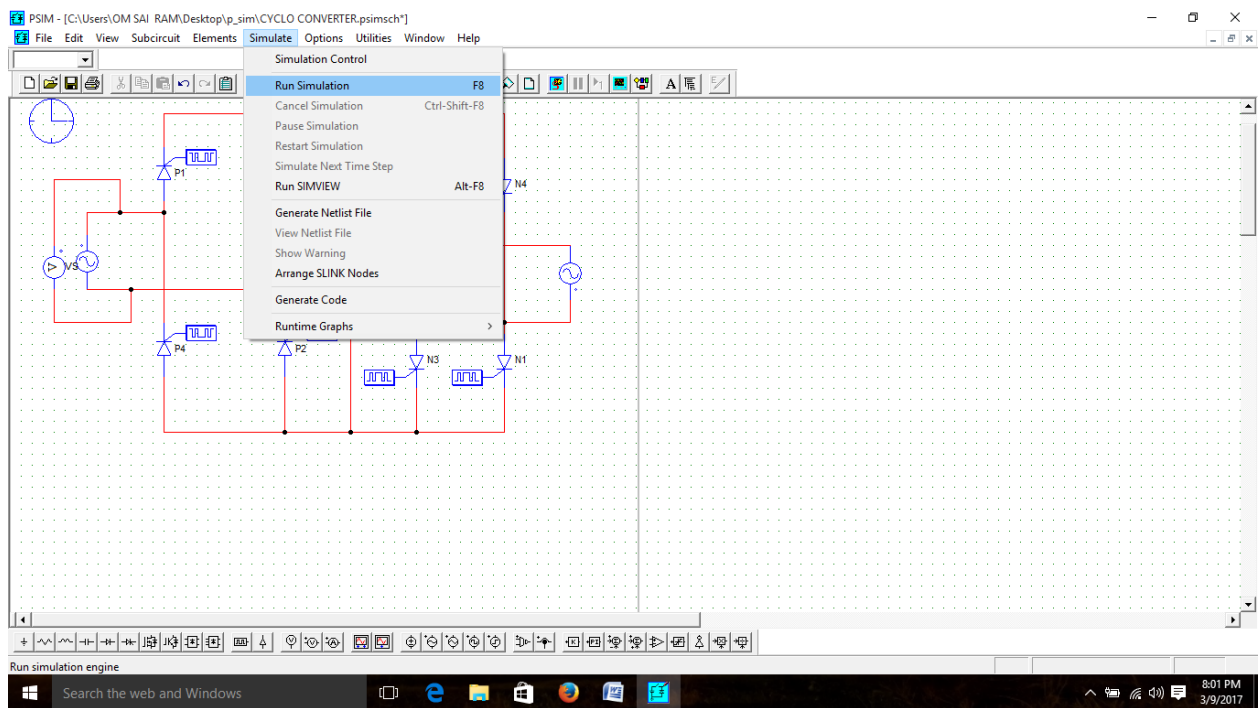Run the circuit by selecting run simulation





## Output waveform

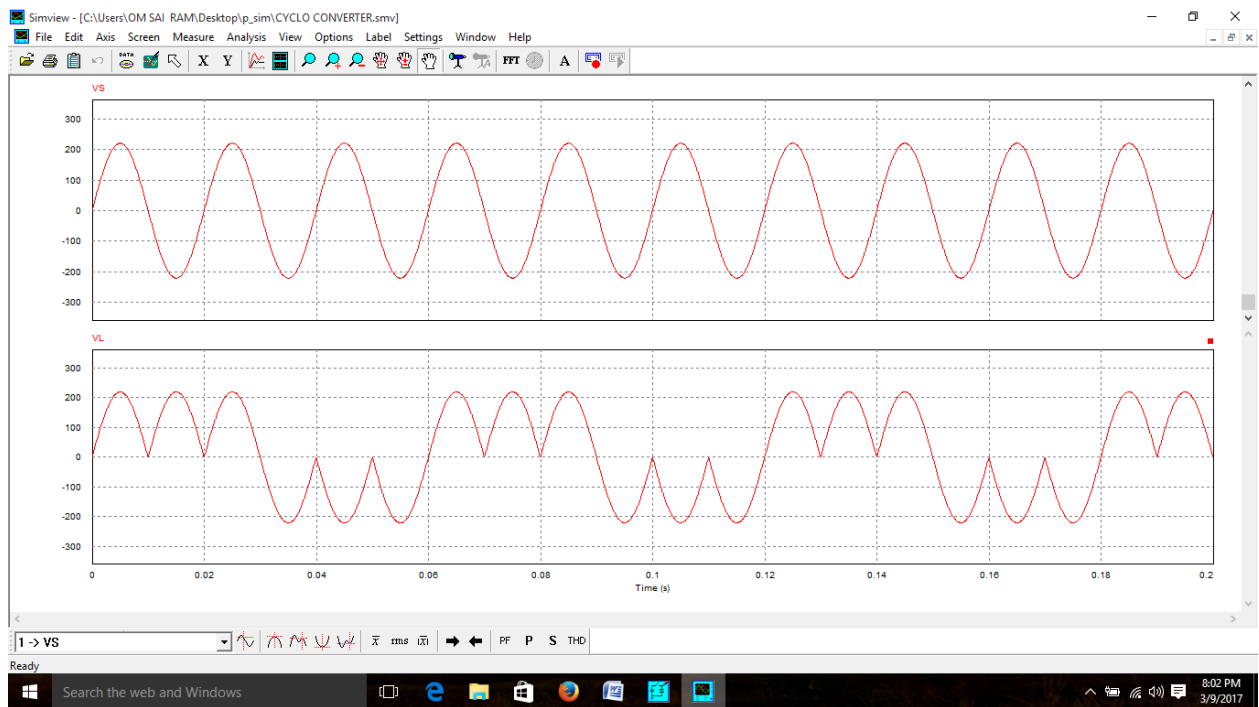





## CLIPPERS

**Above reference:**

Select source

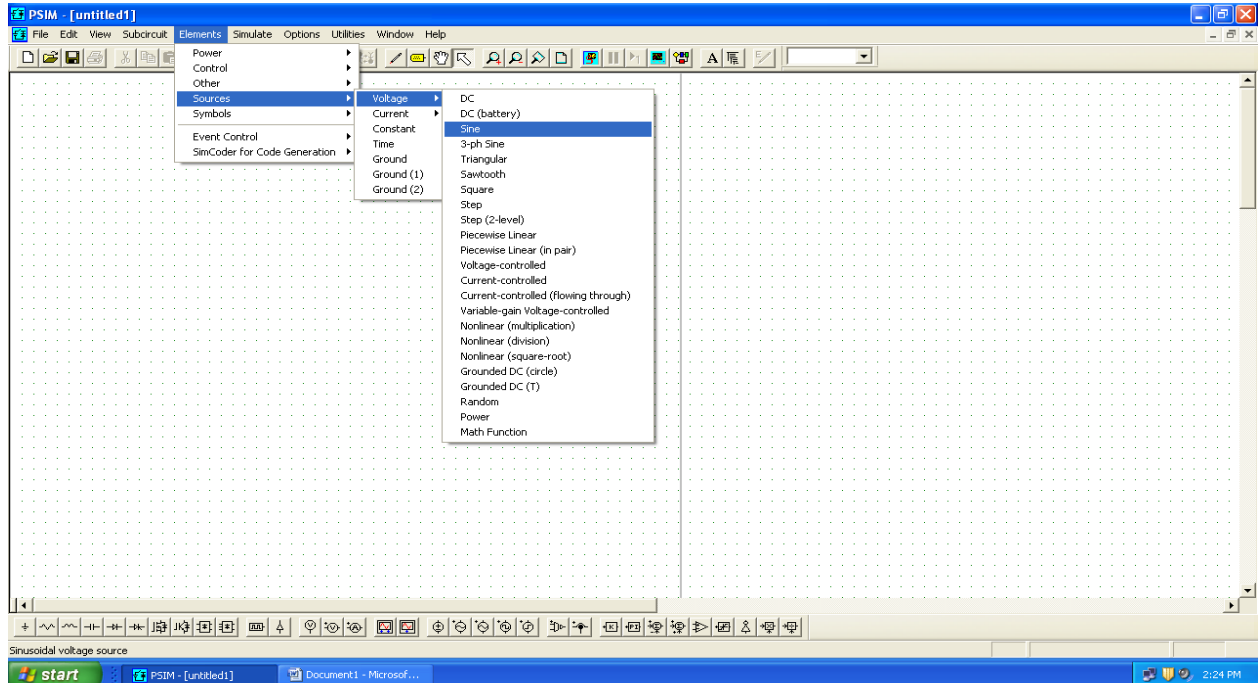


Select the resistor

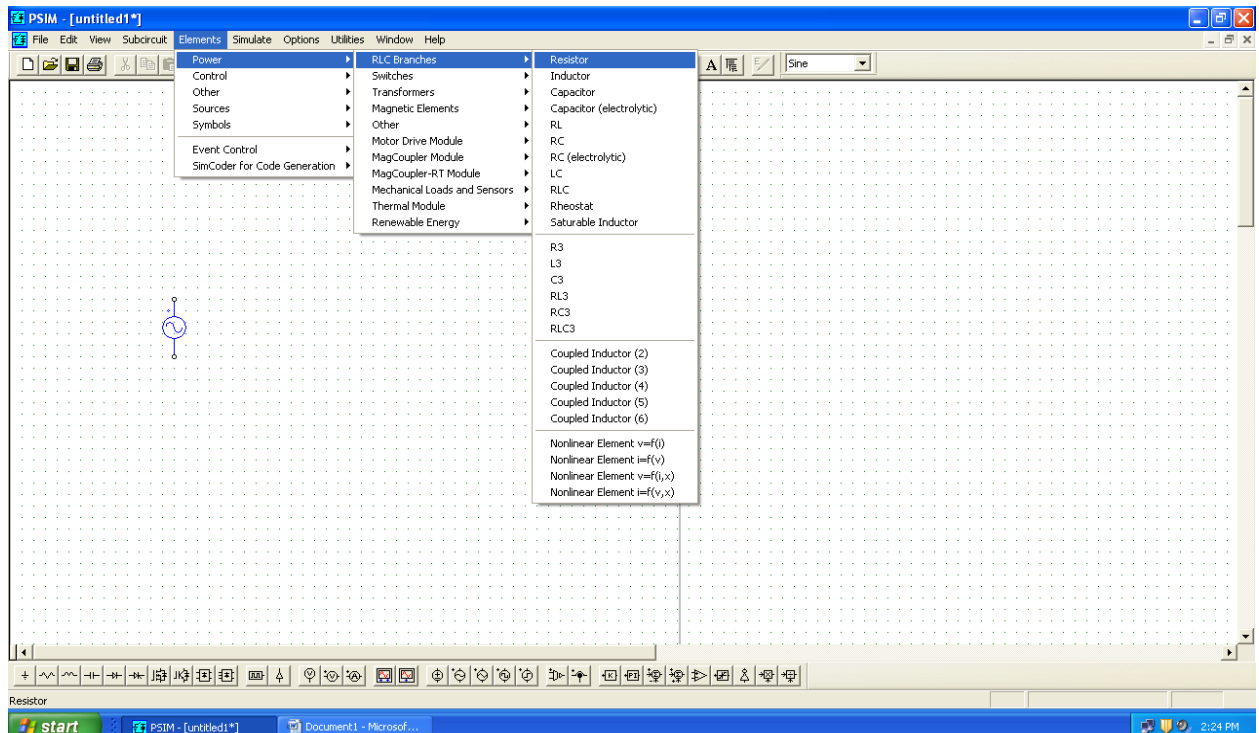




## Select the diode

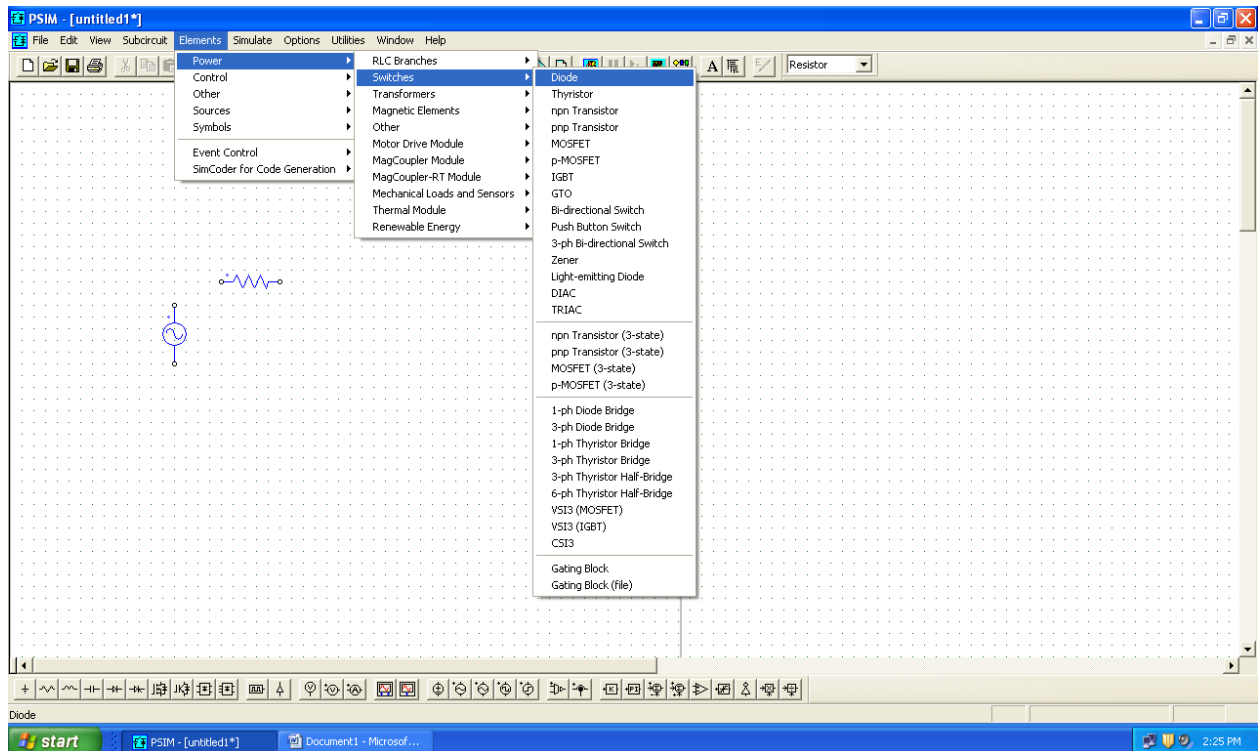


## Select the dc source

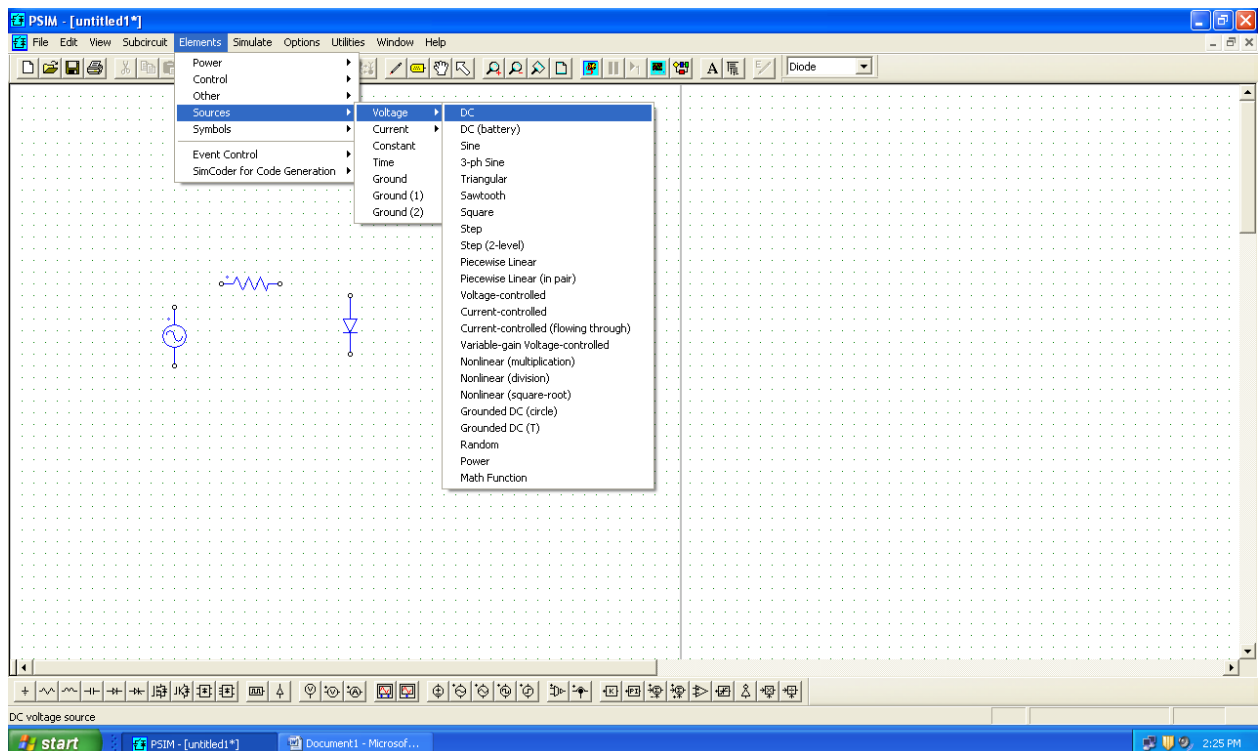




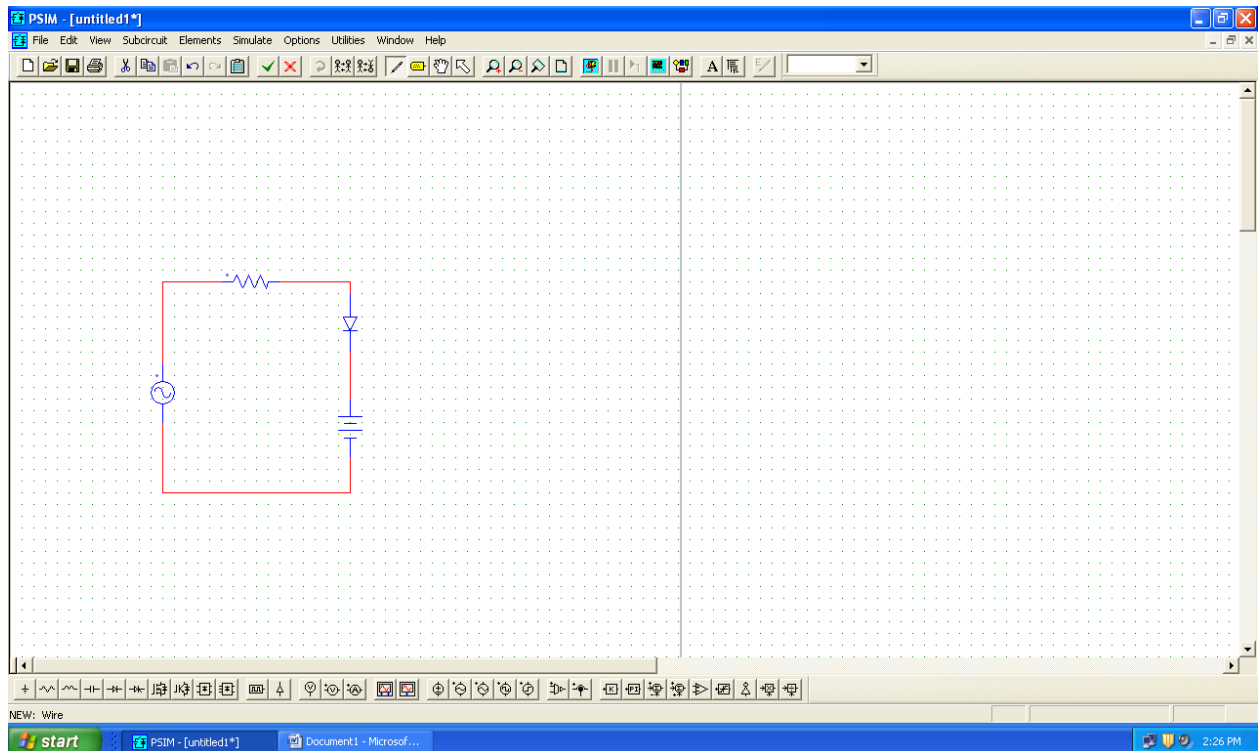Connect the elements by using wiring tool




Select the volt meter

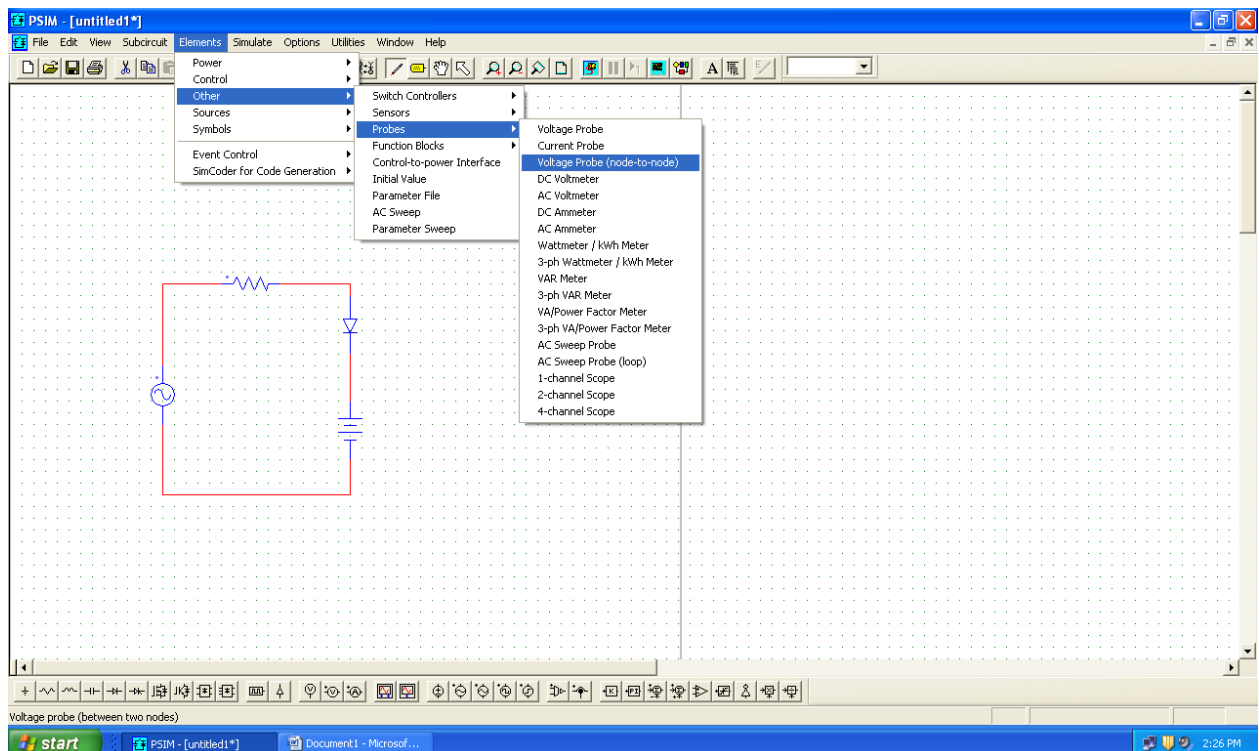




Connect the circuit as shown below

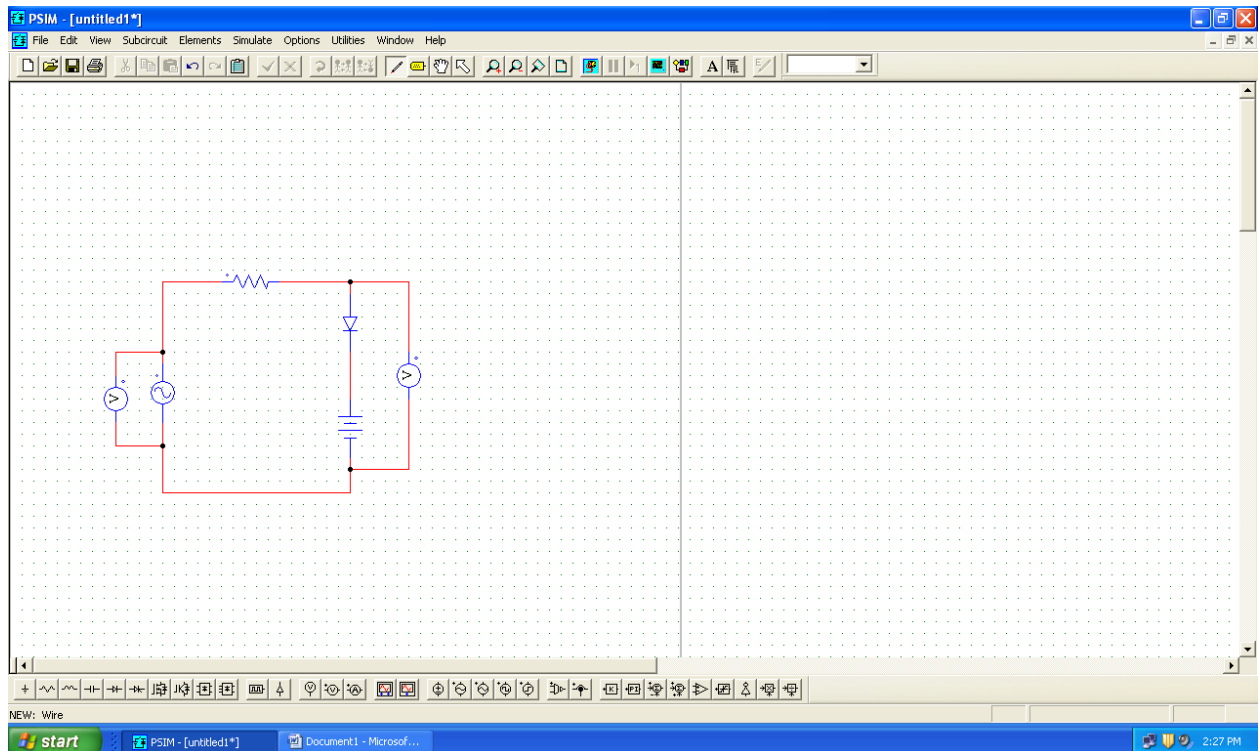



Give the labeling to every element

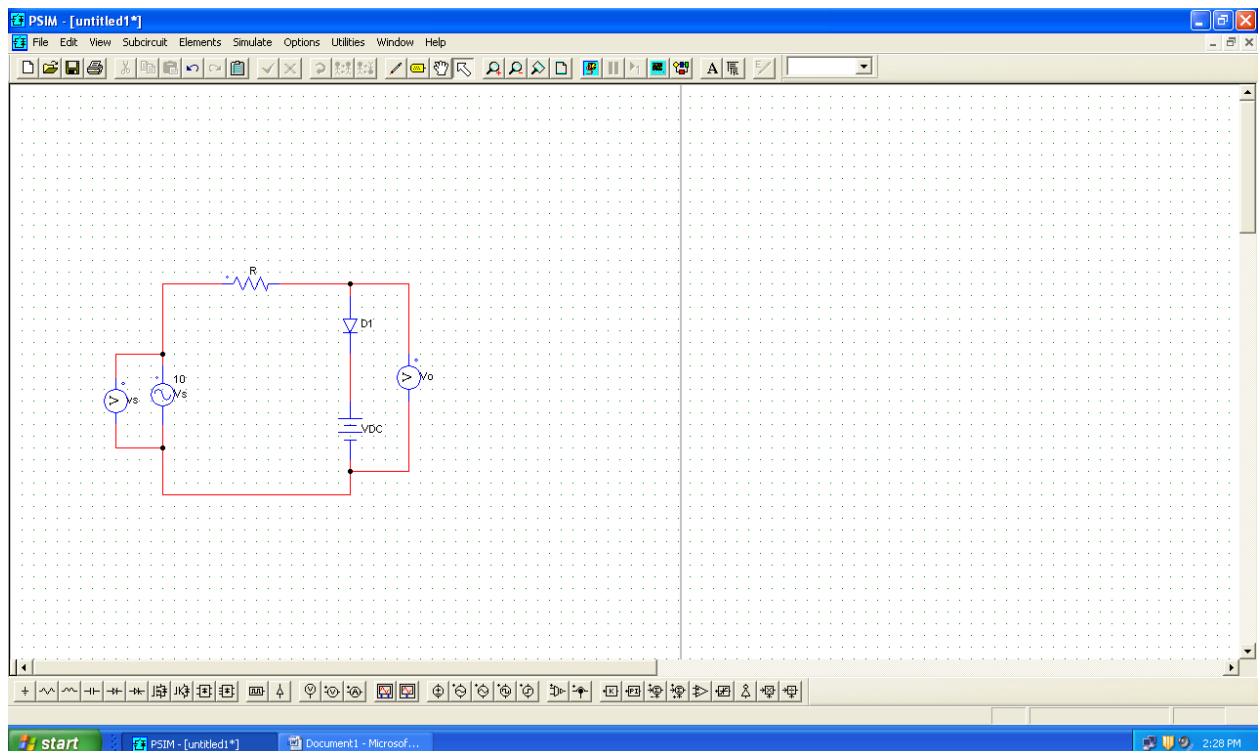






## Select the simulation control

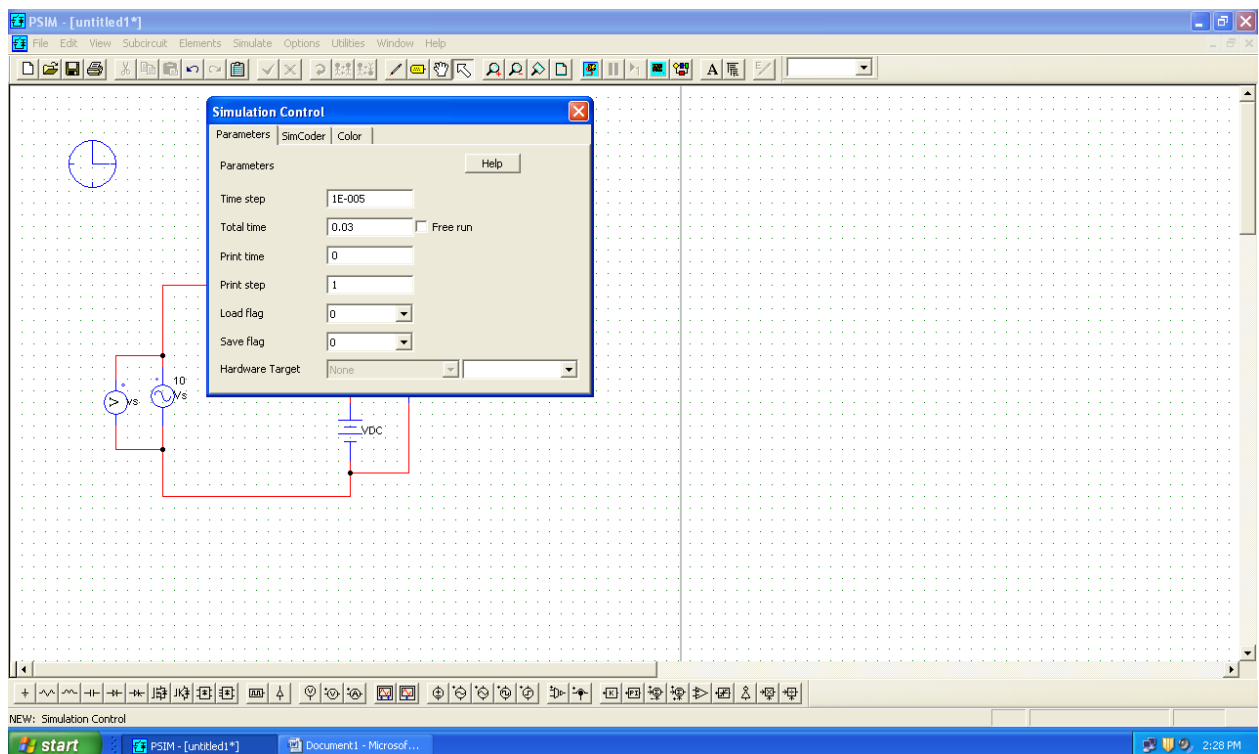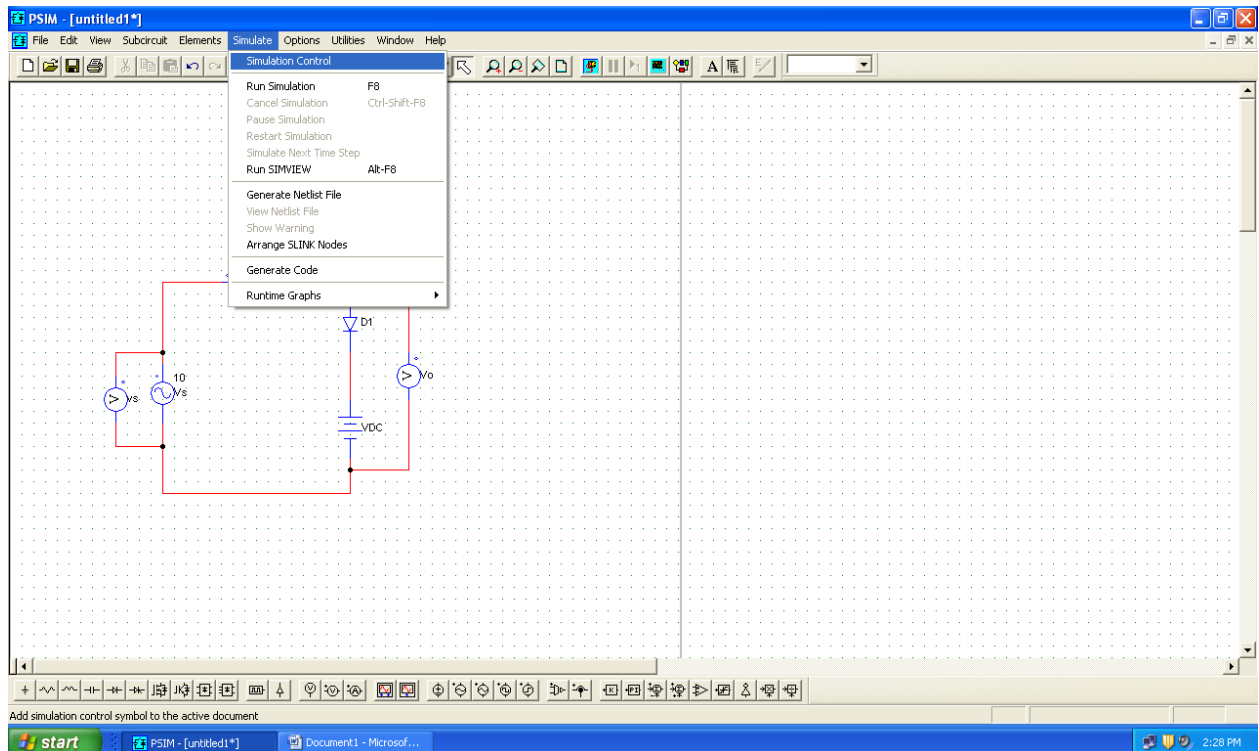





run the circuit by using run simulation

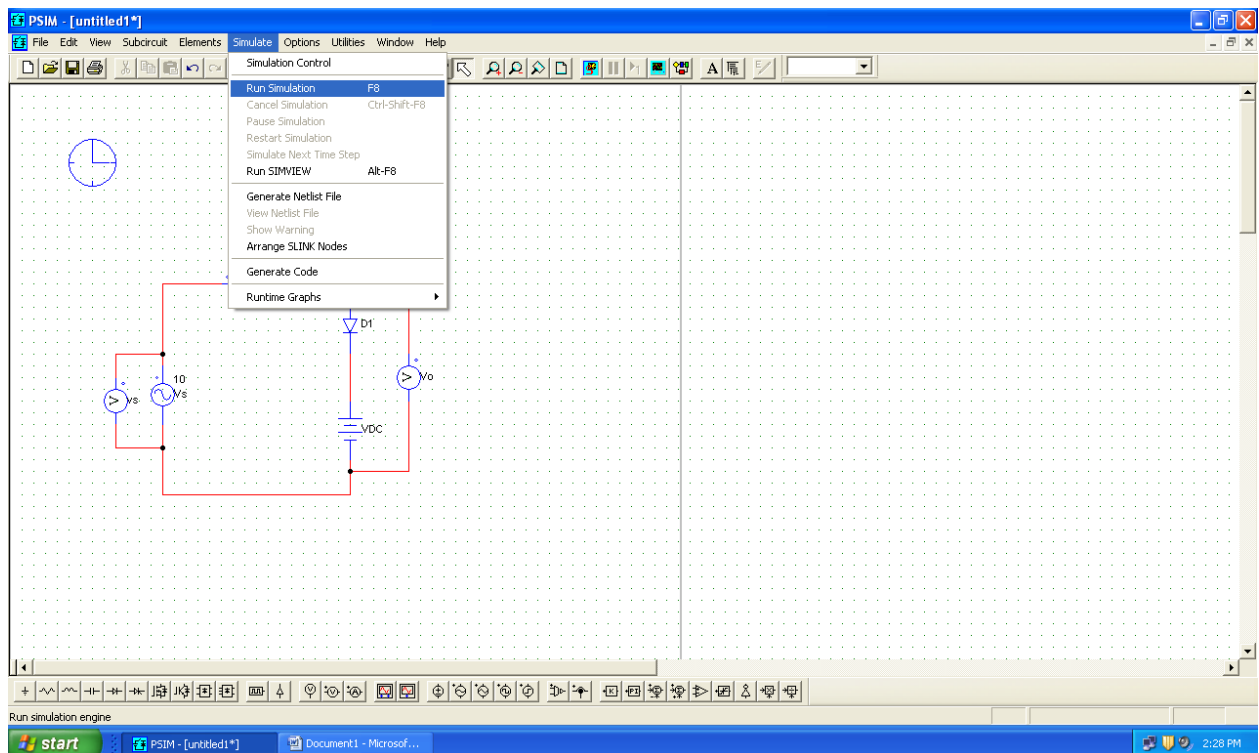


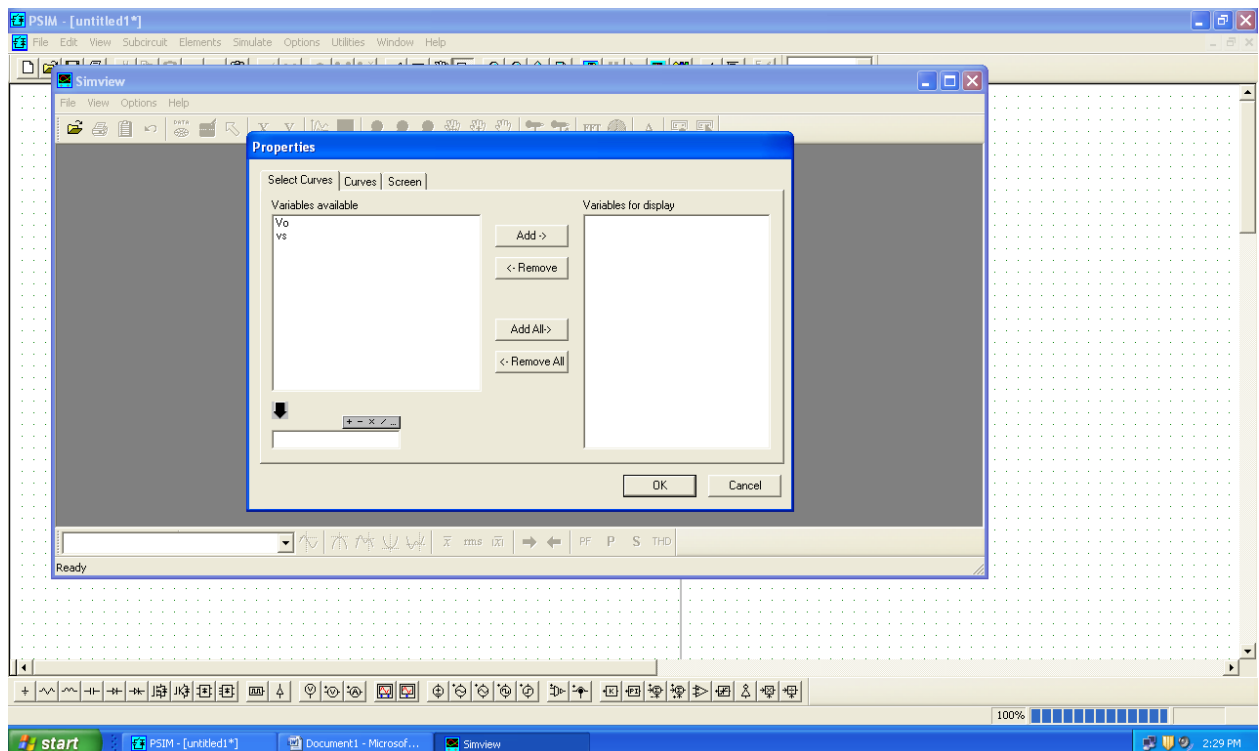Select any measurable quantity to measure



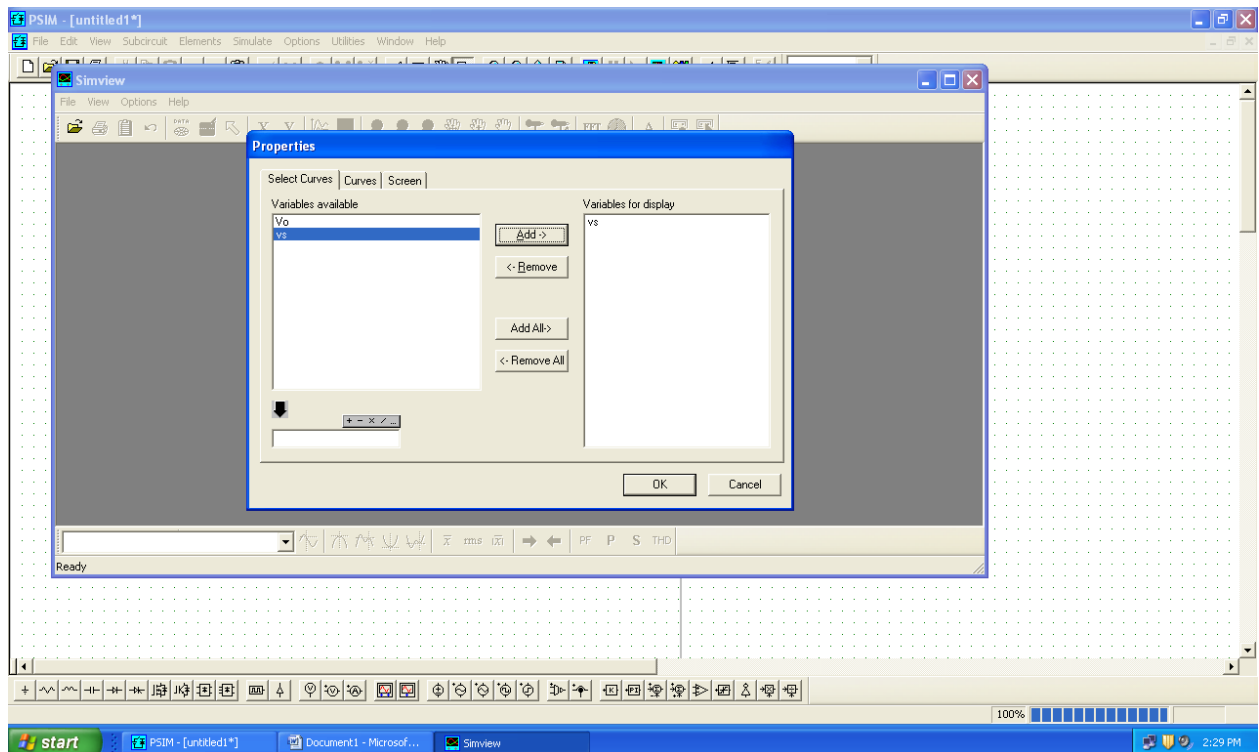

## Output waveforms

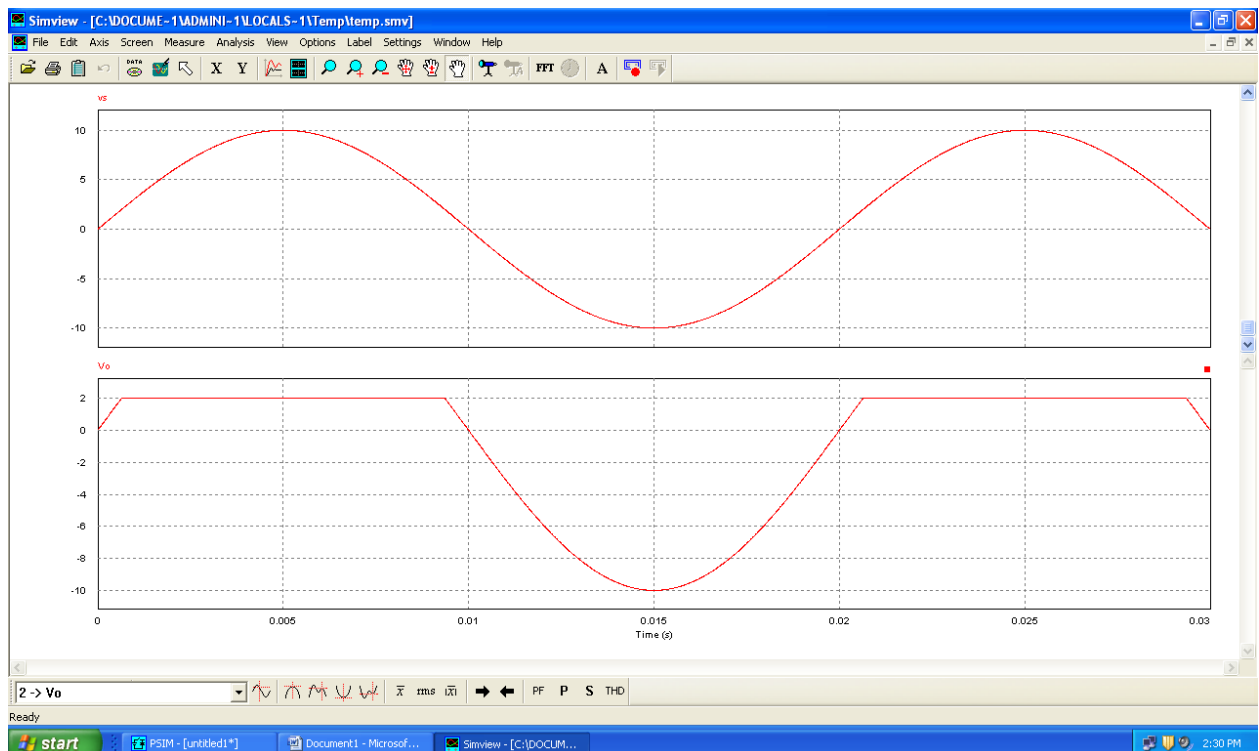





## Below reference

Select the elements as shown above and connect them as shown in below figure with proper labeling

Circuit diagram

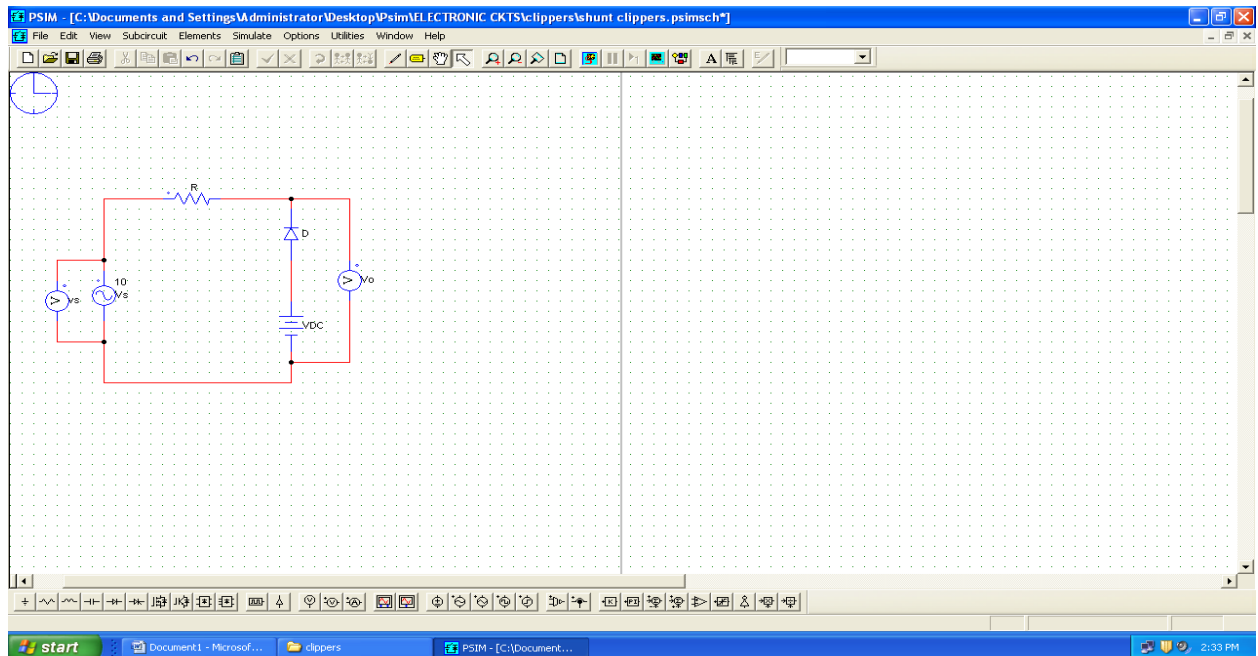


Output waveforms

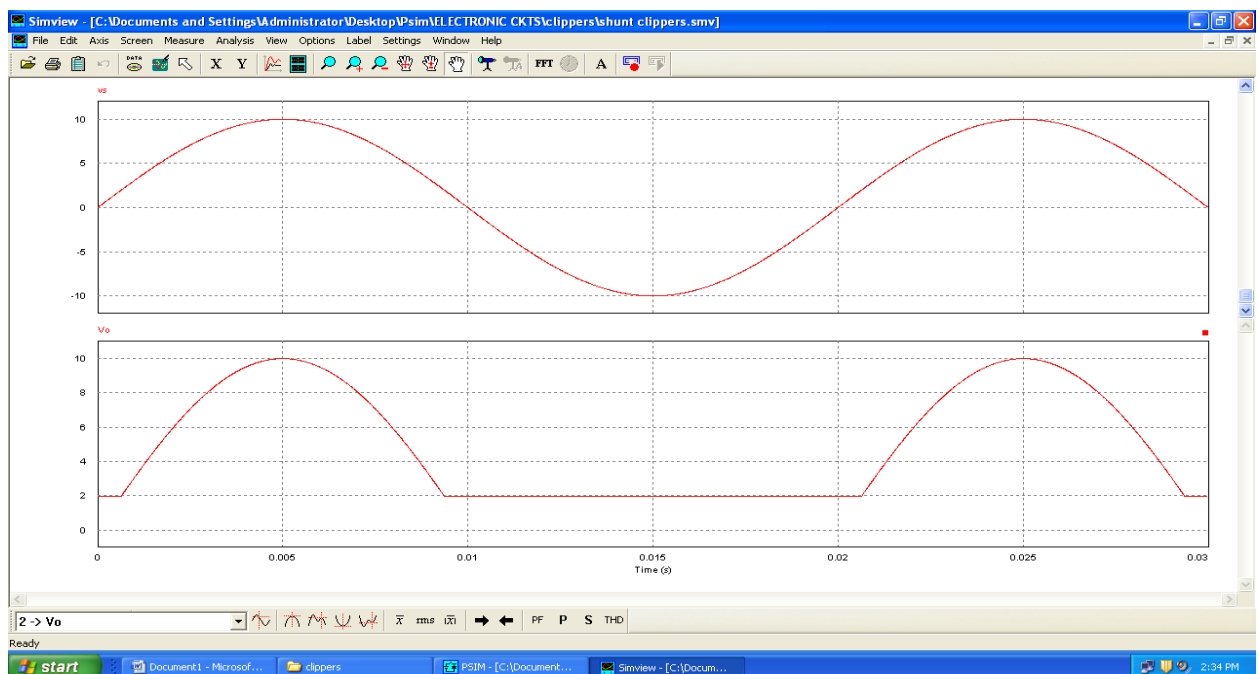




## Clipper above and below the reference

Selection of Zener diode:

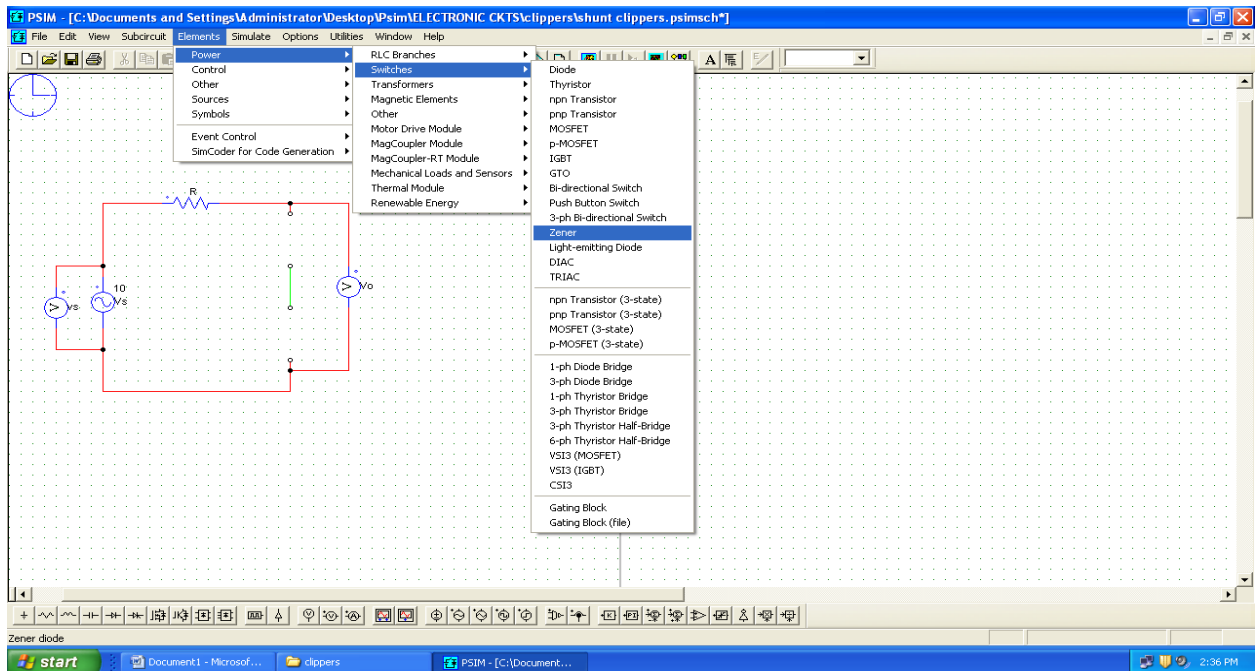


Select the elements as shown above and connect them as shown in below figure with proper labeling

Circuit diagram

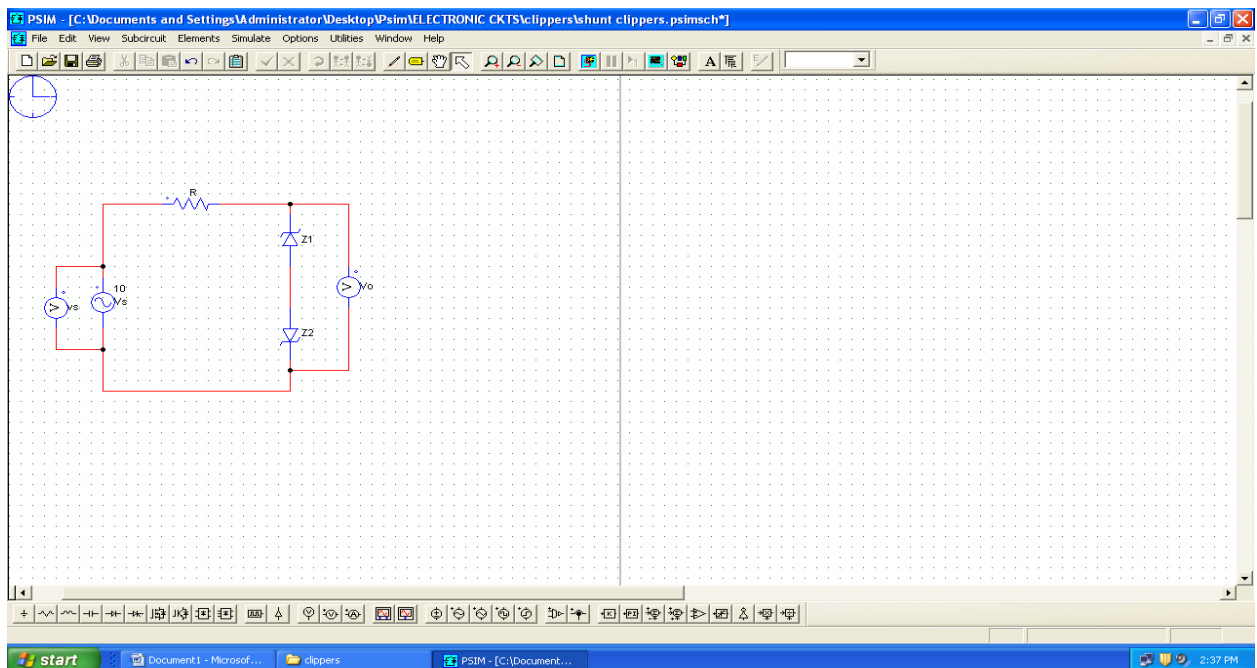



## Output waveforms

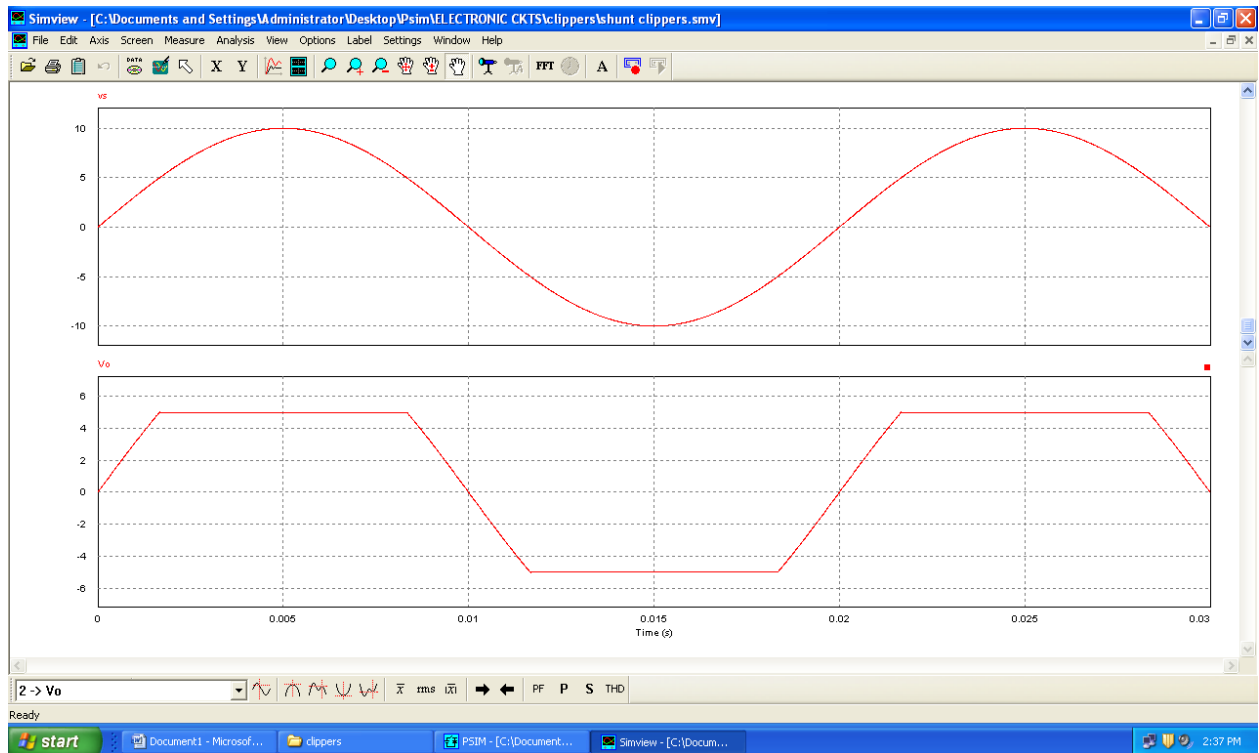





# CLAMPERS

## Negative clampers

Select source

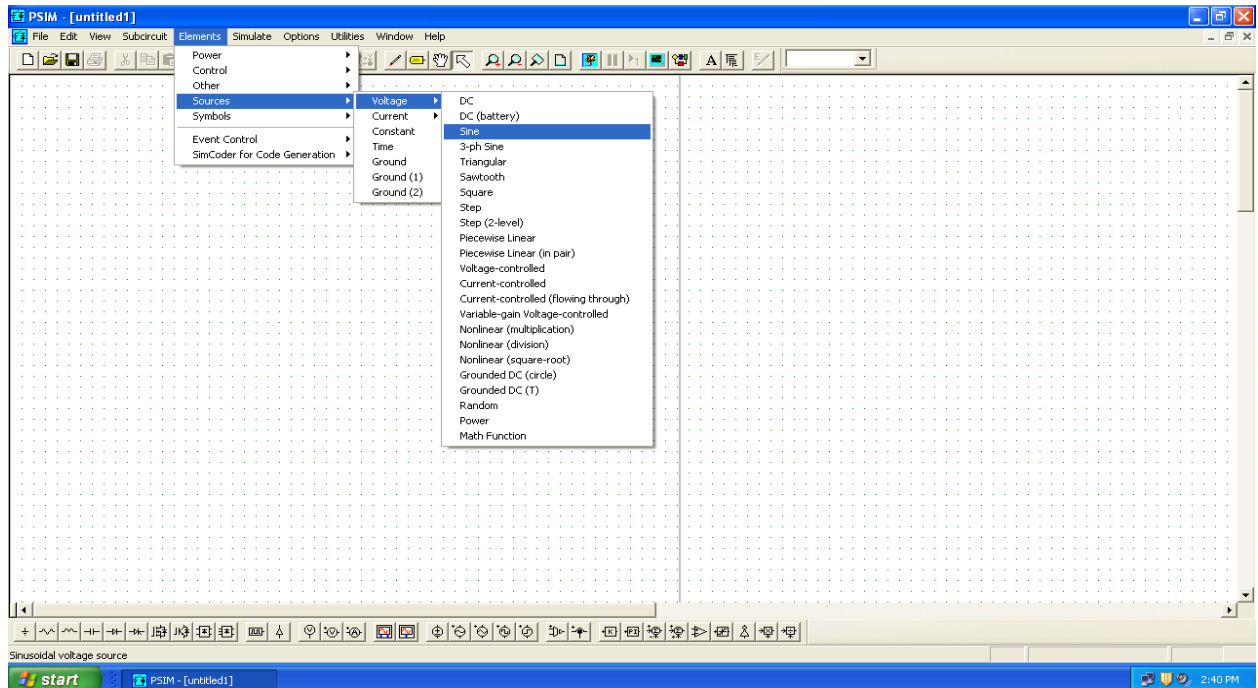


Select the capacitor

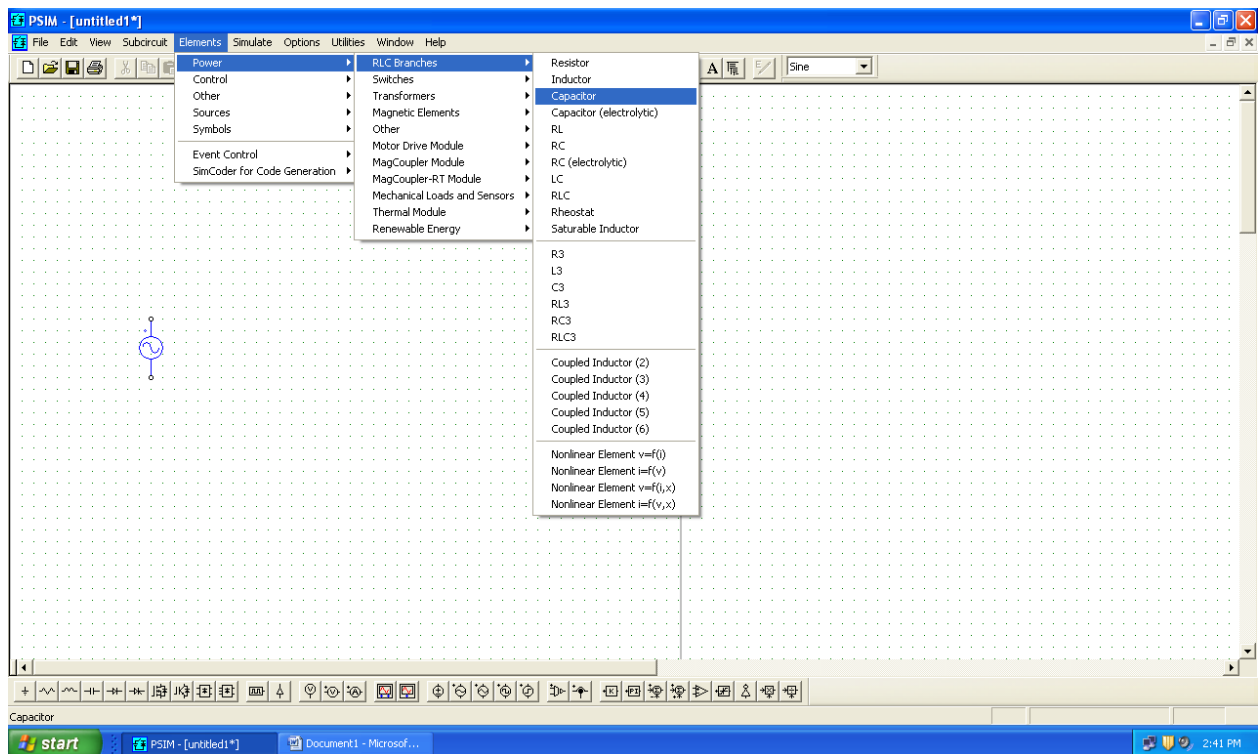




Select the diode

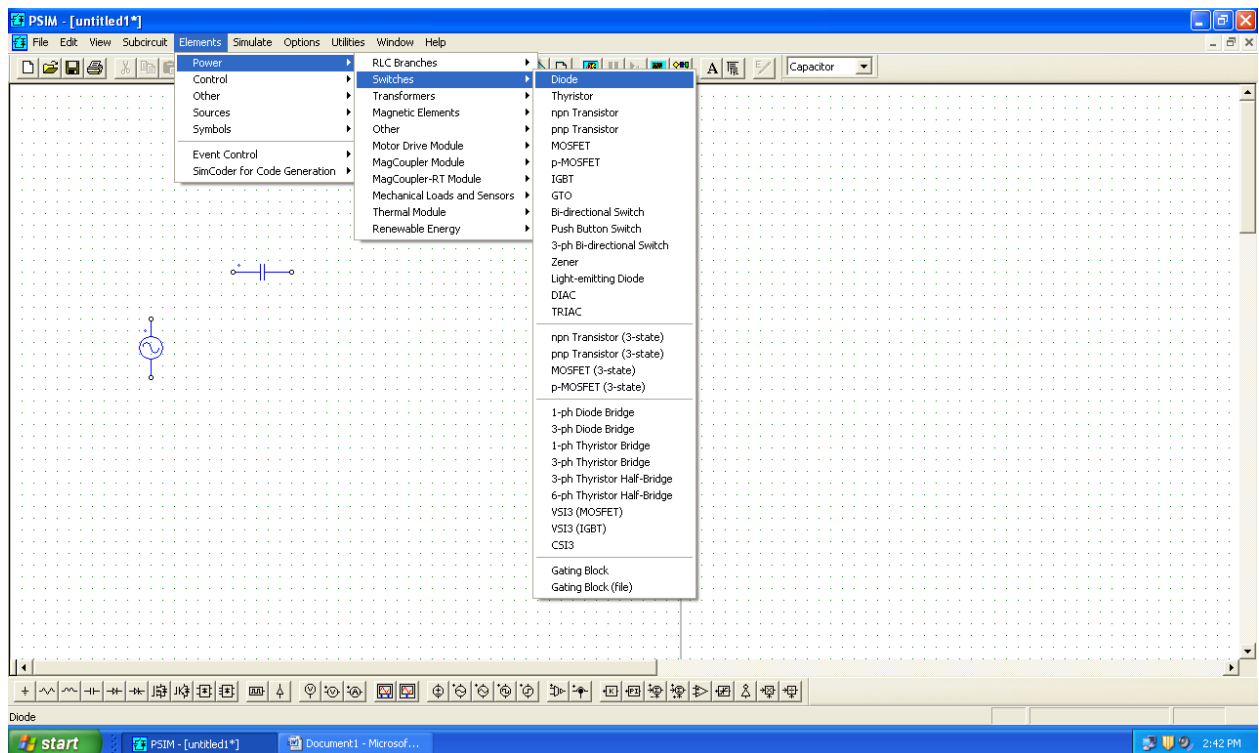


Connect the circuit using wiring tool

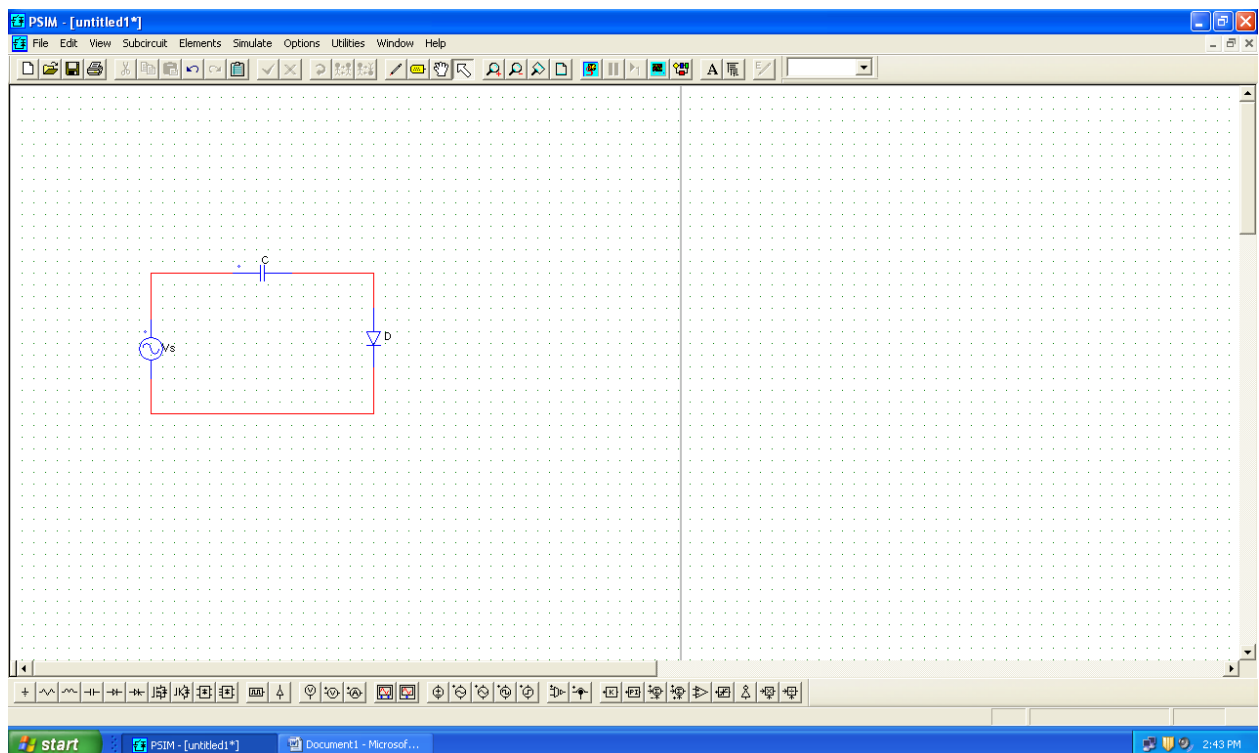






## Select volt meter

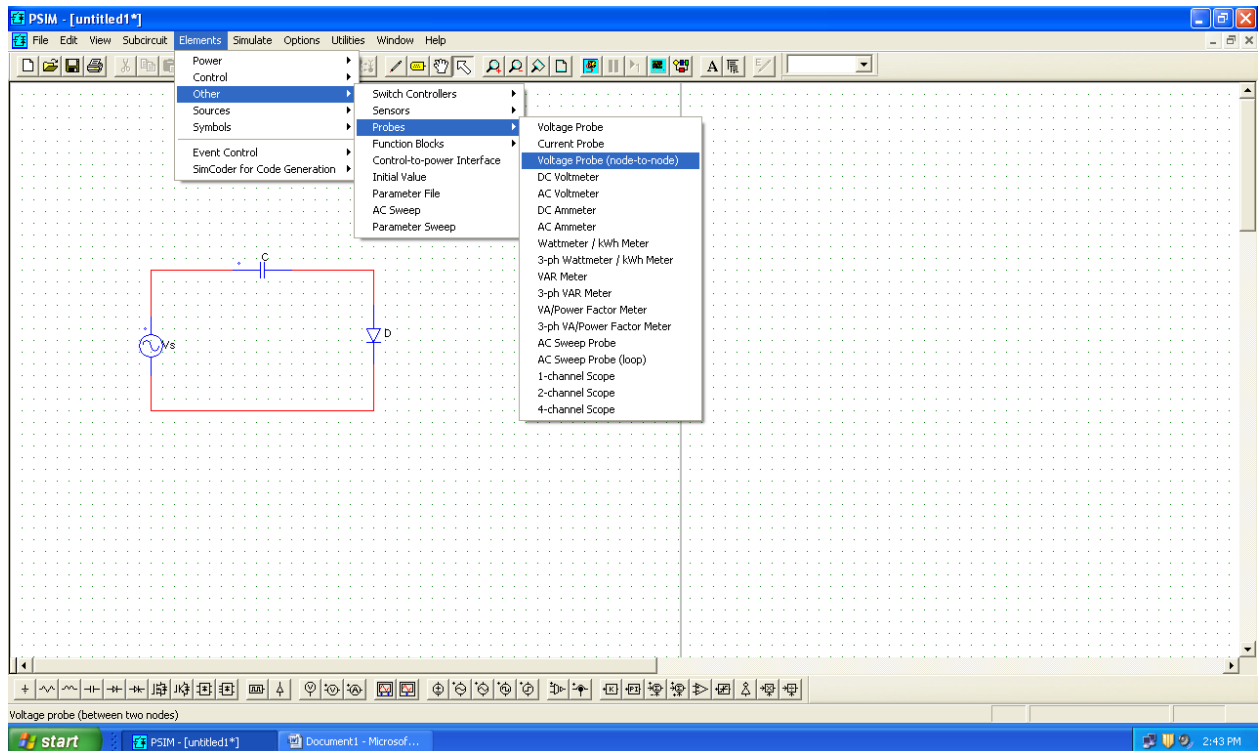


## select simulation control

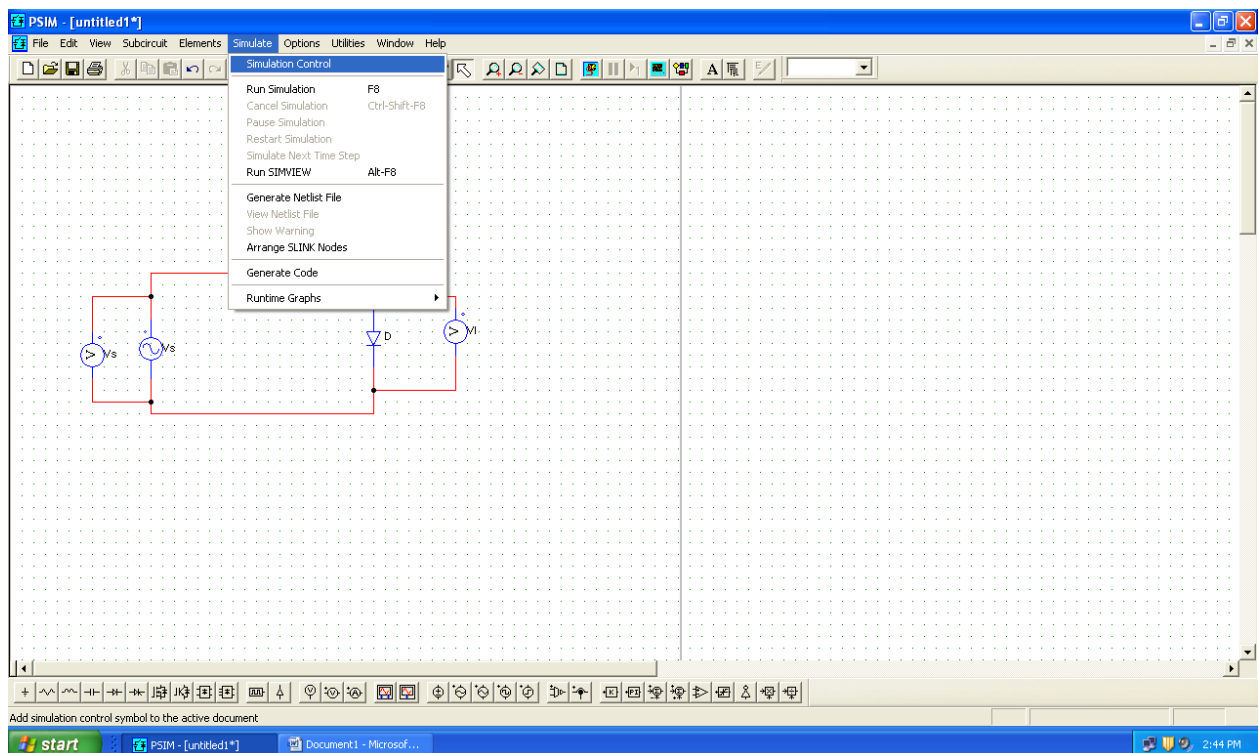




Give the values as shown below

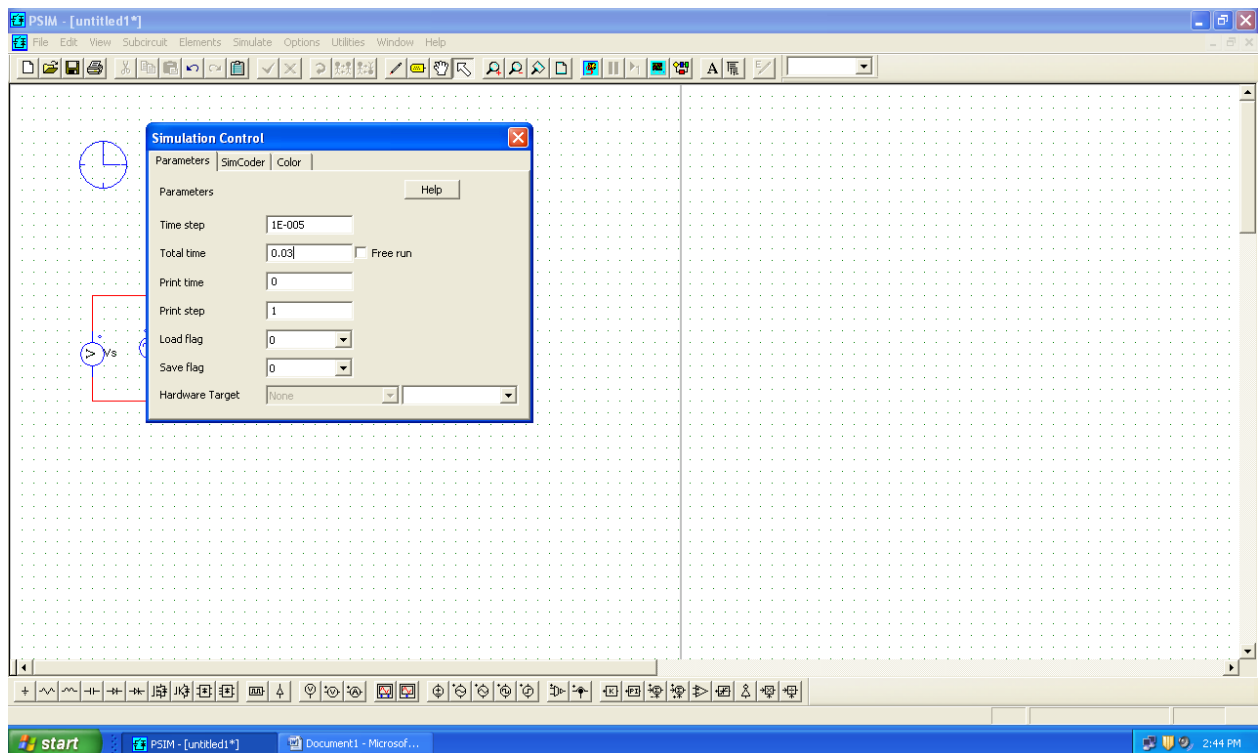


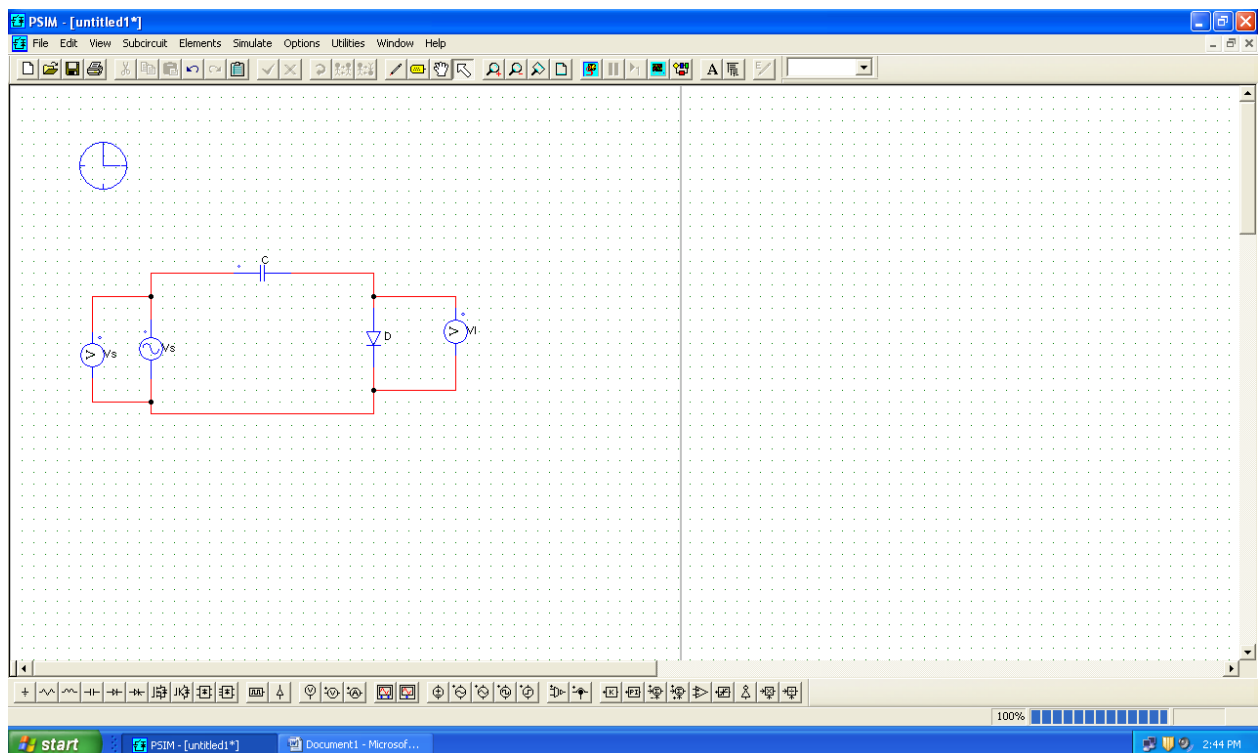Give the proper labeling to all the elements






## Run circuit using run simulation

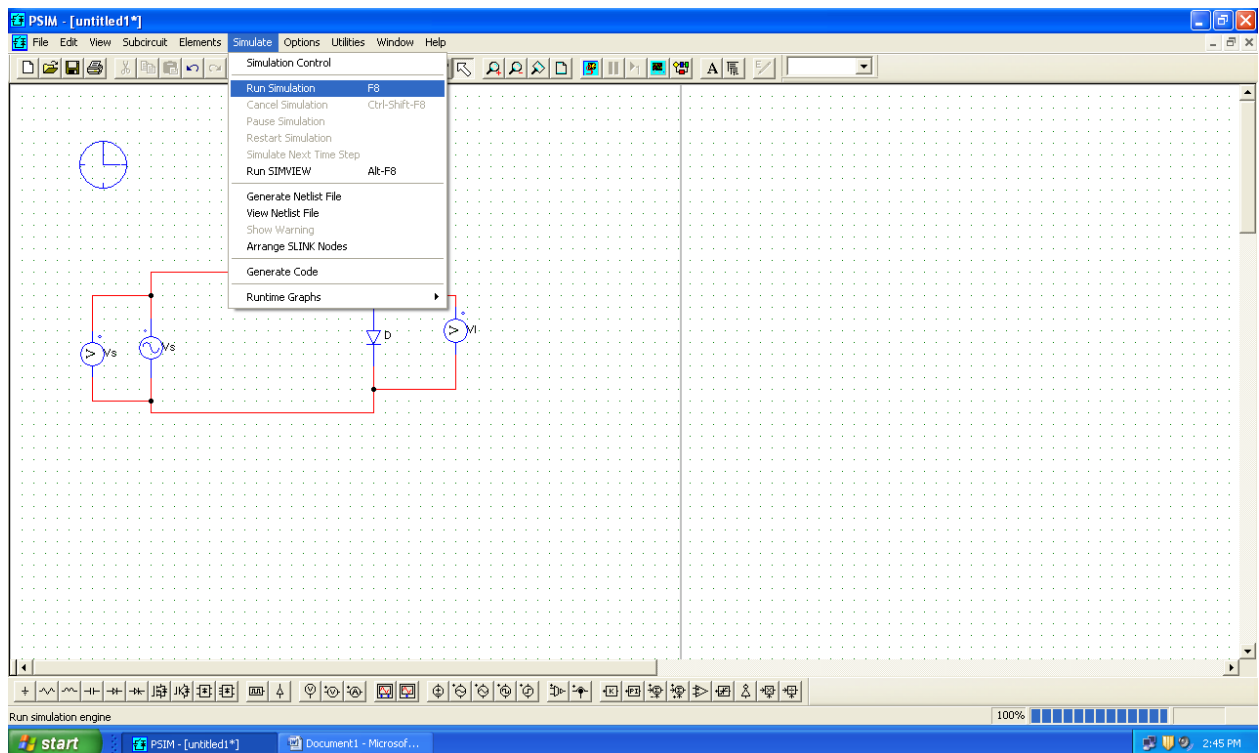


## Selection of output waveform

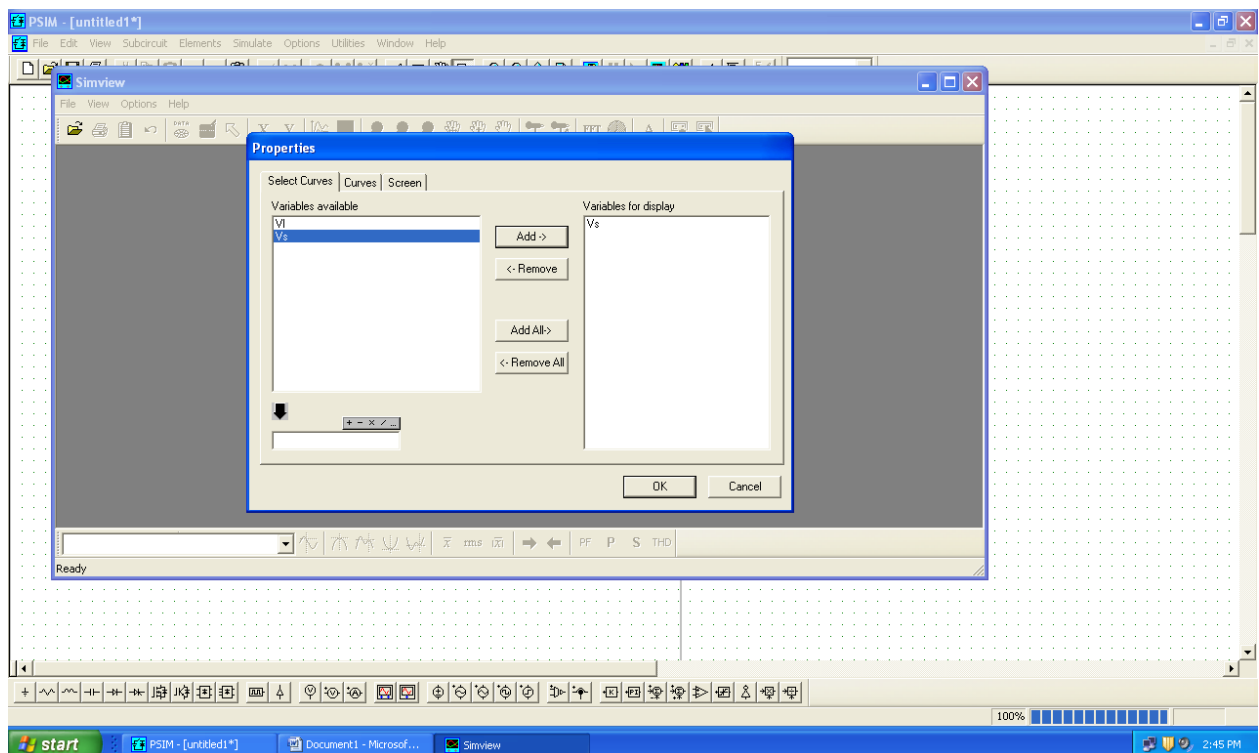




## Selected waveform

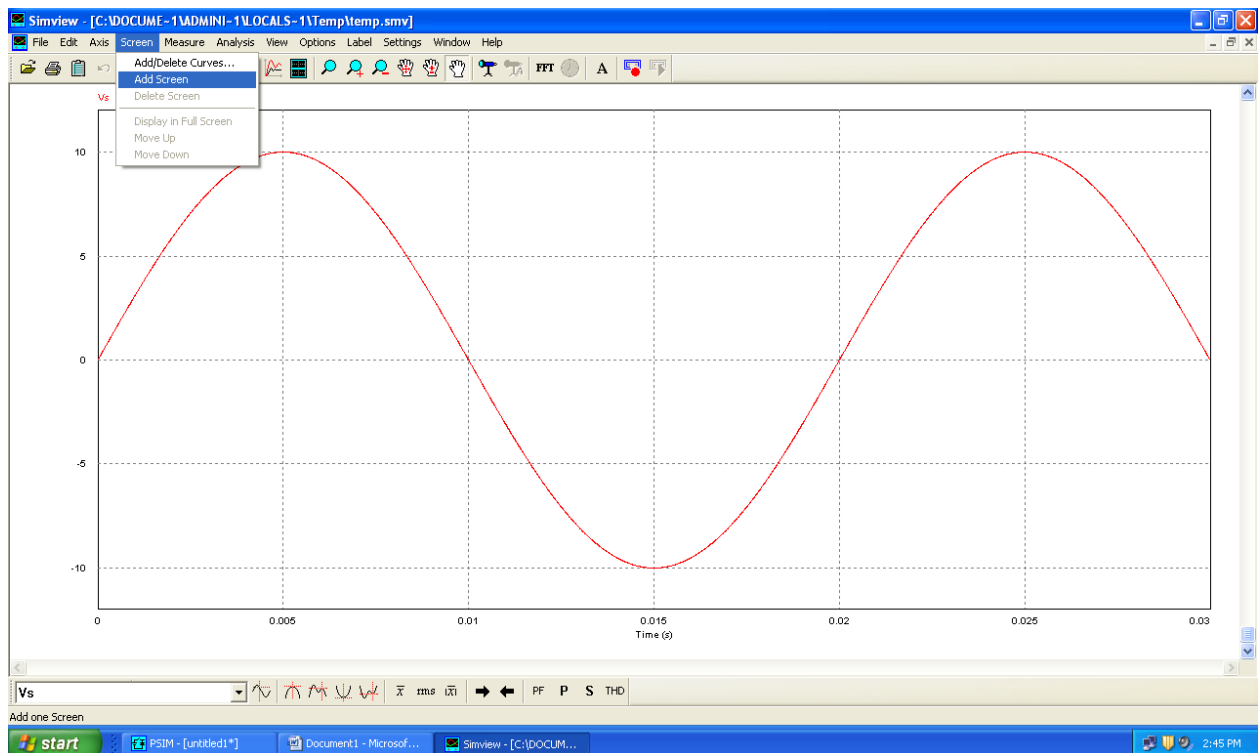


## Addition of other waveform

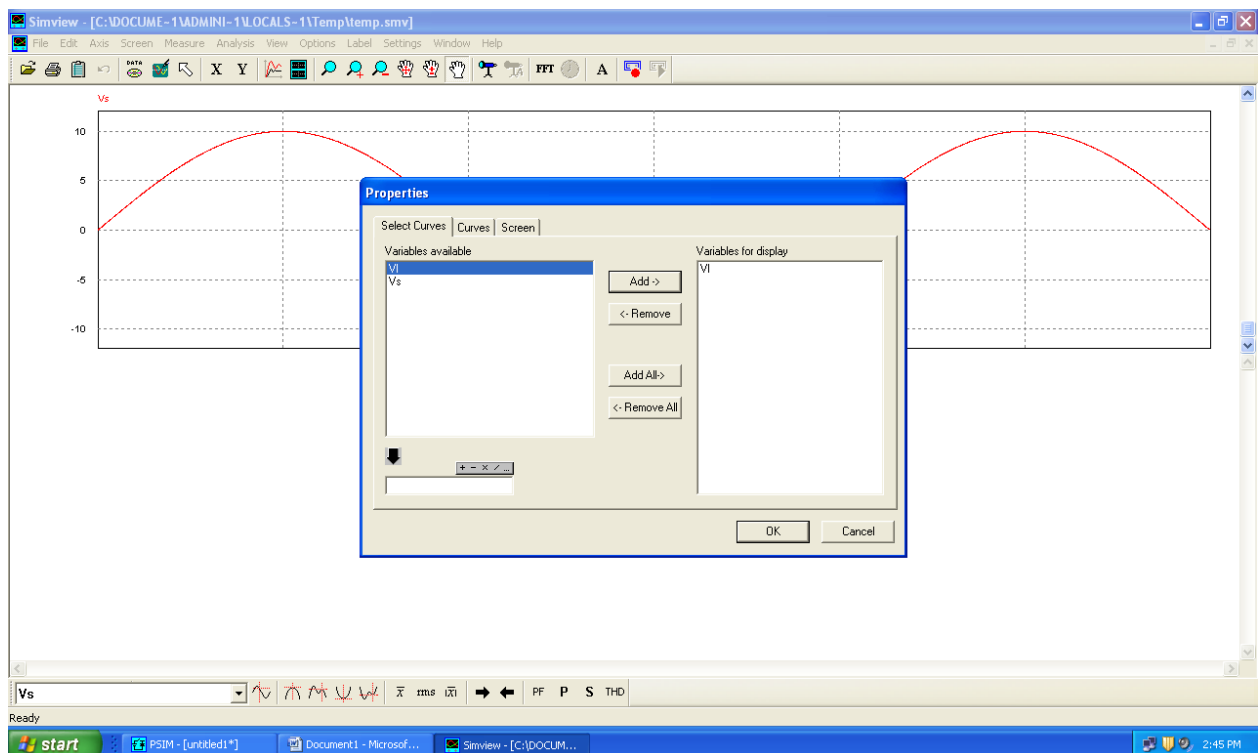



## Output waveforms

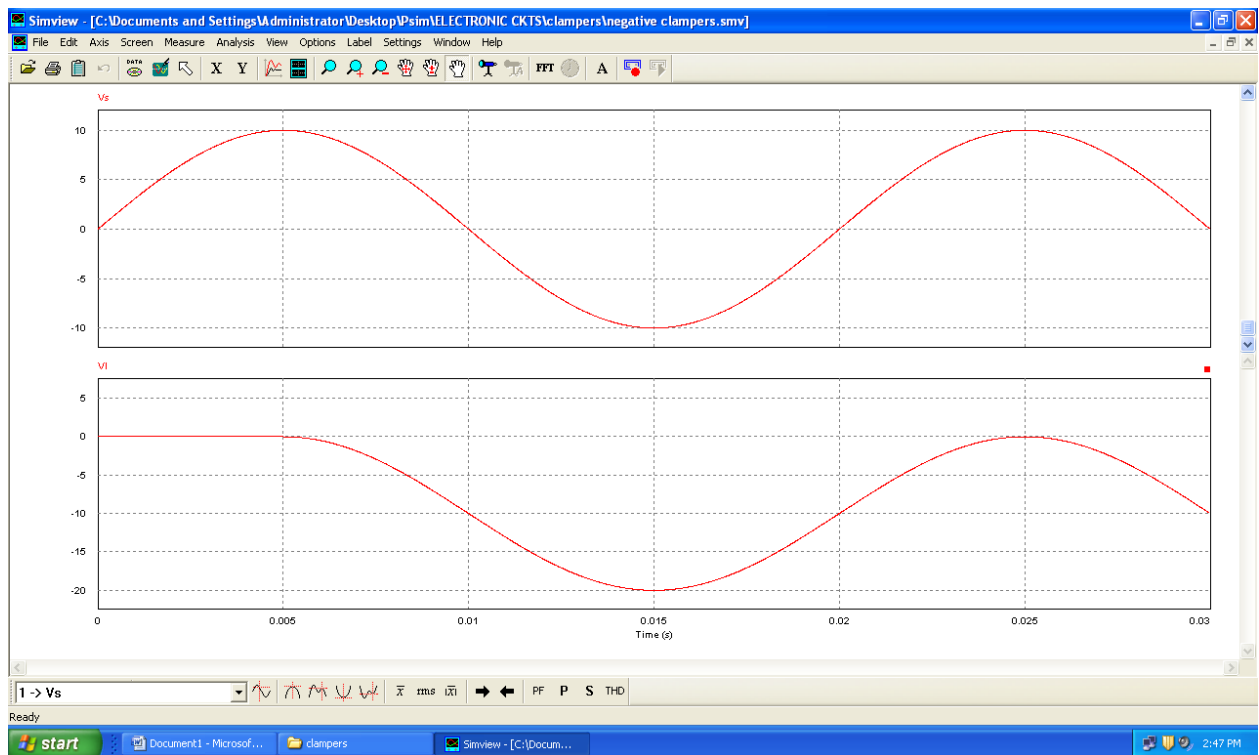





## Positive clamper

Select the elements as shown above and connect them as shown in below figure with proper labeling

Circuit diagram

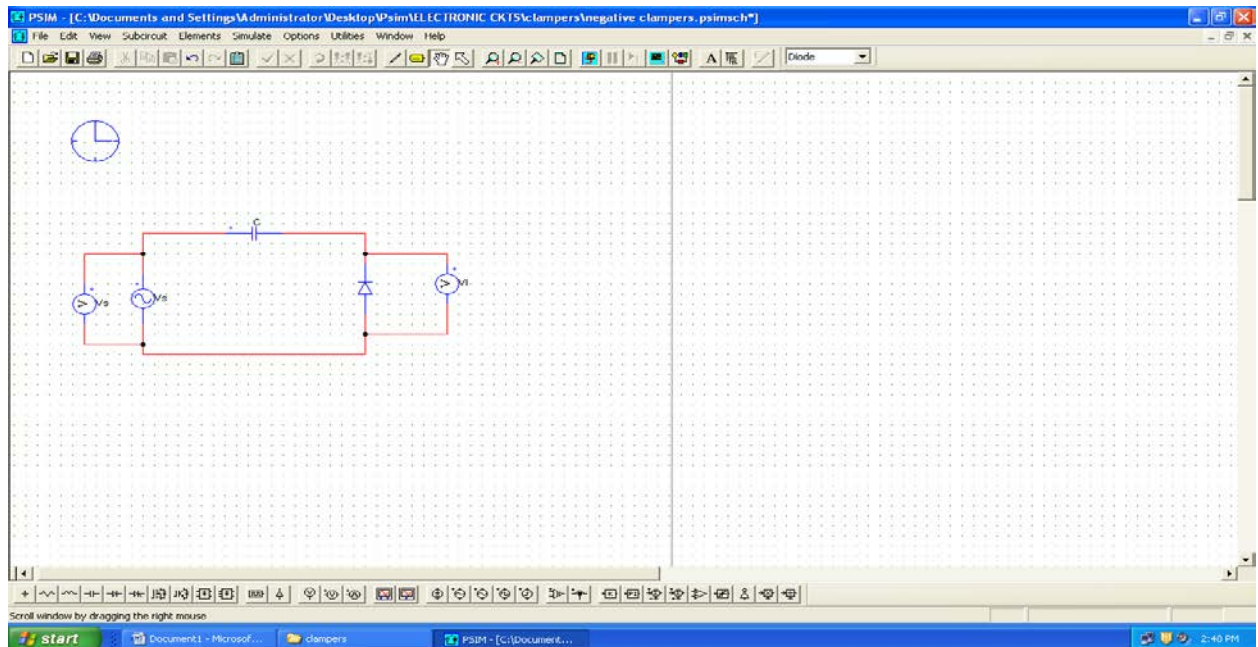


Output waveforms

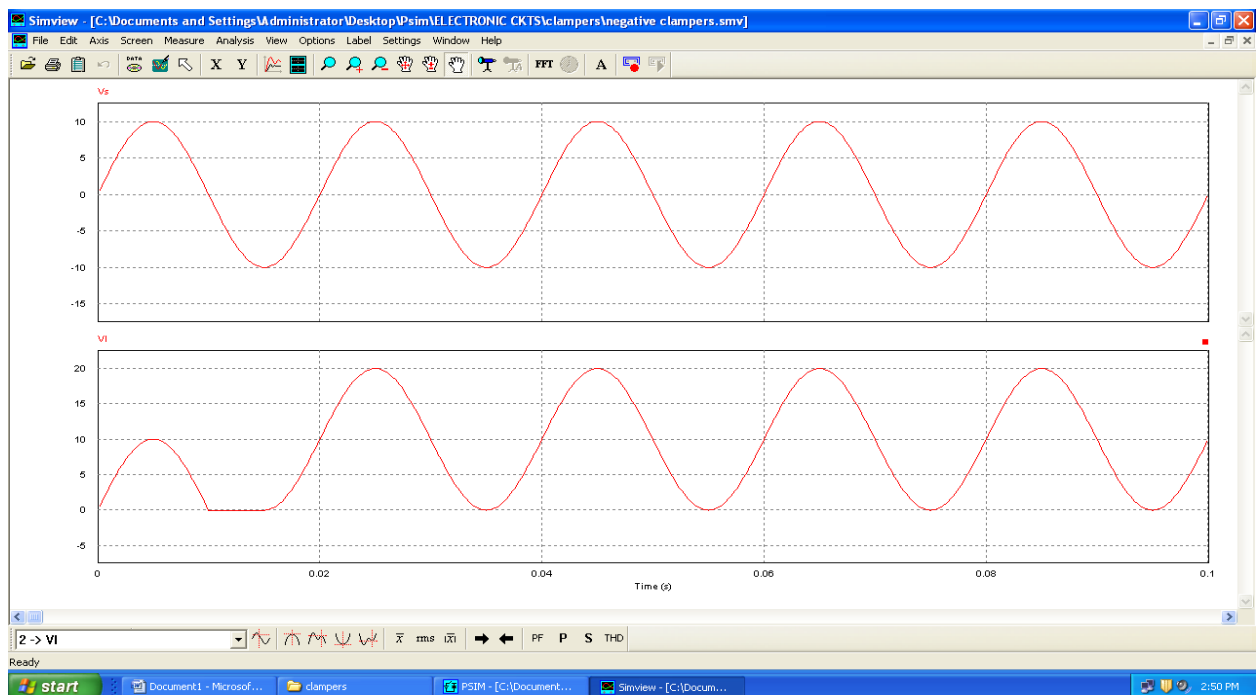




## Multiplier circuit

Select the source

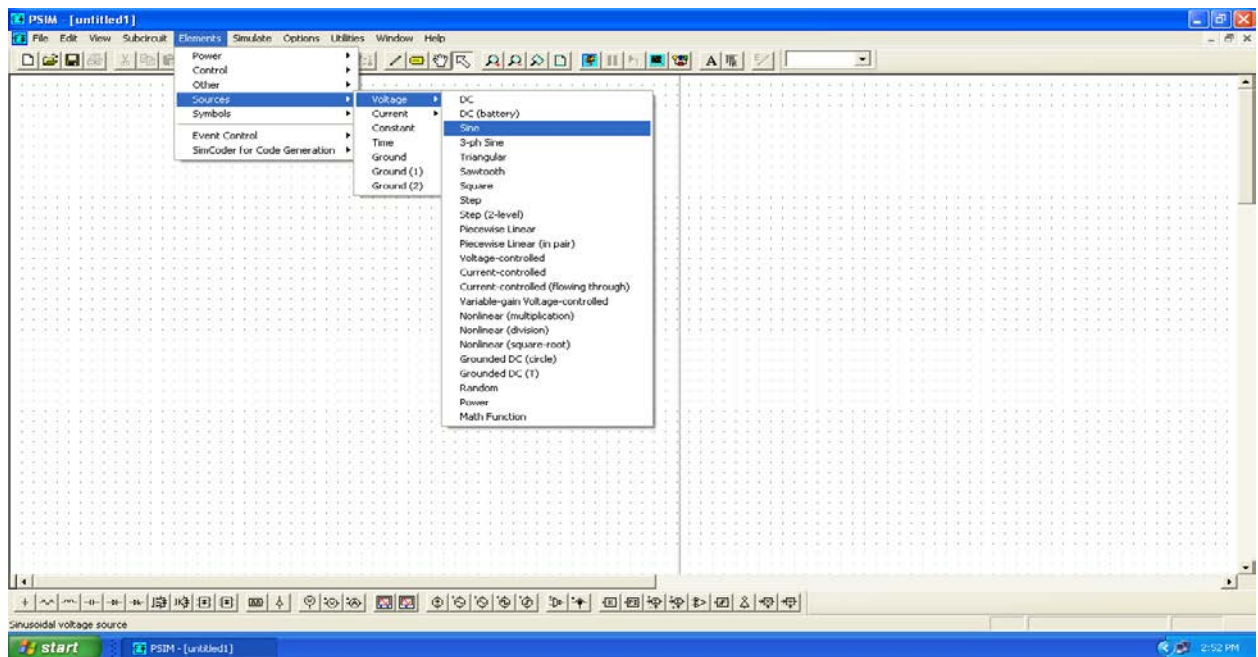


Select the capacitor

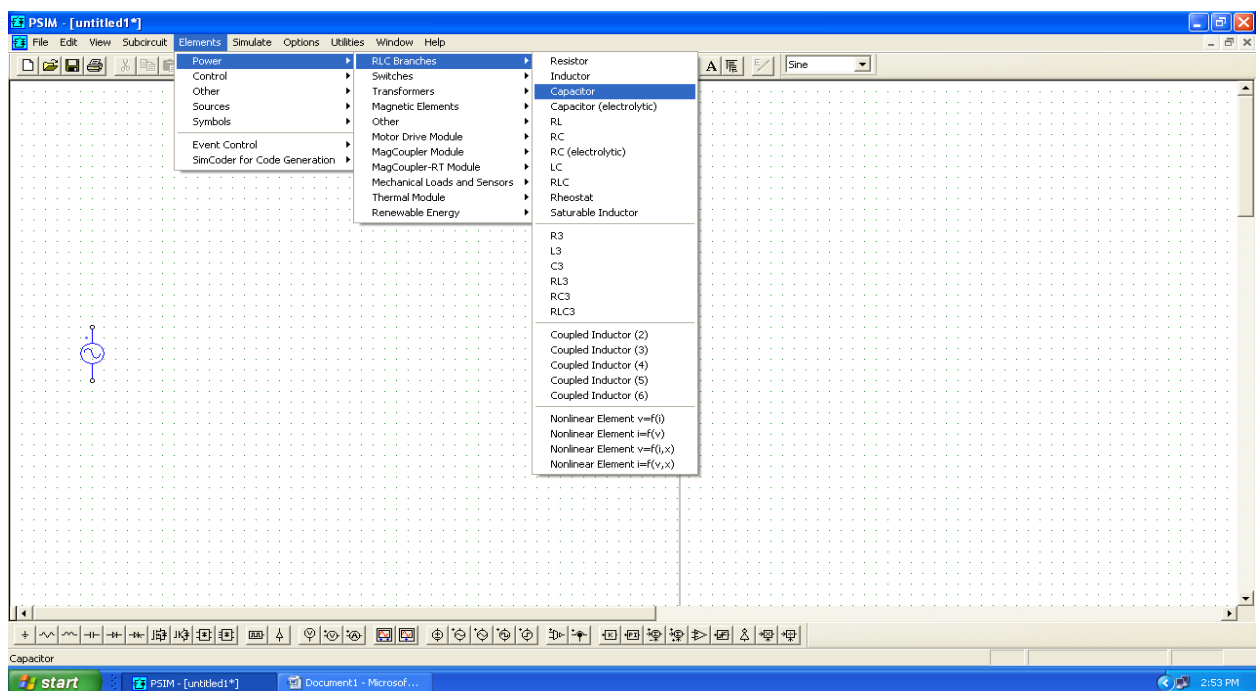





Select 4 capacitors

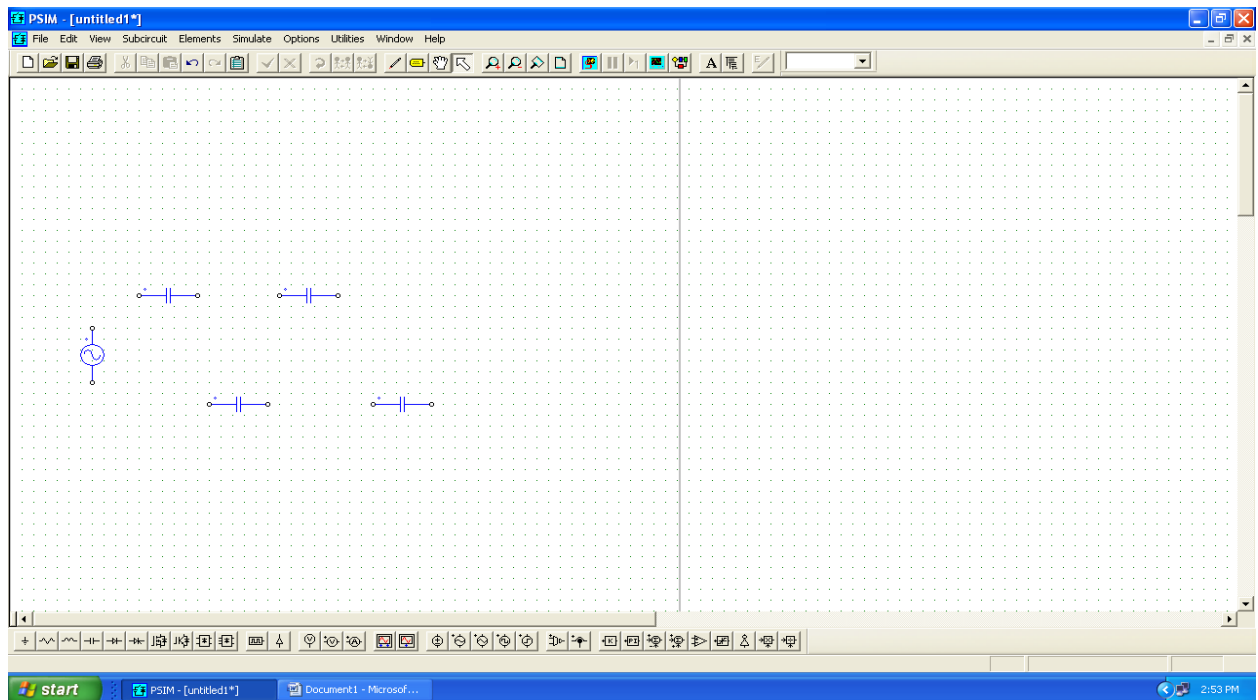


Select the diode

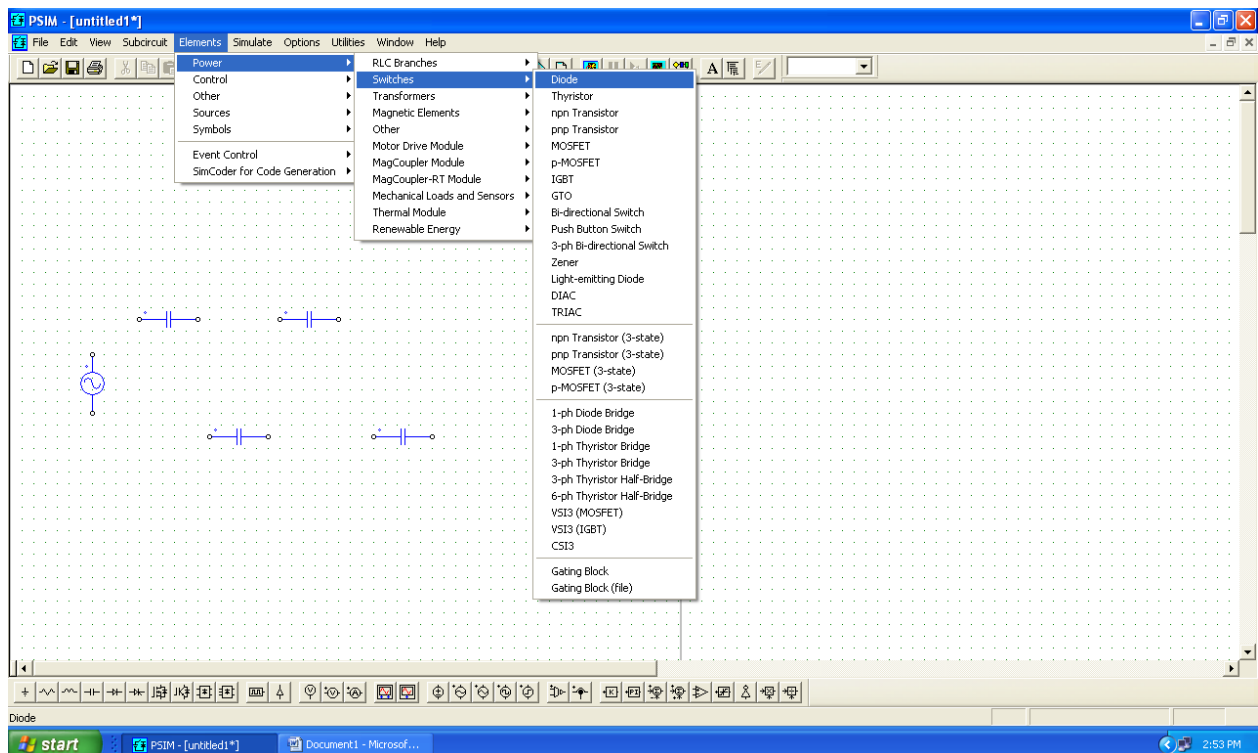



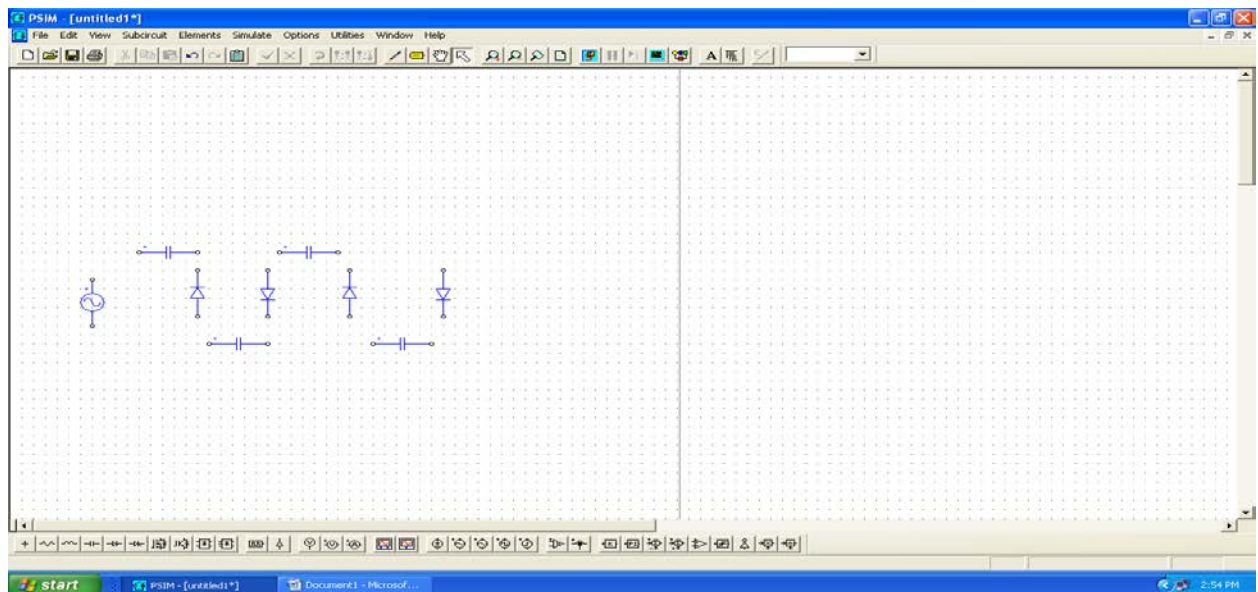


Connect the circuit using wiring tool

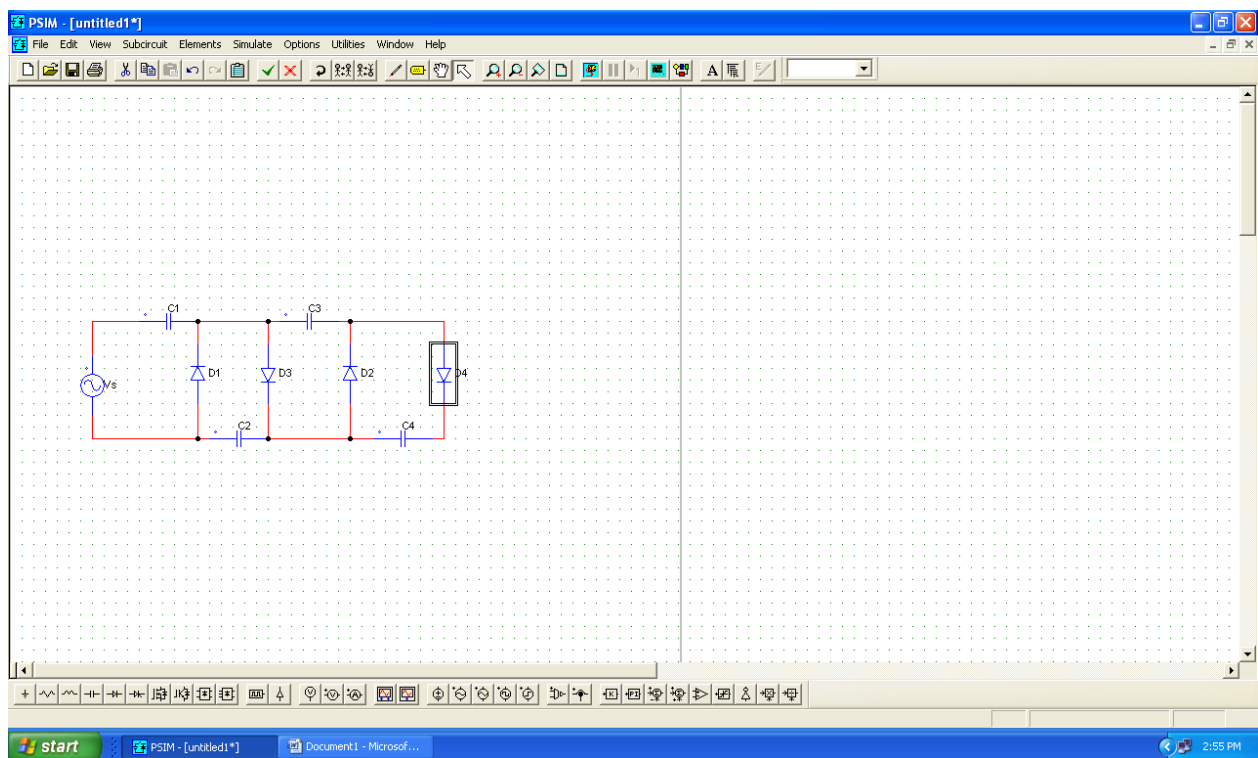




Select the volt meter

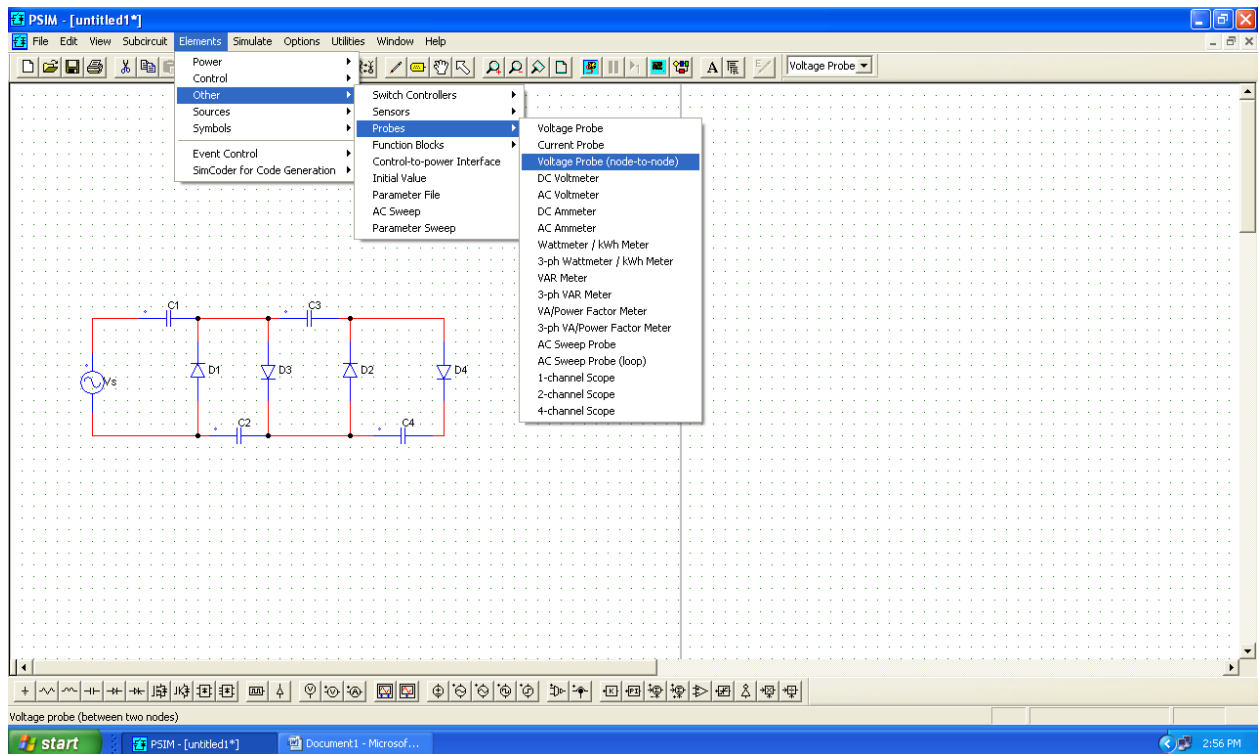

Connect as shown below using wiring tool

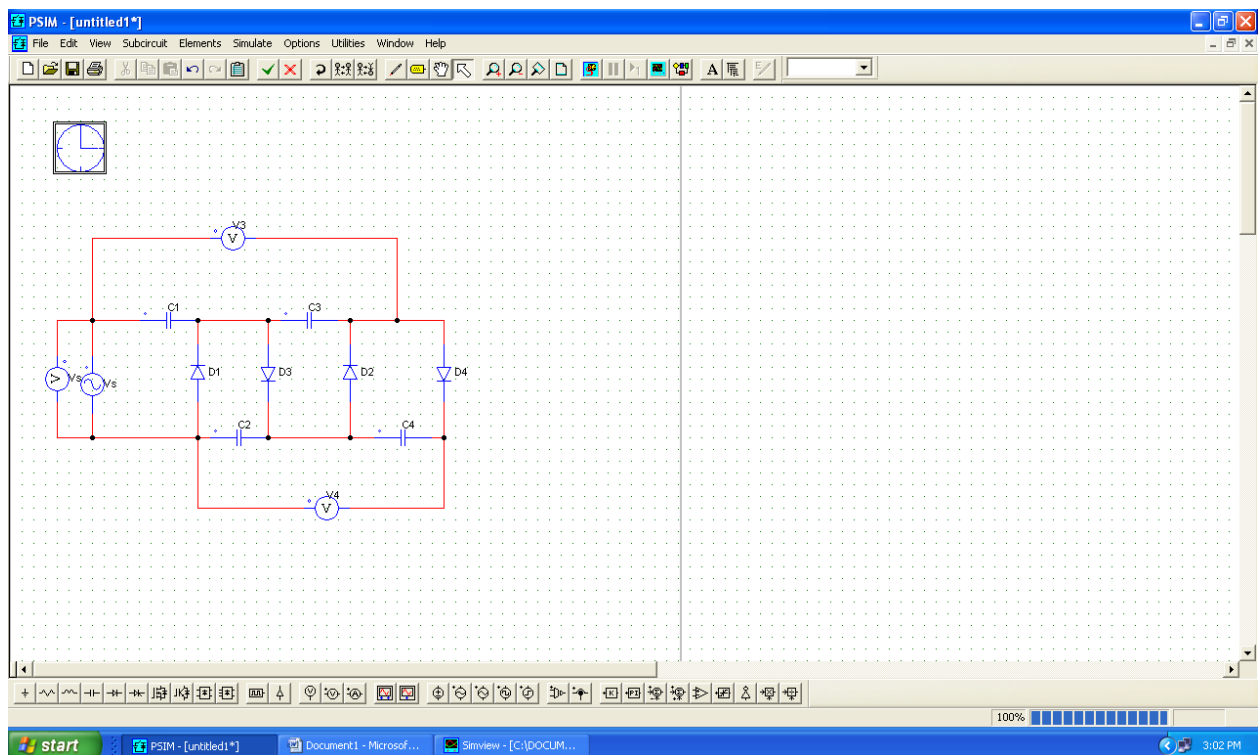




## Output waveforms






## INTEGRATOR

Select the op-amp

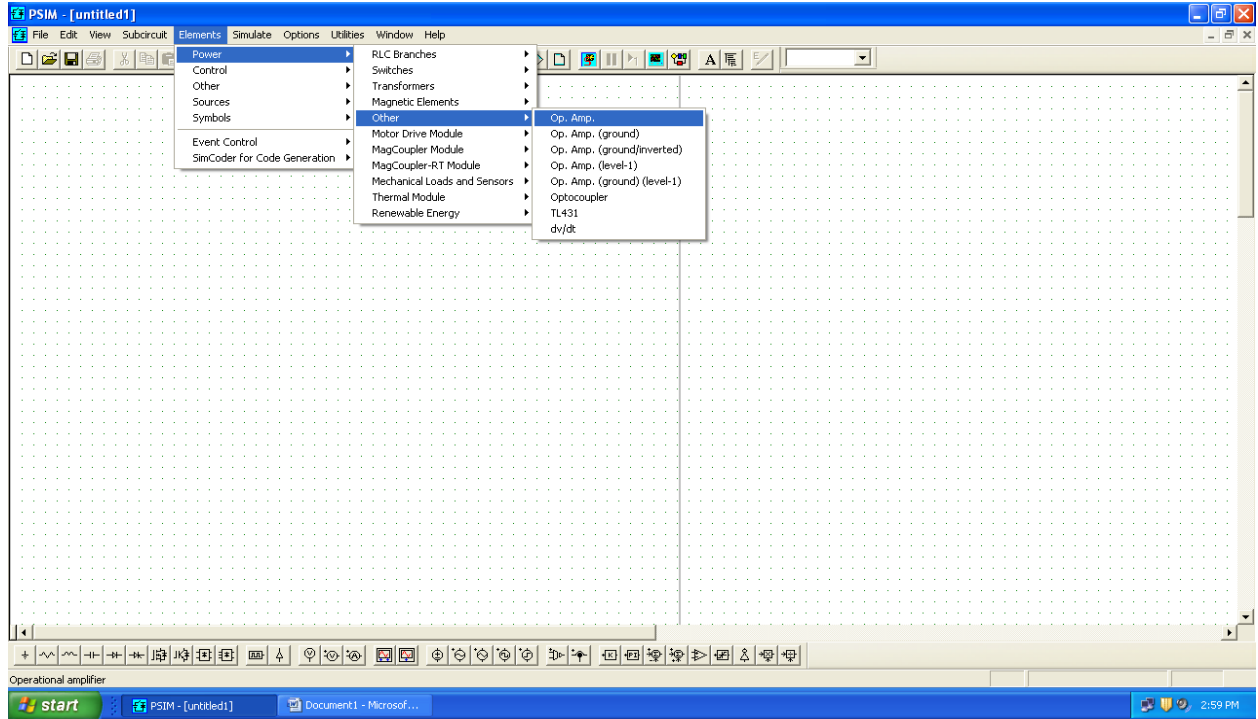


Select the triangular source

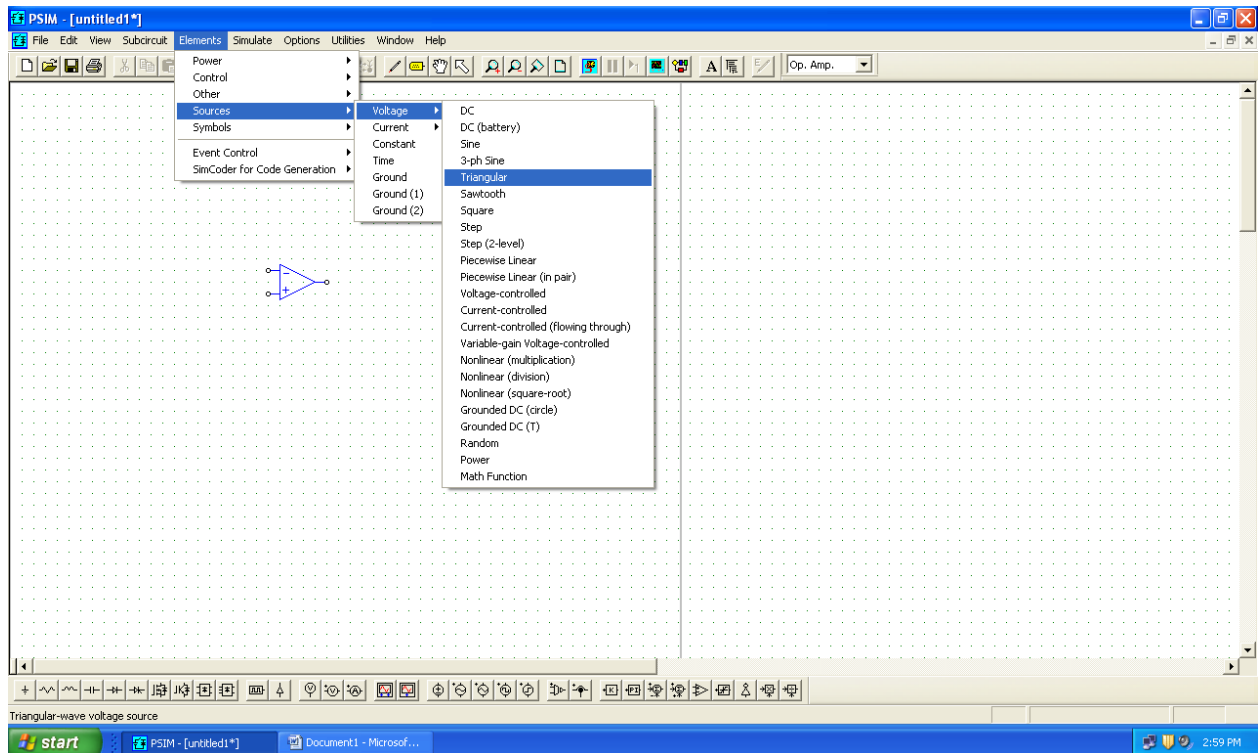




Select the resistor

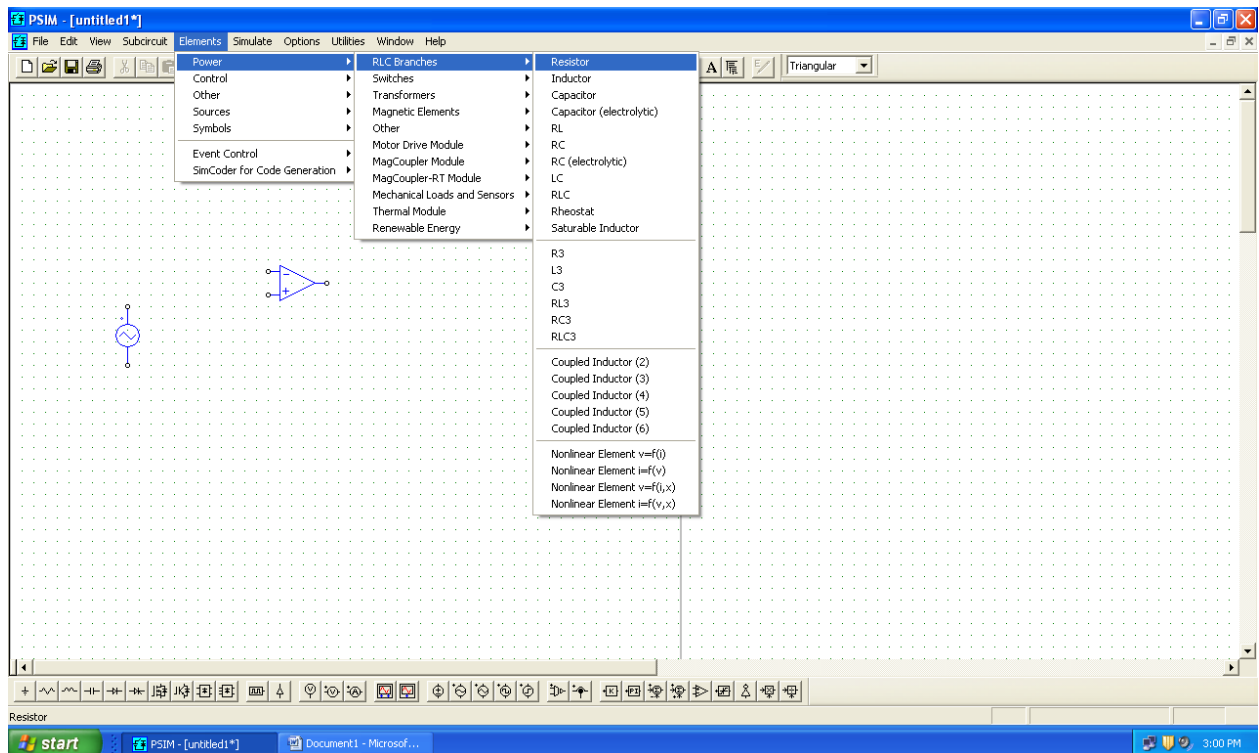


Select the capacitor

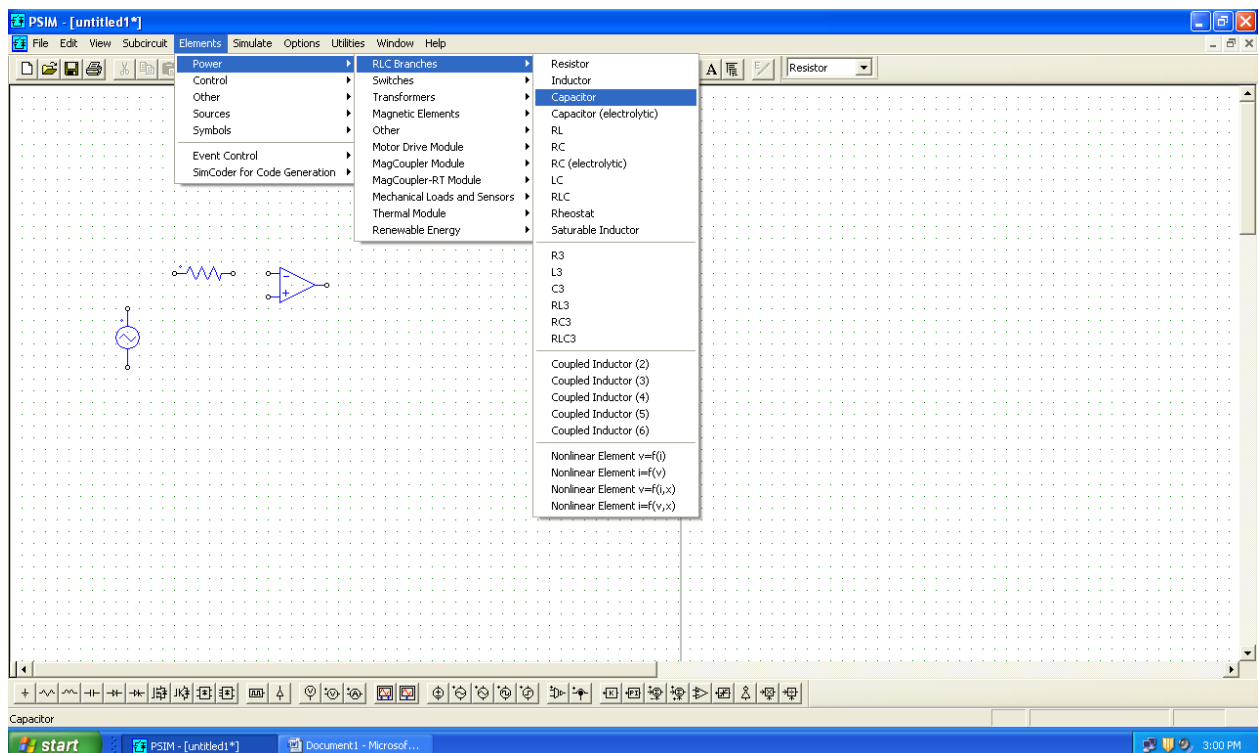




Select the volt meter

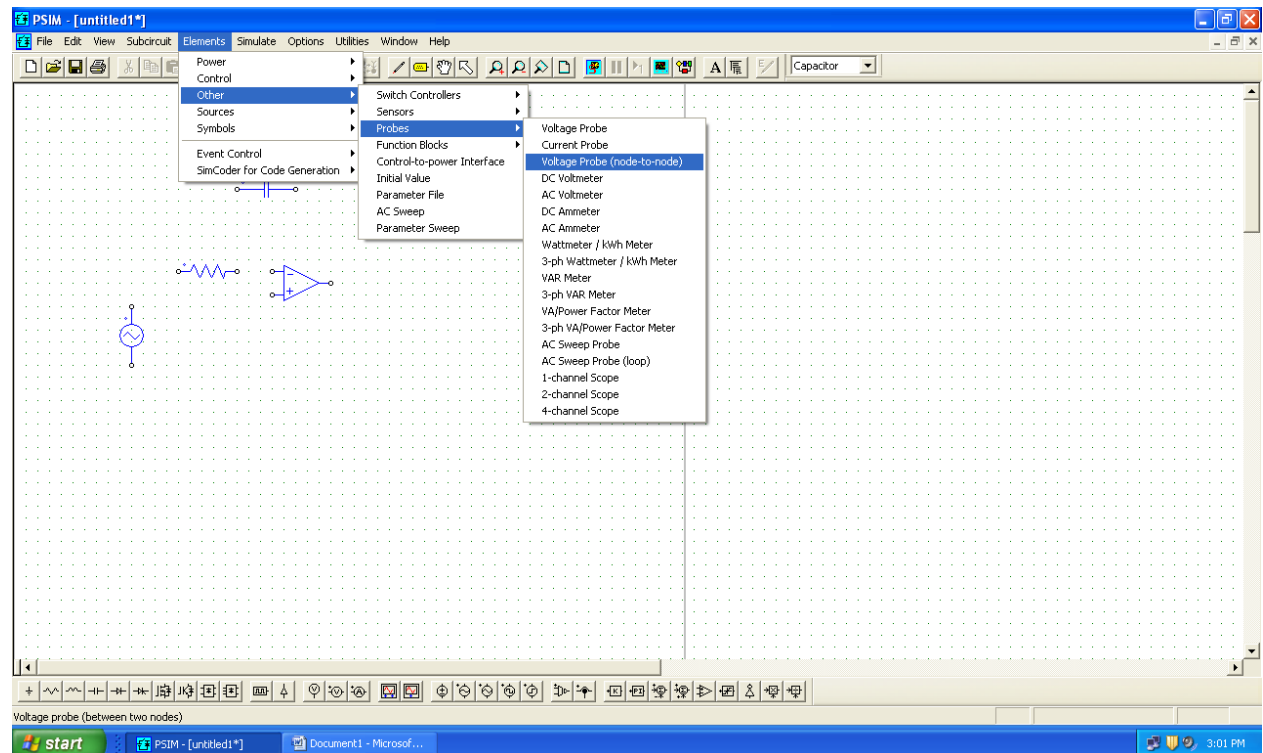


Select the ground

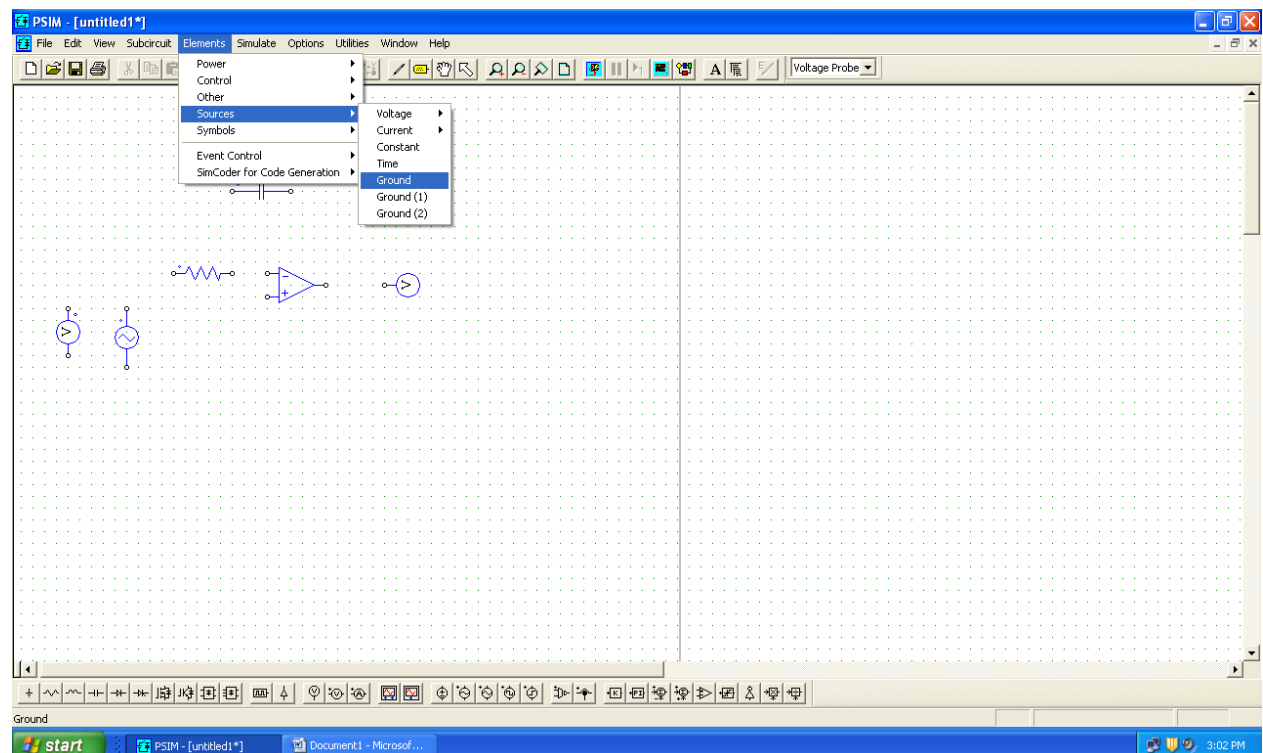





Connect the circuit using wiring tool

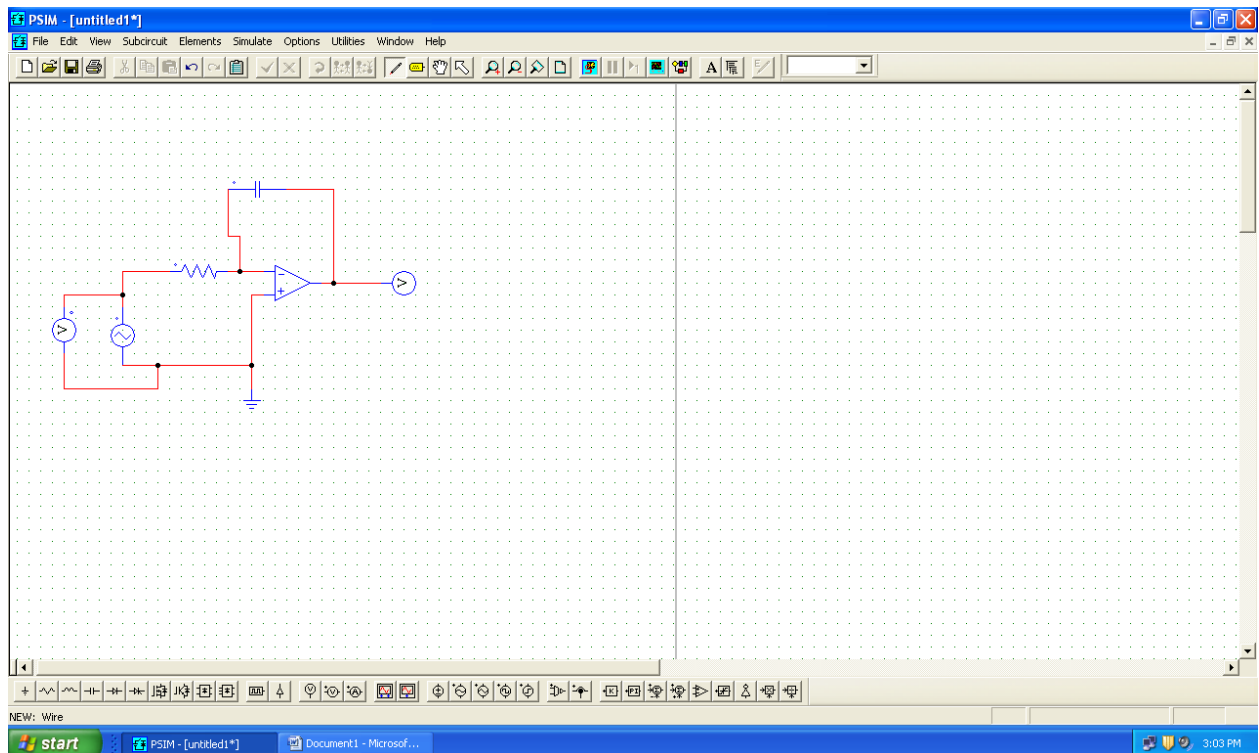


Select the simulate control


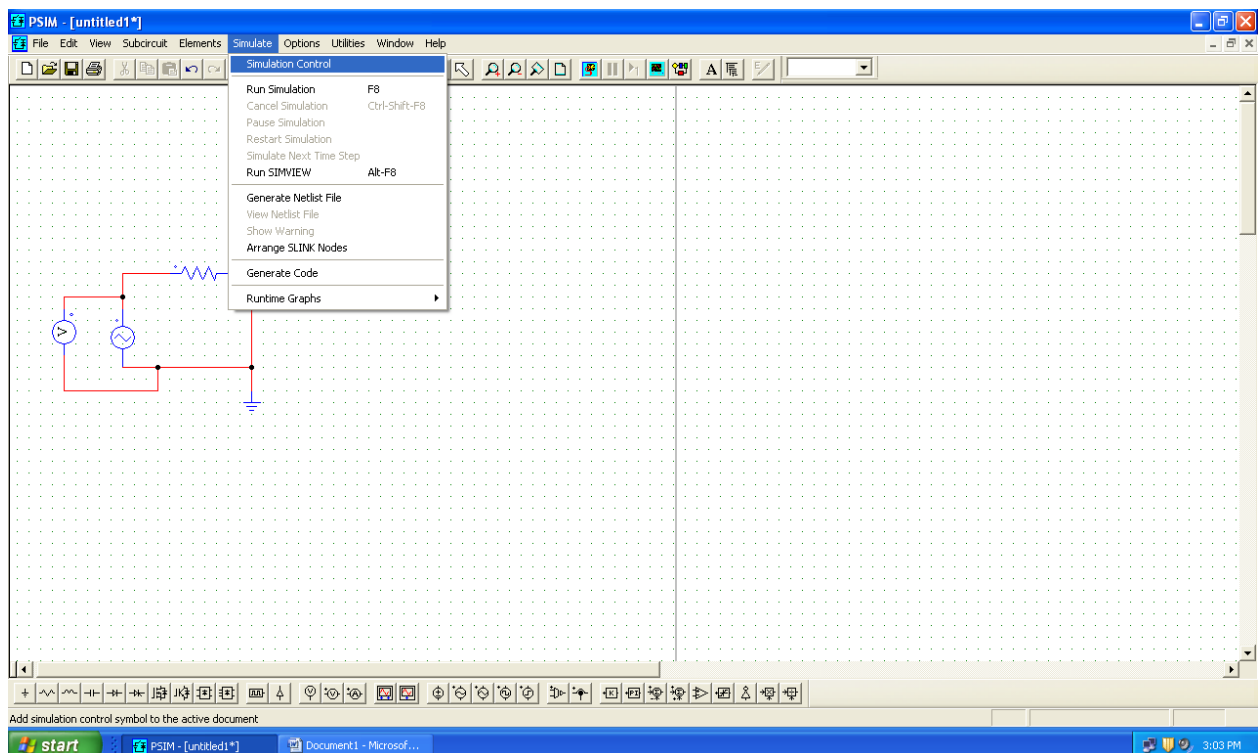


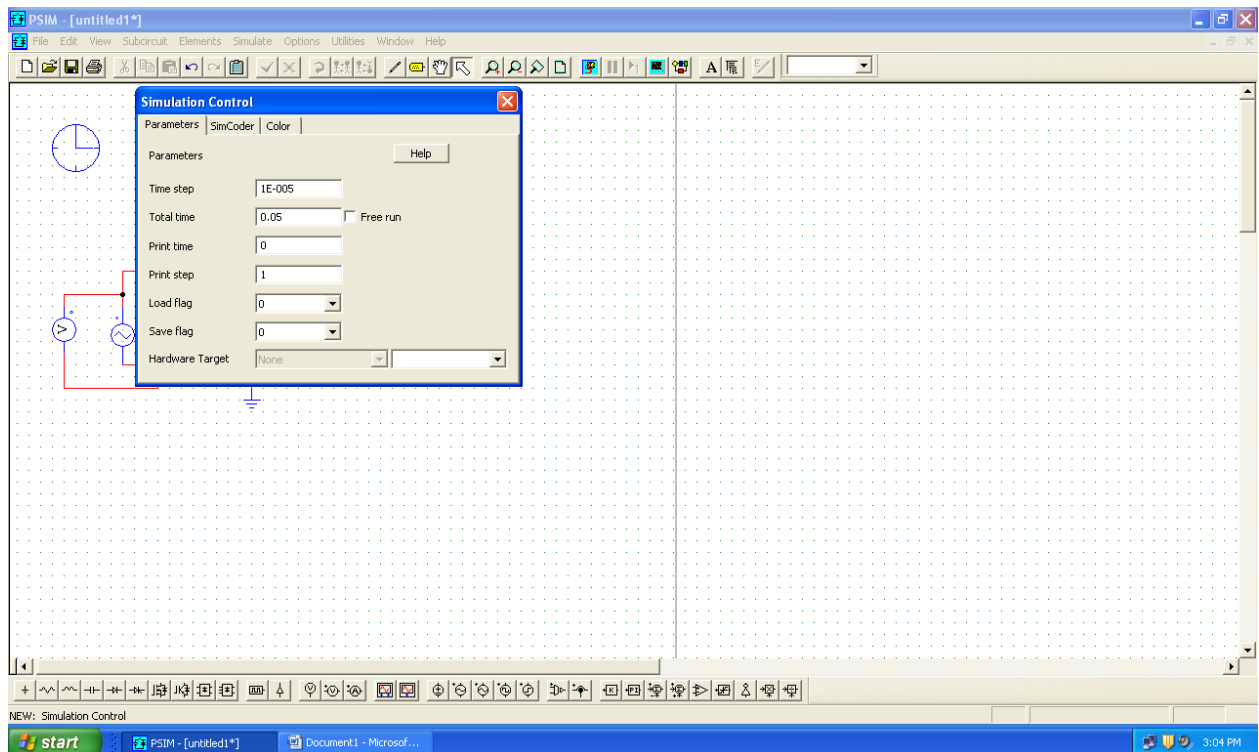


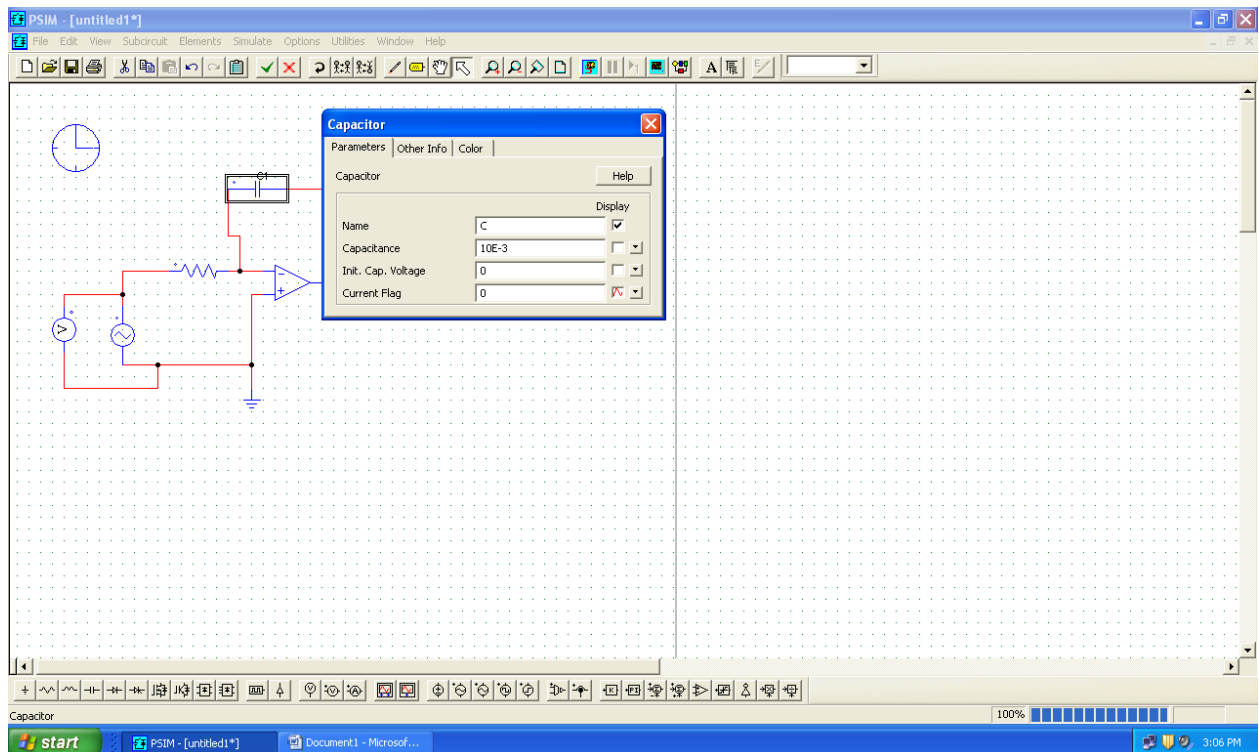Select the proper values R,C and triangular source






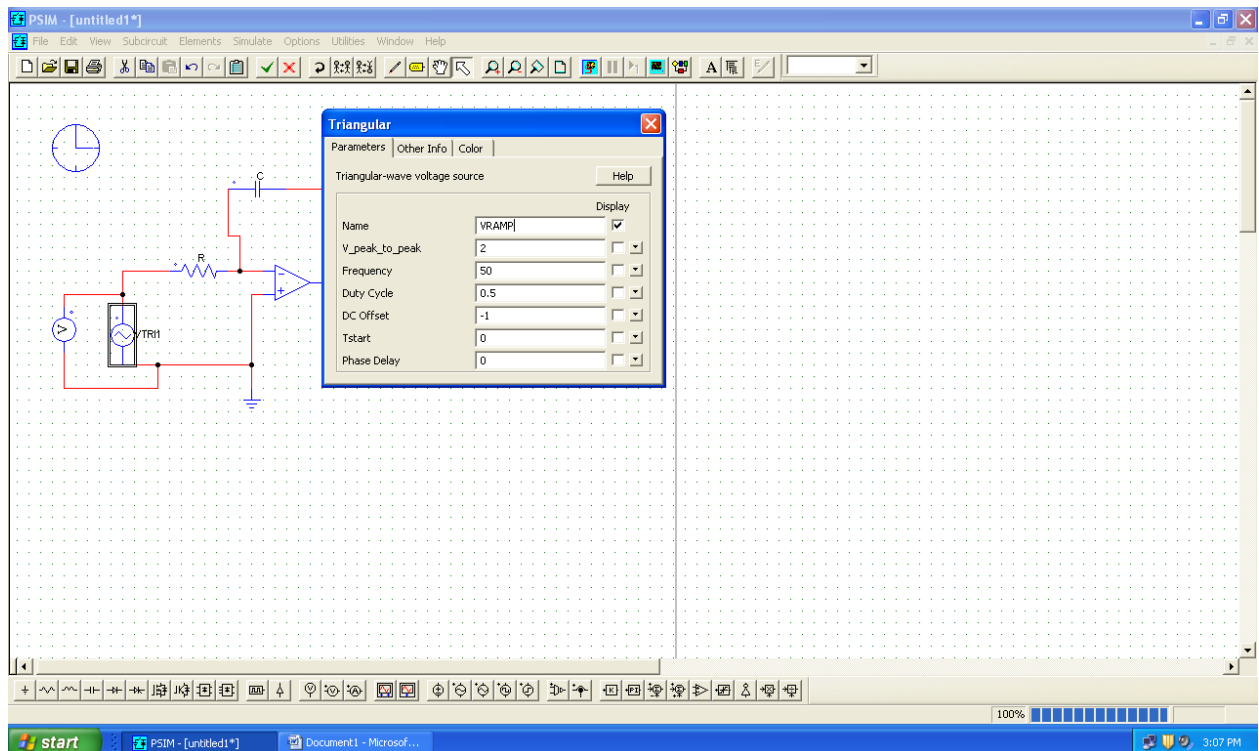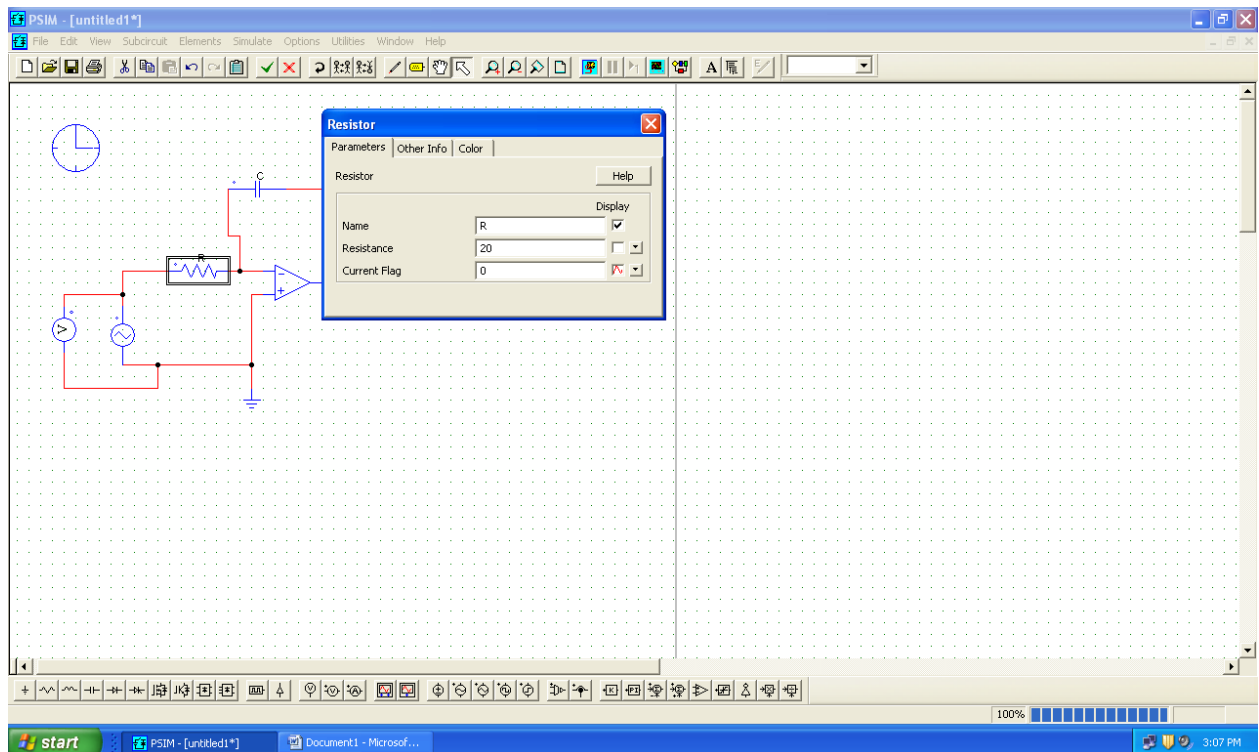

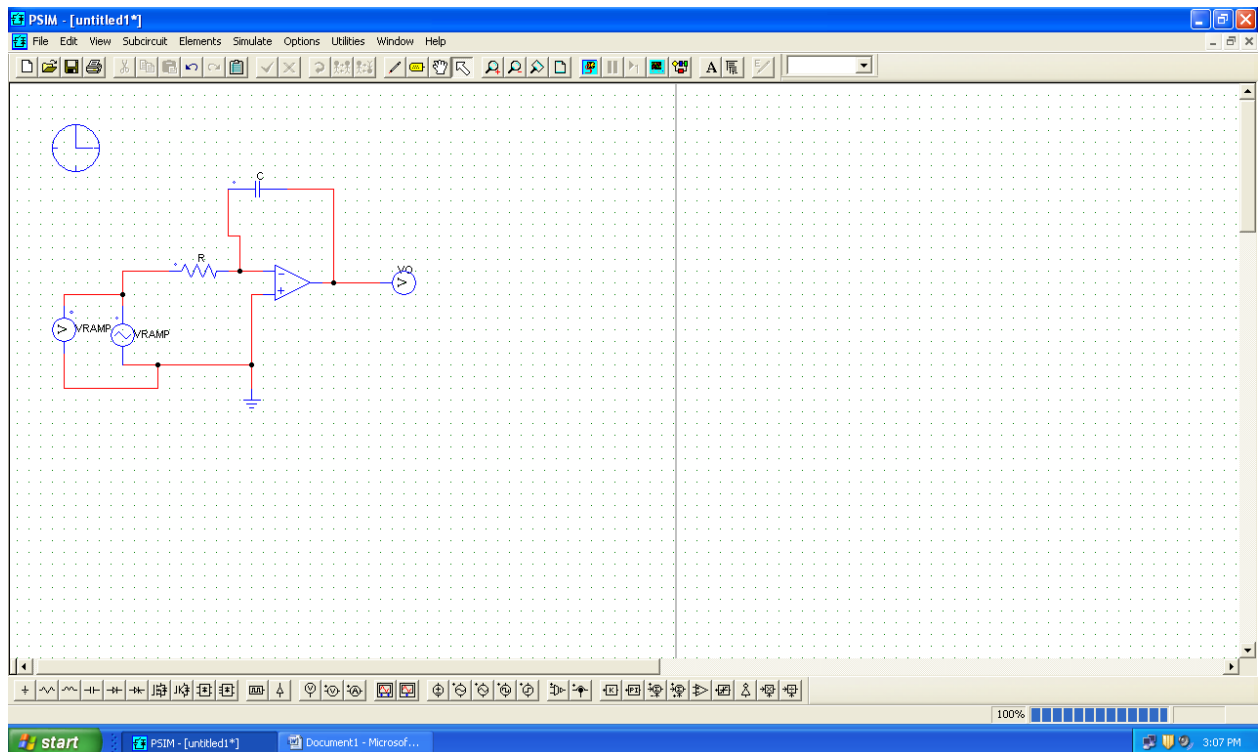


Run the circuit

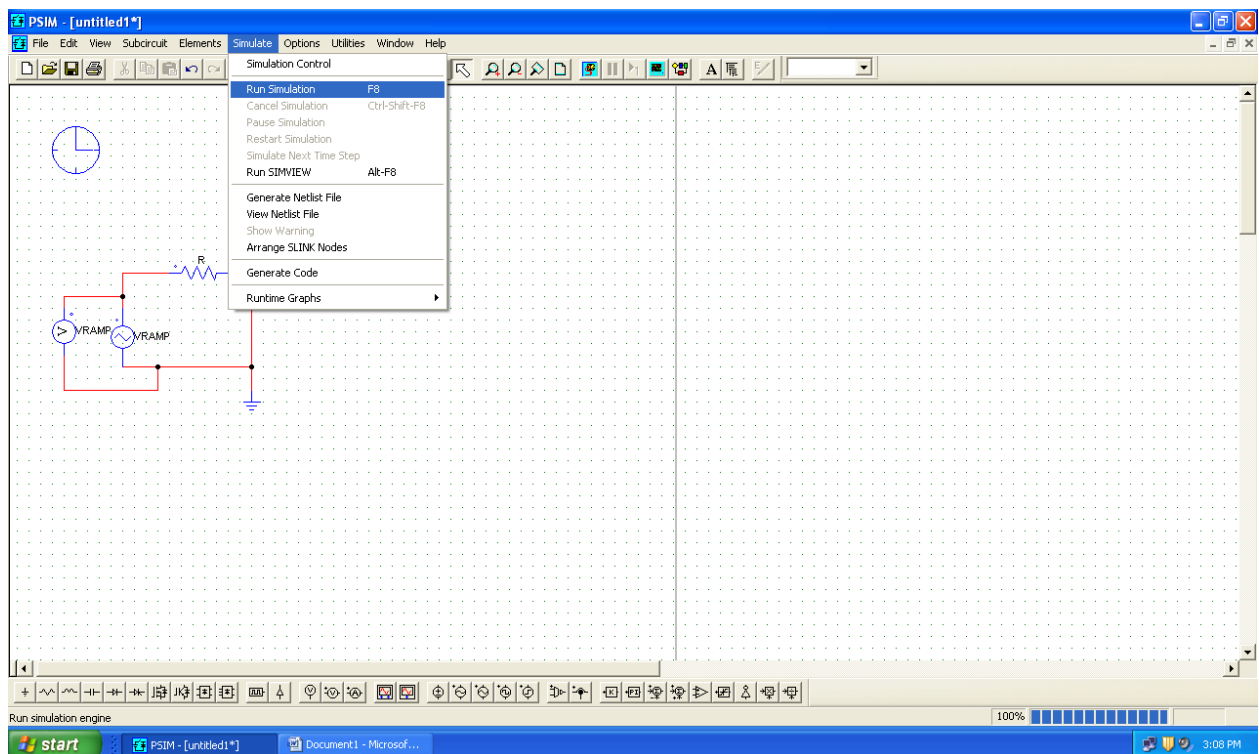




## Output waveforms

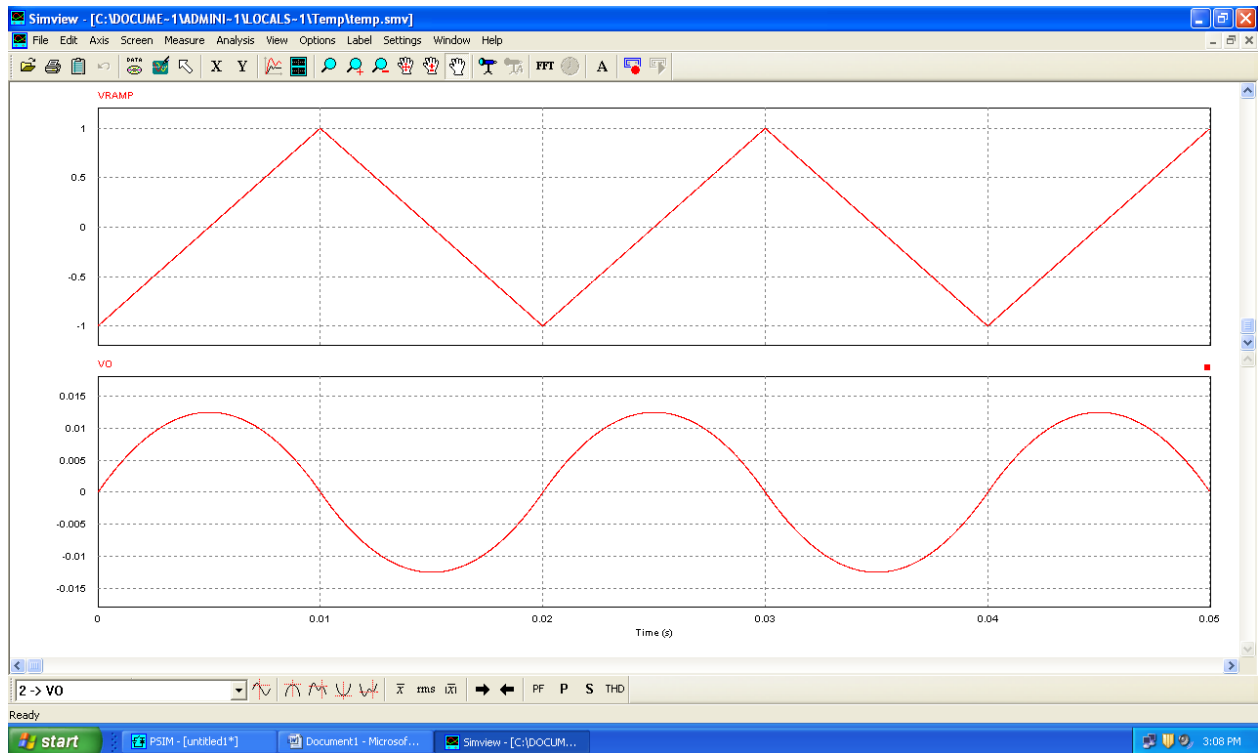




## DIFFERENTIATOR

Select the op-amp

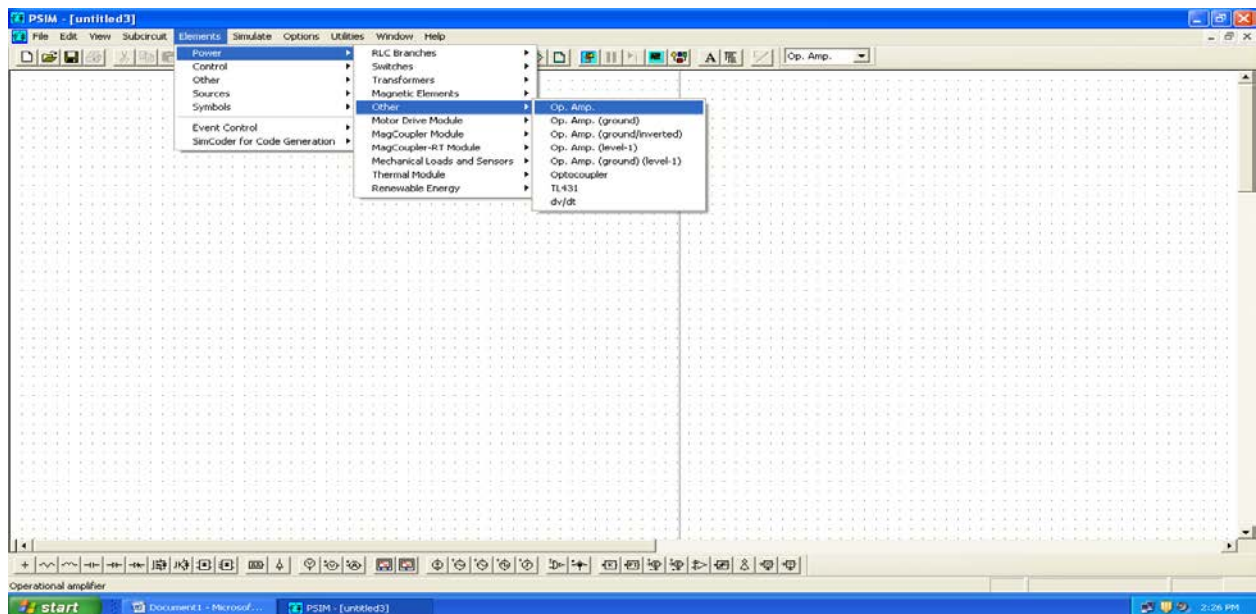


Select the triangular source

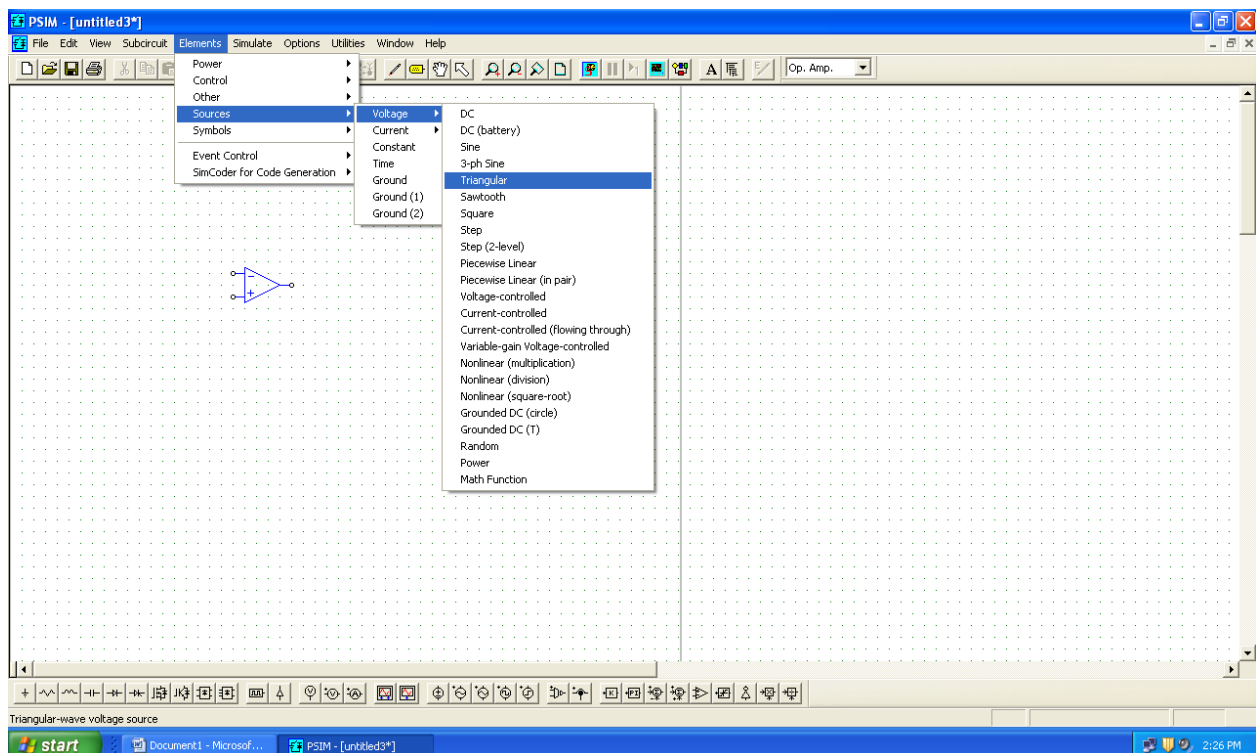




Select the resistor

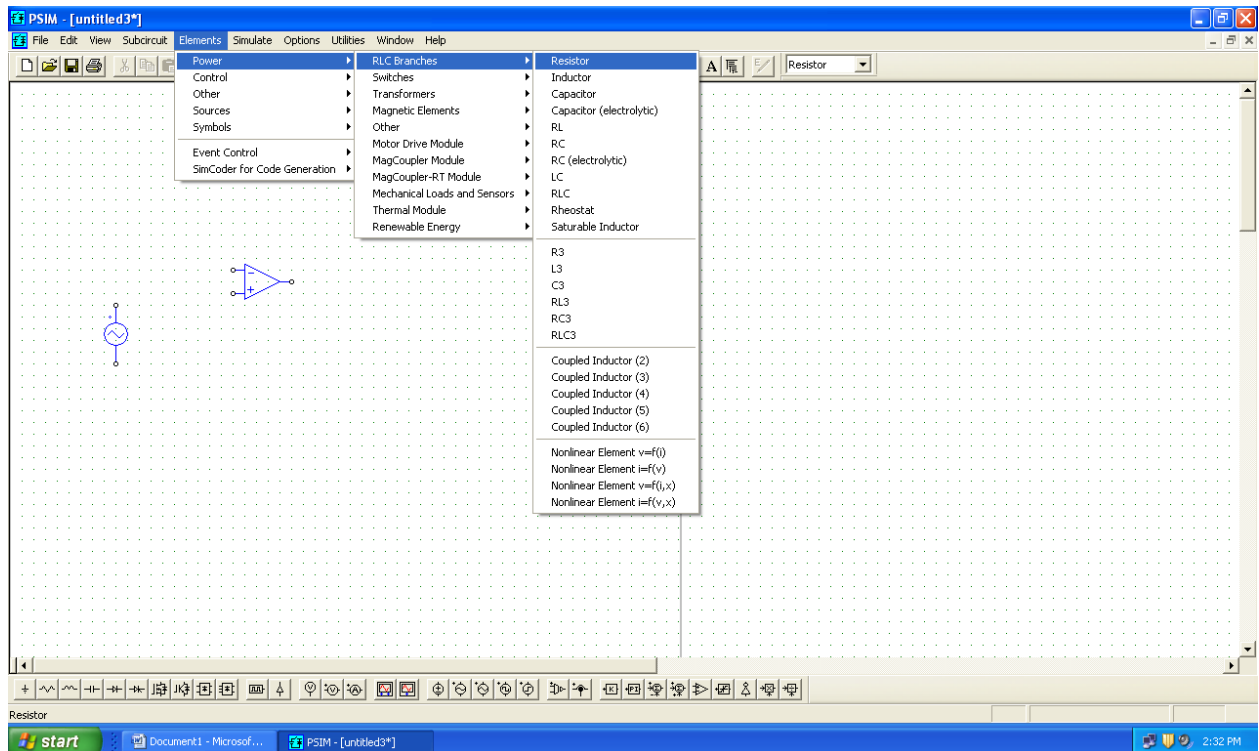


Select the capacitor

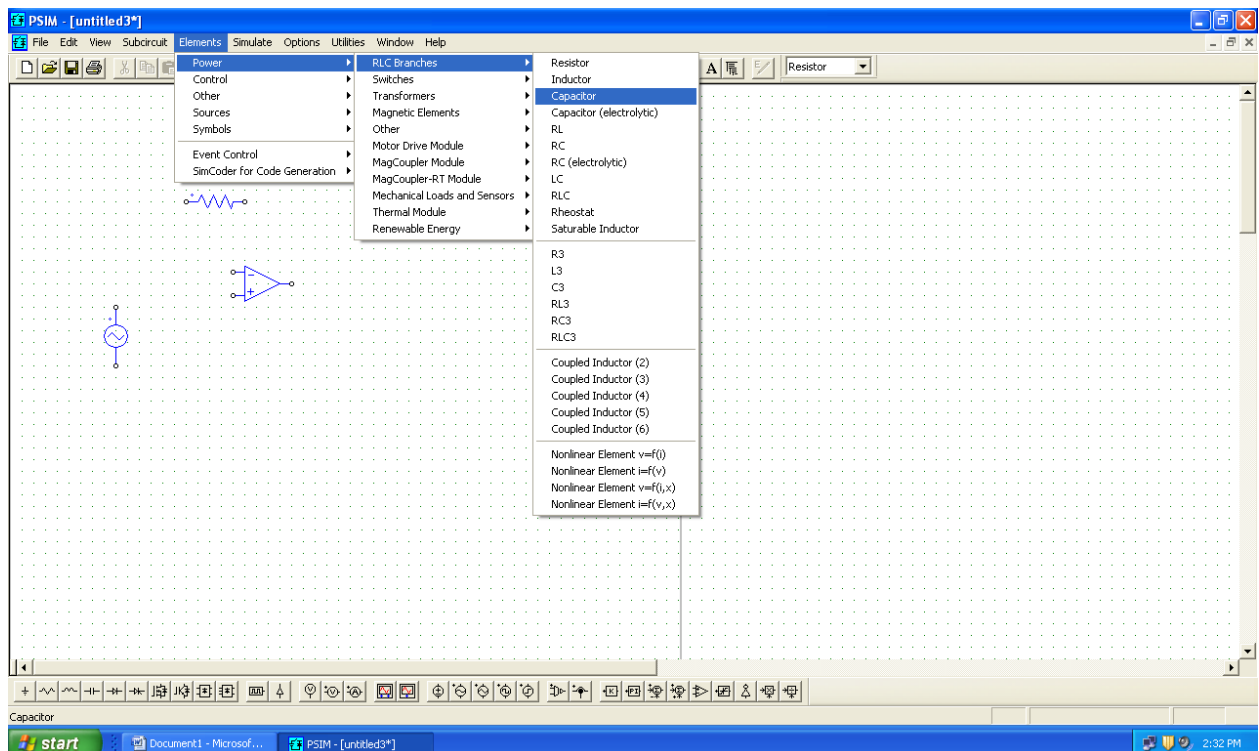




## Select the volt meter

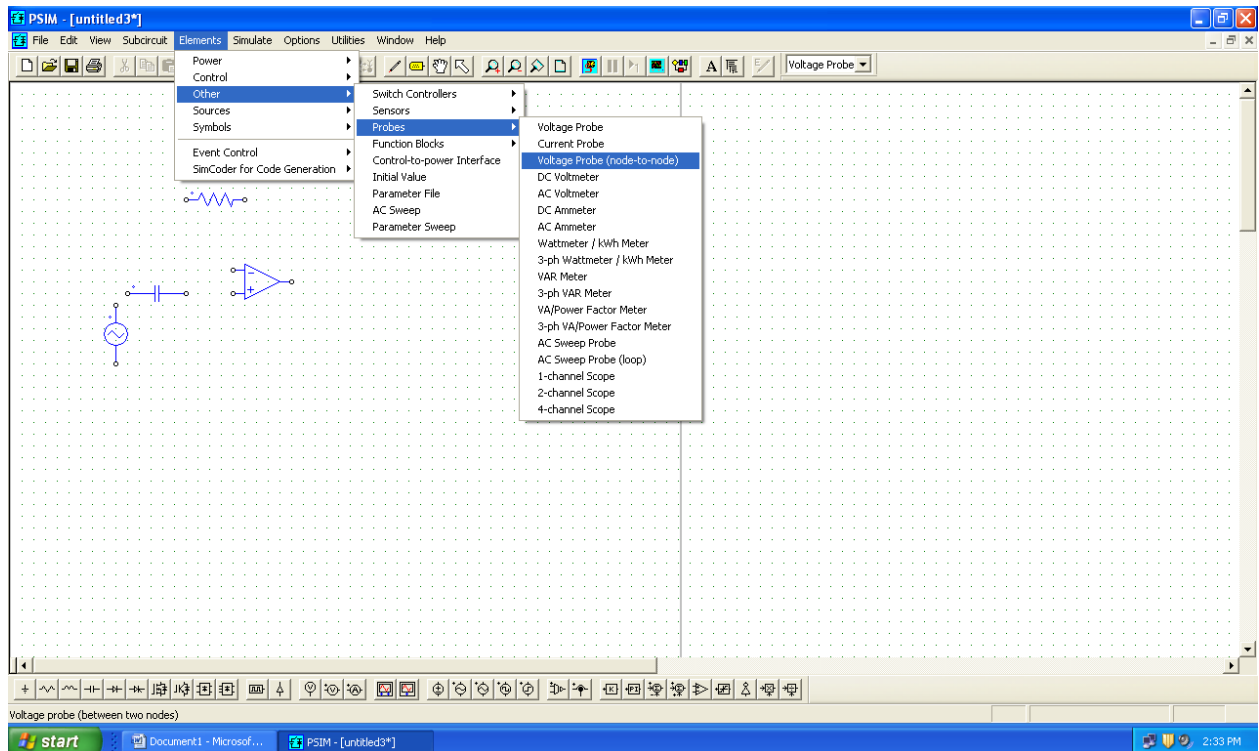


## Select the ground

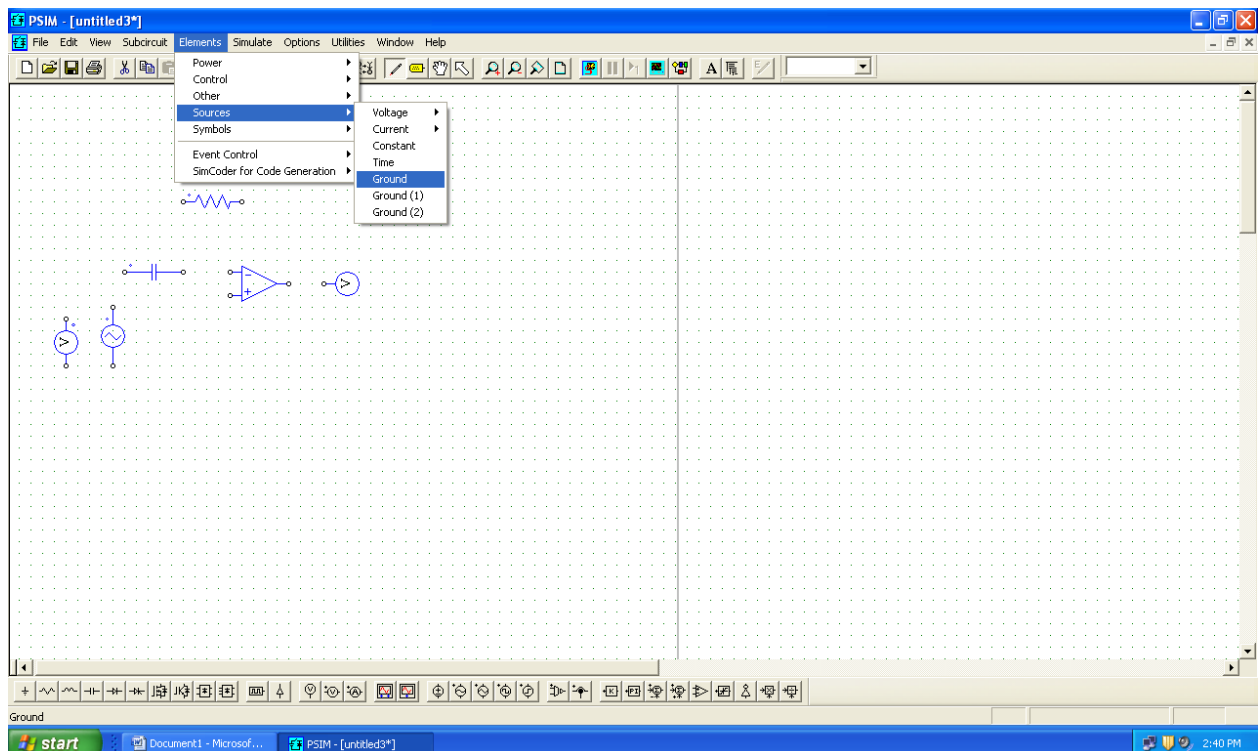






## Connect the circuit using wiring tool

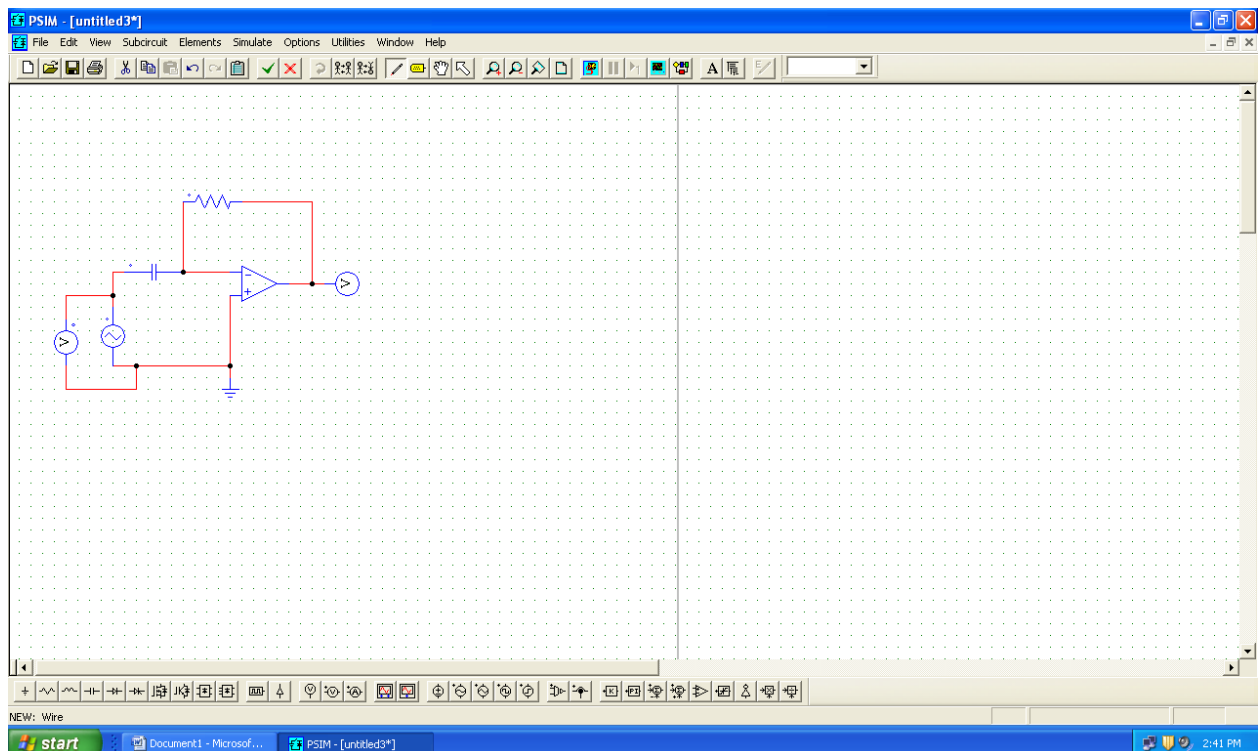

## Select the simulation control


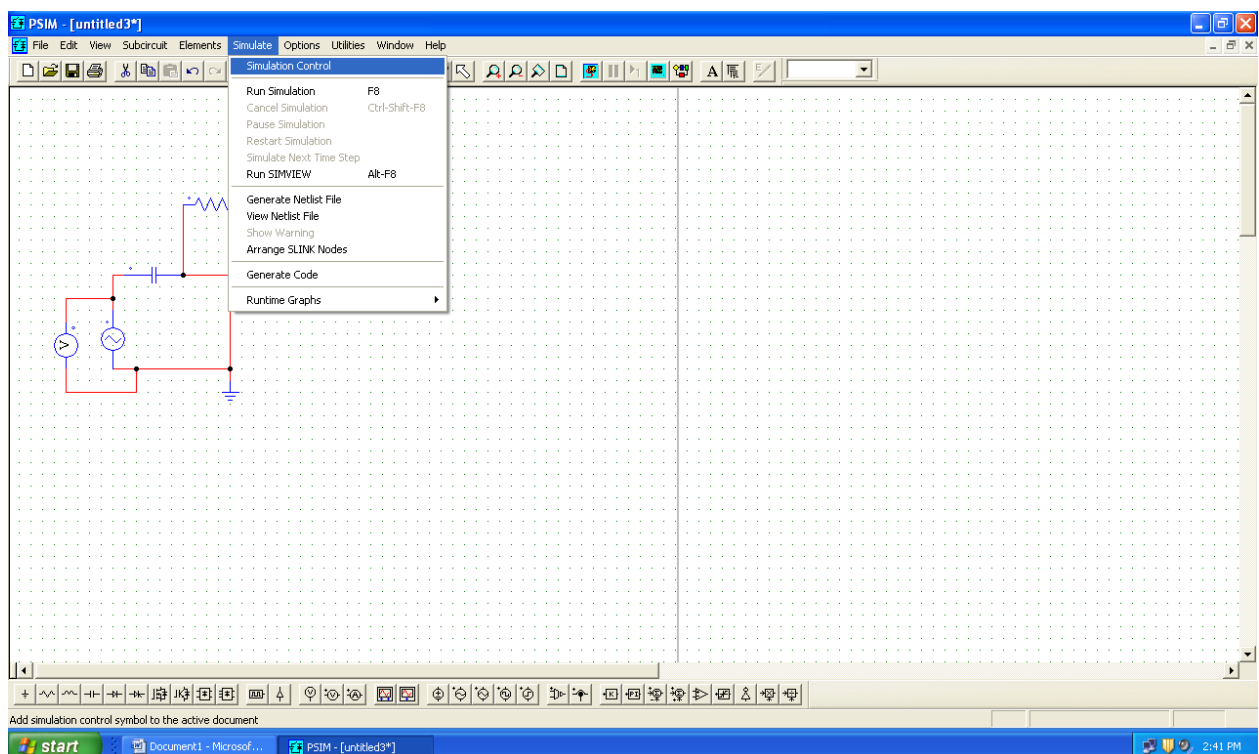


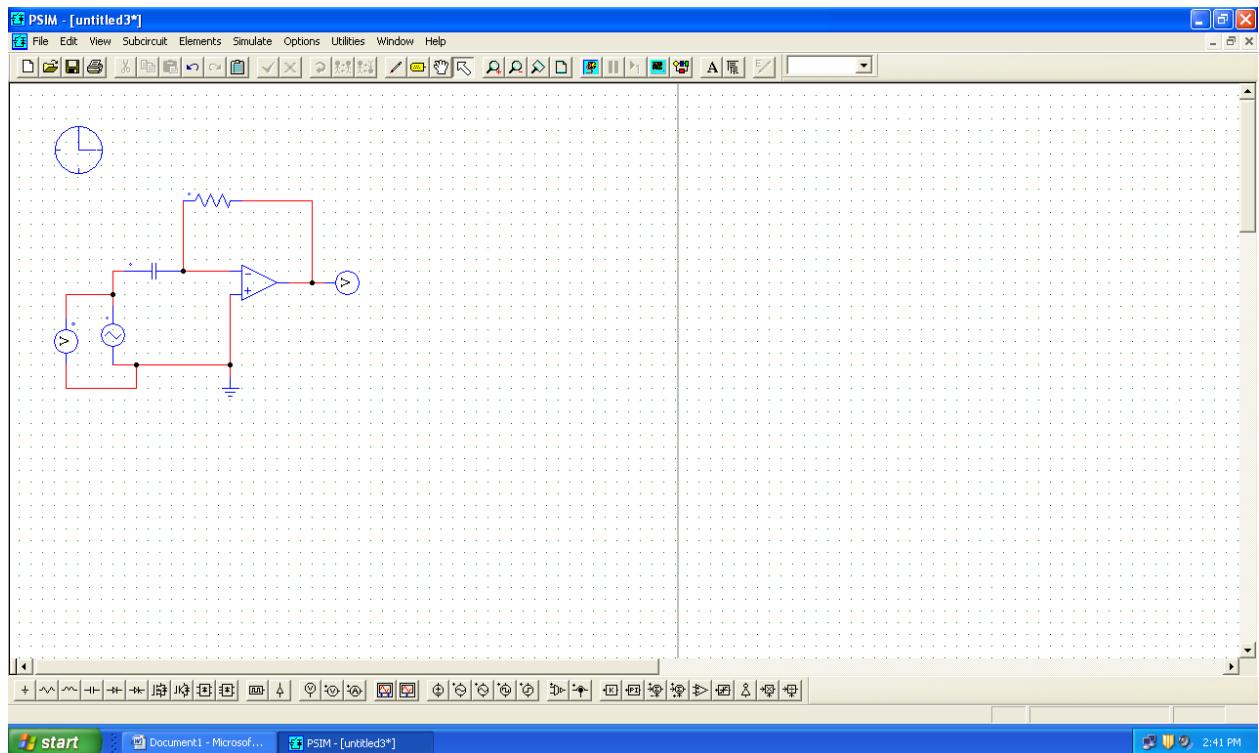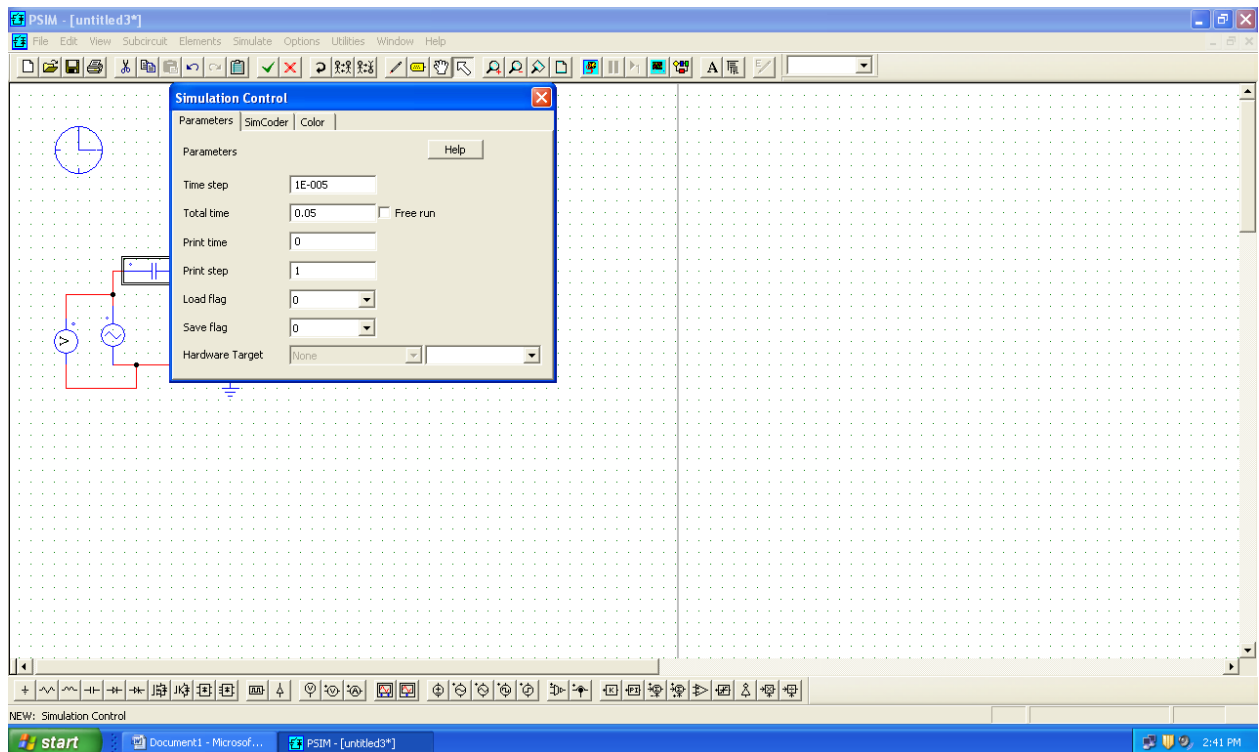







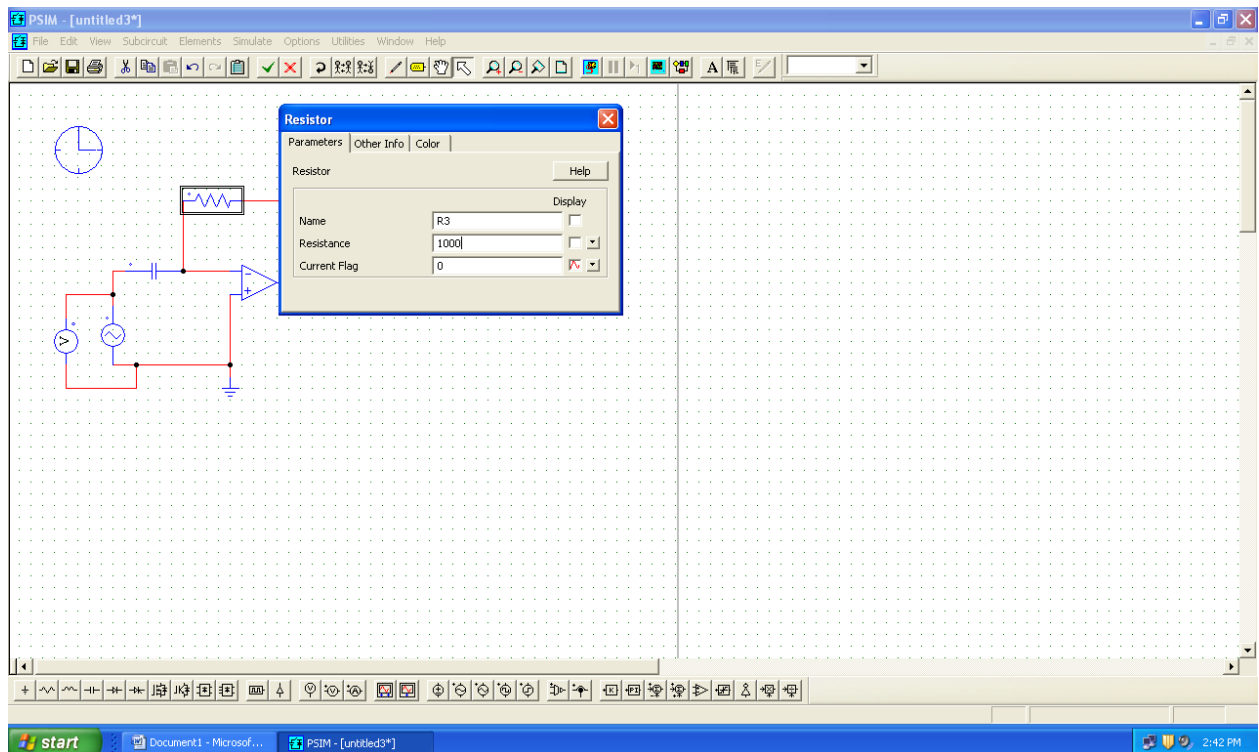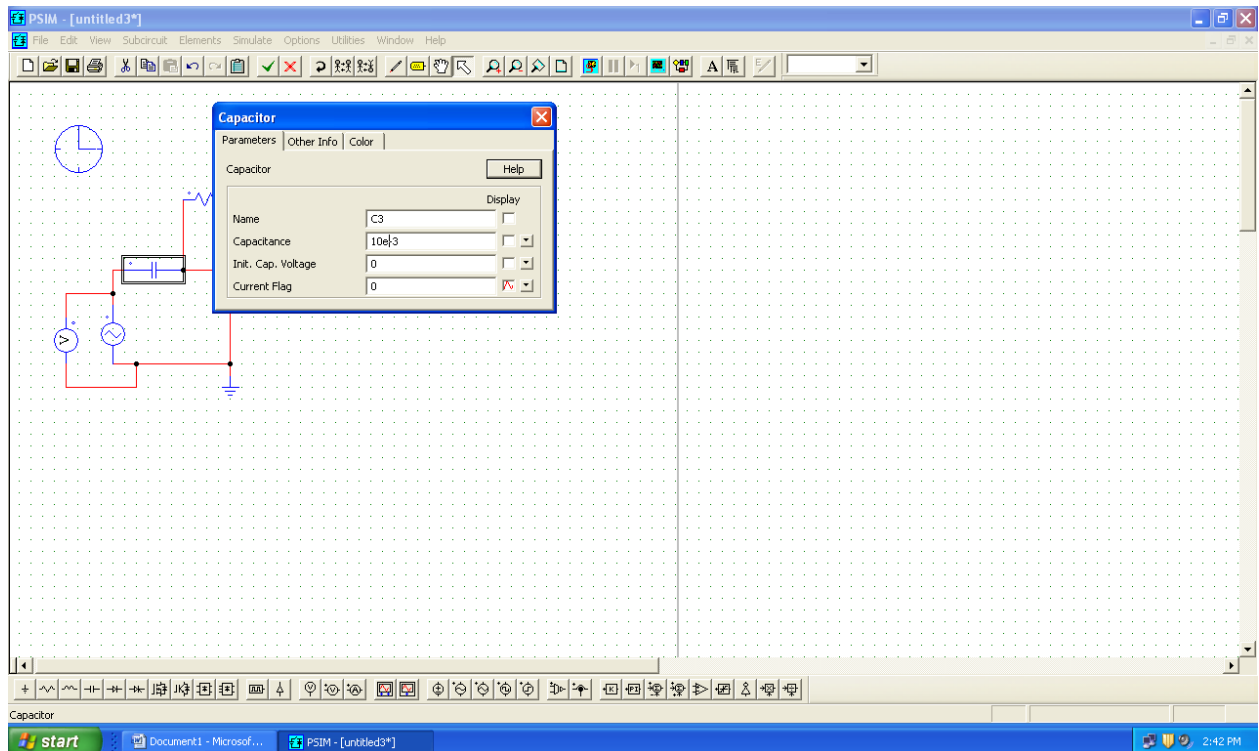Select the proper values to R,C and triangular source



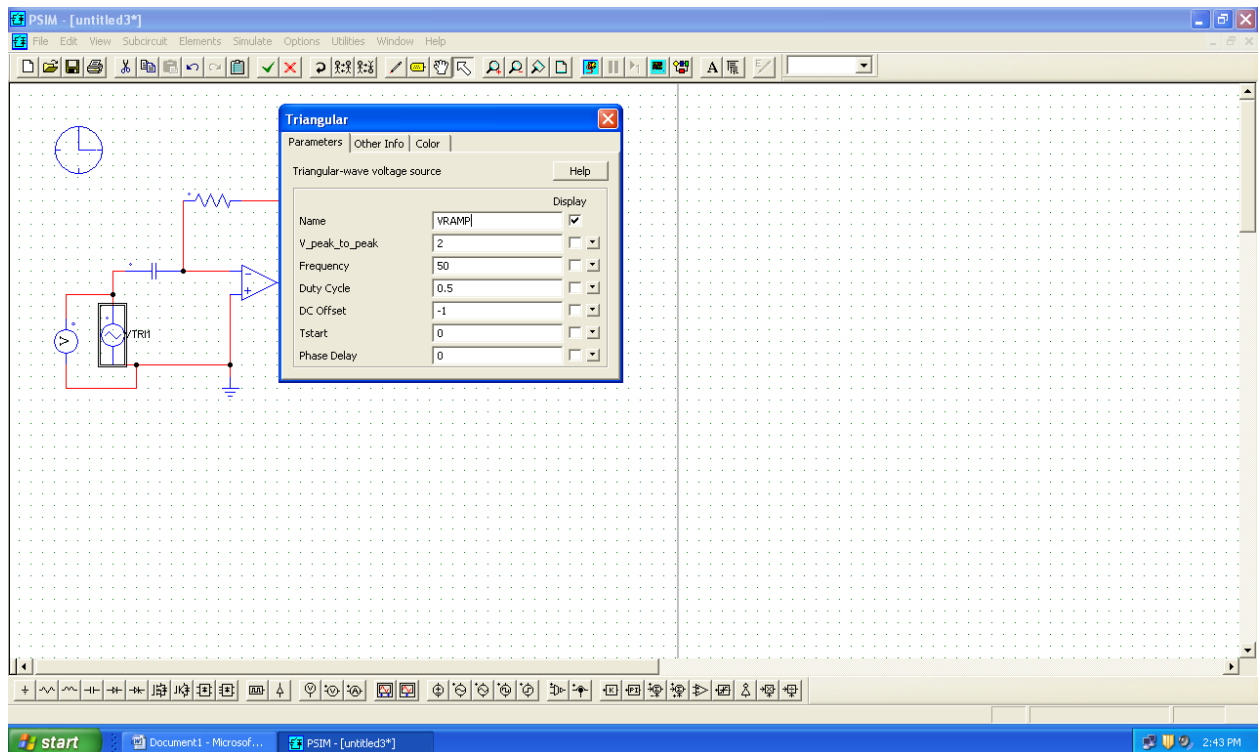


Run circuit using run simulation

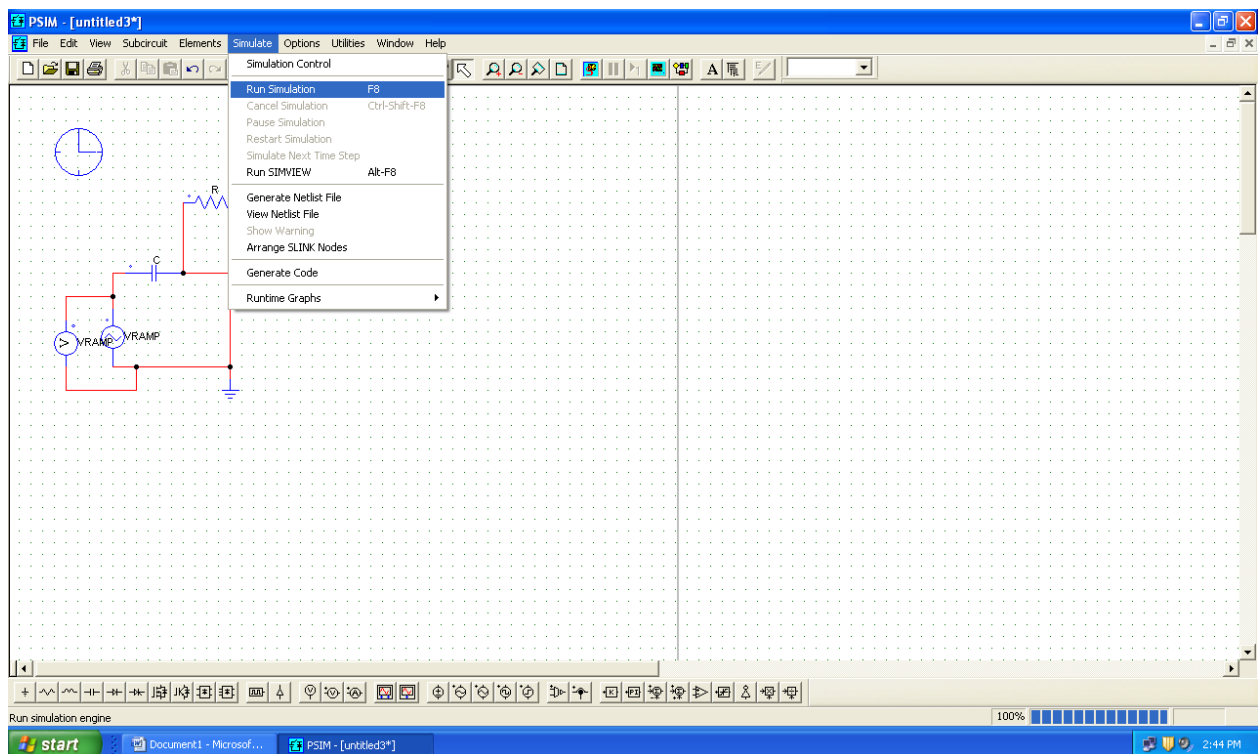



## Output waveforms

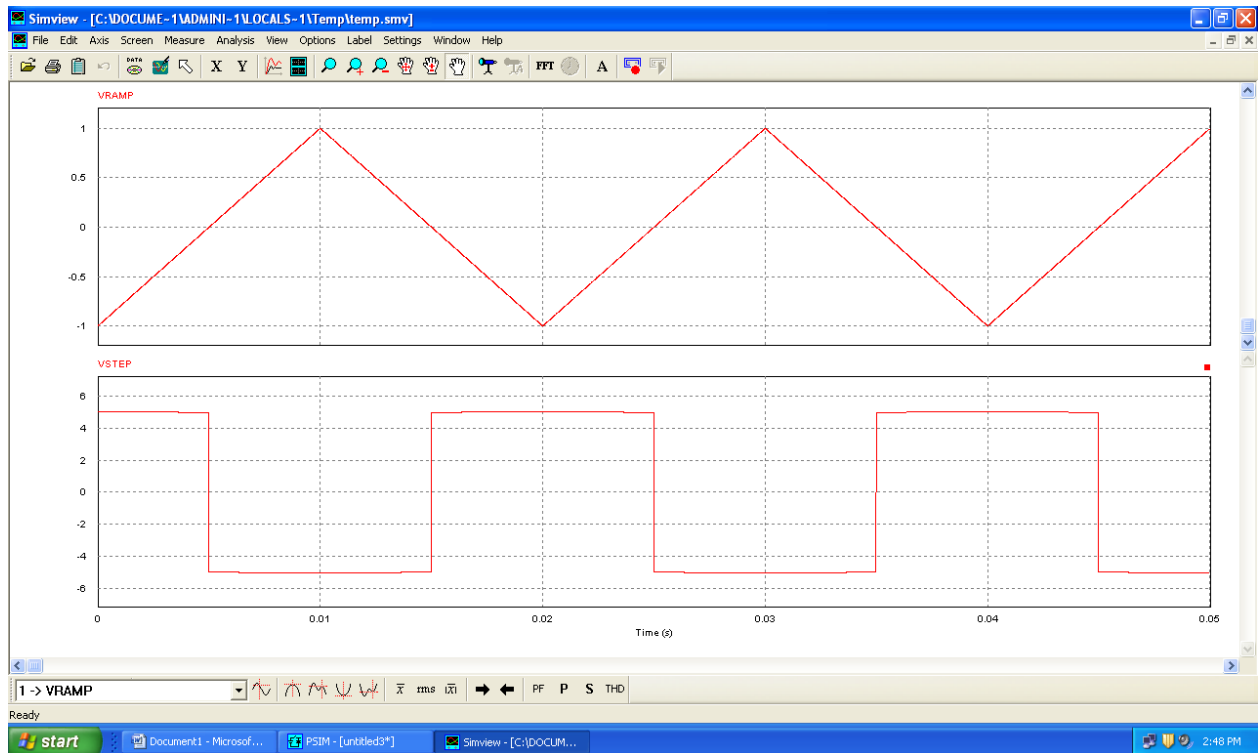

For more details contact

Mr. P. Rajasekhara Reddy

Assistant Professor

Department of Electrical and Electronics Engineering

Vasavi College of Engineering (Autonomous)

Email: [rajashekhar.p@staff.vce.ac.in](mailto:rajashekhar.p@staff.vce.ac.in)

Mobile: +91-9177207976

&

Dr. M. Chakravarthy

Professor and Head of the Department

Department of Electrical and Electronics Engineering

Vasavi College of Engineering (Autonomous)

Email: [hodeeee@staff.vce.ac.in](mailto:hodeeee@staff.vce.ac.in)

Mobile: +91-9849979136